

# Chapter 10. Transmission Lines


- **Transmission line:** carrier to transmit electric energy and signals from one point to another

Ex.] Source  $\leftrightarrow^*$  Load, Transmitter  $\leftrightarrow^*$  Receiver,  
Computer  $\leftrightarrow^*$  Computer,  
Hydroelectric generating plant  $\leftrightarrow^*$  Home  
Audio System  $\leftrightarrow^*$  Speaker,  
Cable service provider  $\leftrightarrow^*$  TV, Device  $\leftrightarrow^*$  Device

- 1) **Lumped elements** (R, L, C, etc.) ignores a time delay to traverse the elements → Per-unit-distance basis
- 2) **Distributed elements** (transmission line) can't be ignored the time delay to traverse the elements → Over-unit-distance basis

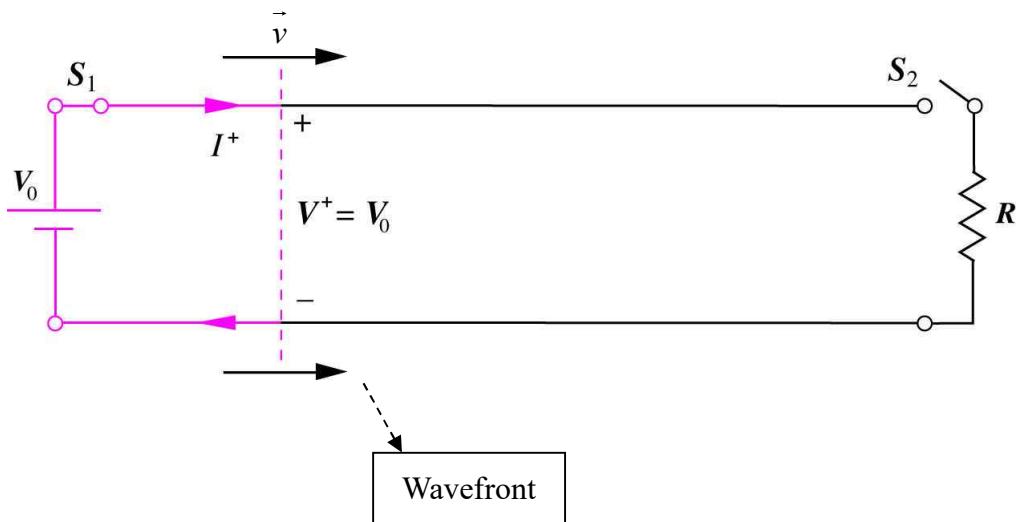
## 10.1 Physical Description of Transmission Line Propagation

- Lossless basic transmission line circuit



- Assume the switch  $S_1$  is closed at  $t = 0$
  - At  $t = 0^+$ , the source voltage ( $V_0$ ) doesn't instantaneously appear everywhere on the line but begins to travel from the battery toward the load ( $R$ ) at a certain velocity ( $v$ ).
  - Wavefront: instantaneous boundary between the sections of the line to be charged or not
- Lumped-element model of transmission line

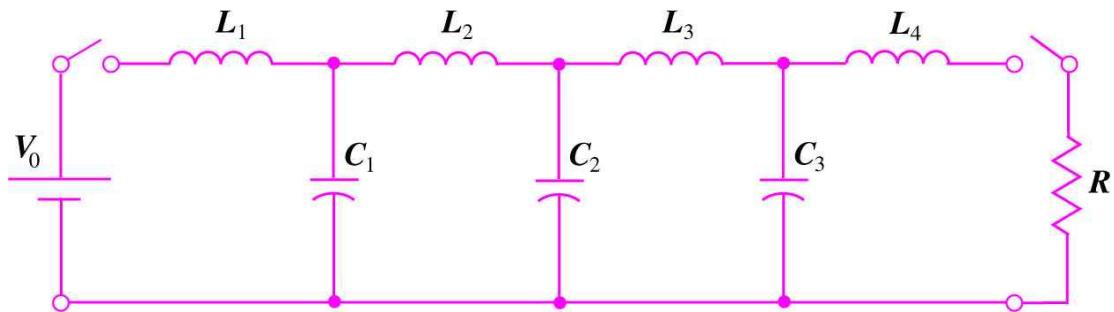Assumptions:  $L_1 = L_2 = L_3 = L_4$  [H/m] and  $C_1 = C_2 = C_3$  [F/m]



$S_1$  On  $\rightarrow$  Current through  $L_1 \rightarrow$  Charging on  $C_1$   
 $\rightarrow$  Current through  $L_2 \rightarrow$  Charging on  $C_2 \rightarrow \dots$   
 $\Leftrightarrow$  Wavefront moving from the left to right

$S_2$  On  $\rightarrow$  Discharging on  $C_3$  (Dissipating by  $R$ )  
 $\rightarrow$  Discharging on  $C_2$  (Dissipating by  $R$ )  $\rightarrow \dots$   
: **Pulse-forming network** (dissipating on  $R$ )

Wave velocity:  $v = 1 / (LC)^{0.5}$  (to be proved in later.)

- Analyzing approaches


1) Maxwell's equations: electromagnetic field method  
(complete & accurate)

Ex.] Wave power, velocity, ...

2) Circuit equations: equivalent voltage and current analysis method  
(intuitive & inaccurate)
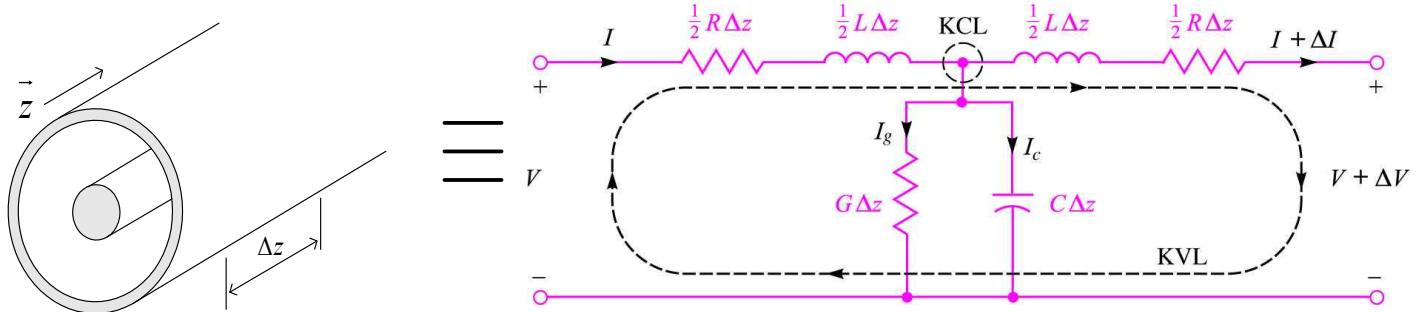
## 10.2 The Transmission Line Equations

- Lumped-element model of a short transmission line section **with losses**  
(length :  $\Delta z$ )



$R$ : series resistance per unit length [ $\Omega/m$ ]

← due to finite conductor conductivity  $\sigma_c$

$L$ : series inductance per unit length [ $H/m$ ]

$G$ : shunt conductance per unit length [ $\Omega^{-1}/m$ ]

← due to finite dielectric conductivity  $\sigma_d$

$C$ : shunt capacitance per unit length [ $F/m$ ] ← due to  $\epsilon_r$

$R, G$ : power loss components ( $=f(\text{freq.})$ )

- 전송선로의 미소길이에 대하여 등가 회로 model을 구하고, 이것으로부터 전압, 전류 방정식을 유도한 후 그 결과식들이 field 이론에서 구한 기본 방정식들(예: wave equation)과 성질이 같다면 uniform plane wave의 전달경로가 전송선로와 같음을 보일 수 있게 됨.

- Propagation direction:  $\vec{a}_z$

- KVL

$$V = \frac{1}{2} RI \Delta z + \frac{1}{2} L \frac{\partial I}{\partial t} \Delta z + \frac{1}{2} L \left( \frac{\partial I}{\partial t} + \frac{\partial \Delta I}{\partial t} \right) \Delta z \quad \leftarrow L = \frac{\Phi}{I} \quad \& \quad V = \frac{d\Phi}{dt}$$

$$+ \frac{1}{2} R(I + \Delta I) \Delta z + (V + \Delta V) \quad (1)$$

$$(V + \Delta V) - V = -\frac{1}{2} RI \Delta z - \frac{1}{2} L \frac{\partial I}{\partial t} \Delta z - \frac{1}{2} L \left( \frac{\partial I}{\partial t} + \frac{\partial \Delta I}{\partial t} \right) \Delta z - \frac{1}{2} R(I + \Delta I) \Delta z$$

$$\frac{\Delta V}{\Delta z} = -\frac{1}{2} RI - \frac{1}{2} L \frac{\partial I}{\partial t} - \frac{1}{2} L \left( \frac{\partial I}{\partial t} + \frac{\partial \Delta I}{\partial t} \right) - \frac{1}{2} R(I + \Delta I)$$

$$= -\left( RI + L \frac{\partial I}{\partial t} + \frac{1}{2} L \frac{\partial \Delta I}{\partial t} + \frac{1}{2} R \Delta I \right) \quad (2)$$

$$\text{Applying } \Delta I = \frac{\partial I}{\partial z} \Delta z \quad \text{and} \quad \Delta V = \frac{\partial V}{\partial z} \Delta z \quad (3)$$

$$\frac{\partial V}{\partial z} = -\left\{ \left( RI + L \frac{\partial I}{\partial t} \right) + \frac{1}{2} L \frac{\partial}{\partial t} \left( \frac{\partial I}{\partial z} \Delta z \right) + \frac{1}{2} R \frac{\partial I}{\partial z} \Delta z \right\}$$

$$= -\left\{ \left( RI + L \frac{\partial I}{\partial t} \right) + \frac{\Delta z}{2} \frac{\partial}{\partial z} \left( RI + L \frac{\partial I}{\partial t} \right) \right\} = -\left( 1 + \frac{\Delta z}{2} \frac{\partial}{\partial z} \right) \left( RI + L \frac{\partial I}{\partial t} \right) \quad (4)$$

As  $\Delta z \rightarrow 0$ ,

$$\frac{\partial V}{\partial z} = - \left( RI + L \frac{\partial I}{\partial t} \right) \quad (5)$$

- KCL at the mid-point using the symmetric property

$$I = I_g + I_c + (I + \Delta I) \quad \leftarrow Q = CV \quad \& \quad I = \frac{dQ}{dt}$$

$$= G\Delta z \left( V + \frac{\Delta V}{2} \right) + C\Delta z \frac{\partial}{\partial t} \left( V + \frac{\Delta V}{2} \right) + (I + \Delta I) \quad (6)$$

$$(I + \Delta I) - I = -G\Delta z \left( V + \frac{\Delta V}{2} \right) - C\Delta z \frac{\partial}{\partial t} \left( V + \frac{\Delta V}{2} \right)$$

$$\frac{\Delta I}{\Delta z} = -G \left( V + \frac{\Delta V}{2} \right) - C \frac{\partial}{\partial t} \left( V + \frac{\Delta V}{2} \right) \quad \leftarrow \Delta V = \frac{\partial V}{\partial z} \Delta z$$

$$= -G \left( V + \frac{\Delta z}{2} \frac{\partial V}{\partial z} \right) - C \frac{\partial}{\partial t} \left( V + \frac{\Delta z}{2} \frac{\partial V}{\partial z} \right)$$

$$= - \left\{ GV \left( 1 + \frac{\Delta z}{2} \frac{\partial}{\partial z} \right) + C \frac{\partial V}{\partial t} \left( 1 + \frac{\Delta z}{2} \frac{\partial}{\partial z} \right) \right\}$$

$$= - \left( 1 + \frac{\Delta z}{2} \frac{\partial}{\partial z} \right) \left( GV + C \frac{\partial V}{\partial t} \right) \quad (7)$$

As  $\Delta z \rightarrow 0$

$$\frac{\partial I}{\partial z} = - \left( GV + C \frac{\partial V}{\partial t} \right) \quad (8)$$

- Telegraphist's equations: Eqs. (5) and (8)

$$\frac{\partial V}{\partial z} = - \left( RI + L \frac{\partial I}{\partial t} \right) \quad (5)$$

$$\frac{\partial I}{\partial z} = - \left( GV + C \frac{\partial V}{\partial t} \right) \quad (8)$$

- $\partial(\text{Eq. (5)})/\partial z$  and  $\partial(\text{Eq. (8)})/\partial t$ :

$$\frac{\partial^2 V}{\partial z^2} = -R \frac{\partial I}{\partial z} - L \frac{\partial^2 I}{\partial t \partial z} \quad (9)$$

$$\frac{\partial^2 I}{\partial z \partial t} = -G \frac{\partial V}{\partial t} - C \frac{\partial^2 V}{\partial t^2} \quad (10)$$

- Eq. (9)  $\leftarrow$  Eqs. (8) and (10):

$$\begin{aligned} \frac{\partial^2 V}{\partial z^2} &= R \left( GV + C \frac{\partial V}{\partial t} \right) + L \left( G \frac{\partial V}{\partial t} + C \frac{\partial^2 V}{\partial t^2} \right) \\ &= LC \frac{\partial^2 V}{\partial t^2} + (LG + RC) \frac{\partial V}{\partial t} + RGV \end{aligned} \quad (11)$$

- $\partial(\text{Eq. (5)})/\partial t$  and  $\partial(\text{Eq. (8)})/\partial z$ :

$$\frac{\partial^2 V}{\partial z \partial t} = -R \frac{\partial I}{\partial t} - L \frac{\partial^2 I}{\partial t^2} \quad (*)$$

$$\frac{\partial^2 I}{\partial z^2} = -G \frac{\partial V}{\partial z} - C \frac{\partial^2 V}{\partial t \partial z} \quad (**)$$

- Eq. (\*\*)  $\leftarrow$  Eqs. (5) and (\*):

$$\begin{aligned} \frac{\partial^2 I}{\partial z^2} &= G \left( RI + L \frac{\partial I}{\partial t} \right) + C \left( R \frac{\partial I}{\partial t} + L \frac{\partial^2 I}{\partial t^2} \right) \\ &= LC \frac{\partial^2 I}{\partial t^2} + (LG + RC) \frac{\partial I}{\partial t} + RGI \end{aligned} \quad (12)$$

- **General wave equations:** Eqs. (11) and (12)

(*V와 I의 방정식이 공간과 시간에 대한 함수로 표현됨*)

## 10.3 Lossless propagation

- Lossless propagation: (input) power isn't dissipated or otherwise deviated as the wave travels down the transmission line.

→  $R = G = 0$

- Lossless general wave equation:

$$\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2} \quad (13) \leftarrow \text{Eq.(11)}$$

→ General solution:

$$V(z, t) = f_1\left(t - \frac{z}{v}\right) + f_2\left(t + \frac{z}{v}\right) = V^+ + V^- \quad (14)$$

where  $v$ : wave velocity

$f_1, f_2$ : forward and backward  $z$ -directional travel functions

$V^+, V^-$ : forward and backward voltage wave components

Ex.] As  $t$  is ↑,  $z$  must be ↑ for  $f_1(0)$ .

→ Positive (or forward)  $z$ -direction traveling

As  $t$  is ↑,  $z$  must be ↓ for  $f_2(0)$ .

→ Negative (or backward)  $z$ -direction traveling

- From Eq. (14),

$$\frac{\partial f_1}{\partial z} = \frac{\partial f_1}{\partial(t - z/v)} \frac{\partial(t - z/v)}{\partial z} = -\frac{1}{v} f'_1 \quad (15)$$

$$\frac{\partial f_1}{\partial t} = \frac{\partial f_1}{\partial(t - z/v)} \frac{\partial(t - z/v)}{\partial t} = f'_1 \quad (16)$$

$$\frac{\partial^2 f_1}{\partial z^2} = \frac{\partial}{\partial z} \left( \frac{\partial f_1}{\partial z} \right) = \frac{1}{v^2} f''_1 \quad \text{and} \quad \frac{\partial^2 f_1}{\partial t^2} = \frac{\partial}{\partial t} \left( \frac{\partial f_1}{\partial t} \right) = f''_1 \quad (17)$$

- Eq. (13) ← Eq. (17):

$$\frac{1}{v^2} f_1'' = LC f_1'' \quad (18)$$

$$v = \frac{1}{\sqrt{LC}} : \text{wave velocity} \quad (19) \leftarrow \text{page 2}$$

- Lossless voltage and current equations along the transmission line:

$$\frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t} \quad (20) \leftarrow \text{Eq. (5)}$$

$$\frac{\partial I}{\partial z} = -C \frac{\partial V}{\partial t} \quad (21) \leftarrow \text{Eq. (8)}$$

- Eq. (20) ← Eq. (14):

$$\frac{\partial I}{\partial t} = -\frac{1}{L} \frac{\partial V}{\partial z} \leftarrow \text{Eq. (14)}$$

$$= -\frac{1}{L} \frac{\partial}{\partial z} \left[ f_1 \left( t - \frac{z}{v} \right) + f_2 \left( t + \frac{z}{v} \right) \right] = \frac{1}{Lv} (f_1' - f_2') \quad (22)$$

- Integrate Eq. (22) over time:

$$I(z, t) = \int \frac{\partial I}{\partial t} dt = \frac{1}{Lv} \left[ f_1 \left( t - \frac{z}{v} \right) - f_2 \left( t + \frac{z}{v} \right) \right] = I^+ + I^- \quad (23) \Leftrightarrow I = \frac{V}{Z}$$

where  $Lv$ : characteristic impedance of lossless line

$\rightarrow (f_1 + f_2)$  voltage wave ⇒ 고,  $(f_1 - f_2)$  current wave ⇒ 므로

- Characteristic impedance ( $Z_0$ ): a ratio of voltage to current waves

$$Z_0 = Lv = L \sqrt{\frac{1}{LC}} = \sqrt{\frac{L}{C}} \quad (24)$$


- By comparing Eqs. (14) and (23),

$$V^+ = Z_0 I^+ \quad (25a)$$

$$V^- = -Z_0 I^- \quad (25b)$$

where minus (-) means backward propagating.

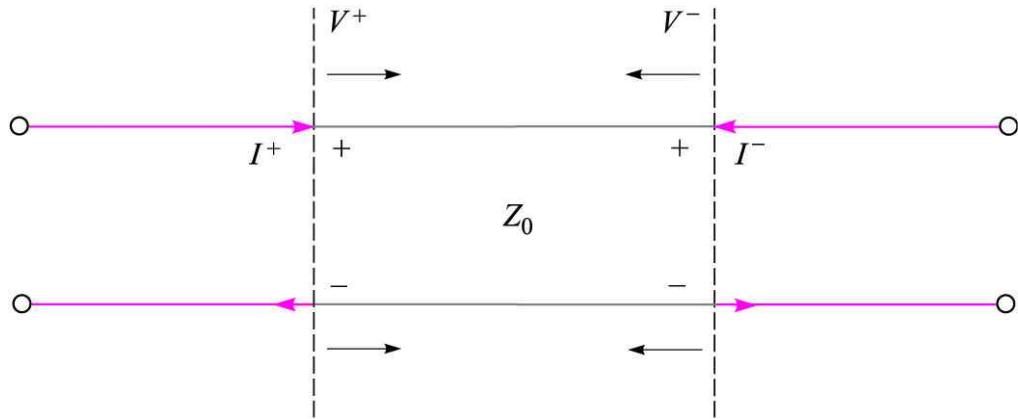- Current directions in waves having positive and negative voltages:



## 10.4 Lossless Propagation of Sinusoidal Voltages

- Any transmitted signal can be composed into a discrete or continuous summation of sinusoids.  
→ Fourier transformation (time domain  $\leftrightarrow$  frequency domain)

- Sinusoidal voltage function:

$$V(z, t) = f_1\left(t - \frac{z}{v}\right) + f_2\left(t + \frac{z}{v}\right) = V^+ + V^- \quad (14)$$

Consider a specific example:

$$\begin{aligned} f &= \omega/2\pi, f_1 = f_2 = V_0 \cos(\omega t + \phi), t \rightarrow t \pm z/v_p \\ \Rightarrow V(z, t) &= |V_0| \cos[\omega(t \pm z/v_p) + \phi] = |V_0| \cos[\omega t \pm \beta z + \phi] \end{aligned} \quad (26)$$

For sine wave,  $\phi = \pi/2$

In case of  $\phi = 0$ ,

$$V_f(z,t) = |V_0| \cos(\omega t - \beta z) \quad (\text{forward } z \text{ propagation}) \quad (27a)$$

$$V_b(z,t) = |V_0| \cos(\omega t + \beta z) \quad (\text{backward } z \text{ propagation}) \quad (27b)$$

→ Real instantaneous forms of transmission-line voltage  
 $V_f$  or  $V_b = f(\omega t, \beta z)$

where  $|V_0|$ : value of  $V$  at  $z = 0$  and  $t = 0$

$\omega$ : angular frequency [rad/sec]

$\beta$ : spatial frequency [rad/m]

- Phase constant ( $\beta$ ):

$$\beta \equiv \frac{\omega}{v_p} \quad (28) : [\text{rad/sec}] / [\text{m/sec}] = [\text{rad/m}]$$

- Instantaneous voltage in case of  $t = 0$ ,

$$V_f(z,0) = V_b(z,0) = |V_0| \cos(\beta z) \quad (29)$$

→ Simple periodic function with distance  $\lambda$

Requirement of wavelength ( $\lambda$ ):  $\beta\lambda = 2\pi$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega/v_p} = \frac{v_p}{f} \quad (30)$$

## 10.5 Complex Analysis of Sinusoidal Waves

- Expressing sinusoidal waves as complex function:  
 usability of the evaluation and visualization of signal phase

- Euler identity:  $e^{\pm jx} = \cos(x) \pm j\sin(x)$  (32)

$$\rightarrow \cos(x) = \operatorname{Re}[e^{\pm jx}] = (e^{jx} + e^{-jx}) / 2 = e^{jx}/2 + c.c. \quad (33a)$$

$$\sin(x) = \pm \operatorname{Im}[e^{\pm jx}] = (e^{jx} - e^{-jx}) / 2j = e^{jx}/2j - c.c. \quad (33b)$$

where  $j = (-1)^{0.5}$

*c.c.:* complex conjugate of the preceding term

$$V(z, t) = |V_0| \cos[\omega(t \pm z/v_p) + \phi] = |V_0| \cos[\omega t \pm \beta z + \phi] \quad (26)$$

$$= \frac{1}{2} \underbrace{|V_0| e^{j\phi}}_{V_0} e^{\pm j\beta z} e^{j\omega t} + c.c. \quad (34)$$

where  $V_0 = (|V_0| e^{j\phi})$ : complex amplitude of the wave

- Complex instantaneous voltage:

$$V_c(z, t) = V_0 e^{\pm j\beta z} e^{j\omega t} \quad (35)$$

- Phasor voltage:

$$V_s(z) = V_0 e^{\pm j\beta z} \quad (36)$$

$\rightarrow$  sinusoidal steady-state condition ( $\neq f(t)$ )

- Real instantaneous voltage:

$$V(z, t) = |V_0| \cos[\omega t \pm \beta z + \phi] = \operatorname{Re}[V_c(z, t)] = \frac{1}{2} V_c + c.c. \quad (37a)$$

- Phasor voltage:

$$V(z, t) = |V_0| \cos[\omega t \pm \beta z + \phi] = \operatorname{Re}[V_s(z) e^{j\omega t}] = \frac{1}{2} V_s e^{j\omega t} + c.c. \quad (37b)$$

(sinusoidal instantaneous voltage:  $V(z, t) = \operatorname{Re}[V_s(z) e^{j\omega t}]$ )

[Ex. 10.1] Two voltage waves having equal frequencies and amplitudes propagate in opposite directions on a lossless transmission line.

→ Phasor form:

$$V_{sT}(z) = V_0 e^{-j\beta z} + V_0 e^{+j\beta z} = 2V_0 \cos(\beta z)$$

Real instantaneous form:

$$\begin{aligned} V(z, t) &= \operatorname{Re}[(V_0 e^{-j\beta z} + V_0 e^{+j\beta z}) e^{j\omega t}] = \operatorname{Re}\left[2 \frac{V_0(e^{-j\beta z} + e^{+j\beta z})}{2} e^{j\omega t}\right] \\ &= \operatorname{Re}[2V_0 \cos(\beta z) e^{j\omega t}] = 2V_0 \cos(\beta z) \cos(\omega t) \end{aligned}$$

→  $V(z, t) = f(z, t)$

## 10.6 Transmission Line Equations and Their Solutions in Phasor Form

- Real instantaneous voltage of general wave equations:

$$\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2} + (LG + RC) \frac{\partial V}{\partial t} + RGV \quad (11)(38)$$

$$\begin{aligned} \frac{\partial V(z, t)}{\partial t} &= \frac{\partial}{\partial t} \operatorname{Re}[V_0 e^{j\beta z} e^{j\omega t}] = \frac{\partial}{\partial t} \operatorname{Re}[V_0 e^{j(\omega t + \beta z)}] = \frac{\partial}{\partial t} [V_0 \cos(\omega t + \beta z)] \\ &= -\omega V_0 \sin(\omega t + \beta z) = j\omega V_0 \cdot \{j \sin(\omega t + \beta z)\} \\ &= \operatorname{Re}[j\omega V_0 e^{j(\omega t + \beta z)}] = \operatorname{Re}[j\omega V_0 e^{j\beta z} e^{j\omega t}] = \operatorname{Re}[j\omega V_s e^{j\omega t}] \end{aligned}$$

$$\therefore \frac{\partial}{\partial t} \underset{\text{instantaneous}}{\leftrightarrow} \underset{\text{phasor}}{j\omega}$$

- Phasor voltage of the general wave equations:

$$\frac{d^2 V_s}{dz^2} = -\omega^2 LCV_s + j\omega(LG + RC)V_s + RGV_s \quad (39)$$

$$= \underbrace{(R + j\omega L)}_Z \underbrace{(G + j\omega C)}_Y V_s = \gamma^2 V_s \quad (40)$$

where  $Z$ ,  $Y$ : net series impedance and shunt admittance of transmission line as per-unit-distance

- Propagation constant:

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{ZY} = \alpha + j\beta \quad (41)$$

- General solution of Eq. (40):

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \quad (42a)$$

- Phasor current of general wave equations:

$$I_s(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} \quad (42b)$$

- Real instantaneous current:

$$I(z, t) = |I_0| \cos(\omega t \pm \beta z + \xi) = \frac{1}{2} \underbrace{\left( |I_0| e^{j\xi} \right)}_{I_0} e^{\pm j\beta z} e^{j\omega t} + c.c. = \frac{1}{2} I_s(z) e^{j\omega t} + c.c. \quad (43)$$

- Eqs. (5) and (8) ← Eqs. (37b) and (43)

$$\frac{\partial V}{\partial z} = - \left( RI + L \frac{\partial I}{\partial t} \right) \Rightarrow \frac{dV_s}{dz} = - (R + j\omega L) I_s = - Z I_s \quad (44a)$$

$$\frac{\partial I}{\partial z} = - \left( GV + C \frac{\partial V}{\partial t} \right) \Rightarrow \frac{dI_s}{dz} = - (G + j\omega C) V_s = - Y I_s \quad (44b)$$

- Eqs. (44a) and (44b) ← Eqs. (42a) and (42b)

$$-\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{\gamma z} = -Z(I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}) \quad (45)$$

- Line characteristic impedance:

$$Z_0 = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{Z}{\gamma} = \frac{Z}{\sqrt{ZY}} = \sqrt{\frac{Z}{Y}} \quad (46) \quad \leftarrow \quad (40)$$

$$= \sqrt{\frac{R + j\omega L}{G + j\omega C}} = |Z_0| e^{j\theta} \quad (47)$$

[Ex. 10.2] Lossless line length  $l = 0.8$  [m],  $f = 600$  [MHz],

Line parameters:  $L = 0.25$  [ $\mu\text{H/m}$ ],  $C = 100$  [ $\text{pF/m}$ ]

→ Because of lossless line,  $R = G = 0$ .

Characteristic impedance:

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.25 \times 10^{-6}}{100 \times 10^{-12}}} = 50 [\Omega]$$

Since  $\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} = j\omega\sqrt{LC}$ ,

$$\alpha = 0$$


$$\beta = 2\pi \times (600 \times 10^6) \times \sqrt{(0.25 \times 10^{-6})(100 \times 10^{-12})} = 18.85 \text{ [rad/m]}$$

$$v_p = \frac{\omega}{\beta} = \frac{2\pi(600 \times 10^6)}{18.85} = 2 \times 10^8 \text{ [m/s]}$$
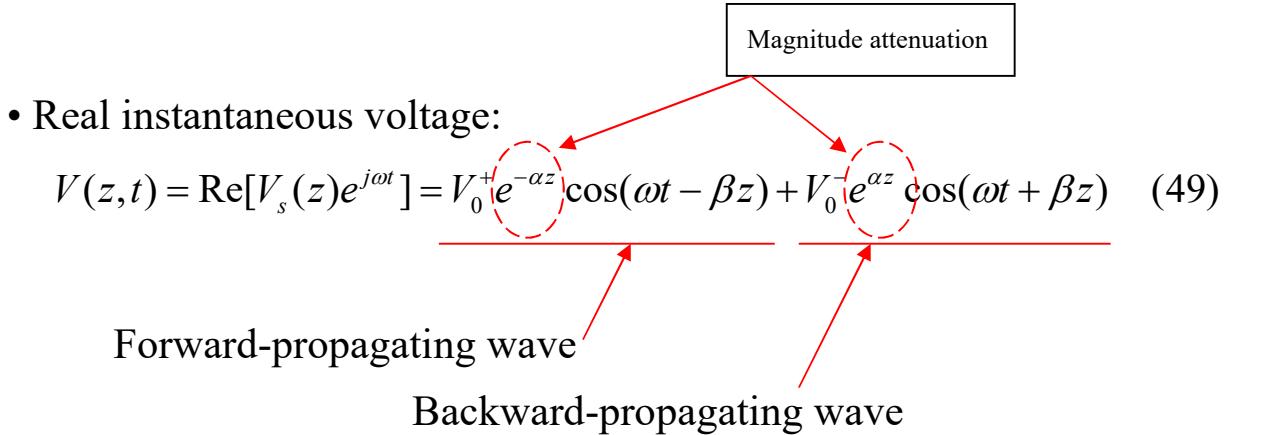
## 10.7 Low-Loss Propagation

- Eq. (42a) ← Eq. (41):

$$V_s(z) = V_0^+ e^{-\alpha z} e^{-j\beta z} + V_0^- e^{\alpha z} e^{j\beta z} \quad (48)$$



Attenuation coefficient:  $\alpha$  [Np/m]

Phase constant:  $\beta (= \omega / v_p)$  [rad/m]

- Lossless case:  $R = G = 0, \alpha = 0, \gamma = j\beta = j\omega(LC)^{0.5}$ ,

$$v_p = 1 / (LC)^{0.5}$$

- Low loss case:  $R \ll \omega L, G \ll \omega C$  (but  $R \neq 0$  and  $G \neq 0$ )

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (41)$$

$$= j\omega\sqrt{LC} \left[ \left( 1 + \frac{R}{j\omega L} \right)^{1/2} \left( 1 + \frac{G}{j\omega C} \right)^{1/2} \right] \quad (50)$$

$$\leftarrow \sqrt{1+x} \cong 1 + \frac{x}{2} - \frac{x^2}{8} + \dots \quad (x \ll 1) \quad (51)$$

$$\gamma \cong j\omega\sqrt{LC} \left[ \left( 1 + \frac{R}{j2\omega L} + \frac{R^2}{8\omega^2 L^2} + \dots \right) \left( 1 + \frac{G}{j2\omega C} + \frac{G^2}{8\omega^2 C^2} + \dots \right) \right] \quad (52)$$

Since  $R \ll \omega L$ ,  $G \ll \omega C$ ,  $RG^2$ ,  $R^2G$  and  $R^2G^2$  can be negligible,

$$\begin{aligned}\gamma &= \alpha + j\beta \approx j\omega\sqrt{LC} \left[ \left( 1 + \frac{R}{j2\omega L} + \frac{R^2}{8\omega^2 L^2} \right) \left( 1 + \frac{G}{j2\omega C} + \frac{G^2}{8\omega^2 C^2} \right) \right] \\ &\approx j\omega\sqrt{LC} \left[ 1 + \frac{1}{j2\omega} \left( \frac{R}{L} + \frac{G}{C} \right) + \frac{1}{8\omega^2} \left( \frac{R^2}{L^2} - \frac{2RG}{LC} + \frac{G^2}{C^2} \right) \right] \quad (53)\end{aligned}$$

$$\alpha = j\omega\sqrt{LC} \left[ \frac{1}{j2\omega} \left( \frac{R}{L} + \frac{G}{C} \right) \right] = \frac{1}{2} \left( R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right) \quad (54a)$$

$$\begin{aligned}\beta &= \omega\sqrt{LC} \left[ 1 + \frac{1}{8\omega^2} \left( \frac{R^2}{L^2} - \frac{2RG}{LC} + \frac{G^2}{C^2} \right) \right] = \omega\sqrt{LC} \left[ 1 + \frac{1}{8} \left( \frac{R}{\omega L} - \frac{G}{\omega C} \right)^2 \right] \\ &= \omega\sqrt{LC} \left[ 1 + \frac{1}{8} \left( \frac{G}{\omega C} - \frac{R}{\omega L} \right)^2 \right] \quad (54b)\end{aligned}$$

- Phase velocity:  $v_p = \omega/\beta$

Signal velocity:  $v_g = d\omega / d\beta \quad \leftarrow \text{signal distortion}$

→ If signal is distortionless,  $\beta = \omega(LC)^{0.5}$  ( $\leftarrow R = G = 0$ )

- Characteristic impedance in case of low-loss line:

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{j\omega L(1+\frac{R}{j\omega L})}{j\omega C(1+\frac{G}{j\omega C})}} \approx \sqrt{\frac{L}{C}} \left[ \frac{1 + \frac{R}{j2\omega L} + \frac{R^2}{8\omega^2 L^2}}{1 + \frac{G}{j2\omega C} + \frac{G^2}{8\omega^2 C^2}} \right] \quad (55)$$

$$\begin{aligned}&\approx \sqrt{\frac{L}{C}} \left[ \left( 1 + \frac{R}{j2\omega L} + \frac{R^2}{8\omega^2 L^2} \right) \left( 1 - \frac{G}{j2\omega C} - \frac{G^2}{8\omega^2 C^2} \right) \right] \leftarrow \frac{1}{1+x} \approx 1-x \\ &\approx \sqrt{\frac{L}{C}} \left[ 1 + \frac{1}{2\omega^2} \left\{ \frac{1}{4} \left( \frac{R^2}{L^2} - \frac{G^2}{C^2} \right) - \frac{RG}{2LC} \right\} + \frac{j}{2\omega} \left( \frac{G}{C} - \frac{R}{L} \right) \right] \quad (56)\end{aligned}$$

[Ex. 10.3] Transmission line with  $G = 0$ ,  $R \neq 0$  and  $R \ll \omega L$

Characteristic impedance:

$$Z_0 = \sqrt{\frac{L}{C}} \left[ 1 + \frac{1}{2\omega^2} \left\{ \frac{1}{4} \left( \frac{R^2}{L^2} - \frac{G^2}{C^2} \right) - \frac{RG}{2LC} \right\} + \frac{j}{2\omega} \left( \frac{G}{C} - \frac{R}{L} \right) \right] \Big|_{G=0, R \ll \omega L}$$

$$\approx \sqrt{\frac{L}{C}} \left[ 1 + \frac{j}{2\omega} \left( -\frac{R}{L} \right) \right] \approx |Z_0| e^{j\theta}$$

where  $|Z_0| \approx \sqrt{L/C}$  and  $\theta = \tan^{-1}(-R / 2\omega L)$

## 10.8 Power Transmission and The Use of Decibels in Loss Characterization

- Consider the forward-propagating voltage and current term with some phase shifting.

$$P(z, t) = V(z, t)I(z, t) = |V_0| |I_0| e^{-2\alpha z} \cos(\omega t - \beta z) \cos(\omega t - \beta z + \theta) \quad (57)$$

- Time-averaged power  $\langle P \rangle$ :

$$\langle P \rangle = \frac{1}{T} \int_0^T |V_0| |I_0| e^{-2\alpha z} \cos(\omega t - \beta z) \cos(\omega t - \beta z + \theta) dt \quad (58)$$

$$= \frac{1}{2T} \int_0^T |V_0| |I_0| e^{-2\alpha z} [\cos(2\omega t - 2\beta z + \theta) + \cos(\theta)] dt \quad (59)$$

$$= \frac{1}{2} |V_0| |I_0| e^{-2\alpha z} \cos(\theta) = \frac{1}{2} \frac{|V_0|^2}{|Z_0|} e^{-2\alpha z} \cos(\theta) \quad [W] \quad (60)$$

where  $T = 2\pi/\omega$

- Another method to obtain the instantaneous power

$$\text{phasor voltage: } V_s(z) = V_0 e^{-\alpha z} e^{-j\beta z} \quad (61)$$

$$\text{phasor current: } I_s(z) = I_0 e^{-\alpha z} e^{-j\beta z} = \frac{V_0}{Z_0} e^{-\alpha z} e^{-j\beta z} \quad (62)$$

$$\text{where } Z_0 = |Z_0| e^{j\theta}$$

$$\langle P \rangle = \frac{1}{2} \operatorname{Re} \{ V_s I_s^* \} \quad (63) : \text{time averaged power}$$

$$\begin{aligned} &= \frac{1}{2} \operatorname{Re} \left\{ V_0 e^{-\alpha z} e^{-j\beta z} \frac{V_0^*}{|Z_0| e^{-j\theta}} e^{-\alpha z} e^{+j\beta z} \right\} \\ &= \frac{1}{2} \operatorname{Re} \left\{ \frac{V_0 V_0^*}{|Z_0|} e^{-2\alpha z} e^{j\theta} \right\} = \frac{1}{2} \frac{V_0 V_0^*}{|Z_0|} e^{-2\alpha z} \cos \theta \quad (64)(60) \end{aligned}$$

$$\langle P(z) \rangle = \frac{1}{2} \frac{V_0 V_0^*}{|Z_0|} \cos \theta \cdot e^{-2\alpha z} = \frac{1}{2} \frac{V_0 V_0^*}{|Z_0|} e^{-2\alpha z} \cos \theta \Big|_{z=0} e^{-2\alpha z} = \langle P(0) \rangle e^{-2\alpha z} \quad (65)$$

→  $V(z, t)$  and  $I(z, t) = f(e^{-\alpha z})$

$$\langle P \rangle = f(e^{-2\alpha z})$$

- Power decreasing ratio:

$$\frac{\langle P(z) \rangle}{\langle P(0) \rangle} = e^{-2\alpha z} = 10^{-\kappa \alpha z} \quad (66)$$

Setting  $\alpha z = 1$

$$e^{-2} = 10^{-\kappa} \Rightarrow \kappa = \log_{10}(e^2) = 0.869 \quad (67)$$

$$\begin{aligned} \text{Power loss (dB)} &= 10 \log_{10} \left[ \frac{\langle P(0) \rangle}{\langle P(z) \rangle} \right] = 10 \log_{10}(10^{\kappa \alpha z}) = 10(\kappa \alpha z) \\ &= 8.69 \alpha z \quad (68) \end{aligned}$$

$$\text{Power Loss (dB)} = 10 \log_{10} \left[ \frac{\frac{1}{2} \frac{|V_0|^2}{|Z_0|} e^{-2\alpha z} \cos \theta \Big|_{z=0}}{\frac{1}{2} \frac{|V_0|^2}{|Z_0|} e^{-2\alpha z} \cos \theta} \right]$$

$$= 20 \log_{10} \left[ \frac{|V_0(0)|}{|V_0(z)|} \right] \quad (69)$$

where  $|V_0(z)| = |V_0(0)| e^{-\alpha z}$

[Ex. 10.4] Insertion loss of line with a 20 m length: 2.0 dB

a) Power fraction:  $\frac{\langle P(20) \rangle}{\langle P(0) \rangle} = 10^{-0.2} = 0.63$


b) Power fraction at the midpoint:  $10^{-0.1} = 0.79$

c) Exponential attenuation coefficient:

$$\alpha = \frac{2.0 \text{ dB}}{(8.69 \text{ dB/Np})(20 \text{ m})} = 0.012 \text{ [Np/m]}$$
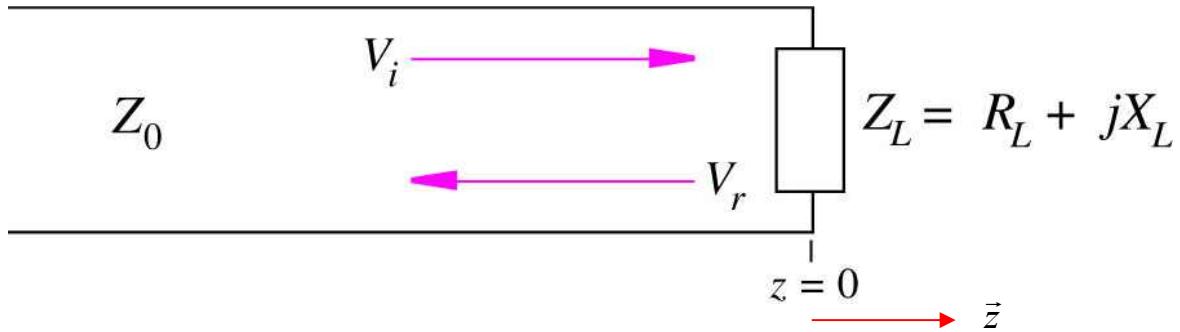
## 10.9 Wave Reflection at Discontinuities

- Voltage wave reflection from a complex load impedance



Characteristic impedance of line:  $Z_0$

Load impedance at  $z = 0$ :  $Z_L = R_L + jX_L$

- (Phase formed) Incident voltage wave on the load:

$$V_i(z) = V_{0i} e^{-\alpha z} e^{-j\beta z} \quad (70a)$$

Reflected voltage wave from the load:

$$V_r(z) = V_{0r} e^{+\alpha z} e^{+j\beta z} \quad (70b)$$

Phasor voltage at the load ( $@z = 0$ ):

$$V_L = V_{0i} + V_{0r} \quad (71)$$

- Phasor current through the load:

$$I_L = I_{0i} + I_{0r} = \frac{1}{Z_0} [V_{0i} - V_{0r}] = \frac{V_L}{Z_L} = \frac{1}{Z_L} [V_{0i} + V_{0r}] \quad (72)$$

- Reflection coefficient ( $\Gamma$ ):

$$\begin{aligned} \Gamma &\equiv \frac{V_{0r}}{V_{0i}} \\ \frac{V_{0i}}{Z_0} \left( 1 - \frac{V_{0r}}{V_{0i}} \right) &= \frac{V_{0i}}{Z_L} \left( 1 + \frac{V_{0r}}{V_{0i}} \right) \quad \leftarrow (72) \\ \frac{Z_L}{Z_0} (1 - \Gamma) &= (1 + \Gamma) \quad \Gamma \left( 1 + \frac{Z_L}{Z_0} \right) = \frac{Z_L}{Z_0} - 1 \\ \Gamma &= \frac{\frac{Z_L}{Z_0} - 1}{\frac{Z_L}{Z_0} + 1} = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\phi_r} \end{aligned} \quad (73)$$

- With Eq. (71) and (73)

$$V_L = V_{0i} + V_{0r} = V_{0i} + \Gamma V_{0i} \quad (74)$$

- Transmission coefficient ( $\tau$ ):


$$\tau \equiv \frac{V_L}{V_{0i}} = \frac{V_{0i} + \Gamma V_{0i}}{V_{0i}} = 1 + \Gamma = 1 + \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{2Z_L}{Z_L + Z_0} = |\tau| e^{j\phi_t} \quad (75)$$

- Circuit design goal: No reflection at load

$$\begin{aligned} \rightarrow \Gamma &= 0 \quad \rightarrow Z_L = Z_0 \\ \rightarrow (\text{Impedance}) &\text{ Matching !!} \end{aligned}$$

- Incident power with Eq. (64),  $z = L$  and line input  $z = 0$ :

$$\langle P_i \rangle = \frac{1}{2} \operatorname{Re} \left\{ \frac{V_0 V_0^*}{|Z_0|} e^{-2\alpha L} e^{j\theta} \right\} = \frac{1}{2} \frac{|V_0|^2}{|Z_0|} e^{-2\alpha L} \cos \theta \quad (76a)$$

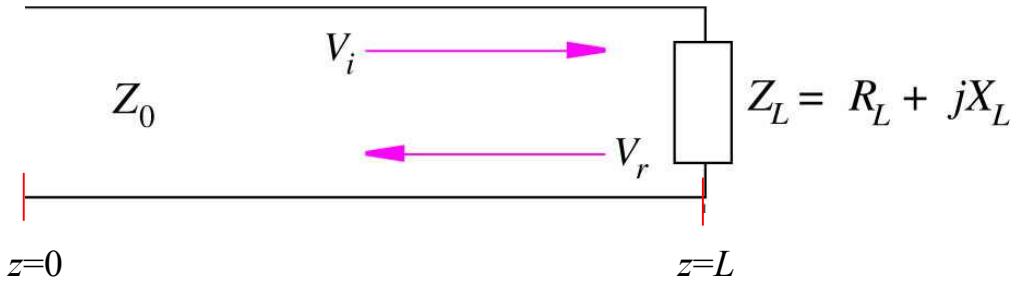

Reflected power:

$$\begin{aligned}\langle P_r \rangle &= \frac{1}{2} \operatorname{Re} \left\{ \frac{V_{0r} V_{0r}^*}{|Z_0|} e^{-2\alpha L} e^{j\theta} \right\} = \frac{1}{2} \operatorname{Re} \left\{ \frac{(\Gamma V_0)(\Gamma^* V_0^*)}{|Z_0|} e^{-2\alpha L} e^{j\theta} \right\} \\ &= |\Gamma|^2 \frac{1}{2} \frac{|V_0|^2}{|Z_0|} e^{-2\alpha L} \cos \theta = \langle P_i \rangle |\Gamma|^2\end{aligned}\quad (76b)$$

Reflected and transmitted power fraction at the load:

$$\frac{\langle P_r \rangle}{\langle P_i \rangle} = \Gamma \Gamma^* = |\Gamma|^2 \quad (77a)$$

$$\frac{\langle P_t \rangle}{\langle P_i \rangle} = 1 - |\Gamma|^2 \quad (77b)$$

- Reflection coefficient at the connection of two semi-infinite lines:

A diagram showing two semi-infinite transmission lines,  $Z_{01}$  and  $Z_{02}$ , connected at a junction point.

$$\Gamma = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} \quad (78)$$

[Ex. 10.5] Lossless line characteristic impedance:  $50 \Omega$

Load impedance:  $Z_L = 50 - j75 \Omega$

Incident Power: 100 mW

→ Reflection coefficient and transmitted power:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 - j75 - 50}{50 - j75 + 50} = \frac{-j75}{100 - j75} = 0.36 - j0.48 = 0.6e^{-j0.93}$$

$$\langle P_t \rangle = \left(1 - |\Gamma|^2\right) \langle P_i \rangle = [1 - (0.6)^2](100) = 64 \text{ mW}$$

[Ex. 10.6] Two lossy lines are jointed end-to-end.

Line 1:  $l_1 = 10 \text{ m}$ , loss rate = 0.2 dB/m

Line 2:  $l_2 = 15 \text{ m}$ , loss rate = 0.1 dB/m

Reflection coefficient at the junction:  $\Gamma = 0.3$

$\langle P_i \rangle = 100 \text{ mW}$

→ (a) dB loss of the joint:

$$L_j (\text{dB}) = 10 \log_{10} \left( \frac{1}{1 - |\Gamma|^2} \right) = 10 \log_{10} \left( \frac{1}{1 - 0.09} \right) = 0.41 \text{ dB}$$


Total loss of the link:

$$L_t (\text{dB}) = (0.2)(10) + 0.41 + (0.1)(15) = 3.91 \text{ dB}$$

(b) Output power:  $P_{\text{out}} = 100 \times 10^{-0.391} = 41 \text{ mW}$
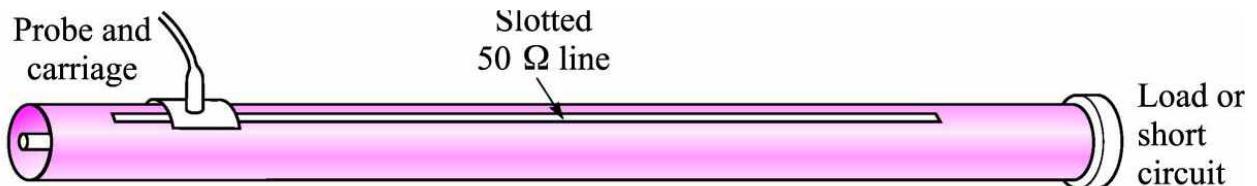
## 10.10 Voltage Standing Wave Ratio

- Coaxial slotted line
  - Ability to measure voltage amplitudes according to the position.
  - Ruler
  - Measuring items
    - 1) Maximum & minimum voltages
    - 2) Distance between the maximum (or minimum) and the next maximum (or minimum) voltage point



- Voltage standing wave ratio (VSWR):  
A ratio of maximum voltage amplitude to minimum voltage amplitude
- Case study
  - 1) Case 1: The slotted line is terminated by a matched impedance.
    - No reflected wave voltage
    - Same voltage amplitude in spite of different instantaneous voltage
  - 2) Case 2: The slotted line is terminated by an open or short circuit.
    - Reflected wave voltage
    - Different voltage amplitude

- Derivation of the (total) voltage at the specific point
  - Load position:  $z = 0$
  - All measuring point  $z < 0$
  - Input voltage wave amplitude:  $V_0$
  - Line impedance:  $Z_0$  (real), load impedance:  $Z_L$  (complex)
  - Total phasor voltage:

$$V_{sT}(z) = V_0 e^{-j\beta z} + \Gamma V_0 e^{j\beta z} \quad (79)$$

- Complex reflection coefficient

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\phi} \quad (80)$$

Ex.]  $Z_L = 0$  or  $Z_L$  (in case of only real value)  $< Z_0 \rightarrow \phi = \pi$

$Z_L$  (in case of only real value)  $> Z_0 \rightarrow \phi = 0$

$$\begin{aligned} V_{sT}(z) &= V_0 e^{-j\beta z} + \Gamma V_0 e^{j\beta z} = V_0 \left( e^{-j\beta z} + |\Gamma| e^{j(\beta z + \phi)} \right) \\ &= V_0 e^{j\phi/2} \left( e^{-j\beta z} e^{-j\phi/2} + |\Gamma| e^{j\beta z} e^{j\phi/2} \right) \quad (81) \\ &= V_0 (1 - |\Gamma|) e^{-j\beta z} + V_0 e^{j\phi/2} \left( e^{-j\beta z} e^{-j\phi/2} + |\Gamma| e^{j\beta z} e^{j\phi/2} \right) - V_0 (1 - |\Gamma|) e^{-j\beta z} \\ &= V_0 (1 - |\Gamma|) e^{-j\beta z} + V_0 e^{-j\beta z} + V_0 |\Gamma| e^{j(\beta z + \phi)} - V_0 e^{-j\beta z} + V_0 |\Gamma| e^{-j\beta z} \\ &= V_0 (1 - |\Gamma|) e^{-j\beta z} + V_0 |\Gamma| e^{j(\beta z + \phi)} + V_0 |\Gamma| e^{-j\beta z} \quad (82) \\ &= V_0 (1 - |\Gamma|) e^{-j\beta z} + V_0 |\Gamma| e^{j\phi/2} \left( e^{j\beta z} e^{j\phi/2} + e^{-j\beta z} e^{-j\phi/2} \right) \\ &= V_0 (1 - |\Gamma|) e^{-j\beta z} + 2V_0 |\Gamma| e^{j\phi/2} \cos(\beta z + \phi/2) \quad (83) \end{aligned}$$

- Real instantaneous form:

$$V(z, t) = \operatorname{Re}[V_{sT}(z)e^{j\omega t}] \\ = \underbrace{V_0(1 - |\Gamma|)\cos(\omega t - \beta z)}_{\text{traveling wave}} + \underbrace{2|\Gamma|V_0 \cos(\beta z + \phi/2)\cos(\omega t + \phi/2)}_{\text{standing wave}} \quad (84)$$

Standing wave: the reflected or back-propagated wave interferes with an equivalent portion of the incident wave to form a standing wave.

- Phasor-formed incident voltage with Eq. (79) and (80):

$$V_{sT}(z) = V_0 \left( e^{-j\beta z} + |\Gamma| e^{j(\beta z + \phi)} \right) \quad (85)$$

Location of the minimum voltage amplitude:

$$-\beta z_{\min} = \beta z_{\min} + \phi + \pi + 2m\pi \quad (m = 0, 1, 2, \dots)$$

$$z_{\min} = -\frac{1}{2\beta} \{\phi + (2m+1)\pi\} \quad (86)$$

Minimum voltage amplitude:

$$V_{sT}(z_{\min}) = V_0(1 - |\Gamma|) \quad (87)$$

In Eq. (84),

$$\begin{aligned} \omega t - \beta z_{\min} &= \omega t - \beta \times \left( -\frac{1}{2\beta} \{\phi + (2m+1)\pi\} \right) = \omega t + \frac{\phi}{2} + \frac{1}{2}(2m+1)\pi \\ \beta z_{\min} + \frac{\phi}{2} &= \beta \times \left( -\frac{1}{2\beta} \{\phi + (2m+1)\pi\} \right) + \frac{\phi}{2} = -\frac{1}{2}(2m+1)\pi \end{aligned}$$

Instantaneous voltage at the minimum point from Eq. (84)

$$\begin{aligned}
 V(z_{\min}, t) &= \underbrace{V_0(1 - |\Gamma|) \cos(\omega t - \beta z)}_{\text{traveling wave}} + \underbrace{2|\Gamma| V_0 \cos(\beta z + \phi/2) \cos(\omega t + \phi/2)}_{\text{standing wave}} \Bigg|_{z=z_{\min}} \quad (84) \\
 &= V_0(1 - |\Gamma|) \cos \left\{ \omega t + \frac{\phi}{2} + \frac{1}{2}(2m+1)\pi \right\} + 2|\Gamma| V_0 \cos \{(2m+1)\pi/2\} \cos(\omega t + \phi/2) \\
 &= V_0(1 - |\Gamma|) \{ \cos(\omega t + \phi/2) \cos \{(2m+1)\pi/2\} - \sin(\omega t + \phi/2) \sin \{(2m+1)\pi/2\} \} \\
 &\quad + 2|\Gamma| V_0 \cos \{(2m+1)\pi/2\} \cos(\omega t + \phi/2) \\
 &= \pm V_0(1 - |\Gamma|) \sin(\omega t + \phi/2) \quad (88)
 \end{aligned}$$

- Location of the maximum voltage amplitude:

$$-\beta z_{\max} = \beta z_{\max} + \phi + 2m\pi \quad (n = 0, \pm 1, \pm 2, \dots)$$

$$z_{\max} = -\frac{1}{2\beta}(\phi + 2m\pi) \quad (89)$$

Maximum voltage amplitude:

$$V_{sT}(z_{\max}) = V_0(1 + |\Gamma|) \quad (90)$$

In Eq. (84),

$$\begin{aligned}
 \omega t - \beta z_{\max} &= \omega t - \beta \times \left( -\frac{1}{2\beta} \right) (\phi + 2m\pi) = \omega t + \frac{\phi}{2} + m\pi \\
 \beta z_{\max} + \frac{\phi}{2} &= \beta \times \left( -\frac{1}{2\beta} \right) (\phi + 2m\pi) + \frac{\phi}{2} = -m\pi
 \end{aligned}$$

Instantaneous voltage at the maximum point from Eq. (84)

$$\begin{aligned}
 V(z_{\max}, t) &= \underbrace{V_0(1 - |\Gamma|) \cos(\omega t - \beta z)}_{\text{traveling wave}} + \underbrace{2|\Gamma|V_0 \cos(\beta z + \phi/2) \cos(\omega t + \phi/2)}_{\text{standing wave}} \Bigg|_{z=z_{\max}} \quad (84) \\
 &= V_0(1 - |\Gamma|) \left[ \cos \left\{ \omega t + \frac{\phi}{2} + m\pi \right\} + 2|\Gamma|V_0 \cos(-m\pi) \cos(\omega t + \frac{\phi}{2}) \right] \\
 &= V_0(1 - |\Gamma|) \left[ \cos(\omega t + \frac{\phi}{2}) \cos(m\pi) + \sin(\omega t + \frac{\phi}{2}) \sin(m\pi) \right] + 2|\Gamma|V_0 \cos \left( \omega t + \frac{\phi}{2} \right) \cos(m\pi) \\
 &= V_0(1 + |\Gamma|) \cos \left( \omega t + \frac{\phi}{2} \right) \cos(m\pi) = \pm V_0(1 + |\Gamma|) \cos \left( \omega t + \frac{\phi}{2} \right) \quad (91)
 \end{aligned}$$

\* Case studies

$$\begin{aligned}
 Z_L > Z_0 \quad &\& (Z_L, Z_0 : \text{real}) \Rightarrow \Gamma : \text{real positive} \Rightarrow \phi = 0 \\
 \Rightarrow \text{Voltage maximum at the load} \\
 \Rightarrow \text{Voltage maxima are found at } z_{\max} = -m\pi / \beta = -m\lambda / 2
 \end{aligned}$$

$$\begin{aligned}
 Z_L = 0 \Rightarrow \Gamma = -1 \Rightarrow \phi = \pi \\
 \Rightarrow \text{Voltage maxima are found at}
 \end{aligned}$$

$$\begin{aligned}
 z_{\max} &= -\frac{1}{2\beta}(\phi + 2m\pi) \Bigg|_{\phi=\pi} = -\frac{\pi}{2\beta}, -\frac{3\pi}{2\beta}, -\frac{5\pi}{2\beta}, \dots \leftarrow \frac{1}{\beta} = \frac{\lambda}{2\pi} \\
 &\stackrel{\text{or}}{=} -\frac{\lambda}{4}, -\frac{3\lambda}{4}, \dots
 \end{aligned}$$

Distance between the minima:  $\lambda/2$


$$\begin{aligned}
 z_{\min} &= -\frac{1}{2\beta}\{\phi + (2m+1)\pi\} \quad (86) \quad \leftarrow \frac{1}{\beta} = \frac{\lambda}{2\pi} \\
 &= -\frac{\phi}{2\beta} - \frac{(2m+1)\pi}{2\beta} = -\frac{\phi}{2\beta} - \frac{(2m+1)\lambda}{4}
 \end{aligned}$$

$$Z_L = 0 \Rightarrow \Gamma = -1 \Rightarrow \phi = \pi$$

$\Rightarrow$  The 1<sup>st</sup> voltage minimum is found at

$$z_{\min} = -\frac{1}{2\beta} \left\{ \phi + (2m+1)\pi \right\} \Bigg|_{\phi=\pi, m=-1} = 0$$

$$Z_L < Z_0 \Rightarrow \phi = \pi \Rightarrow z_{\min} = -\frac{1}{2\beta} \left\{ \phi + (2m+1)\pi \right\} \Bigg|_{\phi=\pi, m=-1} = 0$$

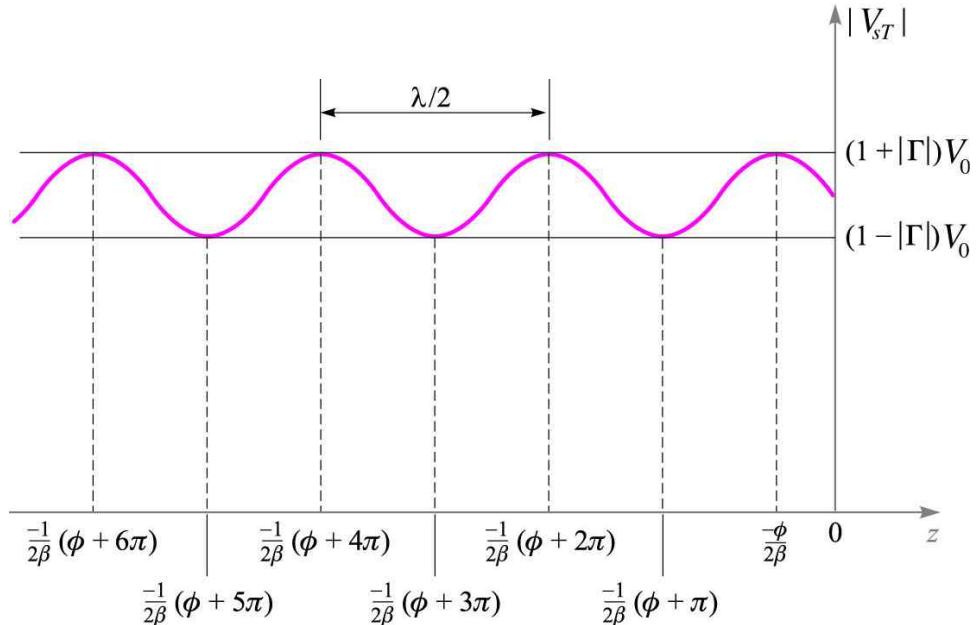

- Voltage standing wave ratio (VSWR):

$$S \equiv \frac{V_{sT}(z_{\max})}{V_{sT}(z_{\min})} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad (92)$$

[Ex. 10.7]  $50 \Omega$  slotted line measurement

- VSWR ( $s$ ) = 5, successive voltage maximum spacing = 15 cm
- Distance of the 1<sup>st</sup> maximum from load = 7.5 cm

$\Rightarrow \lambda/2 = 0.15, \lambda = 0.3$

$$f = c / \lambda = (3 \times 10^8) / 0.3 = 1 \times 10^9 = 1 \text{ GHz}$$

7.5 cm  $\leftrightarrow \lambda/4 \leftrightarrow$  Voltage minimum occurs at the load.

$$\leftrightarrow Z_L < Z_0$$

$$\leftrightarrow \phi = \pi$$


$$|\Gamma| = \frac{s-1}{s+1} = \frac{5-1}{5+1} = \frac{2}{3}$$

$$\Gamma = -\frac{2}{3} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_L = \frac{1}{5} Z_0 = 10 \Omega$$
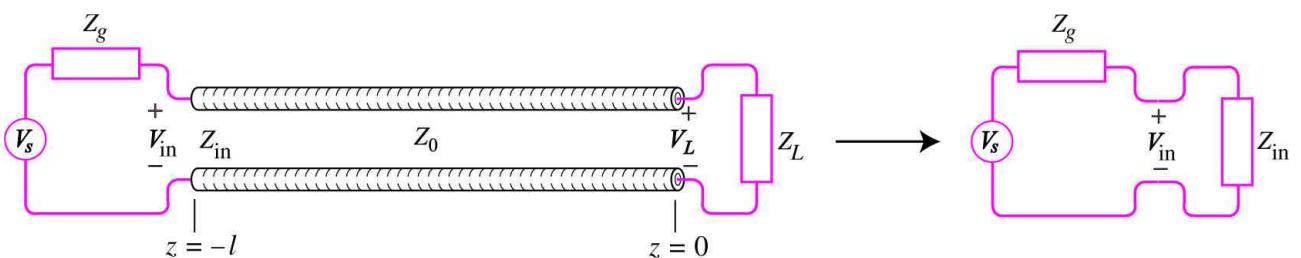
## 10.11 Transmission Lines of Finite Length

- Finite-length transmission line configuration and its equivalent circuit



- Total voltage in the line

$$V_{sT}(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad (93)$$

Where  $V_0^+$ : sum of all individual forward waves

$V_0^-$ : sum of all individual backward waves

- Total current in the line:

$$I_{sT}(z) = I_0^+ e^{-j\beta z} + I_0^- e^{j\beta z} \quad (94)$$

- Wave impedance  $Z_w(z)$ : a ratio of total phasor voltage to total phasor current at  $z = -l$

$$Z_w(z) \equiv \frac{V_{sT}(z)}{I_{sT}(z)} = \frac{V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}}{I_0^+ e^{-j\beta z} + I_0^- e^{j\beta z}} \quad (95) \leftarrow V_0^- = \Gamma V_0^+, I_0^+ = V_0^+ / Z_0, I_0^- = -V_0^- / Z_0$$

$$= \frac{V_0^+ e^{-j\beta z} + \Gamma V_0^+ e^{j\beta z}}{(V_0^+ e^{-j\beta z} - \Gamma V_0^+ e^{j\beta z}) / Z_0} = Z_0 \left[ \frac{e^{-j\beta z} + \Gamma e^{j\beta z}}{e^{-j\beta z} - \Gamma e^{j\beta z}} \right] \quad (96) \leftarrow \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= Z_0 \left[ \frac{(Z_L + Z_0)e^{-j\beta z} + (Z_L - Z_0)e^{j\beta z}}{(Z_L + Z_0)e^{-j\beta z} - (Z_L - Z_0)e^{j\beta z}} \right]$$

$$= Z_0 \left[ \frac{Z_L(e^{j\beta z} + e^{-j\beta z}) - Z_0(e^{j\beta z} - e^{-j\beta z})}{Z_0(e^{j\beta z} + e^{-j\beta z}) - Z_L(e^{j\beta z} - e^{-j\beta z})} \right]$$

$$= Z_0 \left[ \frac{Z_L(e^{j\beta z} + e^{-j\beta z})/2 - jZ_0(e^{j\beta z} - e^{-j\beta z})/j2}{Z_0(e^{j\beta z} + e^{-j\beta z})/2 - jZ_L(e^{j\beta z} - e^{-j\beta z})/j2} \right]$$

$$= Z_0 \left[ \frac{Z_L \cos(\beta z) - jZ_0 \sin(\beta z)}{Z_0 \cos(\beta z) - jZ_L \sin(\beta z)} \right] \quad (97) \leftarrow z = -l$$

$$= Z_0 \left[ \frac{Z_L \cos(\beta l) + jZ_0 \sin(\beta l)}{Z_0 \cos(\beta l) + jZ_L \sin(\beta l)} \right] \quad (98)$$

$$= Z_0 \left[ \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right]$$

- In case of  $\beta l = \frac{2\pi}{\lambda} \frac{m\lambda}{2} = m\pi$  ( $m = 0, 1, 2, \dots$ ),


$$Z_{in}(l = m\lambda/2) = Z_L \quad (99)$$

→ 부하(load)에서  $m\lambda/2$  떨어진 지점에서의 입력 임피던스는 부하 임피던스와 같음.

- In case  $\beta l = \frac{2\pi}{\lambda} (2m+1) \frac{\lambda}{4} = (2m+1) \frac{\pi}{2}$  ( $m = 0, 1, 2, \dots$ ),

$$Z_{in}(l = \lambda/4) = \frac{Z_0^2}{Z_L} \quad (100)$$

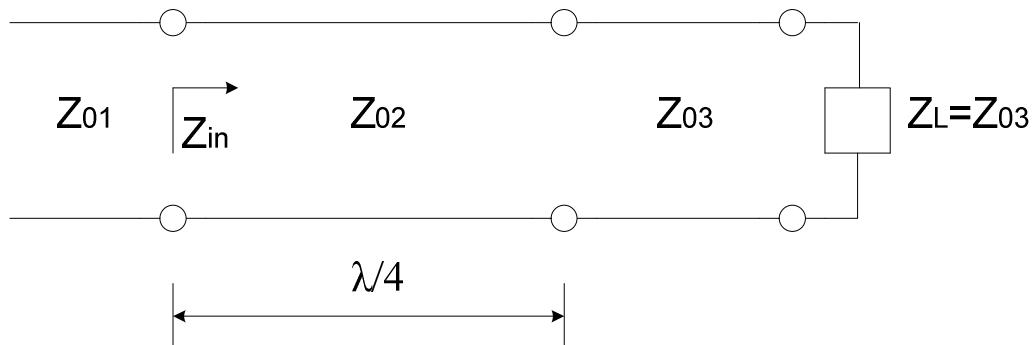- Joining two lines having different characteristic impedances



Input impedance to line 2:

$$Z_{in} = Z_{02} \frac{Z_{03} \cos(\beta_2 l) + j Z_{02} \sin(\beta_2 l)}{Z_{02} \cos(\beta_2 l) + j Z_{03} \sin(\beta_2 l)} \quad (101) \quad \leftarrow l = \frac{\lambda}{4}, \beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$


$$= \frac{Z_{02}^2}{Z_{03}} \quad (102)$$

Quarter-wave matching:

$$Z_{02} = \sqrt{Z_{01} Z_{03}} \quad (@l = (2m+1)\lambda/4) \quad (103)$$

## 10.12 Some Transmission Line Examples

[Ex. 1]

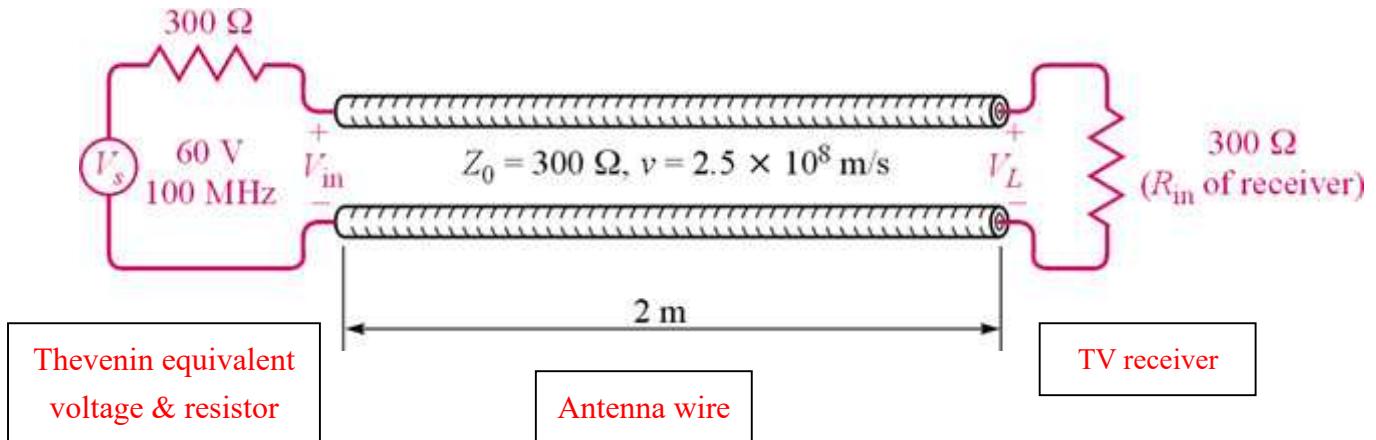

$$\bullet R_s = R_C = R_L \Rightarrow \text{Matched} \Rightarrow \Gamma = 0 \Rightarrow S = 1$$

$$\bullet \lambda = \frac{v}{f} = \frac{2.5 \times 10^8}{100 \times 10^6} = 2.5 \text{ [m]} \quad (\text{wavelength})$$

$$\bullet \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{2.5} = 0.8\pi \text{ [rad/m]} \quad (\text{phase constant})$$

$\alpha = 0$  (lossless assumption)

$$\bullet \beta l = 0.8\pi \times 2 = 1.6\pi \text{ [rad]} \quad (\text{electric length})$$

$$\Leftrightarrow \frac{1.6\pi}{2\pi} \times 360^\circ = 288^\circ \quad \Leftrightarrow \frac{1.6\pi}{2\pi} \times \lambda = 0.8\lambda$$

$$\bullet V_s = 60 \cos 2\pi 10^8 t \text{ [V]}$$

$$V_{in} = \frac{300}{300+300} V_s = 30 \cos 2\pi 10^8 t \text{ [V]}$$


$$V_L = 30 \cos(\omega t - \beta l) = 30 \cos(2\pi 10^8 t - 1.6\pi) \text{ [V]}$$

$$I_{\text{in}} = \frac{V_{\text{in}}}{Z_{\text{in}}} = \frac{30 \cos 2\pi 10^8 t}{300} = 0.1 \cos 2\pi 10^8 t \text{ [A]}$$

$$I_L = \frac{V_L}{Z_L} = 0.1 \cos(2\pi 10^8 t - 1.6\pi) \text{ [A]}$$

$$P_{\text{in}} = P_L = \frac{1}{2} \times 30 \times 0.1 = 1.5 \text{ [W]} \leftarrow P_L = 30 \cos(2\pi 10^8 t) \times 0.1 \cos(2\pi 10^8 t) = 3 \cos^2(2\pi 10^8 t)$$

[Ex. 2]

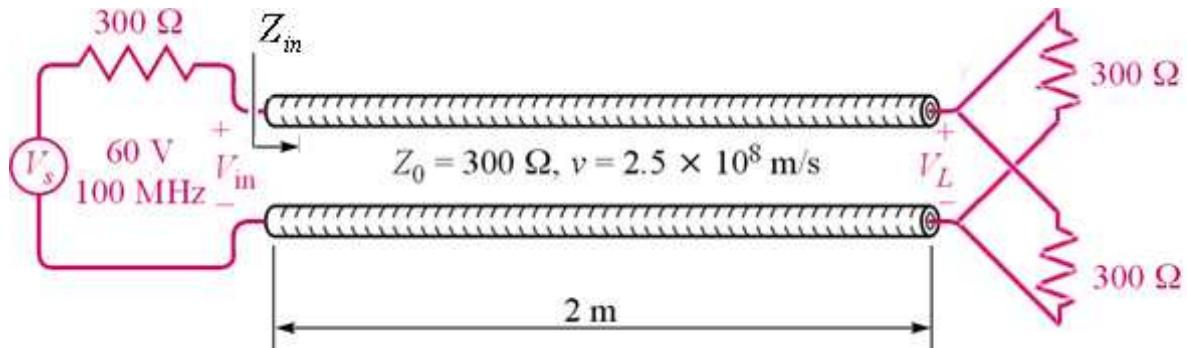

$$Z_{L1} = Z_{L2} = 300 \text{ } [\Omega], \quad Z_L = Z_{L1} // Z_{L2} = 150 \text{ } [\Omega]$$

$$\Gamma = \frac{150 - 300}{150 + 300} = -\frac{1}{3} = \frac{1}{3} \angle \pi, \quad s = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{4/3}{2/3} = 2$$

$$\begin{aligned} Z_{\text{in}} &= Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = 300 \frac{150 + j300 \tan 288^\circ}{300 + j150 \tan 288^\circ} = 300 \frac{150 - j923.3}{300 - j461.7} \\ &= 300 \frac{935.1 \angle -80.77^\circ}{550.6 \angle -56.99^\circ} = 509.5 \angle -23.78^\circ \\ &= 466.2 \angle -j205.4 \end{aligned}$$

capacitive  $\Rightarrow$  store electric field energy

$$I_{s,\text{in}} = \frac{V_{s,\text{in}}}{Z_s + Z_{\text{in}}} = \frac{60 \angle 0^\circ}{300 + (466.2 - j205.4)} = \frac{60 \angle 0^\circ}{766.2 - j205.4}$$

$$= \frac{60\angle 0^\circ}{793.3\angle -15^\circ} = 0.0756\angle 15^\circ \quad [\text{A}]$$

$$P_{\text{in}} = \frac{1}{2} |I_{s,\text{in}}|^2 \cdot \text{Re}(Z_{\text{in}}) = \frac{1}{2} \times 0.0756^2 \times 466.2 = 1.332 \quad [\text{W}]$$

$= P_L \quad \because \text{lossless transmission line}$

$< 1.5 \text{ [W]}$  (in previous example result)

$P_L$  is divided equally between two receivers.  $\Rightarrow 0.666 \text{ [W / receiver]}$

Voltage across the receiver:

$$\frac{1}{2} P_L = \frac{1}{2} \left( |V_{s,L}|^2 / R_L \right)$$

$$0.666 = \frac{1}{2} \frac{|V_{s,L}|^2}{300}$$

$$|V_{s,L}| = \sqrt{0.666 \times 600} = 19.99 \quad [\text{V}]$$

$< 30 \text{ [V]}$  (in previous example result)

• Voltage maxima:

$$-\beta z_{\max} = \frac{\phi}{2} + n\pi \quad (n = 0, \pm 1, \pm 2, \dots) \quad \text{cf.)} \quad -\beta z_{\min} = \frac{\phi}{2} + n\pi + \frac{\pi}{2}$$

$$\Gamma = |\Gamma| e^{j\phi}$$

$$\because \Gamma = -\frac{1}{3} = \frac{1}{3} \angle \pi$$

When  $\beta = 0.8\pi$ ,  $\phi = \pi$ ,  $\leftarrow$  region 2가 conductor이거나  
 $Z_L < Z_0$ 인 경우이므로

$$z_{\max} = -\frac{1}{0.8\pi} \left[ \frac{\pi}{2} + n\pi \right] = -0.625 - 1.25n$$

$$= -0.625 \quad \text{or} \quad -1.875 \quad \text{m}$$

$$z_{\min} = z_{\max} \pm \frac{\lambda}{4} \quad \leftarrow \quad \text{Fig 11.6}$$

$$= 0 \quad \text{or} \quad -1.25 \quad [\text{m}]$$

General conclusion: voltage minimum at the load if  $Z_L < Z_0$   
 in case  $Z_L$  and  $Z_0$  are real  
 voltage maximum at the load if  $Z_L > Z_0$   
 in case  $Z_L$  and  $Z_0$  are real

$$\bullet V_{s,\text{in}} = I_{s,\text{in}} Z_{\text{in}} = (0.0756 \angle 15^\circ) \times (509.5 \angle -23.78^\circ)$$

$$= 38.52 \angle -8.78^\circ$$

$$\text{cf.) } \begin{cases} |V_{s,L}| = 19.99 \text{ V} \approx 20 \text{ V} \quad \because Z_L < Z_0 \text{ 이므로.} \\ V_{s,\text{max}} = S \times V_{s,\min} = 2 \times 20 = 40 \text{ V} \\ V_{s,\text{in}} \text{ 은 } 40 \text{ V} \text{ 에 근접함} \quad \because L = 2 \text{ m} \text{ 이고 } \lambda = 2.5 \text{ m} \text{ 이므로} \\ (3/4)\lambda = 1.875 \text{ m} \text{ 로 } L \text{ 은 } (3/4)\lambda \text{ 근처이므로} \end{cases}$$

Near voltage maximum location

• Voltage at an arbitrary point on the line:

$$V_s = (e^{-j\beta z} + \Gamma e^{j\beta z}) V_0^+ \quad (104)$$

At  $z = -l$ , ( $z = -2 \text{ m}$ )

$$V_{s,\text{in}} = (e^{j\beta l} + \Gamma e^{-j\beta l}) V_0^+ \quad (105)$$

$$V_0^+ = \frac{V_{s,\text{in}}}{e^{j\beta l} + \Gamma e^{-j\beta l}} = \frac{38.52 \angle -8.78^\circ}{e^{j1.6\pi} - (1/3)e^{-j1.6\pi}} = \frac{38.52 \angle -8.78^\circ}{(0.309 - j0.957) - (0.103 + j0.317)}$$


$$= \frac{38.52 \angle -8.78^\circ}{0.206 - j1.268} = \frac{38.52 \angle -8.78^\circ}{1.285 \angle -80.77^\circ} = 29.98 \angle 71.99^\circ$$

At  $z = 0$ ,

$$V_{s,L} = (1 + \Gamma) V_0^+ = \frac{2}{3} \times 29.98 \angle 71.99^\circ = 19.99 \angle 71.99^\circ = 19.99 \angle -288.1^\circ$$

: Same result with the previous

[Ex. 10.8]

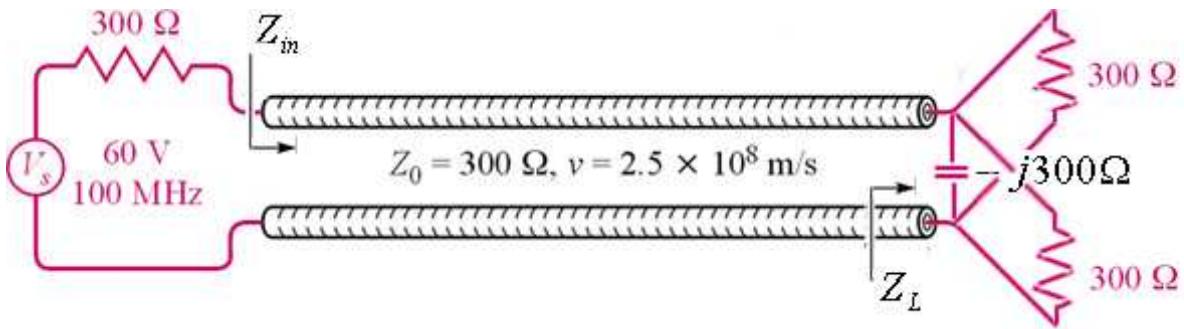

$$Z_L = \frac{150(-j300)}{150-j300} = \frac{-j300}{1-j2} = -j\frac{300}{5}(1+j2) = 120-j60 \quad \Omega$$

$$\Gamma = \frac{(120-j60)-300}{(120-j60)+300} = \frac{-180-j60}{420-j60} = \frac{189.7 \angle -161.6^\circ}{424.3 \angle -8.13^\circ} = 0.447 \angle -153.47^\circ$$

$$s = \frac{1+0.447}{1-0.447} = 2.62$$

⇒ Standing wave ratio is higher than example 2.

$$\begin{aligned} Z_{in} &= 300 \frac{(120-j60)+j300 \tan 288^\circ}{300+j(120-j60) \tan 288^\circ} = 300 \frac{(120-j60)+j300 \times (-3.08)}{300+j(120-j60)(-3.08)} \\ &= 300 \frac{120-j984}{115.2-j369.6} = 300 \frac{991.3 \angle -83^\circ}{387.1 \angle -72.7^\circ} \end{aligned}$$

$$= 768.3 \angle -10.3^\circ = 755.9 - j137.4$$


$$I_{s,\text{in}} = \frac{V_{Th}}{Z_{Th} + Z_{\text{in}}} = \frac{60}{300 + 755.9 - j137.4} = \frac{60}{1065 \angle -7.41^\circ} = 0.0563 \angle 7.41^\circ \text{ A}$$

$$P_{\text{in}} = \frac{1}{2} \times 0.0563^2 \times 755.9 = 1.198 \text{ W}$$

$$= P_L \quad (\because \text{Transmission line is lossless.})$$

→ Each load dissipates about 0.6 W and less than the previous Ex.

[Ex. 10.9]

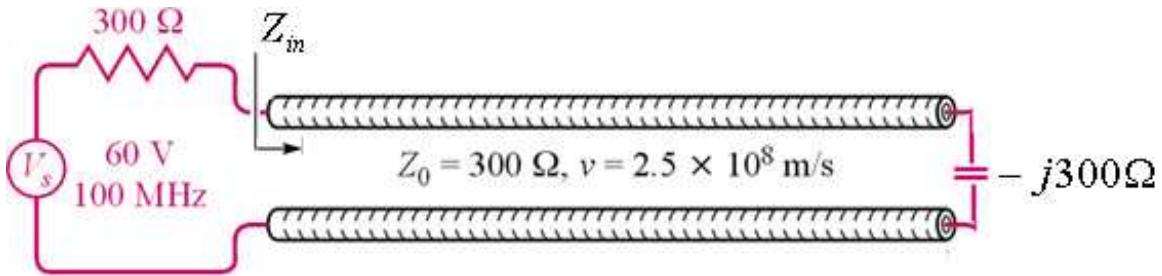

$$Z_L = -j300$$

$$\Gamma = \frac{-j300 - 300}{-j300 + 300} = \frac{\sqrt{2} \angle -135^\circ}{\sqrt{2} \angle -45^\circ} = 1 \angle -90^\circ$$


$$s = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \infty$$

$$Z_{\text{in}} = 300 \frac{(-j300) + j300 \tan 288^\circ}{300 + j(-j300) \tan 288^\circ} = 300 \frac{-j1224}{300 - 924} = -j588.5$$

⇒ No average power can be delivered.  $(\because \frac{1}{2} I_{s,\text{in}}^2 \cdot R_{\text{in}})$

## 10.13 Graphic Methods: The Smith Chart

- Polar coordinates of the Smith chart

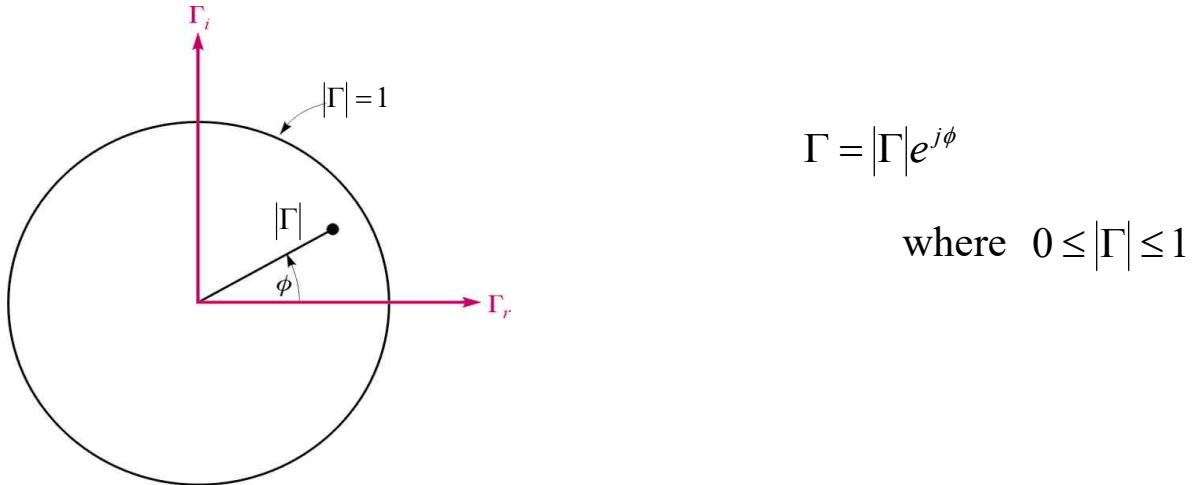

- Basic relationship

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (106)$$

Normalized load impedance

$$z_L = r + jx = \frac{Z_L}{Z_0} = \frac{R_L + jX_L}{Z_0}$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(Z_L/Z_0) - 1}{(Z_L/Z_0) + 1} = \frac{z_L - 1}{z_L + 1} = \Gamma_r + j\Gamma_i \quad (108)$$

$$z_L = \frac{1 + \Gamma}{1 - \Gamma} \quad (107)$$

$$\begin{aligned} &= \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i} = \frac{[(1 + \Gamma_r) + j\Gamma_i][(1 - \Gamma_r) + j\Gamma_i]}{(1 - \Gamma_r)^2 + \Gamma_i^2} \\ &= \frac{[(1 - \Gamma_r^2) - \Gamma_i^2] + j[\Gamma_i(1 - \Gamma_r) + \Gamma_i(1 + \Gamma_r)]}{(1 - \Gamma_r)^2 + \Gamma_i^2} \end{aligned}$$

$$= \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} + j \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} = r + jx \quad (109)$$

$$\therefore r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad (110)$$

$$x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad (111)$$

### 1) Real part

$$\frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} = r$$

$$(1 - \Gamma_r^2) - \Gamma_i^2 = r(1 - \Gamma_r)^2 + r\Gamma_i^2$$


$$\Gamma_r^2(r+1) - 2r\Gamma_r + \Gamma_i^2(r+1) = 1 - r$$

$$\Gamma_r^2 - \frac{2r}{1+r}\Gamma_r + \Gamma_i^2 = \frac{1-r}{1+r}, \quad \Gamma_r^2 - \frac{2r}{1+r}\Gamma_r + \left(\frac{r}{r+1}\right)^2 + \Gamma_i^2 = \frac{1-r}{1+r} + \left(\frac{r}{r+1}\right)^2$$

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \frac{1-r}{1+r} + \left(\frac{r}{r+1}\right)^2 = \frac{1}{(r+1)^2} \quad (112)$$

Constant  $r$ -circles: radius -  $\frac{1}{r+1}$

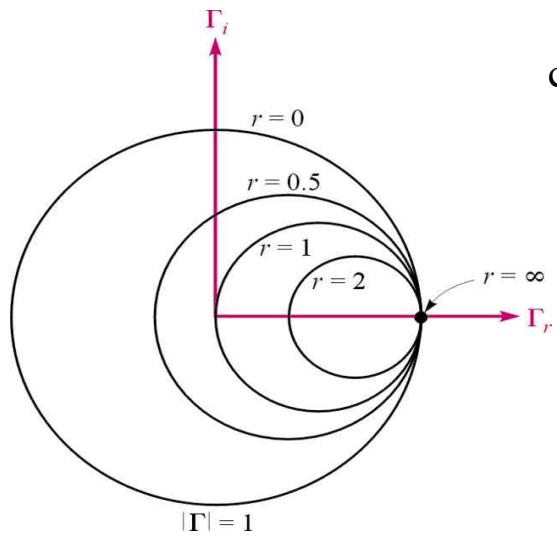center -  $\left(\frac{r}{r+1}, 0\right)$






## 2) Imaginary part

$$\frac{2\Gamma_i}{(1-\Gamma_r)^2 + \Gamma_i^2} = x$$

$$(\Gamma_r - 1)^2 + \Gamma_i^2 - \frac{2\Gamma_i}{x} = 0$$
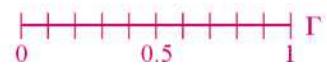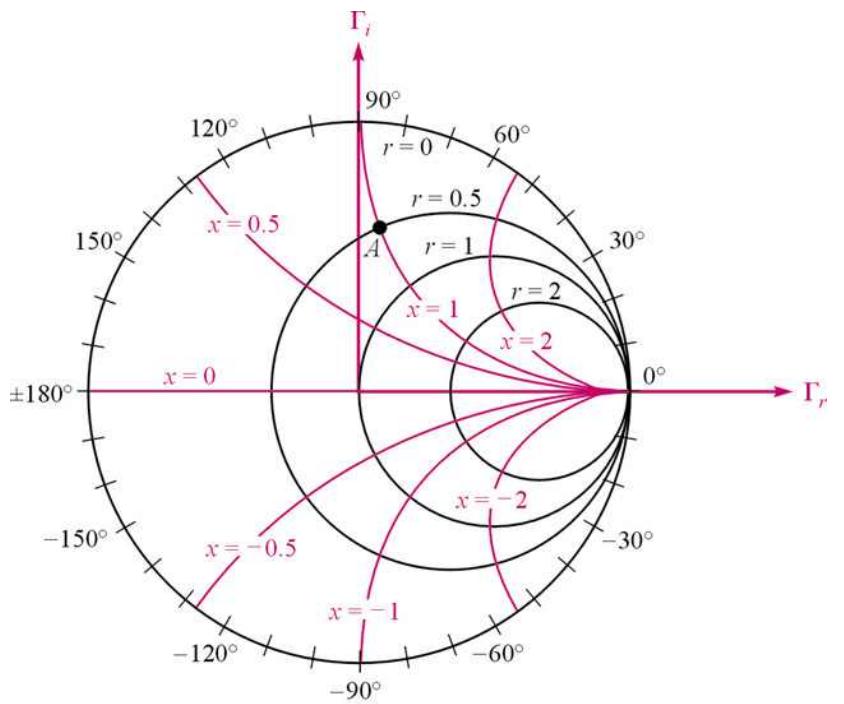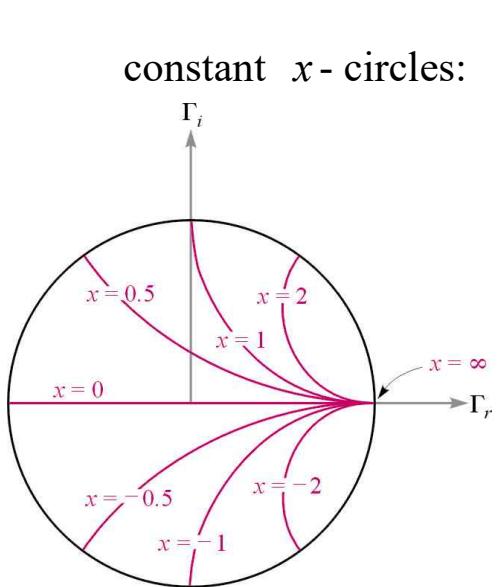
$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x} \right)^2 = \left( \frac{1}{x} \right)^2 \quad (113)$$



$$[\text{Ex.}] \quad Z_L = 25 + j50 \quad \rightarrow \quad z_L = 0.5 + j1$$

From the Smith chart,  $|\Gamma| = 0.62$ ,  $\phi = 83^\circ$

- Second scale on the circumference

$$V_s = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

$$I_s = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z})$$

$$\begin{aligned} z_{\text{in}} &= \frac{Z_{\text{in}}}{Z_0} = \frac{1}{Z_0} \cdot \frac{V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})}{(V_0^+/Z_0)(e^{-j\beta z} - \Gamma e^{j\beta z})} = \frac{e^{-j\beta z} + \Gamma e^{j\beta z}}{e^{-j\beta z} - \Gamma e^{j\beta z}} \leftarrow z = -l \\ &= \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} = \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} = \frac{1 + |\Gamma| e^{j(\phi - 2\beta l)}}{1 - |\Gamma| e^{j(\phi - 2\beta l)}} \quad (114) \end{aligned}$$

If  $l = 0$ ,

$$z_{\text{in}} = \frac{1 + \Gamma}{1 - \Gamma} = z_L$$

If  $z = -l$

$$z_{\text{in}} = \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} : \leftarrow (\Gamma e^{-j2\beta l} \leftarrow \Gamma)$$

(위 두 식을 비교하면,  $\Gamma$  대신에  $\Gamma e^{-j2\beta l}$ 을 대입한 것과 동일. 부하에서  $l$ 만큼 떨어진 지점에서의 입력 임피던스는 반사계수 평면에서 부하에서의 반사계수  $\Gamma$ 를 전기각  $-2\beta l$  만큼 신호원 방향으로 회전시켜 측정하는 것과 같음)

- As we proceed from the load  $z_L$  to the input impedance  $z_{in}$ , we move toward the generator a distance  $l$  and move through a clockwise angle of  $2\beta l$  on the Smith chart.
- Since the magnitude of  $\Gamma$  stays constant, the movement toward the source is made along a constant-radius circle  
( $\because$  전송선로가 lossless 이므로)

( $l$  만큼의 물리적 위치 변화에  $2\beta l$  만큼의 위상 변화를 가져옴. 따라서 부하에서  $l = \lambda/2$  떨어진 지점은  $2\beta l = 2\pi$  가 되어 부하와 동일한 임피던스를 갖게 됨. 동일지점.  $\Rightarrow$  외곽 테두리에 반파장 을 명시.)

[Ex. 10.10]

$$Z_L = 25 + j50 \quad \Omega$$

$$z_L = 0.5 + j1 \rightarrow \text{point A}$$


$\lambda = 2 \text{ m}$  일 때 load로부터 60 cm 떨어진 곳의 입력 임피던스:

$$\frac{l}{\lambda} = \frac{0.6}{2} = 0.3\lambda$$

$$0.135\lambda + 0.3\lambda = 0.435\lambda \rightarrow \text{point B}$$

$$\therefore z_{in} = 0.28 - j0.4,$$

$$Z_{in} = 14 - j20$$

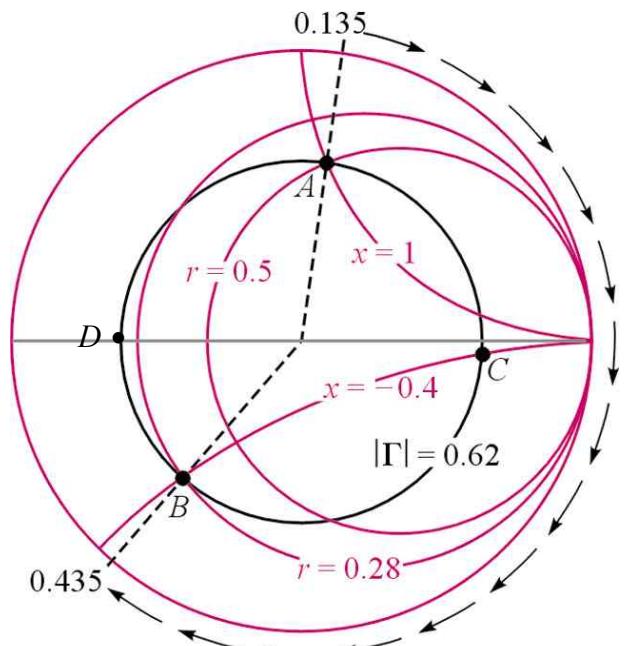

- Voltage maxima: @wtg = 0.25      wtg : wavelength toward generator  
 $\therefore$  point C ( $\because R_L > Z_0$ , pure resistance )

- Voltage minima: @  $\text{wtg} = 0$  or  $0.5$
- $\therefore$  point D ( $\because R_L < Z_0$ , pure resistance)


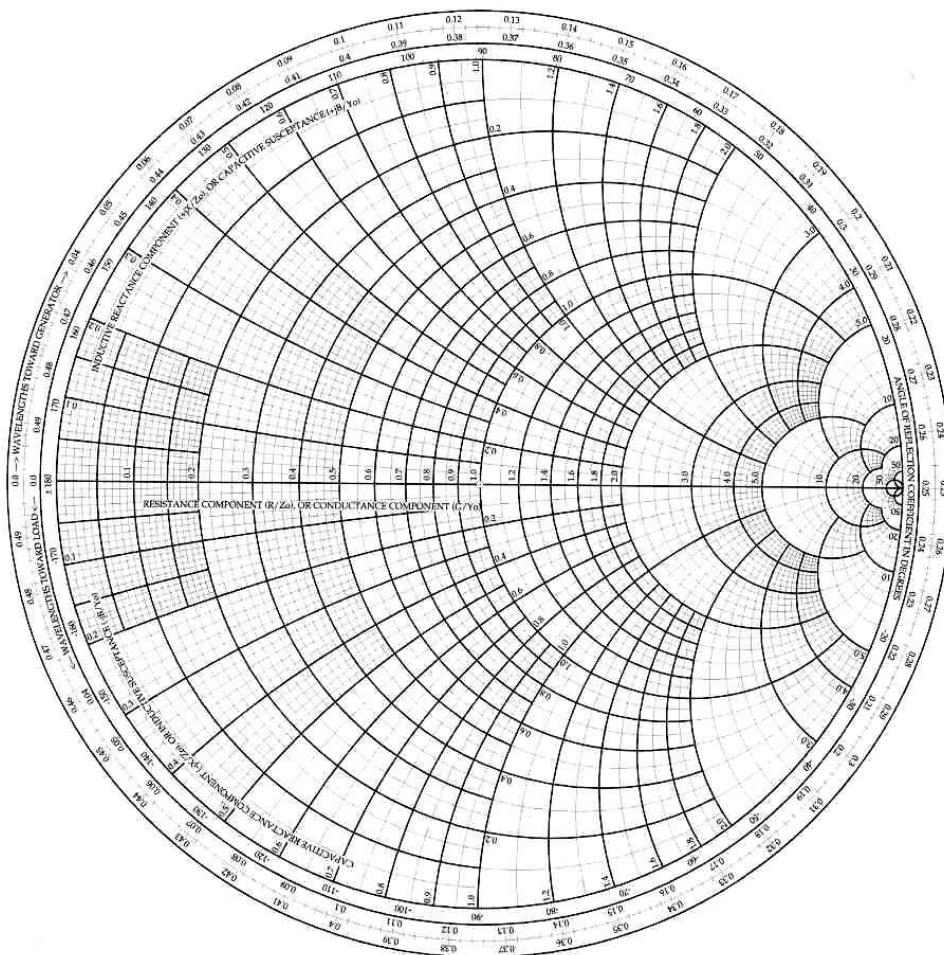




Figure 10.13 A photographic reduction of one version of a useful Smith chart.

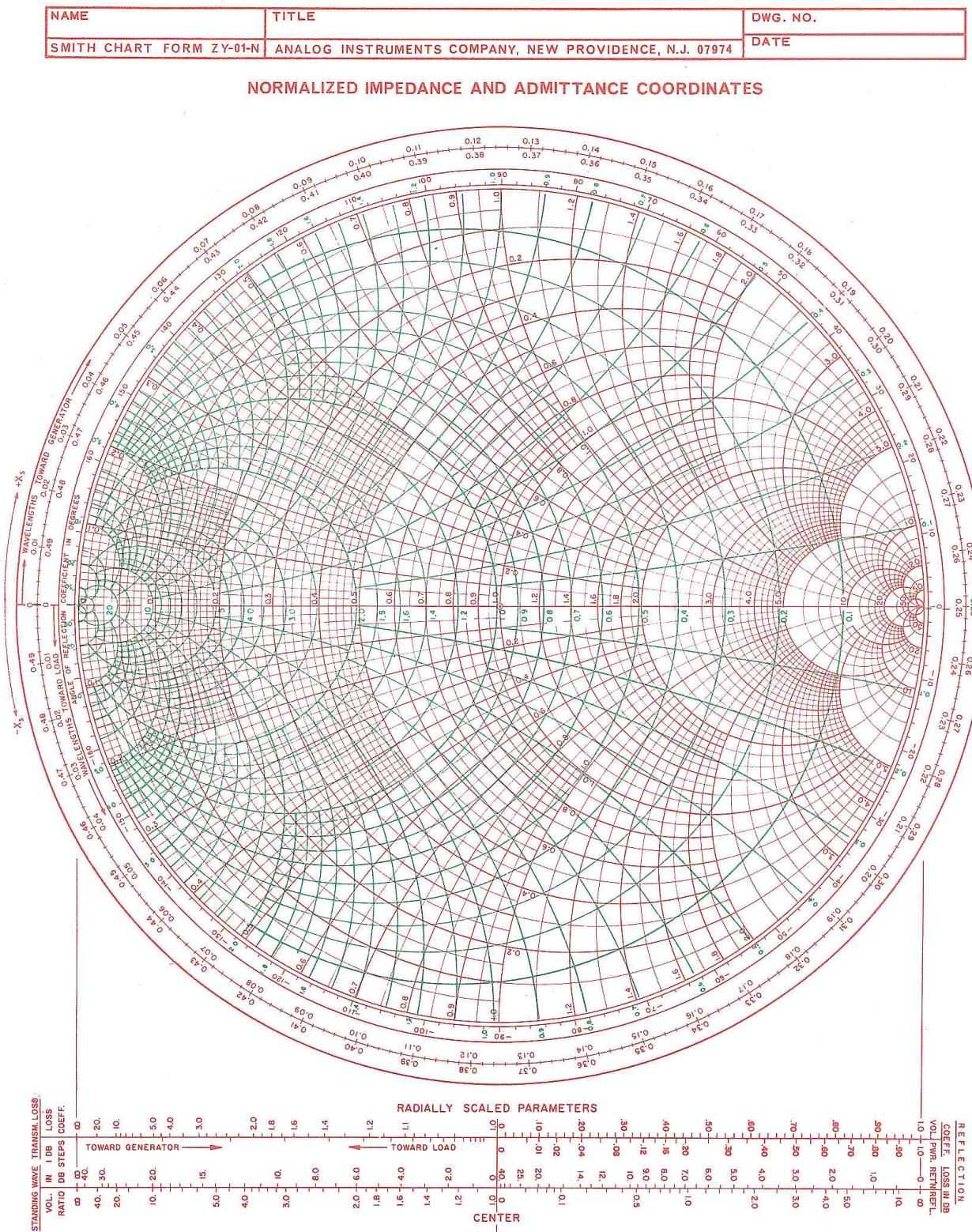- Normalized Impedance and Admittance Coordinates


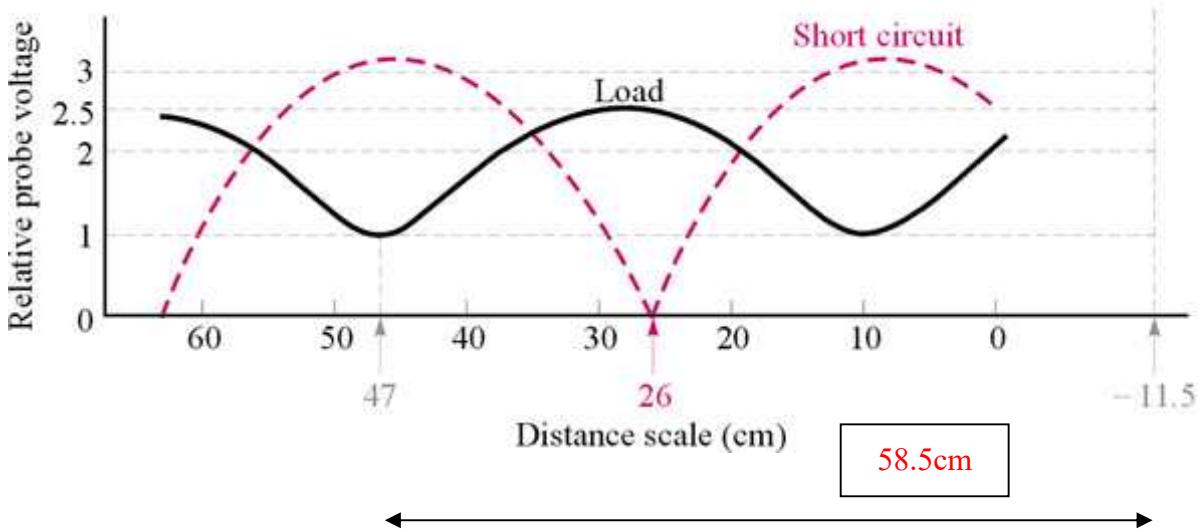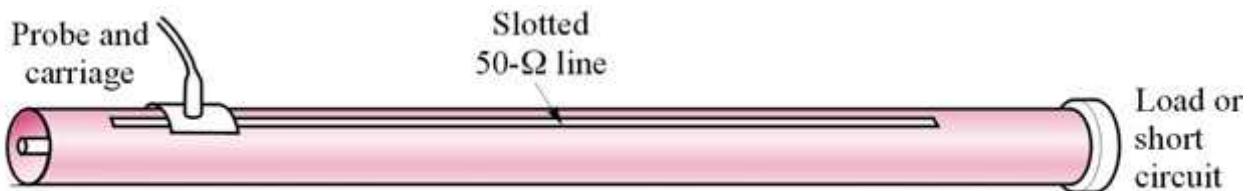
## [Ex.] The determination of load impedance

- ①  $s = 2.5$ , operating freq. = 400 MHz  $\Rightarrow \lambda = 75$  cm
- ② The carriage moves indicates that a minimum occurs at 47 cm
- ③ Replace load with a short circuit
- ④ Repeat step ②. Minimum at 26cm.
- ⑤ Short circuit locates one half-wavelength away and this is  
load location :  $26 - 37.5 = -11.5$  cm



- ⑥ The minimum is  $47.0 - (-11.5) = 58.5$  cm from the load.  
(load를 달고 시험할 때 minimum point 가 load로부터 58.5 cm 이격)
- ⑦ The maximum is  $58.5 - \left(\frac{3}{4} \times 75\right) = 58.5 - 56.25 = 2.25$  cm from the load.

(47 cm 지점(= load로부터 58.5 cm지점)에서  $\lambda/2$  이격되면 또 minimum. 다시  $\lambda/4$  이격하면 maximum.)

$$\textcircled{8} \text{ So } 2.25 \text{ cm} \rightarrow \frac{2.25}{75} = 0.03\lambda$$

$$\textcircled{9} \quad |\Gamma| = \frac{s-1}{s+1} = \frac{1.5}{3.5} = 0.4258$$

$$\textcircled{10} \quad z_L = 2.1 + j0.8 \quad \rightarrow \quad Z_L = 105 + j40$$


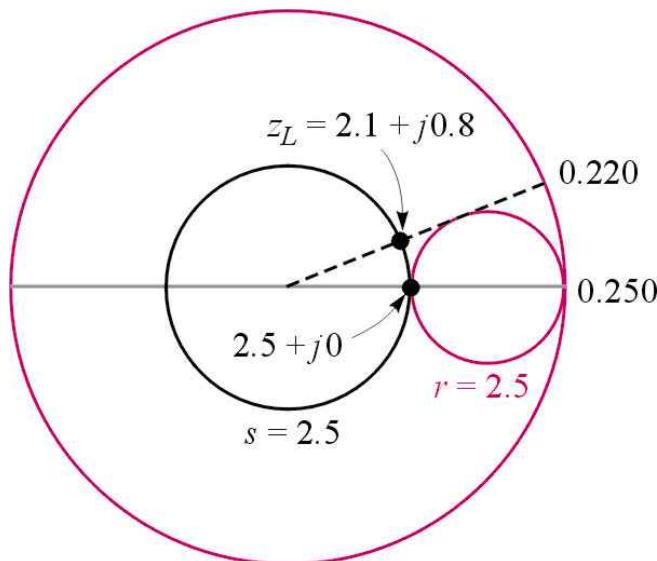


Figure 10.16

If  $z_{in} = 2.5 + j0$  on a line 0.03 wavelength long, then

$$z_L = 2.1 + j0.8$$

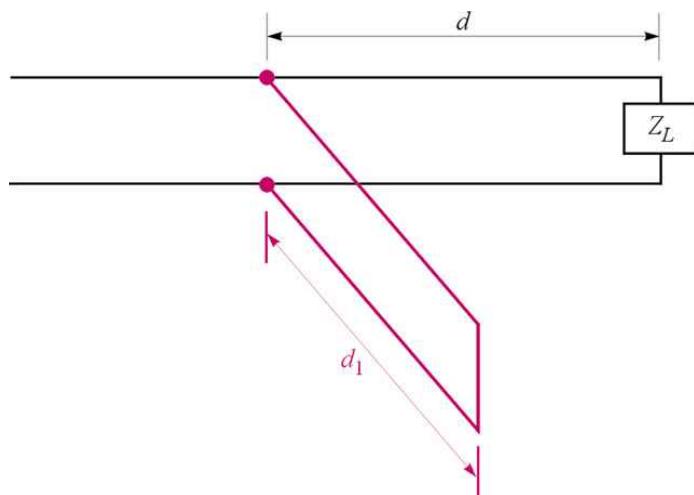[Ex.] Match the above load to the  $50 \Omega$  by placing a short-circuited stub of length  $d_1$  at a distance  $d$  from the load.



- Adding one-quarter wavelength ( $\lambda/4$ ) to  $Z_{in}$ . ( $z_{in}$ )

$$z_{in}' = \frac{z_{in} + j \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}}{1 + j z_{in} \tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}} = \frac{1}{z_{in}} = y_{in}$$

(load 임피던스를  $180^\circ$  rotation시키면 load admittance 와 동일)

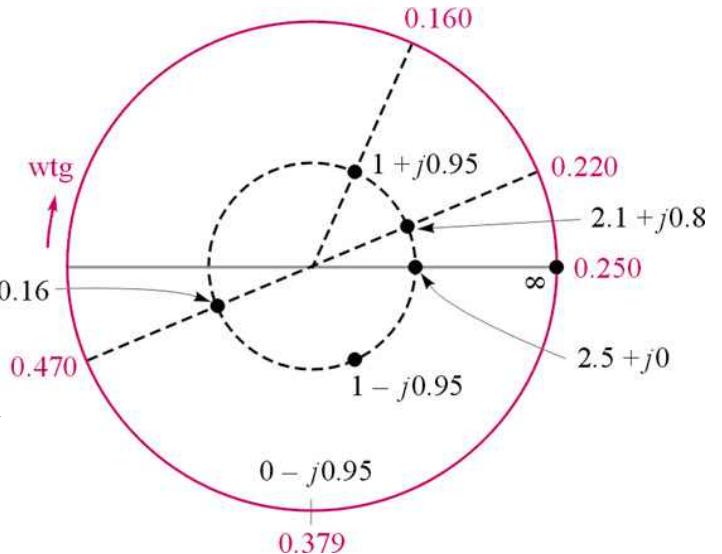


Figure 10.18

A normalized load  $z_L = 2.1 + j0.8$  is matched by placing a 0.129-wavelength short-circuited stub 0.19 wavelength from the load.

- Target:  $y_{in} = 1 + j0 \rightarrow z_{in} = 1$



- $y_L = 0.41 - j0.16$

- Moving toward generator by  $0.16\lambda + (0.5 - 0.47)\lambda = 0.19\lambda$

$$\Rightarrow d = 0.19 \times 75 \text{ cm} = 14.25 \text{ cm}$$

$$\Rightarrow y_{in}' = 1 + j0.95$$

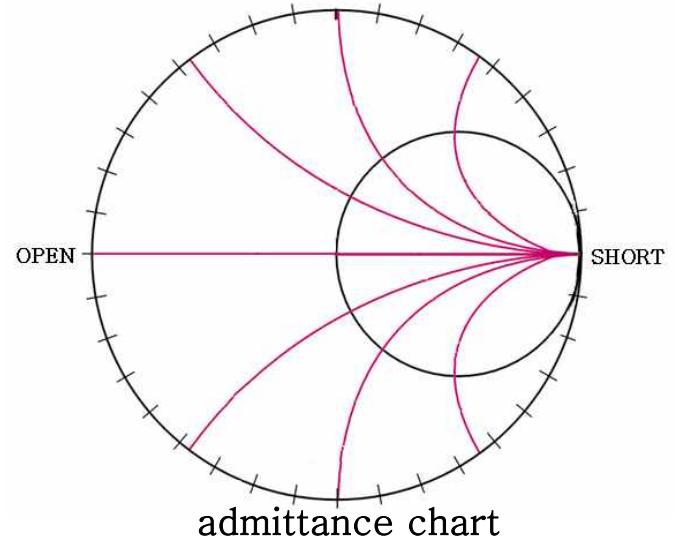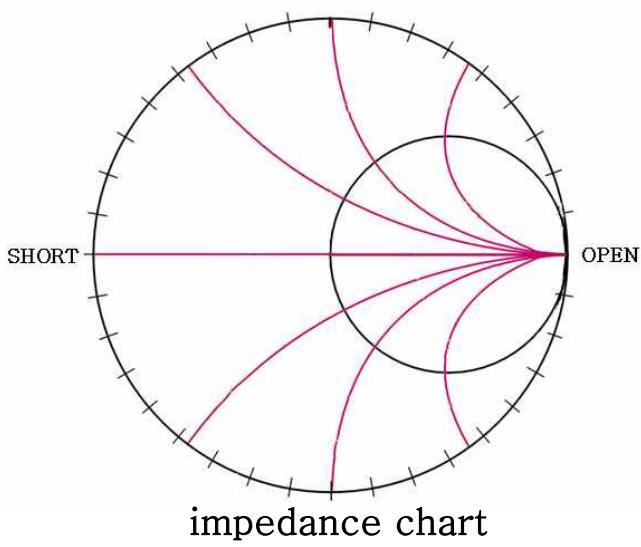- $y_{in}'' = 0 - j0.95 \rightarrow (0.379 - 0.25)\lambda = 0.129\lambda$  short stub.



$$0.129\lambda \rightarrow d_1 = 0.129 \times 75 \text{ cm} = 9.675 \text{ cm}$$

$$\therefore y_{in} = y'_{in} + y''_{in} = (1 + j0.95) + (-0.95\lambda) = 1 \quad (\text{Matching})$$