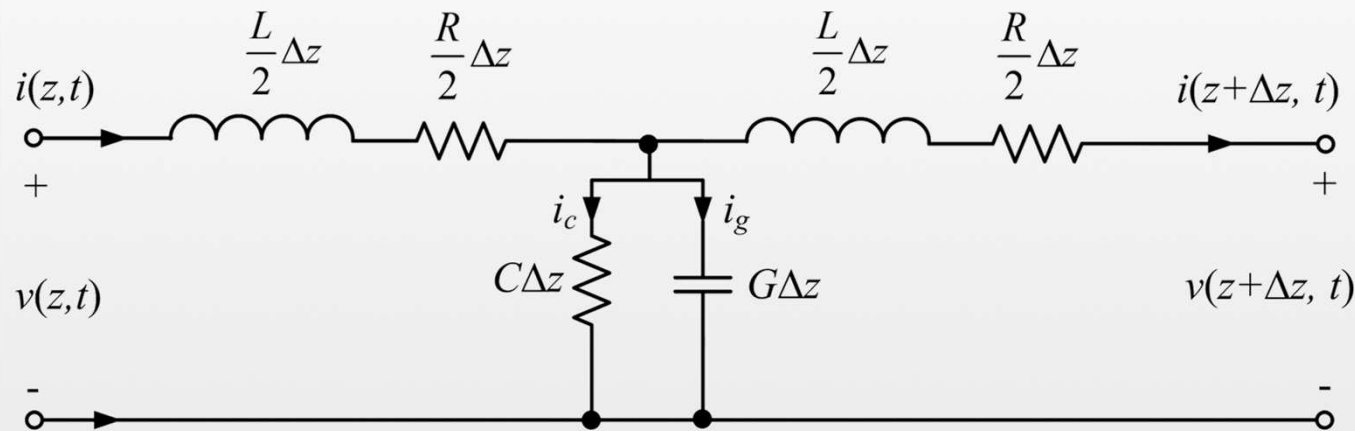


Chapter 2

Transmission Line

Prof. Jeong, Yongchae



Learning Objectives

- Learn limitation of low frequency circuit elements in microwave frequency.
- Learn general transmission line characteristics.
- Learn operation of terminated lossless transmission line


Learning contents

- Frequency dependance of microwave components
- Wave equations of transmission Line
- Terminated lossless transmission lines


1 Frequency Dependence of Microwave Components

- General lumped elements (R , L , C , etc.) frequency dependent characteristics


- Inductor

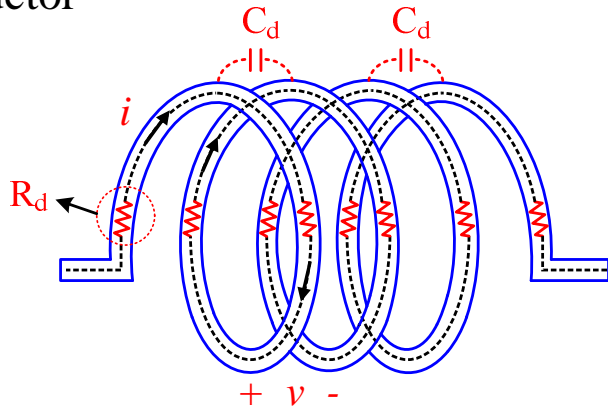

Coil inductor

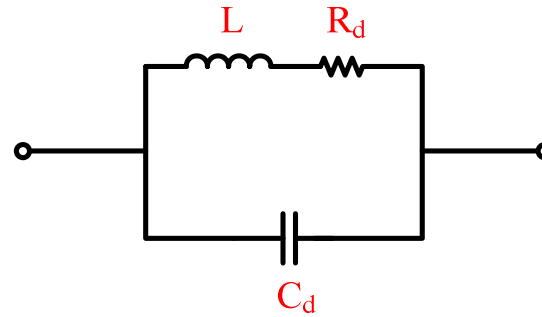

Equivalent circuit

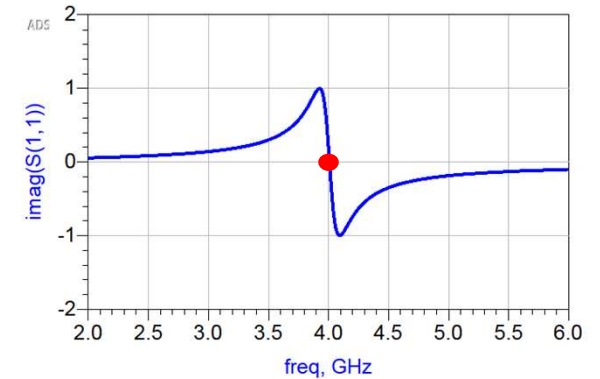

Electrical characteristic

$$\phi = Li, \quad v = \frac{d\phi}{dt} = L \frac{di}{dt}$$


$$R = \frac{L}{\sigma S}, \quad Q = Cv$$

- **Self resonance frequency (SRF)**: a resonant frequency where the reactive component is zero. ($\text{Im}(Z) = 0$)


➔ It is not easy to fabricate inductor on microwave frequency range.

1 Frequency Dependence of Microwave Components



- Capacitor

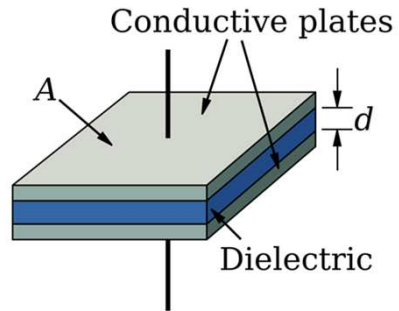

Typical capacitor coil inductor

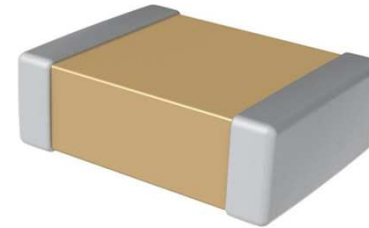

Chip capacitor

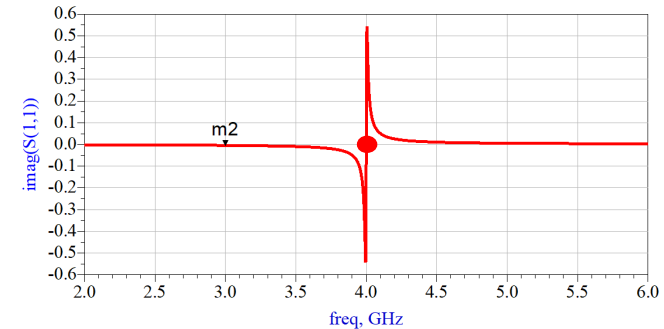
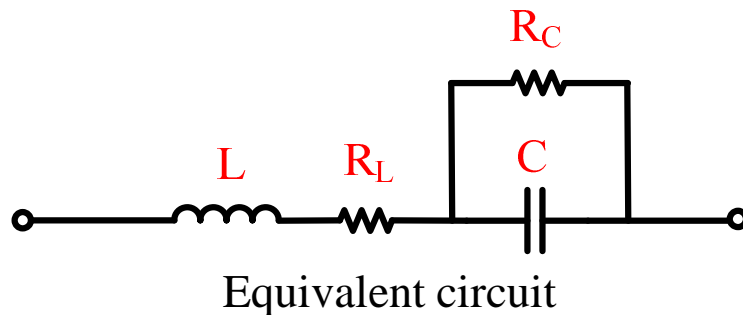


→ Even though relatively easy to fabricated than inductor, it is also not easy to fabricated capacitor in microwave frequency.

⊕ *How to realize R, L, and C on the microwave/millimeter frequency ranges?*

2 Wave Equations of Transmission Line

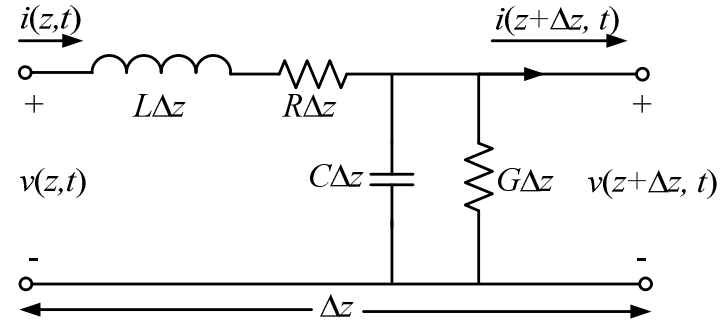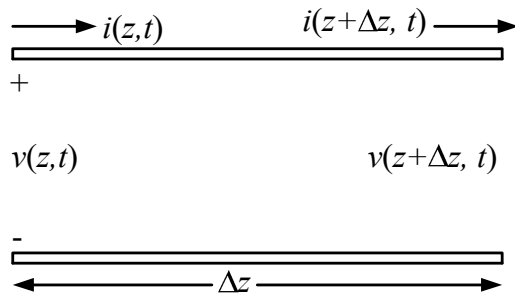- Two-wire line as typical transmission line and its equivalent circuits for short piece length (Δz)




- Low pass characteristics

$$\phi = Li, \quad v = \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$Q = Cv, \quad i = \frac{dQ}{dt} = C \frac{dv}{dt}$$
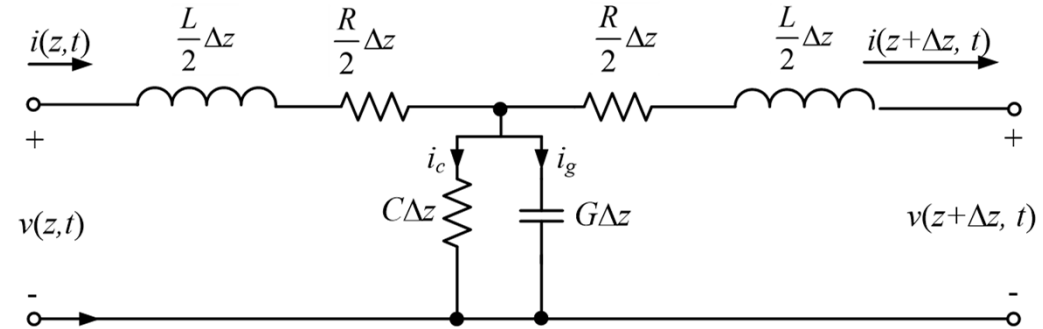
$$R = \frac{L}{\sigma S}, \quad C = \frac{\epsilon S}{d} \leftarrow \epsilon = \epsilon' - j\epsilon''$$



- L : series inductance per unit length [H/m]
- C : shunt capacitance per unit length [F/m]

- R : series resistance per unit length [Ω /m]
- G : shunt conductance per unit length [S/m or \bar{U} /m]


2 Wave Equations of Transmission Line

- Kirchhoff's voltage law

$$v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0 \quad (1)$$

Kirchhoff's current law
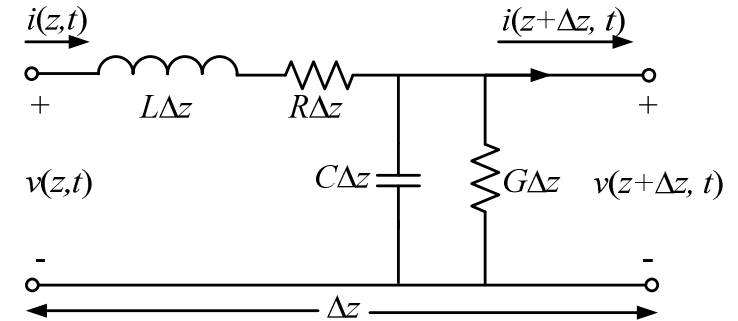
$$i(z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - G\Delta z v(z + \Delta z, t) - i(z + \Delta z, t) = 0 \quad (2)$$



- Dividing (2.1a) and (2.1b) by Δz and taking the limit as $\Delta z \rightarrow 0$:

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = \frac{\partial v(z, t)}{\partial z} = -L \frac{\partial i(z, t)}{\partial t} - Ri(z, t)$$

$$\lim_{\Delta z \rightarrow 0} \frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} = \frac{\partial i(z, t)}{\partial z} = -C \frac{\partial v(z, t)}{\partial t} - Gv(z, t)$$

- By assuming sinusoidal steady state condition, time domain forms can be changed cosine-based **phasor forms**.

$$\frac{dV(z)}{dz} = -(R + j\omega L)I(z) \quad (3) \quad \frac{dI(z)}{dz} = -(G + j\omega C)V(z) \quad (4)$$

$$\text{cf.}) \quad v(z, t) \leftrightarrow V(z)$$

$$i(z, t) \leftrightarrow I(z)$$

2 Wave Equations of Transmission Line

- By differentiating (3) with (4)

$$\frac{d^2V(z)}{dz^2} = -(R + j\omega L) \frac{dI}{dz} = (R + j\omega L)(G + j\omega C)V(z) = \gamma^2 V(z)$$

$$\frac{d^2V(z)}{dz^2} - \gamma^2 V(z) = 0 \quad (5)$$

By same manner

$$\frac{d^2I(z)}{dz^2} - \gamma^2 I(z) = 0 \quad (6)$$

where $\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} = f(\omega)$: complex **propagation** constant
 α : attenuation constant, β : phase constant


- Traveling wave equations on space domain:

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z} \quad (7)$$

$$I(z) = I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z} \quad (8)$$

where $e^{-\gamma z}$: wave propagation for +z direction (or forward direction)

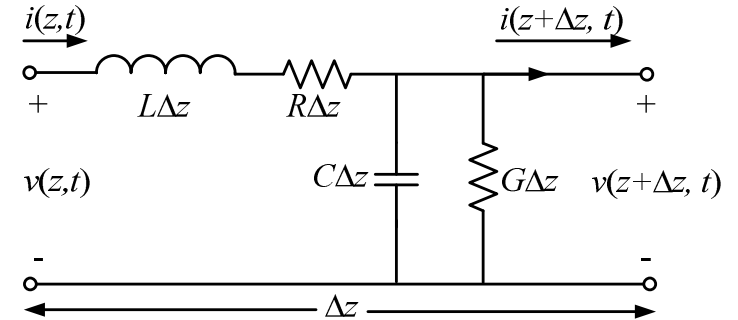$e^{\gamma z}$: wave propagation for -z direction (or backward direction)




2 Wave Equations of Transmission Line

- From (3) and (4),

$$I(z) = -\frac{1}{R + j\omega L} \frac{dV(z)}{dz} = \frac{\gamma}{R + j\omega L} [V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z}] = I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z}$$
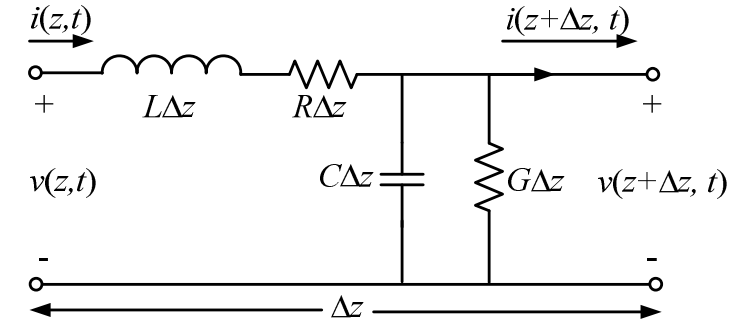
$$I_o^+ = \frac{\gamma}{R + j\omega L} V_o^+ \quad I_o^- = -\frac{\gamma}{R + j\omega L} V_o^-$$



- Characteristic impedance: a ratio of voltage wave to current wave

$$Z_0 = \frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-} = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (9) \quad \leftarrow \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

- Voltage-current combined current waveform

$$I(z) = \frac{V_o^+}{Z_0} e^{-\gamma z} - \frac{V_o^-}{Z_0} e^{\gamma z} = I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z} \quad (10)$$

- Sinusoidal voltage wave can be recovered by using $v(z, t) = \text{Re}[V(z)e^{j\omega t}]$ and $\gamma = \alpha + j\beta$.

$$v(z, t) = |V_o^+| \cos(\omega t - \beta z + \phi^+) e^{-\alpha z} + |V_o^-| \cos(\omega t + \beta z + \phi^-) e^{\alpha z}$$

where ϕ^\pm : phase angle of voltage wave V_o^\pm ex.) $V_o^+ = |V_o^+| e^{j\phi^+}$

2 Wave Equations of Transmission Line

- Wavelength (: distance between consecutive corresponding points of same phase (2π)) on transmission line:

$$\lambda = \frac{2\pi}{\beta} \quad \left[\frac{\text{rad}}{\text{rad/m}} \right] = [\text{m}] \quad (11)$$

- Phase velocity (rate at the wave propagates in any medium) on transmission line:

$$v_p = \frac{\lambda}{t} = \frac{2\pi f}{\beta} = \frac{\omega}{\beta} = f\lambda \quad [\text{m/sec}] \quad (12)$$


- For lossless transmission line (@ $R = G = 0$),

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \Big|_{R=G=0} = j\omega\sqrt{LC} \quad (= \alpha + j\beta) \quad \Leftrightarrow \quad \alpha = 0 \quad \& \quad \beta = \omega\sqrt{LC}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \Big|_{R=G=0} = \sqrt{\frac{L}{C}} \quad (13)$$


$$\text{Wave equations: } V(z) = V_o^+ e^{-j\beta z} + V_o^- e^{j\beta z} \quad (14) \quad I(z) = I_o^+ e^{-j\beta z} + I_o^- e^{j\beta z} = \frac{V_o^+}{Z_0} e^{-j\beta z} - \frac{V_o^-}{Z_0} e^{j\beta z} \quad (15)$$
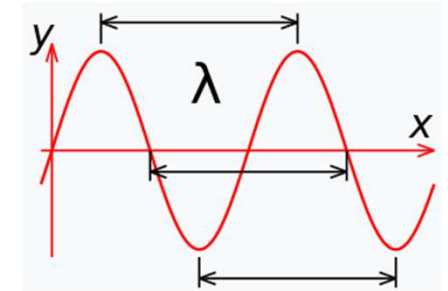
$$\text{Wavelength: } \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}} \quad (16) \quad \text{Phase velocity: } v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} \quad (17)$$



3 Terminated Lossless Transmission Lines

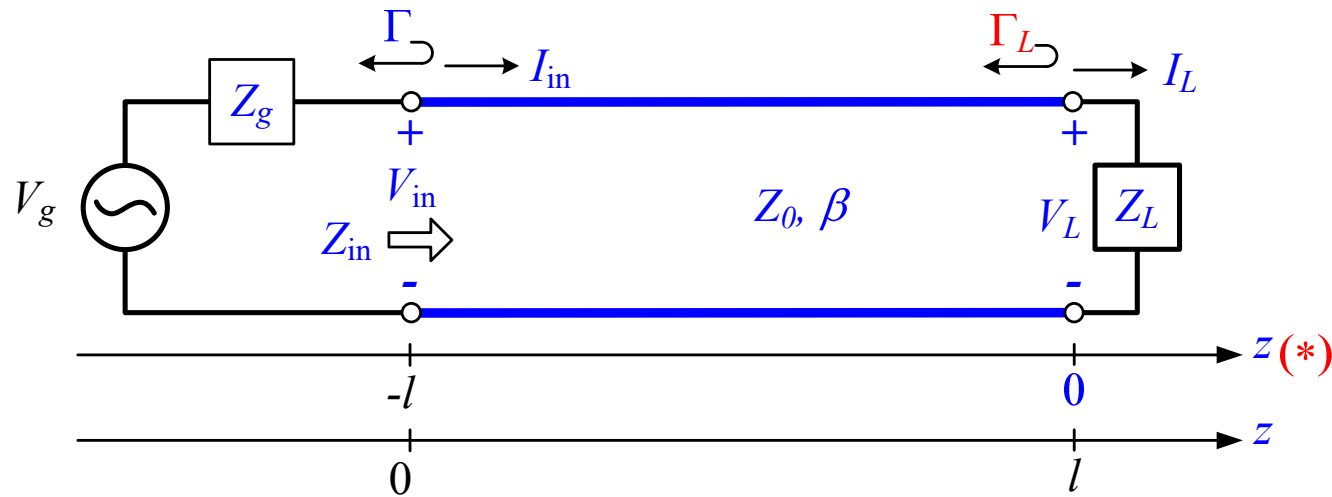- A lossless transmission line terminated in an arbitrary load impedance Z_L
 - Incident voltage wave: $V_0^+ e^{-j\beta z}$
 - Z_0 ($\neq Z_L$, typ.): ratio of traveling voltage wave to traveling current wave on transmission line



- Total voltage and current waves consisted of incident and reflected voltage/current waves due to $Z_0 \neq Z_L$:


$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad (1)$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} \quad (2)$$

3 Terminated Lossless Transmission Lines

- Load impedance: $Z_L = \left. \frac{V(z)}{I(z)} \right|_{z=0} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} Z_0$

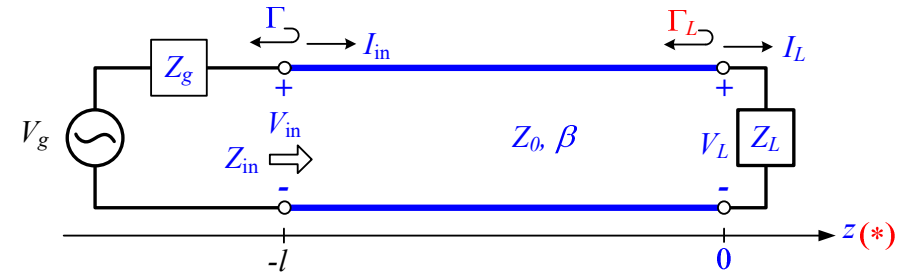Reflected voltage wave: $V_o^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_o^+$



- Voltage reflection coefficient (Γ) = Reflected voltage wave amplitude / Incident voltage wave amplitude

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{|V_0^-| e^{j\phi^-}}{|V_0^+| e^{j\phi^+}} = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\theta} \quad (3) \quad : \text{complex } (:: Z_L: \text{complex})$$

→ phase deviation between incident and reflected voltage waves

- Total voltage and current waves on transmission line:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} = V_0^+ [e^{-j\beta z} + (V_0^- / V_0^+) e^{j\beta z}] = V_0^+ [e^{-j\beta z} + \Gamma e^{j\beta z}] \quad (4)$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - \Gamma e^{j\beta z}] \quad (5)$$

- Standing waves: superposition of an incident and reflected waves as $V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$ and $I_0^+ e^{-j\beta z} + I_0^- e^{j\beta z}$

- **If $\Gamma = 0$, no reflected wave.** → $Z_L = Z_0$ ((Impedance) Matching!!)

3 Terminated Lossless Transmission Lines

- Time-average power flowing along transmission line (@ z)

$$P_{av} = \frac{1}{2} \operatorname{Re}[V(z)I(z)^*] = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \operatorname{Re}\{1 - \Gamma^* e^{-2j\beta z} + \Gamma e^{2j\beta z} - |\Gamma|^2\} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2)$$

- Incident power: $|V_0^+|^2 / 2Z_0$

- Reflected power: $|V_0^+|^2 |\Gamma|^2 / 2Z_0$

- Delivered power (P_{av}) = Incident power - Reflected power

- If $\Gamma = 0$, the maximum power is delivered to the load

If $|\Gamma| = 1$, no power is delivered.

- When the load is mismatched ($|\Gamma| \neq 0$ or $Z_L \neq Z_0$), then not all of the available power from the generator is delivered to the load.

- Return loss (RL) = Reflected power / Incident power

- $RL = -20 \log |\Gamma|$ [dB]

- Ex.) $RL = \infty$ dB @ $\Gamma = 0$

$RL = 0$ dB @ $|\Gamma| = 1$

3 Terminated Lossless Transmission Lines

- In case of $Z_L \neq Z_0$, voltage standing wave due to reflected wave at $z = -l$

$$|V(-l)| = |V_0^+| |e^{j\beta l} + \Gamma e^{-j\beta l}| = |V_0^+| |e^{j\beta l}| |1 + \Gamma e^{-2j\beta l}| = |V_0^+| |1 + \Gamma e^{-2j\beta l}| = |V_0^+| |1 + |\Gamma| e^{j(\theta - 2\beta l)}|, \quad (6)$$

where $\Gamma = |\Gamma| e^{j\theta}$ and θ : phase of reflection coefficient

- In case of $e^{j(\theta - 2\beta l)} = 1$, $V_{\max} = |V_0^+| (1 + |\Gamma|)$

- In case of $e^{j(\theta - 2\beta l)} = -1$, $V_{\min} = |V_0^+| (1 - |\Gamma|)$

- (Voltage) Standing wave ratio (V**SWR**):

$$\text{SWR} = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad (7)$$


→ $1 \leq \text{SWR} \leq \infty$ ($\because 0 \leq |\Gamma| \leq 1$) : another expression of reflection coefficient

- Two successive voltage maxima (or minima) on transmission line:

$$(\theta - 2\beta l_1) - (\theta - 2\beta l_2) = 2\beta(l_2 - l_1) = 2\beta l = 2\pi \quad \leftarrow l = l_2 - l_1$$

$$l = 2\pi / 2\beta = \pi / \beta = \pi\lambda / 2\pi = \lambda / 2$$

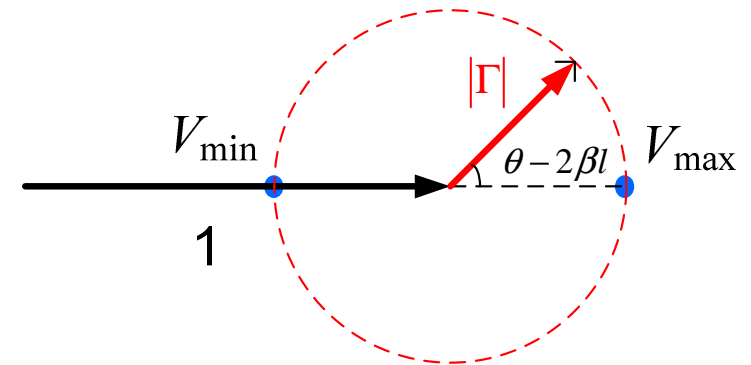- Distance between two successive voltage maximum and minimum points: $l = \pi/2\beta = \lambda/4$



3 Terminated Lossless Transmission Lines

- Reflection coefficient at $z = -l$: $\Gamma(-l) = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \Gamma(0) e^{-j2\beta l}$

- $\Gamma(0)$: reflection coefficient @ $z = 0$

- ‘Load reflection @ $z = 0$ ’ + ‘two times phase shift’

- Input impedance seen looking toward the load at $z = -l$: Z_{in}


$$Z_{in} = \frac{V(-l)}{I(-l)} = \frac{V_0^+ [e^{j\beta l} + \Gamma e^{-j\beta l}]}{V_0^+ [e^{j\beta l} - \Gamma e^{-j\beta l}]} Z_0 = \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} Z_0 \quad (8)$$

$$= \frac{e^{j\beta l} + \frac{Z_L - Z_0}{Z_L + Z_0} e^{-j\beta l}}{e^{j\beta l} - \frac{Z_L - Z_0}{Z_L + Z_0} e^{-j\beta l}} Z_0 \quad \leftarrow \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= Z_0 \frac{(Z_L + Z_0)e^{j\beta l} + (Z_L - Z_0)e^{-j\beta l}}{(Z_L + Z_0)e^{j\beta l} - (Z_L - Z_0)e^{-j\beta l}} = Z_0 \frac{Z_L(e^{j\beta l} + e^{-j\beta l}) + Z_0(e^{j\beta l} - e^{-j\beta l})}{Z_0(e^{j\beta l} + e^{-j\beta l}) + Z_L(e^{j\beta l} - e^{-j\beta l})}$$

$$= Z_0 \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \quad (9)$$

$$= f(Z_0, Z_L, l)$$

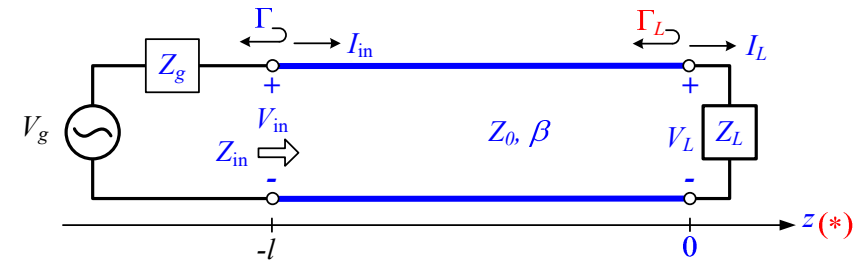

4 Review

- Lumped elements (L and C) frequency dependances
 - Self resonance
 - Element value variation according to frequency
- Terminated lossless transmission lines
 - Reflection coefficient (Γ)
 - (V)SWR
 - Input impedance of transmission line circuit terminated with load