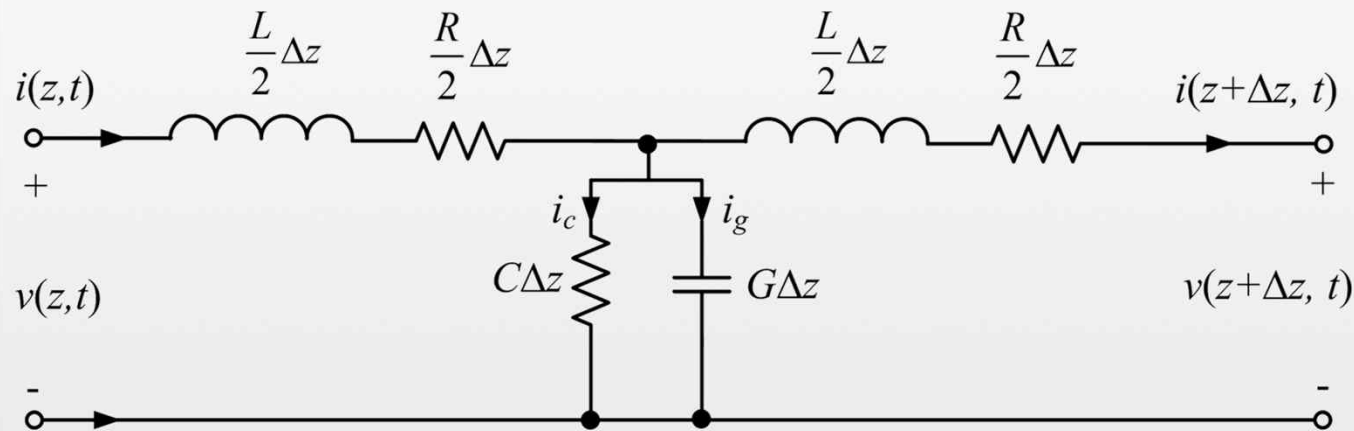


Chapter 2

Transmission Line

Prof. Jeong, Yongchae



Learning Objectives

- Learn how to realize microwave L and C with transmission line
- Learn what will be done in transmission lines connection
- Understanding decibel units
- Learn utilities of Smith chart

Learning contents

- Microwave L and C using Transmission Line
- Transmission Lines Connection
- Decibel
- Smith Chart

1 Microwave L and C using Transmission Line

- Transmission line circuit **terminated with short circuit ($Z_L = 0$)**

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \Big|_{Z_L=0} = -1 = \frac{V^+}{V^-}$$

- At load, $V = 0$ and $I = \infty$


- Input impedance

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \Big|_{Z_L=0} = jZ_0 \tan \beta l = jX_{in}$$

$$\rightarrow -j\infty \leq Z_{in} \leq +j\infty$$

$$\theta = \beta l = \frac{2\pi}{\lambda} l, 0 < \theta < \frac{\pi}{2} \Leftrightarrow 0 < \frac{2\pi}{\lambda} l < \frac{\pi}{2} \Leftrightarrow 0 < l < \frac{\pi}{2} \frac{\lambda}{2\pi} = \frac{\lambda}{4}$$

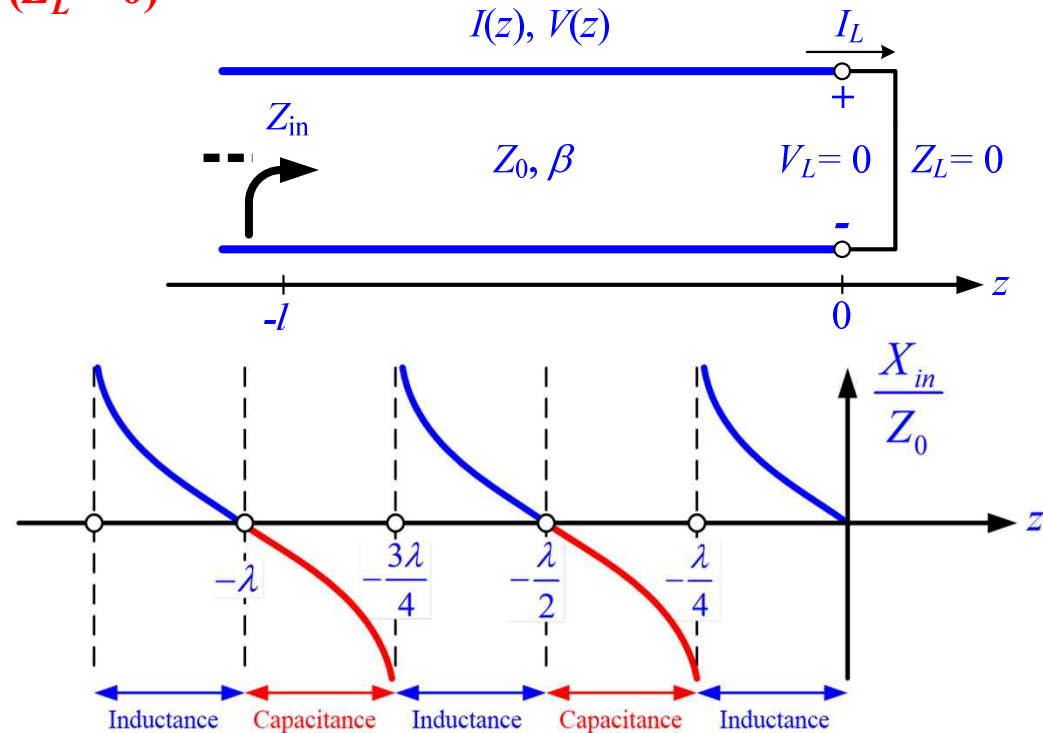- **Repeated inductive & capacitive** characteristics along transmission line
- Different reactance characteristics according to frequency (or wavelength)
- Repeated reactance characteristics according to harmonics ($f_0, 3f_0, \dots, (2n+1)f_0$)



1 Microwave L and C using Transmission Line

- Transmission line circuit **terminated with open circuit** ($Z_L = \infty$)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \Big|_{Z_L = \infty} = 1 = \frac{V^+}{V^-}$$

- At load, $I = 0$ and $V = \infty$

- Input impedance


$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \Big|_{Z_L = \infty} = -jZ_0 \cot \beta l$$

$$\rightarrow -j\infty \leq Z_{in} \leq +j\infty$$

$$\theta = \beta l = \frac{2\pi}{\lambda} l, \quad 0 < \theta < \frac{\pi}{2} \Leftrightarrow 0 < \frac{2\pi}{\lambda} l < \frac{\pi}{2} \Leftrightarrow 0 < l < \frac{\pi}{2} \frac{\lambda}{2\pi} = \frac{\lambda}{4}$$

- Same electrical characteristics as like transmission line terminated with short circuit

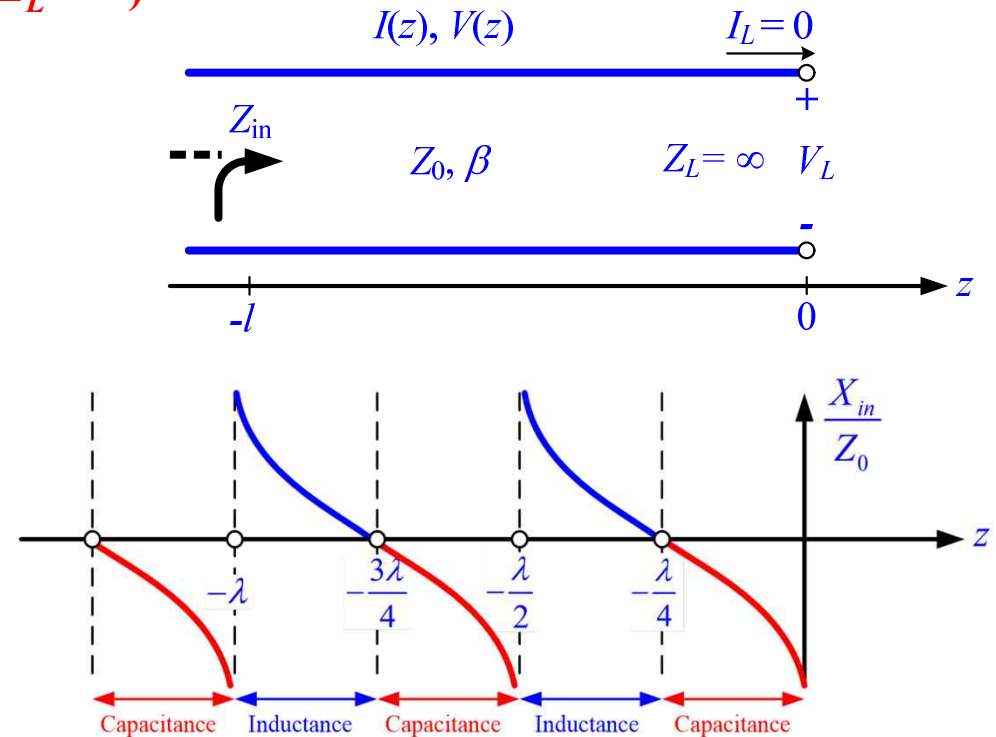- Microwave inductor (L) and capacitor (C) can be realized by using transmission line circuit terminated with short or open circuits!!!**



2 Transmission Lines Connection

- Input impedance in case of $l = \lambda/2$ transmission line terminated with load (Z_L)

$$Z_{\text{in}} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \Big|_{l=\lambda/2} = Z_0 \frac{Z_L + jZ_0 \tan \frac{2\pi}{\lambda} \frac{\lambda}{2}}{Z_0 + jZ_L \tan \frac{2\pi}{\lambda} \frac{\lambda}{2}} = Z_L \Leftrightarrow Z_{\text{in}} = Z_L$$

- Input impedance in case of $l = \lambda/4 + n\lambda/2$ transmission line terminated with load (Z_L)

$$Z_{\text{in}} = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell} \Big|_{\ell=\lambda/4} = Z_0 \frac{Z_L + jZ_0 \tan \frac{2\pi}{\lambda} \frac{\lambda}{4}}{Z_0 + jZ_L \tan \frac{2\pi}{\lambda} \frac{\lambda}{4}} = \frac{Z_0^2}{Z_L} : \text{Quarter-wave (length) transformer}$$

2 Transmission Lines Connection

- Transmission line of characteristic impedance Z_0 feeding different characteristic impedance (Z_1) transmission line

- Reflection coefficient

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

→ Some portion of the incident wave is reflected and the remained is transmitted into the second line.

- Voltage waves on each transmission lines


$$V(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}) \quad @ z < 0$$

$$V(z) = V_0^+ T e^{-j\beta z} \quad @ z > 0$$

- Continuity of transmission coefficient at $z = 0$:

$$T = 1 + \Gamma = 1 + \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{2Z_1}{Z_1 + Z_0}$$

- Insertion loss (IL): $IL = -20 \log |T|$ dB

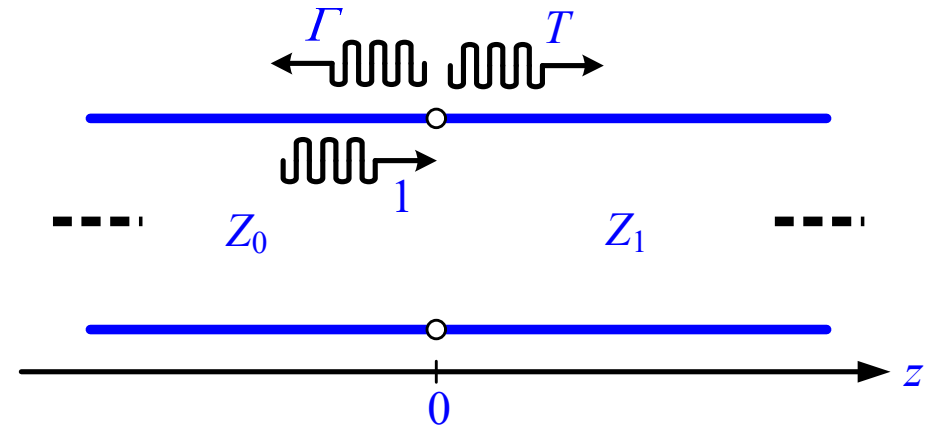

3 Decibel [dB]

- Decibel (dB): **relative unit** of measurement equal to one tenth of a **bel (B)**

- Power gain in decibel = $10 \log \frac{P_1}{P_2}$ [dB]

Ex.] $P_1/P_2 = 0.5 = 1/2 \rightarrow -3$ dB, $P_1/P_2 = 10 \rightarrow 10$ dB

- Voltage gain in decibel: $10 \log \frac{P_1}{P_2} = 10 \log \frac{V_1^2 / R_1}{V_2^2 / R_2} = 10 \log \frac{V_1^2 R_2}{V_2^2 R_1} = 20 \log \frac{V_1}{V_2} \sqrt{\frac{R_2}{R_1}}$ [dB]
 $= 20 \log \frac{V_1}{V_2}$ [dB] ← If $R_1 = R_2$

- Current gain in decibel: $10 \log \frac{P_1}{P_2} = 10 \log \frac{I_1^2 R_1}{I_2^2 R_2} = 10 \log \frac{I_1^2}{I_2^2} = 20 \log \frac{I_1}{I_2}$ [dB] ← If $R_1 = R_2$

where R_1, R_2 : load resistances

$V_{1,2}, I_{1,2}$: voltages across specific ports and currents passing specific nodes

- Neper [Np]: ratio of voltages across equal load resistances

$$\text{neper} = \ln \frac{V_1}{V_2} = \ln \left[\left(\frac{V_1}{V_2} \right)^2 \right]^{1/2} = \ln \left[\left(\frac{V_1^2 / R}{V_2^2 / R} \right) \right]^{1/2} = \frac{1}{2} \ln \frac{P_1}{P_2} \quad [\text{Np}]$$

Ex.] $1 \text{ Np} = 10 \log e^2 = 8.686$ dB

3 Decibel [dB]

- Absolute decibel units: **absolute units** of measurement equal to one tenth to specific value

- If we let $P_2 = 1 \text{ mW}$, $P_1 [\text{dBm}] = 10 \log \frac{P_1 [\text{mW}]}{1 \text{ mW}}$

Ex.] $P_1 = 1 \text{ mW} \rightarrow 0 \text{ dBm}$, $P_1 = 1 \text{ W} \rightarrow 30 \text{ dBm}$

- If we let $V_2 = 1 \text{ mV}$, $V_1 = 20 \log \frac{V_1}{1 \text{ mV}} [\text{dBmV}]$

Ex.] $V_1 = 1 \text{ mV} \rightarrow 0 \text{ dBmV}$, $V_1 = 1 \text{ V} \rightarrow 60 \text{ dBmV}$

- If we let $I_2 = 1 \text{ }\mu\text{A}$, $I_1 = 20 \log \frac{I_1}{1 \text{ }\mu\text{A}} [\text{dB}\mu\text{A}]$

Ex.] $I_1 = 1 \text{ }\mu\text{A} \rightarrow 0 \text{ dB}\mu\text{A}$, $I_1 = 1 \text{ mA} \rightarrow 60 \text{ dB}\mu\text{A}$

4 Smith Chart


Reflection coefficient plane

$$\Gamma = |\Gamma| e^{j\theta}$$

where $0 \leq |\Gamma| \leq 1$, $0^\circ \leq \theta \leq 360^\circ$ (or $0 \leq \theta \leq 2\pi$)

- Developed by P. Smith at Bell Telephone Laboratories in 1939
- Very useful when solving transmission line problems
 - Visualizing transmission line phenomenon
 - Intuition about transmission line and impedance-matching problems
- **Normalized** impedance (or admittance):
 $z = Z / Z_0$ (or $y = Y / Y_0$)
- Z_0 (or Y_0): arbitrary value

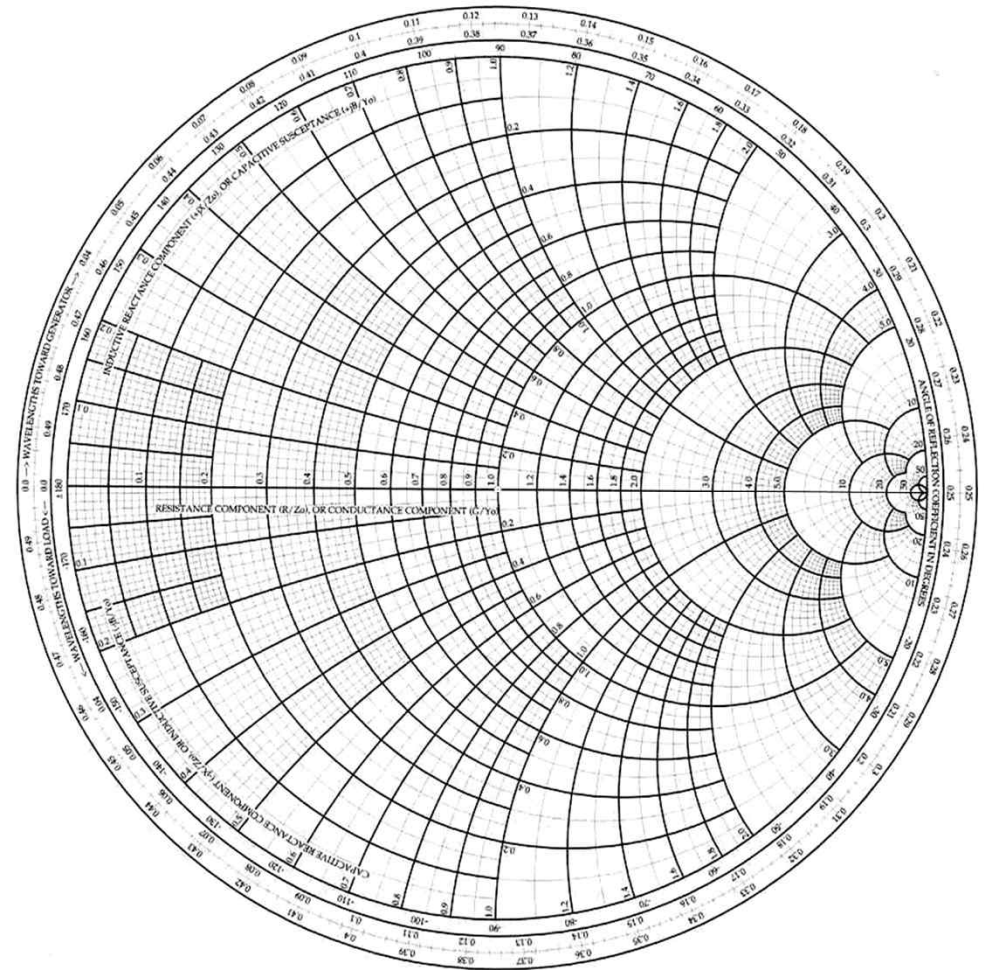Normalized Impedance or Admittance Coordinates





4

Smith Chart

Normalized Impedance **or** Admittance Coordinates

NAME	TITLE	DWG. NO.
SMITH CHART FORM ZY-01-N	ANALOG INSTRUMENTS COMPANY, NEW PROVIDENCE, N.J. 07974	DATE

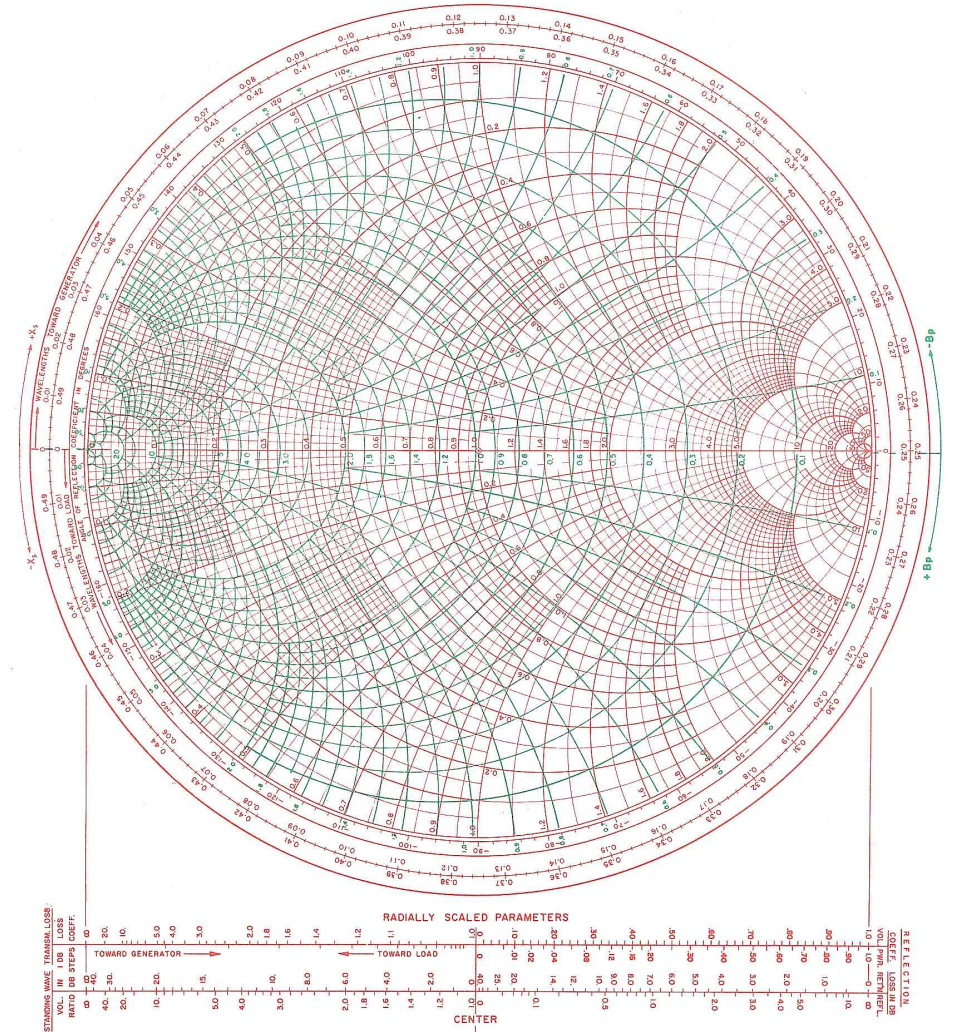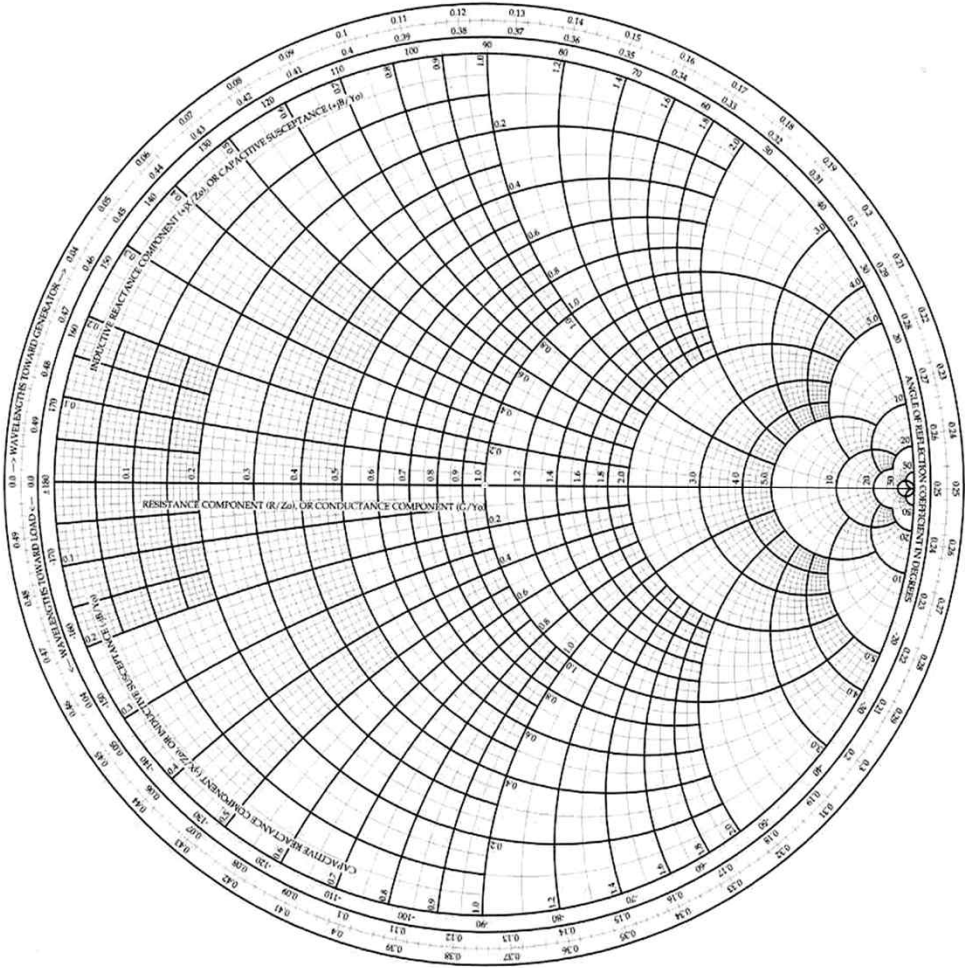NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



4 Smith Chart

- If a lossless transmission line of characteristic impedance Z_0 is terminated with a load impedance Z_L ,

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(Z_L / Z_0) - 1}{(Z_L / Z_0) + 1} = \frac{z_L - 1}{z_L + 1} = |\Gamma| e^{j\theta}, \quad \leftarrow \Gamma = f(Z_L)$$

where $z_L = Z_L / Z_0$: normalized load impedance

- Since $Z_{in} = \frac{V(-l)}{I(-l)} = \frac{V_0^+ [e^{j\beta l} + \Gamma e^{-j\beta l}]}{V_0^+ [e^{j\beta l} - \Gamma e^{-j\beta l}] / Z_0} = \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} Z_0 = \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} Z_0$,

$$Z_{in}|_{l=0} = Z_L = \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}} Z_0 \Big|_{l=0} = \frac{1 + \Gamma}{1 - \Gamma} Z_0 \quad \leftarrow \Gamma = |\Gamma| e^{j\theta} = \Gamma_r + j\Gamma_i$$

$$z_L = \frac{Z_L}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + |\Gamma| e^{j\theta}}{1 - |\Gamma| e^{j\theta}} \quad \leftarrow z_L = g(Z_L)$$

- Let $\Gamma = \Gamma_r + j\Gamma_i$ and $z_L = r_L + jx_L$.

$$\begin{aligned} z_L = r_L + jx_L &= \frac{1 + \Gamma}{1 - \Gamma} = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i} = \frac{\{(1 + \Gamma_r) + j\Gamma_i\} \{(1 - \Gamma_r) + j\Gamma_i\}}{(1 - \Gamma_r)^2 + \Gamma_i^2} \\ &= \frac{(1 - \Gamma_r^2) - \Gamma_i^2 + j\Gamma_i(1 + \Gamma_r) + j\Gamma_i(1 - \Gamma_r)}{(1 - \Gamma_r)^2 + \Gamma_i^2} = \frac{(1 - \Gamma_r^2 - \Gamma_i^2) + j2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} \end{aligned}$$

4 Smith Chart

- Real and imaginary parts:

$$r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}, \quad x_L = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

- Rearrangement of real part (or resistance)

$$r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


$$r_L(1 - \Gamma_r)^2 + r_L\Gamma_i^2 = 1 - \Gamma_r^2 - \Gamma_i^2$$

$$\Gamma_r^2(r_L + 1) - 2r_L\Gamma_r + (r_L + 1)\Gamma_i^2 = 1 - r_L$$

$$\Gamma_r^2 - \frac{2r_L}{r_L + 1}\Gamma_r + \Gamma_i^2 = \frac{1 - r_L}{1 + r_L} \leftarrow x^2 - 2ax + y^2 = b$$

$$\left(\Gamma_r - \frac{r_L}{r_L + 1}\right)^2 + \Gamma_i^2 = \frac{1 - r_L}{1 + r_L} + \left(\frac{r_L}{r_L + 1}\right)^2 = \frac{1}{(1 + r_L)^2}$$

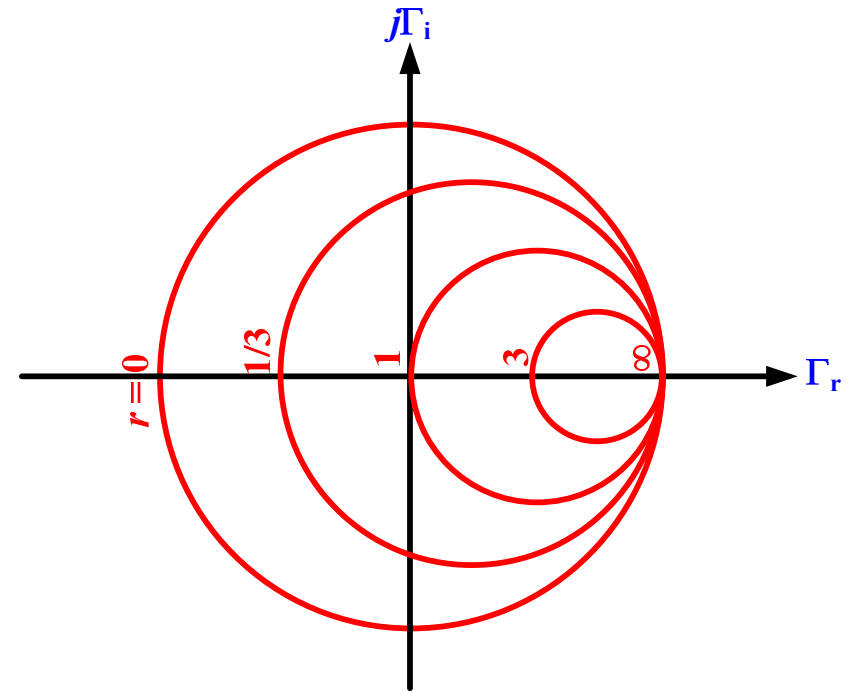- Resistance circles- Center: $\left(\frac{r_L}{r_L + 1}, 0\right)$ Radius: $\frac{1}{1 + r_L}$



4 Smith Chart

- Rearrangement of imaginary part (or reactance)



$$x_L = \frac{2\Gamma_i}{(1-\Gamma_r)^2 + \Gamma_i^2}$$

$$(1-\Gamma_r)^2 + \Gamma_i^2 = \frac{2\Gamma_i}{x_L}, \quad (1-\Gamma_r)^2 + \Gamma_i^2 - \frac{2\Gamma_i}{x_L} = 0$$

$$(\Gamma_r - 1)^2 + \Gamma_i^2 - \frac{2\Gamma_i}{x_L} + \left(\frac{1}{x_L}\right)^2 = (\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2$$

- Reactance circles- Center: $\left(1, \frac{1}{x_L}\right)$

Radius: $\left|\frac{1}{x_L}\right|$

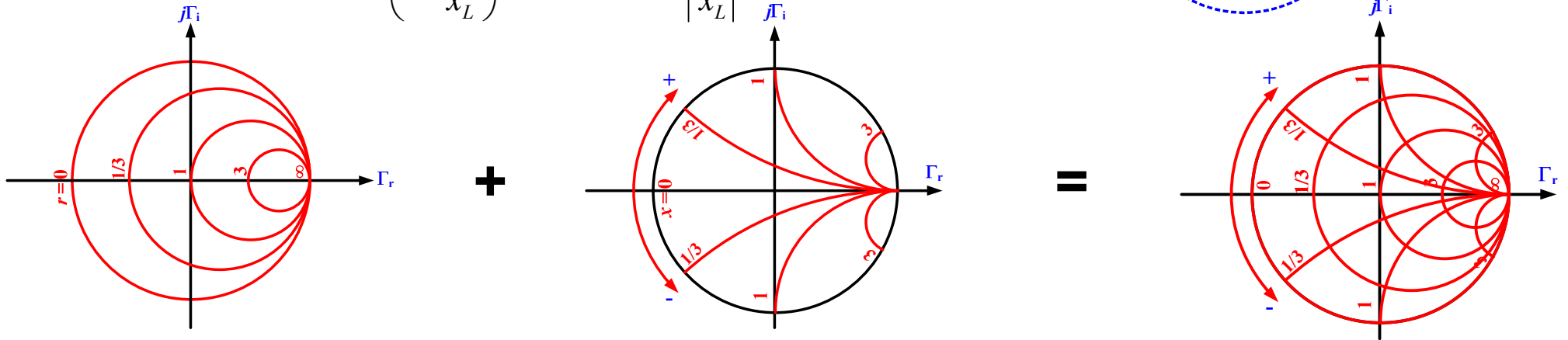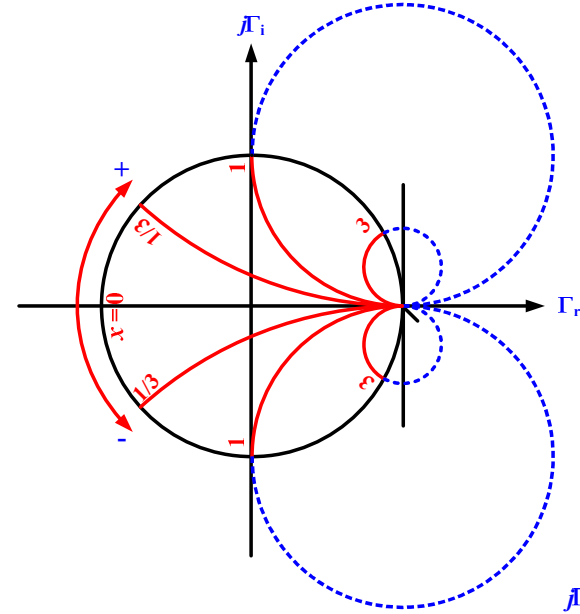


4 Smith Chart

- The Smith chart can also be graphical solution of the transmission line impedance equation in terms of the generalized reflection coefficient as

$$Z_{in} = Z_0 \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}}$$

$$\leftarrow \Gamma = |\Gamma| e^{j\theta}$$

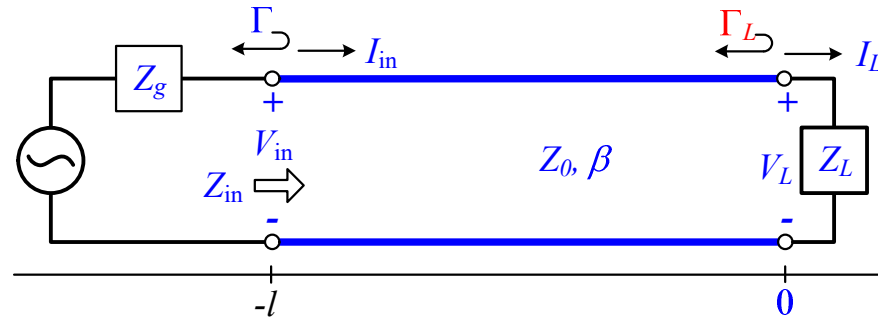


where Γ : reflection coefficient at load

l : (positive) length of transmission line from load


- The normalized input impedance seen looking into a length l of transmission line terminated with z_L can be found by rotating the point **clockwisely** an amount $2\beta l$ (subtracting $2\beta l$ from θ) around the center of the chart.

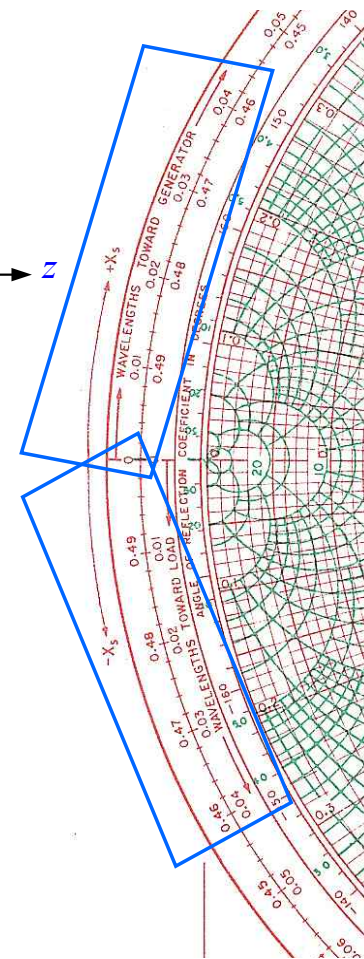- The same radius is maintained, since the magnitude of Γ does not change with position along the transmission line. (\because lossless transmission line)



4 Smith Chart

- Accessory grids

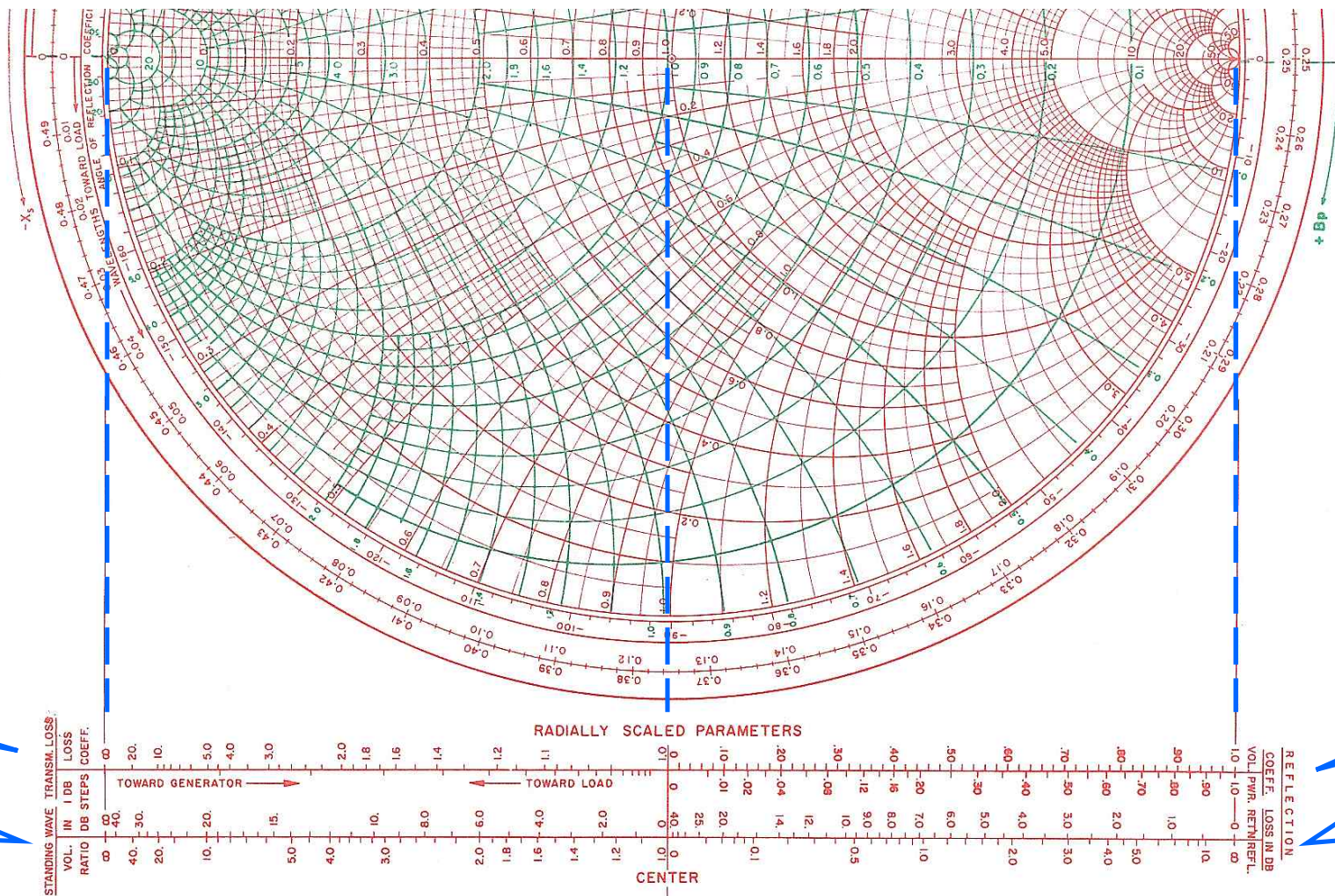

Transmission Loss
(dB, coeff.-)

Voltage standing
wave ratio (VSWR)

Reflection
coefficient

Return
loss (RL)

5 Review

- Microwave L and C using Transmission Line
 - Equivalent inductor
 - Equivalent capacitor
- Transmission lines connection
 - Reflection
 - Transmission
- Smith chart
 - Reflection coefficient plane
 - Impedance and/or admittance chart
 - Transmission calculation tools