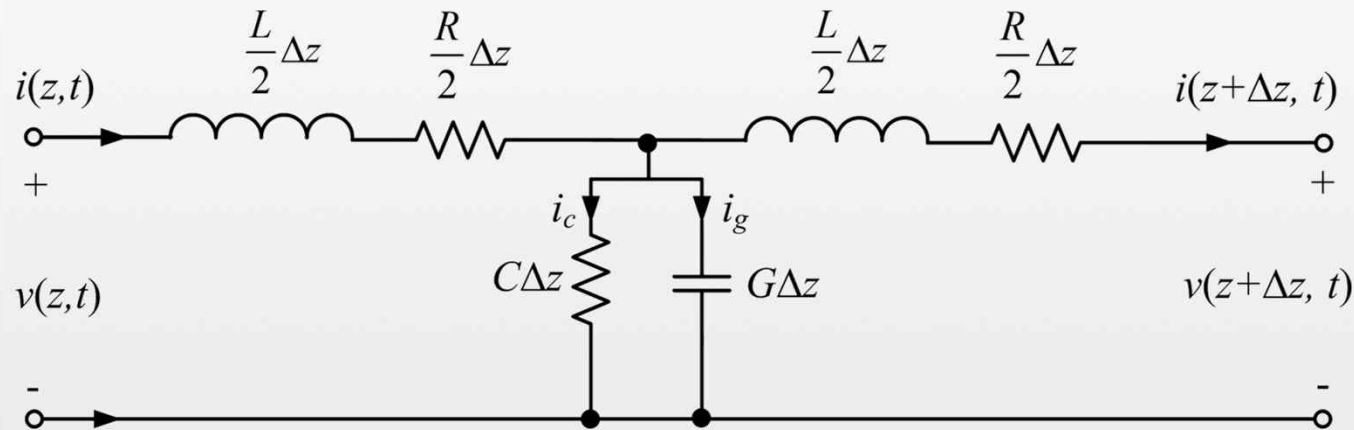


Chapter 2

Transmission Line

Prof. Jeong, Yongchae



Learning Objectives

- Understanding combined impedance and admittance Smith chart
- Exercise Smith chart examples
- Learn traveling (or standing) wave on transmission line by using slotted transmission line

Learning contents

- Combined Impedance and Admittance Smith Chart
- Smith Chart Examples
- Slotted Transmission Line


1 Combined Impedance and Admittance Smith Chart

- Input impedance of a load z_L connected to a $\lambda/4$ line:

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell}$$


$$Z_{in} \Big|_{\ell=\lambda/4} = \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell} \Big|_{\ell=\lambda/4} = \frac{Z_L + jZ_0 \tan(2\pi / \lambda \cdot \lambda / 4)}{Z_0 + jZ_L \tan(2\pi / \lambda \cdot \lambda / 4)} = \frac{Z_0}{Z_L} = \frac{1}{z_L}$$

$$= y_L = g_L + jb_L$$

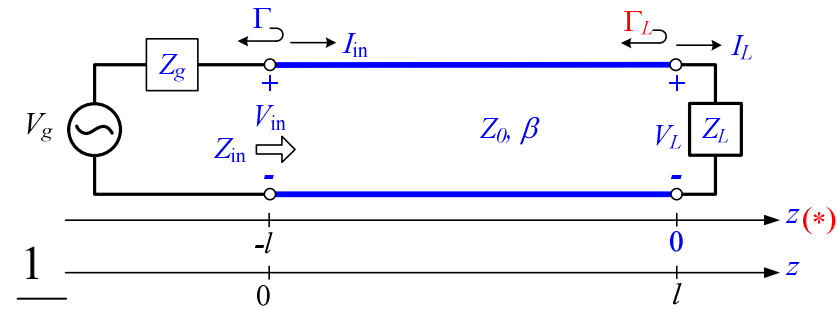


→ Converting a normalized impedance to a normalized admittance.

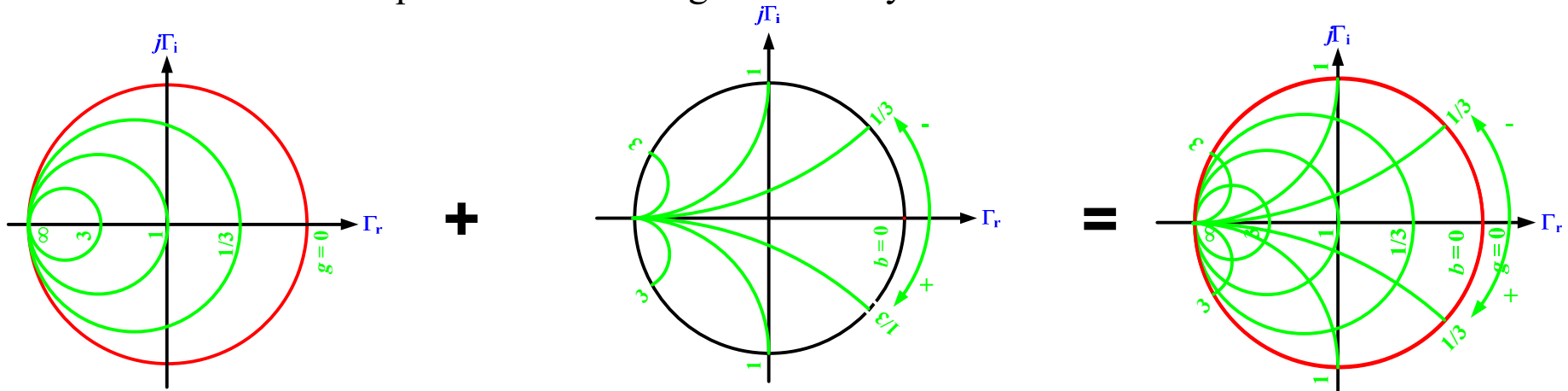→ A $\lambda/4$ transformation is equivalent to rotating the chart by 180° .




1 Combined Impedance and Admittance Smith Chart

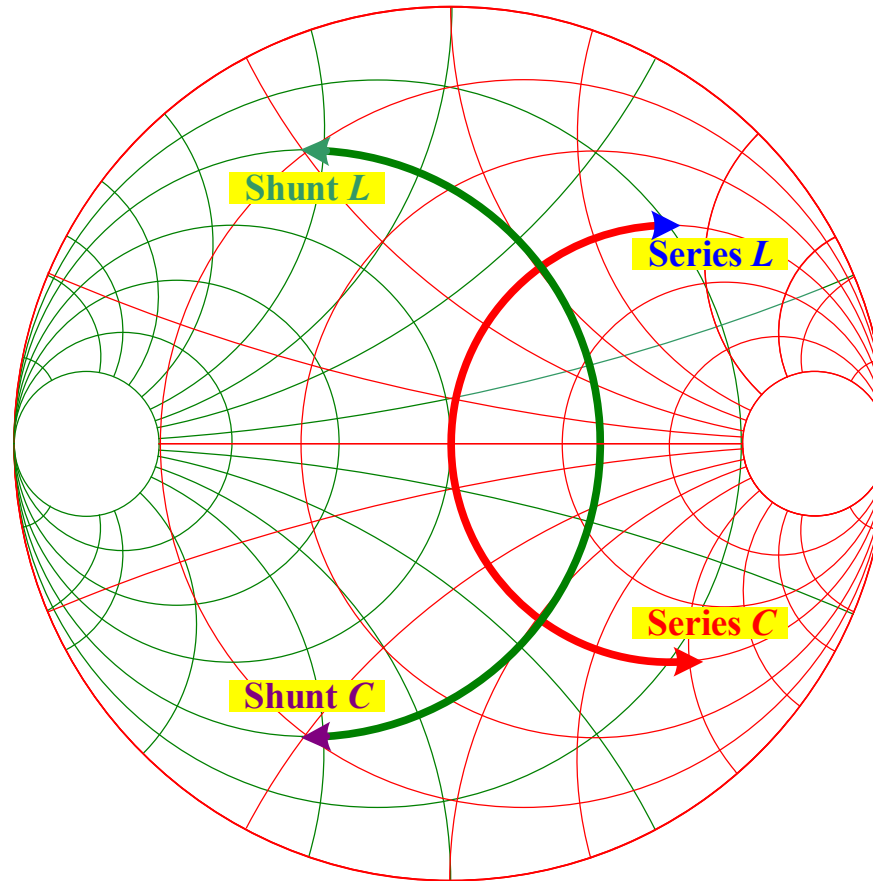- Impedance trace movement of lumped elements on combined impedance and admittance Smith chart



1 Combined Impedance and Admittance Smith Chart

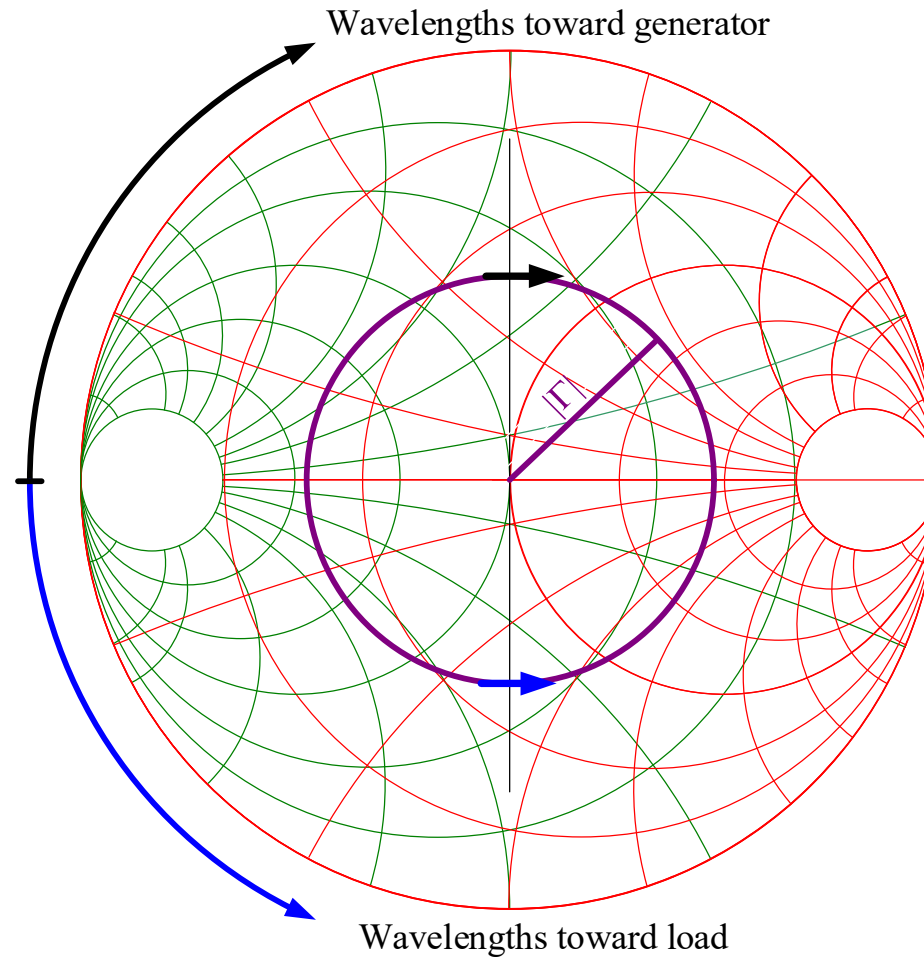- Impedance trace movement of transmission line on combined impedance and admittance Smith chart
 - Constant reflection coefficient magnitude



2 Smith Chart Example (1)

- Transmission line ($Z_0 = 50 \text{ } [\Omega]$) circuit terminated with $Z_L = 130 + j90 \text{ } [\Omega]$ and line length of $l = 0.3\lambda$
Find Γ @load, Γ @line input node, Z_{in} , (V)SWR @line input node, and the return loss.

1) Theoretical solutions

- Normalized load impedance: $z_L = \frac{Z_L}{Z_0} = 2.60 + j1.8 \text{ } [\Omega]$

- Reflection coefficient magnitude at the load:


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \bigg|_{z_L} = \frac{Z_L / Z_0 - 1}{Z_L / Z_0 + 1} \bigg|_{z_L} = \frac{z_L - 1}{z_L + 1} \bigg|_{z_L=2.6+j1.8} = \frac{(2.6 + j1.8) - 1}{(2.6 + j1.8) + 1} = \frac{1.6 + j1.8}{3.6 + j1.8} = \frac{(1.6 + j1.8)(3.6 - j1.8)}{(3.6)^2 + (1.8)^2}$$

$$= 0.556 + j0.222 = 0.6 \angle 21.8^\circ \quad \Rightarrow \quad |\Gamma_L| = 0.6$$

- Γ @ line input node: $\Gamma_{in} = \Gamma_L e^{-j2\beta l} \bigg|_{l=0.3\lambda} = \Gamma_L e^{-j2\frac{2\pi}{\lambda} \cdot 0.3\lambda} = \Gamma_L e^{-j1.2\pi} = \Gamma_L e^{-j144^\circ} = 0.6 \angle -122.2^\circ$

- Input impedance (Z_{in})

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \bigg|_{l=0.3\lambda} = 50 \frac{Z_L + jZ_0 \tan \frac{2\pi}{\lambda} \cdot 0.3\lambda}{Z_0 + jZ_L \tan \frac{2\pi}{\lambda} \cdot 0.3\lambda} = 50 \frac{(130 + j90) + j50 \tan 0.6\pi}{50 + j(130 + j90) \tan 0.6\pi} = 12.75 + j5.83$$

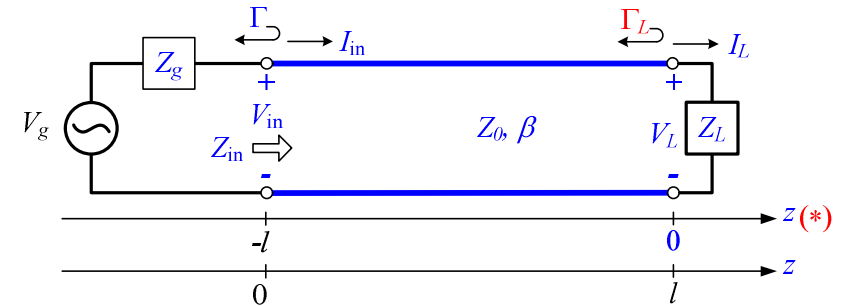


2 Smith Chart Example (1)

- SWR @line input node: $SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.6}{1 - 0.6} = \frac{1.6}{0.4} = 4$

- Return loss: $RL = -20 \log |\Gamma| = -20 \log(0.6) = -4.4 \text{ dB}$

2) Smith chart solutions

- Normalized load impedance: $z_L = 2.60 + j1.8 [\Omega]$
- Reflection coefficient magnitude at load: $\Gamma = 0.6 \angle 21.8^\circ$
- $|\Gamma| = 0.60$
- $SWR = 3.98$
- $RL = 4.4 \text{ dB}$
- Reading reference position of load: 0.22λ
- Moving down 0.3λ of line according to wavelengths-toward-generator (WTG): $0.22\lambda + 0.3\lambda = 0.52\lambda = 0.02\lambda$
- New normalized input impedance at intersection with SWR circle: $z_{in} = 0.255 + j0.117 \rightarrow Z_{in} = Z_0 z_{in} = 12.7 + j5.8 [\Omega]$

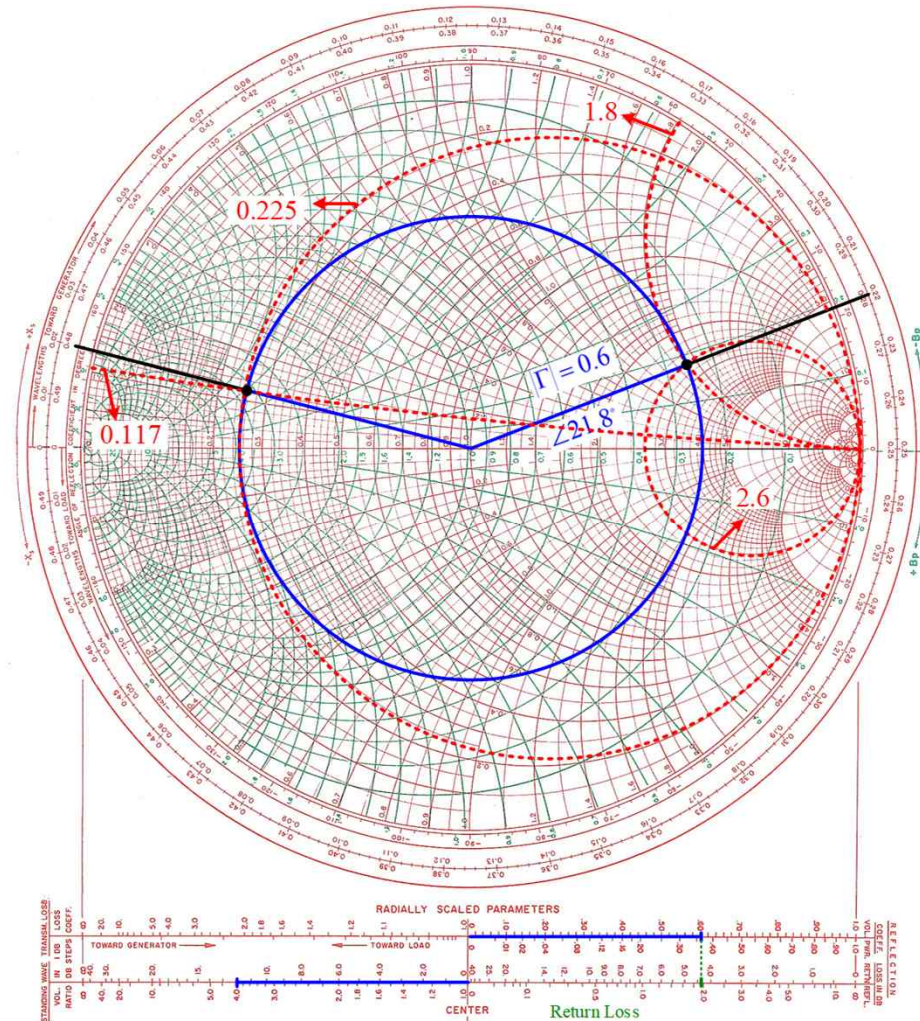

2 Smith Chart Example (2)

- Transmission line ($Z_0 = 50 \text{ } [\Omega]$) circuit terminated with $Z_L = 100 + j50[\Omega]$ and line length of $l = 0.15\lambda$
Find load admittance (Y_L) and Z_{in} .

1) Theoretical solutions

- Normalized load impedance: $z_L = 2 + j1 \text{ } [\Omega]$

- Normalized load admittance: $y_L = \frac{1}{z_L} = \frac{1}{2 + j1} = \frac{2 - j1}{2^2 + 1^2} = 0.4 - j0.2$

- Load admittance: $Y_L = y_L Y_0 = \frac{y_L}{Z_0} = \frac{0.4 - j0.2}{50} = 0.008 - j0.004 \text{ } [S]$

- Input impedance (Z_{in}): $Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \theta}{Z_0 + jZ_L \tan \theta} \Big|_{l=0.15\lambda} = 50 \frac{(100 + j50) + j50 \tan\left(\frac{2\pi}{\lambda} \times 0.15\lambda\right)}{50 + j(100 + j50) \tan\left(\frac{2\pi}{\lambda} \times 0.15\lambda\right)}$

$$= 50 \frac{100 + j50 + j50 \tan(0.3\pi)}{50 - 50 \tan(0.3\pi) + j100 \tan(0.3\pi)} = 37.50 - j41.45 \text{ } [\Omega]$$

2 Smith Chart Examples (2)

2) Smith chart solutions

- Load admittance:

$$y_L = 0.4 - j0.2$$

$$Y_L = y_L Y_0 = \frac{y_L}{Z_0} = \frac{0.4 - j0.2}{50} = 0.008 - j0.004 [\text{S}]$$

(electrical length: 0.22λ)


- Moving down 0.15λ of line according to wavelengths-toward-generator (WTG):

$$0.22\lambda + 0.15\lambda = 0.37\lambda$$

$$y_{in} = 0.61 + j0.66 \text{ or } z_{in} = \frac{1}{y_{in}} = 0.755 - j0.817$$

$$\rightarrow Z_{in} = z_{in} \times Z_0 = (0.755 - j0.817) \times 50$$
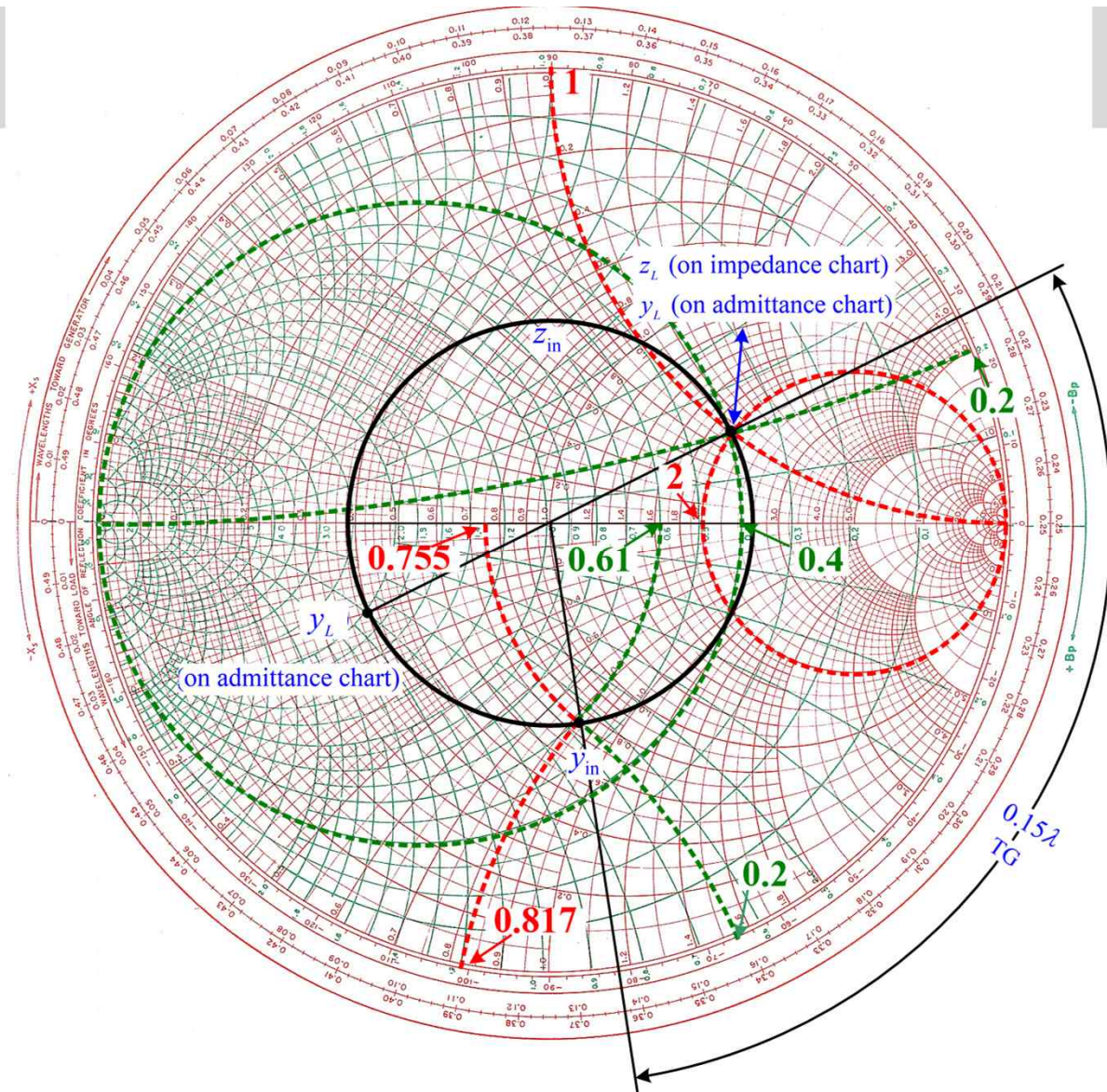
$$\therefore Z_{in} = 37.75 - j40.85 [\Omega]$$



2 Smith Chart Examples (3)

- A 10 [mm] long lossless transmission line with $Z_0 = 50$ [Ω] operating at 3 GHz is terminated with $Z_L = 80 + j30$ [Ω] If the phase velocity (u) is $0.8c$ (c : speed of light) on the transmission line, find

- Reflection coefficient (Γ)
- (Voltage) Standing wave ratio (s)
- Input impedance (Z_{in})


1) Theoretical solutions

$$(a) \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(80 + j30) - 50}{(80 + j30) + 50} = \frac{30 + j30}{130 + j30} = 0.318 \angle 32^\circ$$

$$(b) s = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.318}{1 - 0.318} = 1.933$$

$$(c) \text{ Since } u = 0.8c \text{ and } l = 0.01 \text{ [m], } \beta l = \frac{2\pi}{\lambda} l = \frac{2\pi fl}{f\lambda} = \frac{\omega l}{u} = \frac{2\pi(3 \times 10^9) \times 10 \times 10^{-3}}{0.8(3 \times 10^8)} = \frac{\pi}{4} = 45^\circ$$
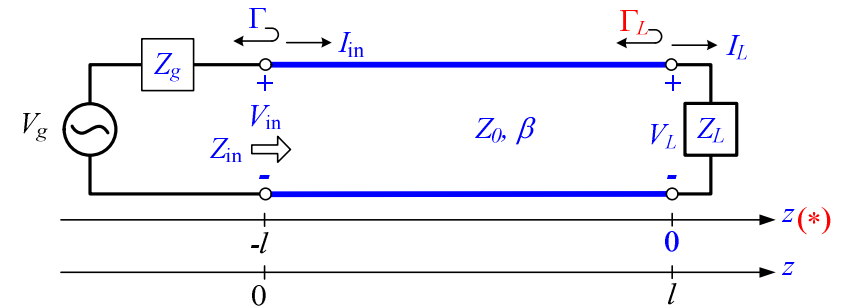
$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] = 50 \frac{(80 + j30 + j50 \tan \beta l)}{[50 + j(80 + j30) \tan \beta l]} = 50 \frac{(80 + j30 + j50 \tan 45^\circ)}{[50 + j(80 + j30) \tan 45^\circ]} = 50 \frac{8 + j3 + j5}{5 + j8 - 3} = 58.82 - j35.29$$



2 Smith Chart Examples (3)

2) Smith chart solutions

(a) Normalized load impedance: $z_L = \frac{Z_L}{Z_0} = \frac{80 + j30}{50} = 1.6 + j0.6$

- Locate z_L on Smith chart
- Draw the line from the center of Smith chart to z_L point.
- Get the length of line and then check reflection coefficient magnitude (represented by blue color) in bottom reflection magnitude and angle from the outside of Smith chart.

$$|\Gamma| = 0.318 \angle 0.32^\circ$$

- (b) Check line length with of line with bottom standing wave magnitude (represented by green color).

$$s = 1.93$$

- (c) To obtain Z_{in} ,


- Wavelength and electrical length of l in terms of λ or in degree

$$\lambda = \frac{u}{f} = \frac{0.8(3 \times 10^8)}{3 \times 10^9} = 0.08 \text{ [m]} \rightarrow l = 10 \text{ [mm]} = \frac{10 \times 10^{-3}}{0.08} \lambda = \frac{\lambda}{8} \leftrightarrow \theta = 45^\circ$$




- z_L is moved toward generator about 45° (or $\lambda/8$), then $z_{in} = 1.18 - j0.71$. $\rightarrow Z_{in} = Z_0 z_{in} = 59 - j35.5 \text{ [\Omega]}$

3 Slotted Transmission Line

- Sampling of electric (or magnetic) field of standing wave along transmission line
 - Waveguide, coaxial cable
 - Measurement issues: (V)SWR, distance of (first) voltage maximum (or minimum) from load, Z_L , λ
 - Because of the large size, the modern vector network analyzer guaranteeing higher accuracy, versatility, and convenience replaces conventional slotted transmission line.
 - *Educational purposes*

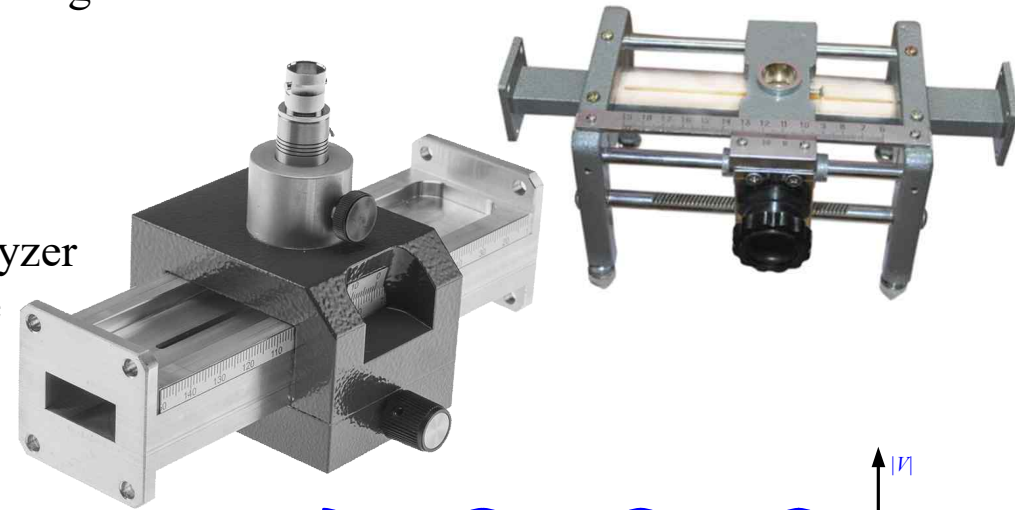

cf.) slot line & rectangular waveguide

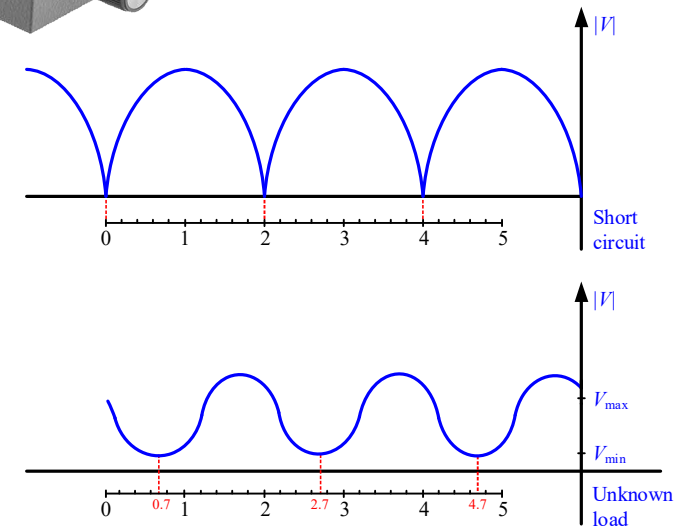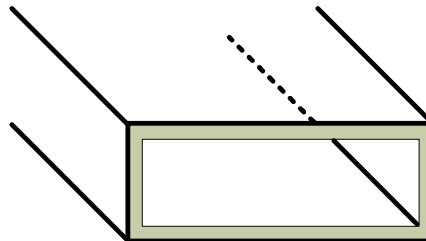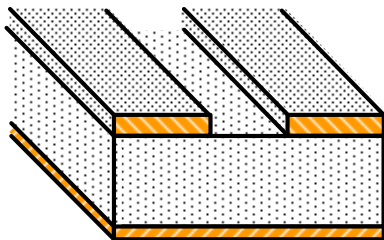

3 Slotted Transmission Line


- (V)SWR = $|V_{\max}/V_{\min}|$

- Magnitude of reflection coefficient along transmission line: $|\Gamma| = \frac{\text{SWR} - 1}{\text{SWR} + 1}$

- Reflection coefficient: $\Gamma = |\Gamma|e^{j\theta}$

$$|V(-l)| = |V_o^+| |e^{j\beta l} + \Gamma e^{-j\beta l}| = |V_o^+| |e^{j\beta l}| |1 + \Gamma e^{-2j\beta l}| = |V_o^+| |1 + \Gamma e^{-2j\beta l}| \leftarrow \Gamma = |\Gamma| e^{j\theta}$$

$$= |V_o^+| |1 + |\Gamma| e^{j(\theta - 2\beta l)}|$$

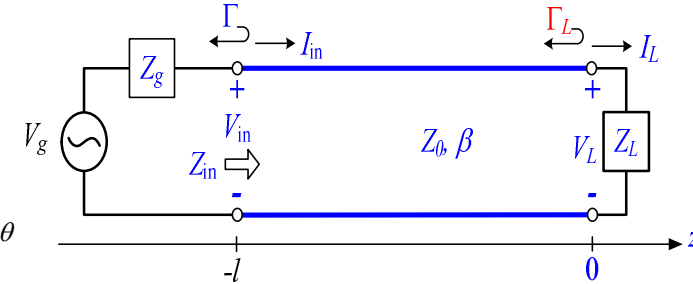

- Voltage minimum: @ $e^{j(\theta - 2\beta l)} = -1 = e^{j\pi}$

Voltage maximum: @ $e^{j(\theta - 2\beta l)} = 0 = e^{j0}$

- Distance from load to first voltage minimum:



$$\theta - 2\beta l_{\min} = \pi$$

$$\theta = \pi + 2\beta l_{\min} \quad \text{or} \quad l_{\min} = \frac{1}{2\beta}(\theta - \pi)$$

- **Voltage minimums repeat every $\lambda/2$** where λ is a wavelength on transmission line.

$$2\beta l = 2 \frac{2\pi}{\lambda} l = 2\pi \quad \rightarrow \quad l = \frac{\lambda}{2}$$

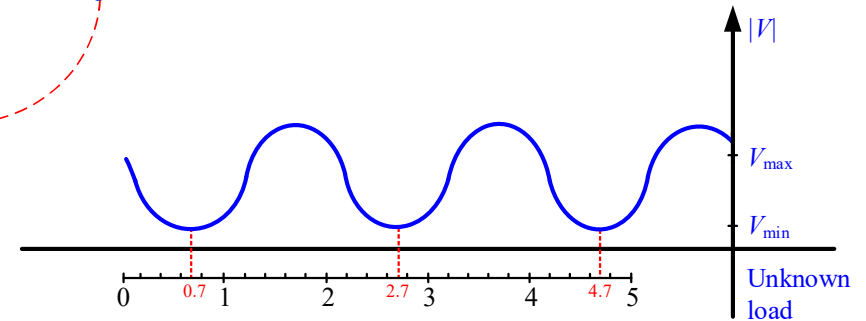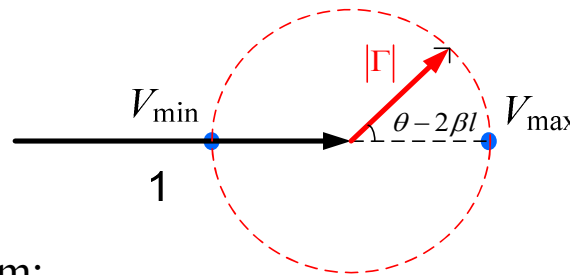- Load impedance from Γ with $l = 0$: $Z_L = Z_0 \frac{1 + \Gamma}{1 - \Gamma} \leftarrow \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$



3 Slotted Transmission Line


- Slotted line example for impedance measurement
 - Two-step procedure
 1. A short circuit is placed at load plane
 - ➔ Resulting in a standing wave on TL with infinite SWR
 - ➔ Voltage minima at $z = 0 \text{ cm}, 2 \text{ cm}, 4 \text{ cm}, \dots$
 2. After short circuit removal, replace with the unknown load.
 - ➔ (V)SWR = 1.5
 - ➔ Voltage minima @ $z = 0.7 \text{ cm}, 2.7 \text{ cm}, 4.7 \text{ cm}, \dots$

Solution)

- Wavelength: $\lambda = (\text{distance between consecutive voltage minimum}) \times 2 = 4 \text{ cm}$
- Since voltage minimum is at 4.7 cm, the next minimum occurs at 2.7 cm.
- Distance from load to first voltage minimum: $l_{\min} = 4 - 2.7 = 1.3 \text{ cm} \rightarrow (1.3/4)\lambda = 0.325\lambda$

$$|\Gamma| = \frac{1.5 - 1}{1.5 + 1} = 0.2 \quad \theta = \pi + 2\beta l_{\min} = \pi + 2\frac{2\pi}{\lambda} l_{\min} = \pi + \frac{4\pi}{4} (1.3) = 2.3\pi = 0.3\pi \rightarrow 54^\circ$$

$$\Gamma = |\Gamma| e^{j\theta} = 0.2e^{j54^\circ} = 0.1176 + j.01618$$

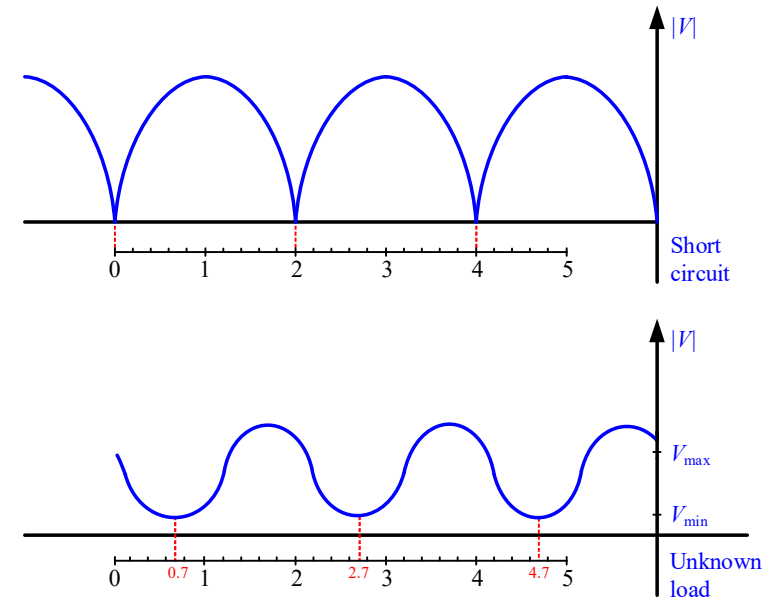

3 Slotted Transmission Line

- Slotted line example for impedance measurement (continued)

- Voltage maximum (or minimum) is occurred at the largest (smallest) resistance.

- Load impedance:

$$Z_L = 50 \frac{1 + \Gamma}{1 - \Gamma} = 50 \frac{1 + (0.1176 + j0.1618)}{1 - (0.1176 + j0.1618)}$$

$$= 59.64 + j20.1 \text{ } [\Omega]$$

- From (V)SWR = 1.5 circle on Smith chart, voltage minimum point must be moved ‘toward load’ (count-clockwise) about 0.325λ .

$$\rightarrow z_L = 1.2 + j0.4$$

$$\rightarrow Z_L = Z_0 \times z_L = 50 \times (1.2 + j0.4) = 60 + j20 \text{ } [\Omega]$$

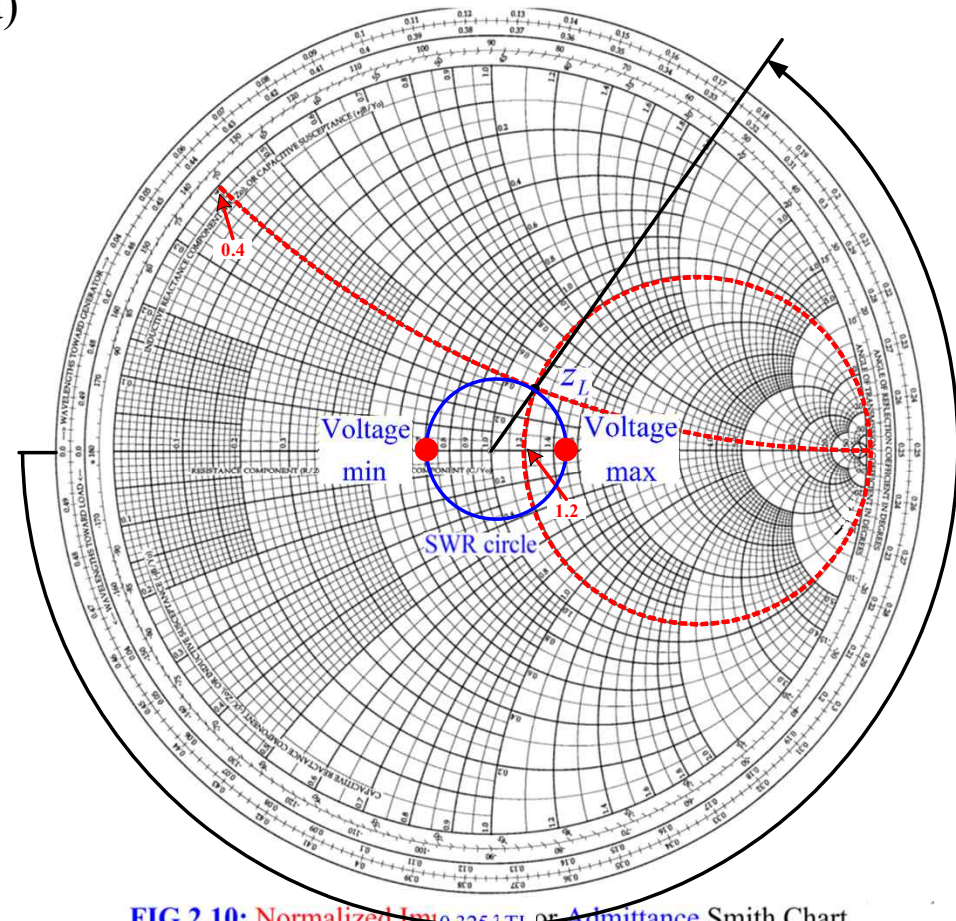


FIG 2.10: Normalized Impedance Smith Chart

4 Review

- Smith chart
 - Reflection coefficient plane
 - Impedance and/or admittance chart
 - Transmission calculation tools
- Smith chart examples
 - Reflection coefficient
 - (V)SWR
 - Input impedance, etc.
- Slotted transmission line for sampling of electric (or magnetic) field of standing wave along transmission line
 - (V)SWR, $|\Gamma|$, Γ , Z_L , etc.
 - Educational tools