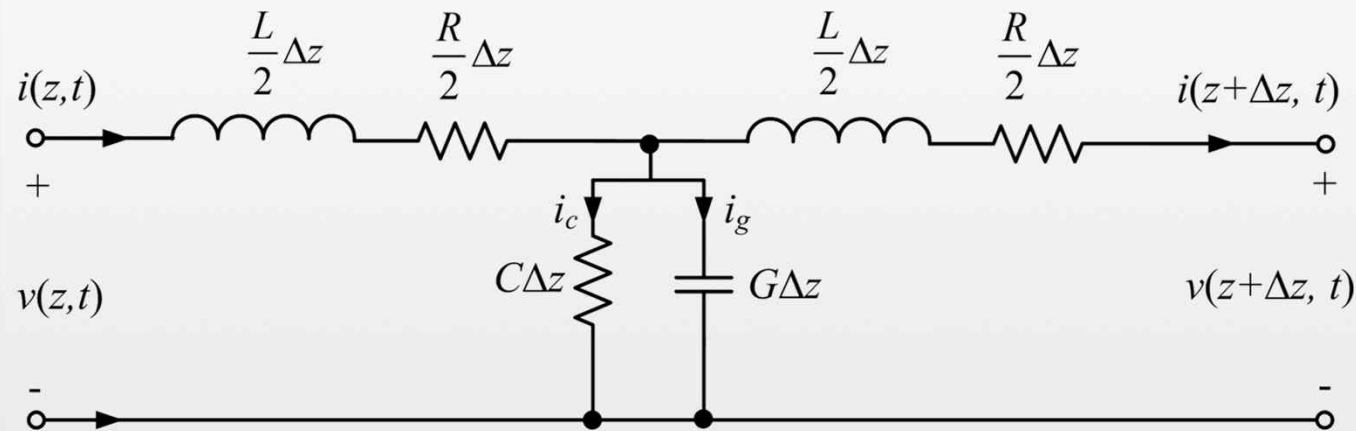


Chapter 2

Transmission Line

Prof. Jeong, Yongchae



Learning Objectives


- Learn circuit parameters measurement with network analyzer
- Understanding $\lambda/4$ impedance transformer operation
- Understanding $\lambda/4$ impedance transformer with multiple reflections
- What is the condition for impedance matching?

Learning contents

- Circuit Measurements: Vector Network Analyzer (VNA)
- Quarter-wavelength ($\lambda/4$) Transformer
- Multiple Reflection Viewpoint for $\lambda/4$ Impedance Transformer
- Impedance Matchings

1 Circuit Measurements: Vector Network Analyzer (VNA)

- In stead of slotted line, modern network analyzers can measure the related parameters.
- Scalar Network analyzer: only signal magnitude measurable
- Vector Network Analyzer (VNA): Magnitude+ phase
- VNAs are extremely versatile instruments that can characterize S -parameters, match complex impedances, (V)SWR, group delay, insertion phase.
- Figure* shows general block diagram of VNA
- Signal can be sent through the device under test (DUT) from input port to output port.
- Network analyzer's receivers measure the incident, reflected, and transmitted signal to calculate S -parameters.

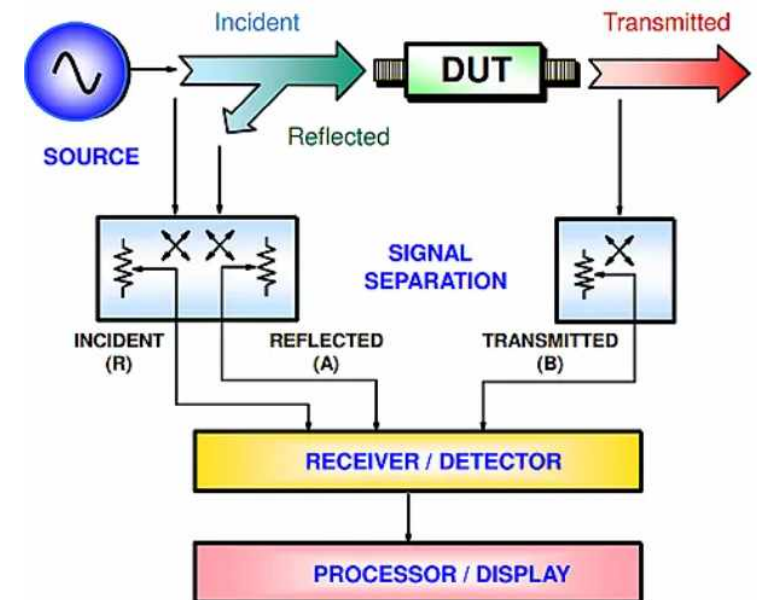


*<https://www.keysight.com/us/en/solutions/measurement-fundamentals/network-analysis.html>

1 Circuit Measurements: Vector Network Analyzer (VNA)

- Reflection measurement: 1-port device under test (DUT)
- Reflection coefficient (or S_{11} -parameters):
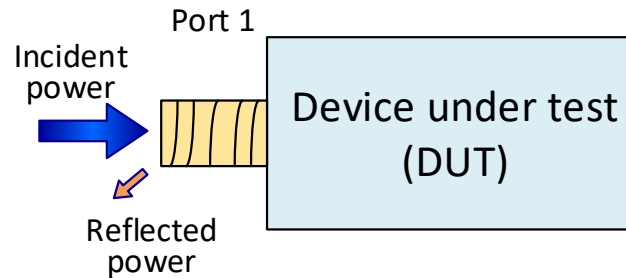
$$S_{11} = \Gamma = \frac{V_{reflected}}{V_{incident}} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$




- Return loss (RL):
- (Voltage) Standing wave ratio ((V)SWR):

$$RL = -20 \log_{10} (|S_{11}|) = -20 \log_{10} (|\Gamma|)$$

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$



- Input impedance:
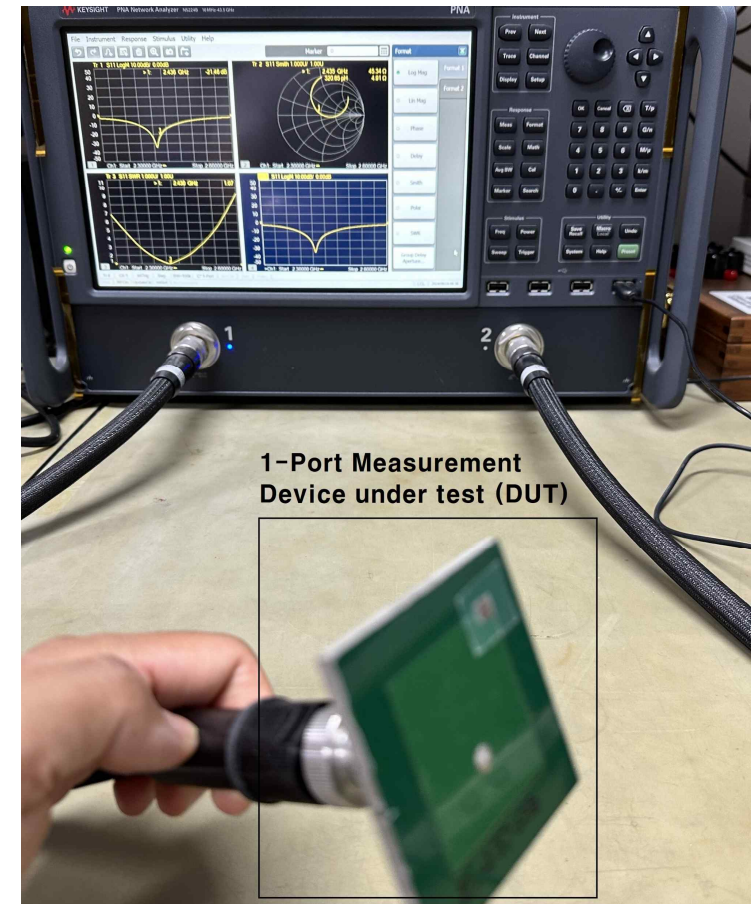
$$Z_{in} = Z_0 \left(\frac{1 + \Gamma}{1 - \Gamma} \right) = Z_0 \left(\frac{1 + S_{11}}{1 - S_{11}} \right)$$





1 Circuit Measurements: Vector Network Analyzer (VNA)

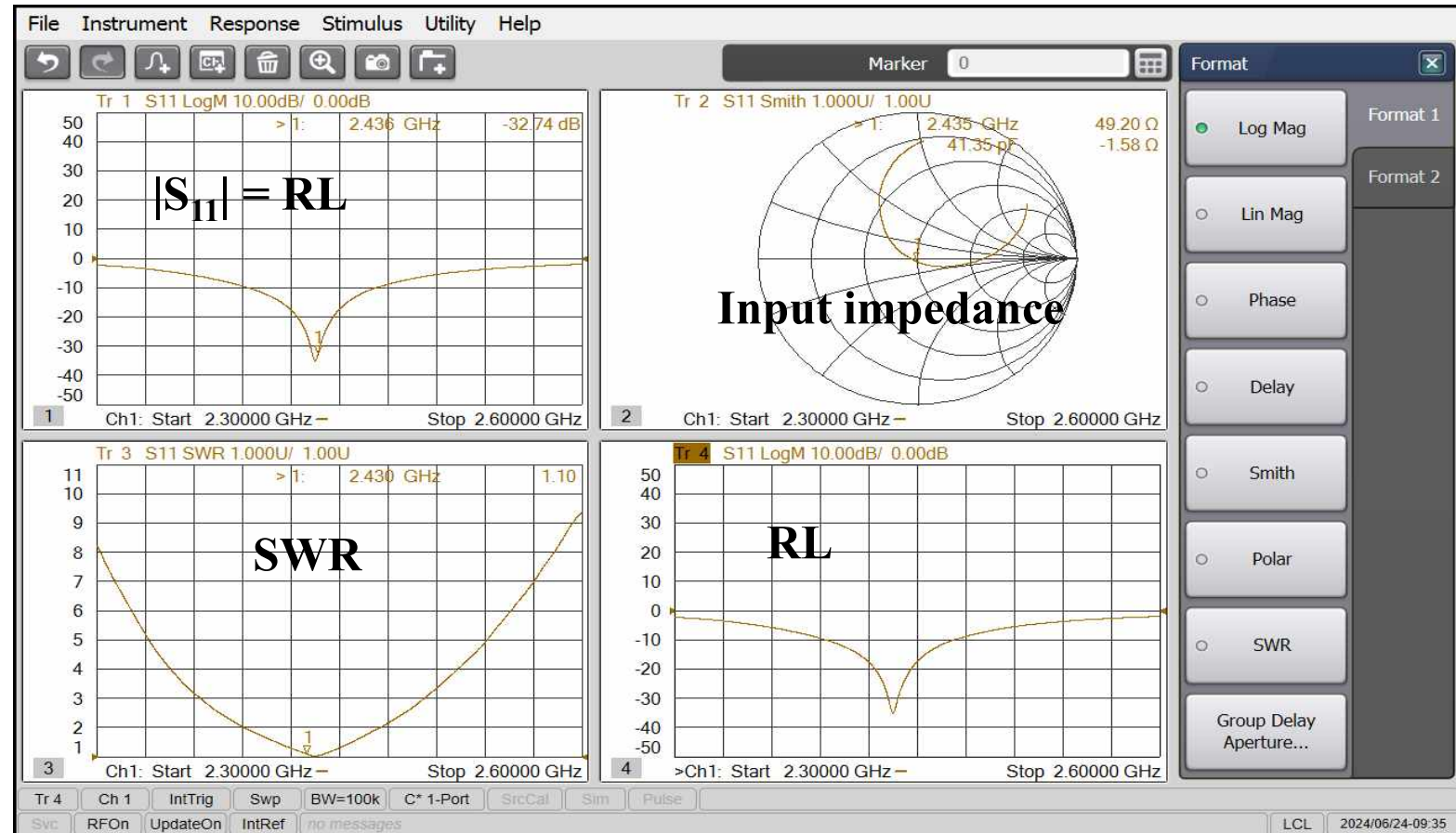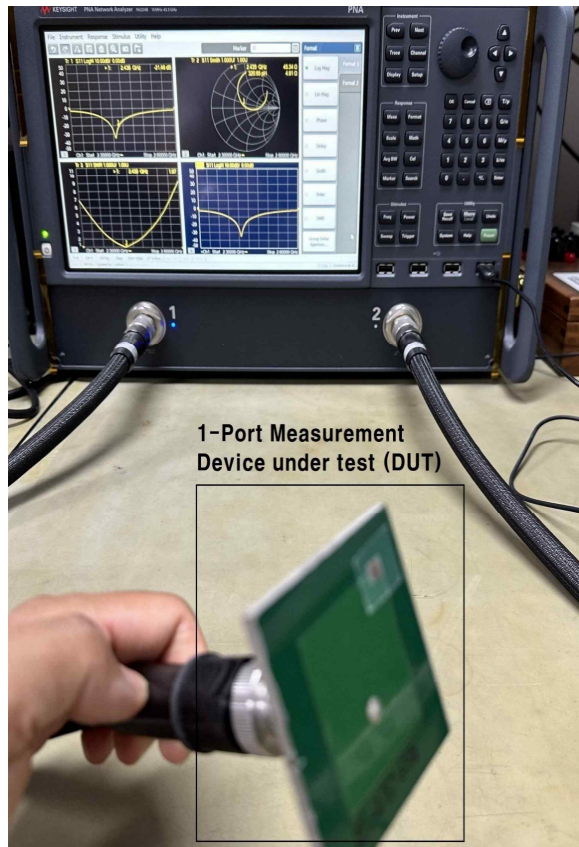- Reflection measurement examples: 1-port device under test (DUT)



1 Circuit Measurements: Vector Network Analyzer (VNA)

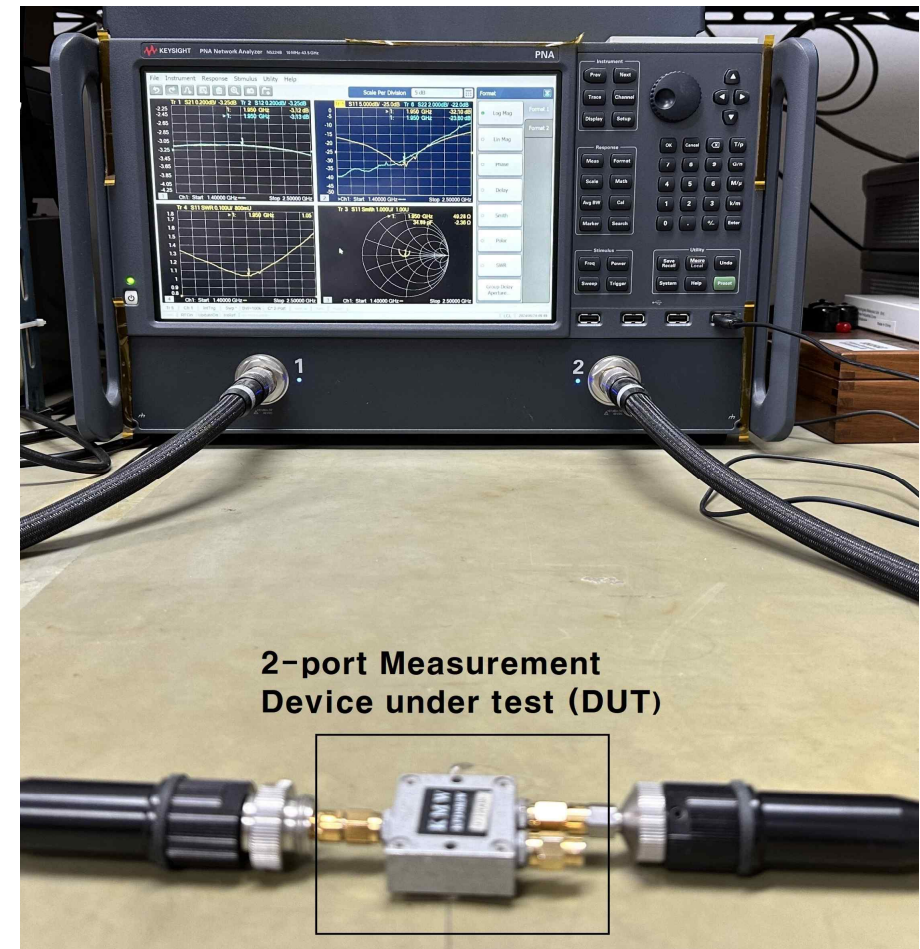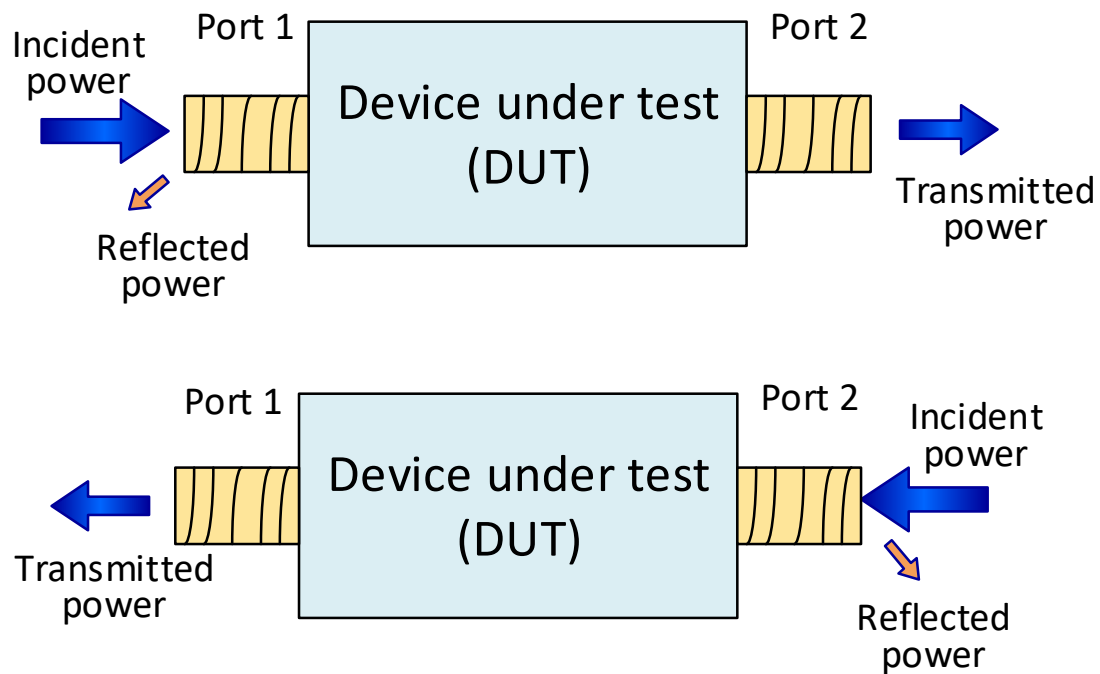- Transmission measurement examples on 2-port devices or circuits



1 Circuit Measurements: Vector Network Analyzer (VNA)

- Transmission measurement: 2-port devices or circuits

- S-parameters: S_{11} , S_{21} , S_{12} , S_{22}

$$S_{11} = \Gamma_{in} = \frac{V_{reflected}^{Port1}}{V_{reflected}^{Port1}} \quad S_{21} = \frac{V_{trasmitted}^{Port2}}{V_{incident}^{Port1}}$$

$$S_{22} = \Gamma_{out} = \frac{V_{reflected}^{Port2}}{V_{reflected}^{Port2}} \quad S_{12} = \frac{V_{trasmitted}^{Port1}}{V_{incident}^{Port2}}$$

- Input and output return losses (RLs):


$$RL_{in} \text{ (dB)} = -20 \log_{10} (|S_{11}|)$$

$$RL_{out} \text{ (dB)} = -20 \log_{10} (|S_{22}|)$$

- Input and output VSWRs:

$$SWR_{in} = \frac{1 - \Gamma_{in}}{1 + \Gamma_{in}}, \quad SWR_{out} = \frac{1 - \Gamma_{out}}{1 + \Gamma_{out}}$$

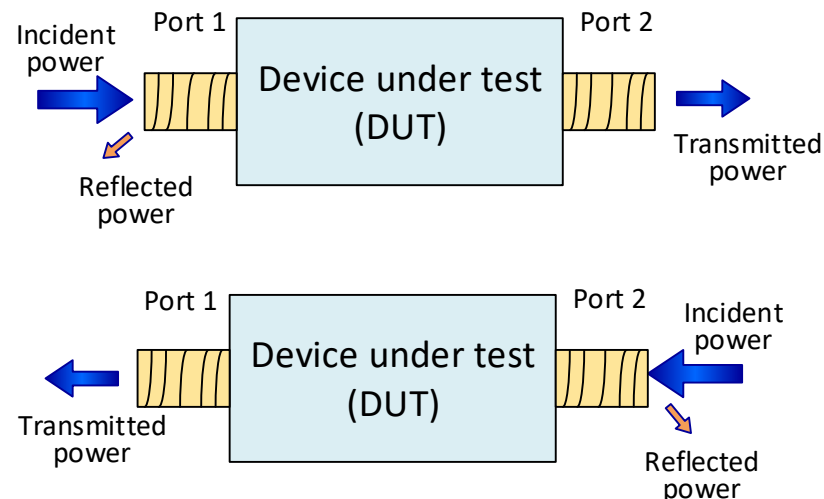- Insertion phase: $IL_{phase} = \angle S_{21}$



- Insertion loss (IL) and Gain:



$$IL_{dB} = -20 \log_{10} (|S_{11}|)$$

$$\text{Gain (dB)} = 20 \log_{10} (|S_{21}|)$$

- Group delay: $\tau = -\frac{d\angle S_{21}}{d\omega}$

1 Circuit Measurements: Vector Network Analyzer (VNA)

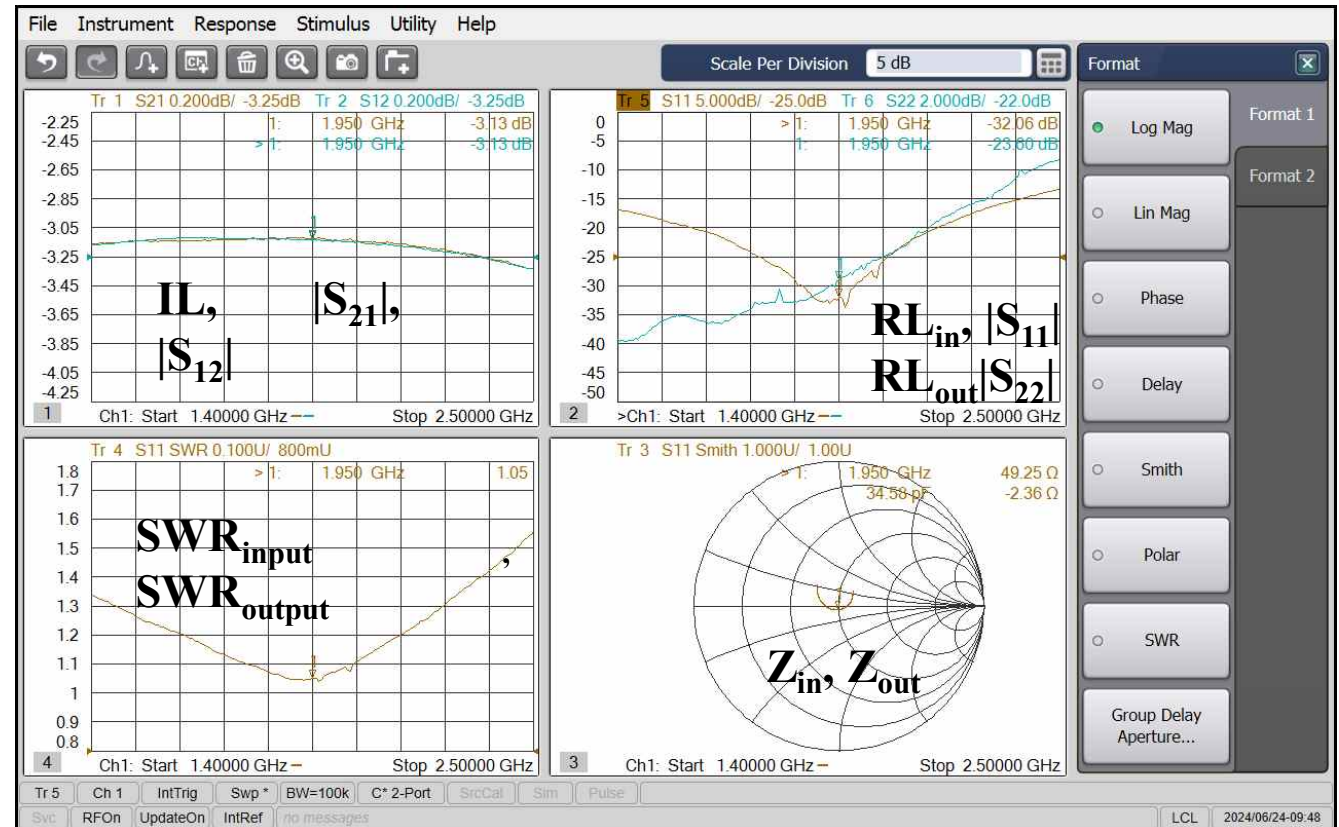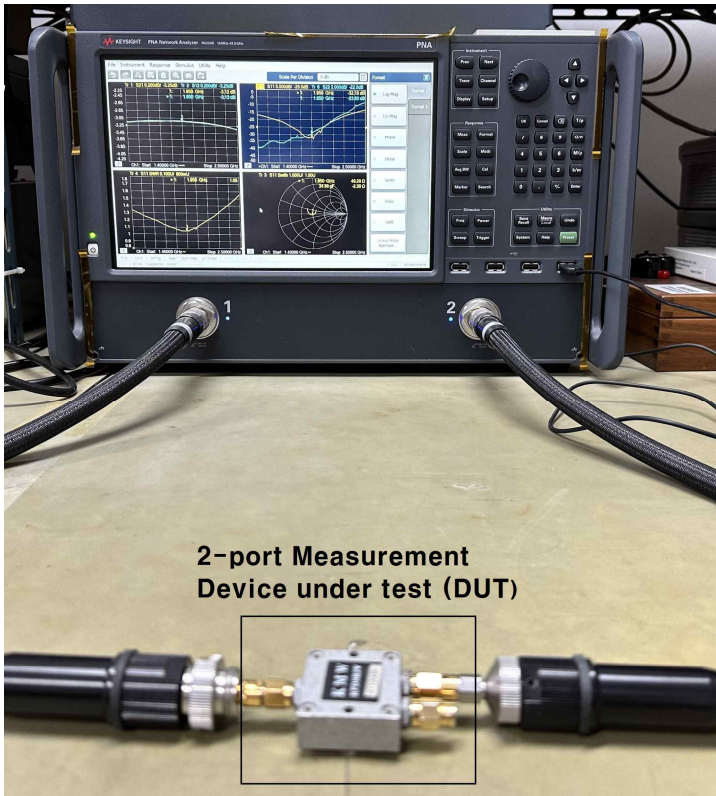- Transmission examples: 2-port device under test (DUT)



2 Quarter-wavelength ($\lambda/4$) Transformer

- Useful and practical circuit in microwave system
- Transmission line terminated with resistance load (R_L)

- quarter-wavelength transmission line of Z_1

- Feedline characteristic impedance: Z_0

- Input impedance:


$$Z_{in} = Z_1 \frac{R_L + jZ_1 \tan \beta l}{Z_1 + jR_L \tan \beta l} \quad \leftarrow \beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2}$$

$$= \frac{Z_1^2}{R_L}$$

- In order for $\Gamma = 0$, we must have $Z_{in} = Z_0$.

$$\frac{Z_1^2}{R_L} = Z_0 \quad \Leftrightarrow \quad Z_1 = \sqrt{Z_0 R_L}$$

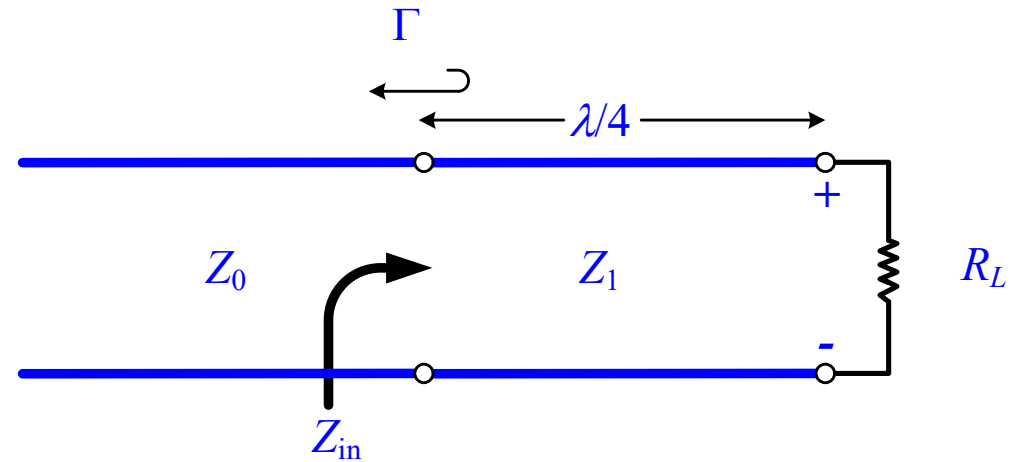- ➔ Geometric mean of load and source impedances
- ➔ No standing waves on feedline (SWR = 1)
- ➔ Only when the length of the matching section is $\lambda/4$ or $(2n + 1)\lambda/4$
- ➔ **A perfect match may be achieved at one frequency (or center frequency)**
- ➔ **Reflection tolerance** permits an operating bandwidth, not only center frequency



2 Quarter-wavelength ($\lambda/4$) Transformer

- Example quarter-wavelength impedance transformer
 - $R_L = 100 \Omega$, $Z_0 = 50 \Omega$,
 - Find characteristic impedance of transmission line of Z_1 and normalized frequency characteristics

Solution) Characteristic impedance of Z_1 :


$$Z_1 = \sqrt{Z_0 R_L} = \sqrt{50 \times 100} = 70.71 [\Omega]$$

- Reflection coefficient magnitude:

$$|\Gamma| = \left| \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right| \quad \leftarrow Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$


$$\beta l = \left(\frac{2\pi}{\lambda} \right) \left(\frac{\lambda_0}{4} \right) = \left(\frac{2\pi f}{v_p} \right) \left(\frac{v_p}{4f_0} \right) = \frac{\pi f}{2 f_0} \quad \leftarrow f \lambda = v_p \text{ or } \lambda = \frac{v_p}{f}$$

$$\beta l \Big|_{f=f_0} = \frac{\pi}{2} : \text{perfect matching}$$

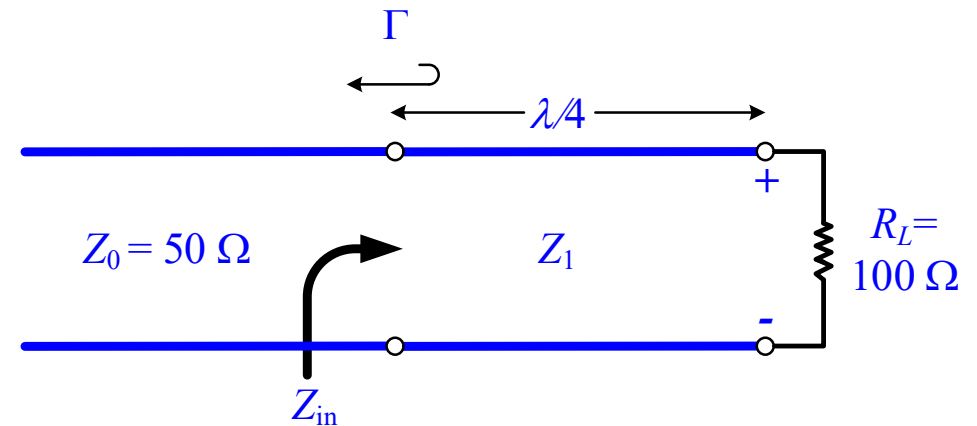

2 Quarter-wavelength ($\lambda/4$) Transformer

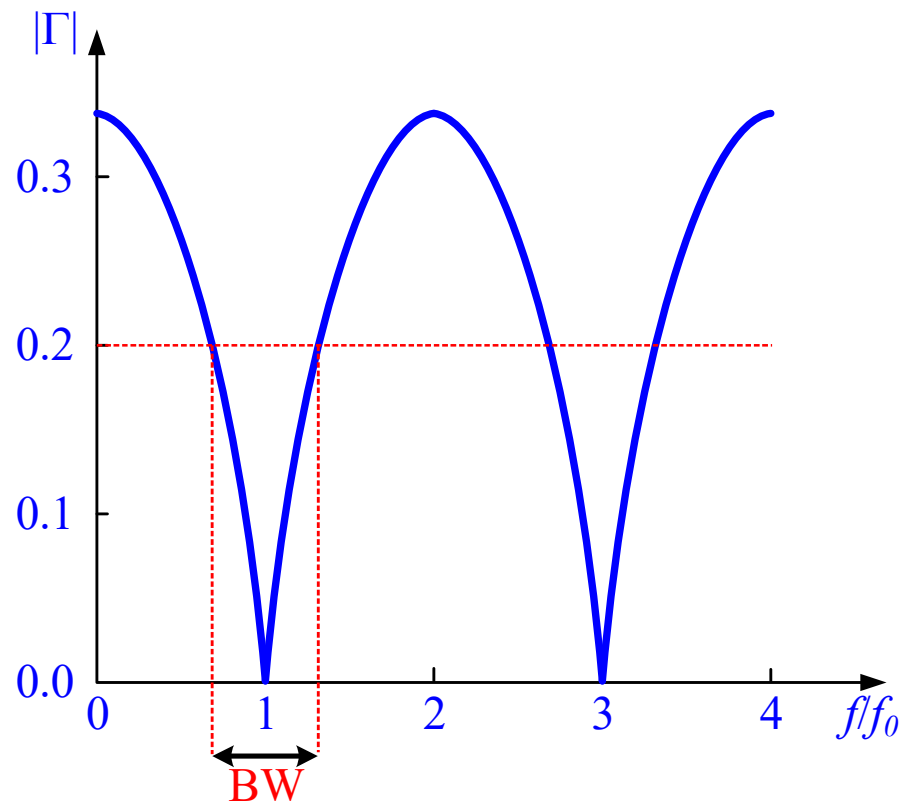- Reflection coefficient characteristics according to normal frequency (f/f_0)




3 Multiple reflection Viewpoint for $\lambda/4$ Impedance Transformer

- Reflection and transmission for $\lambda/4$ impedance transformer
 - Γ : overall reflection coefficient of incident wave
 - Γ_1 : partial reflection coefficient of wave incident on load Z_1 from Z_0 line
 - Γ_2 : partial reflection coefficient of wave incident on load Z_0 from Z_1 line
 - Γ_3 : partial reflection coefficient of wave incident on load R_L from Z_1 line
 - T_1 : partial transmission coefficient of wave from Z_0 line into Z_1 line
 - T_2 : partial transmission coefficient of a wave from Z_1 line into Z_0 line

- Individual coefficients

$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0}, \quad \Gamma_2 = \frac{Z_0 - Z_1}{Z_0 + Z_1} = -\Gamma_1, \quad \Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1},$$
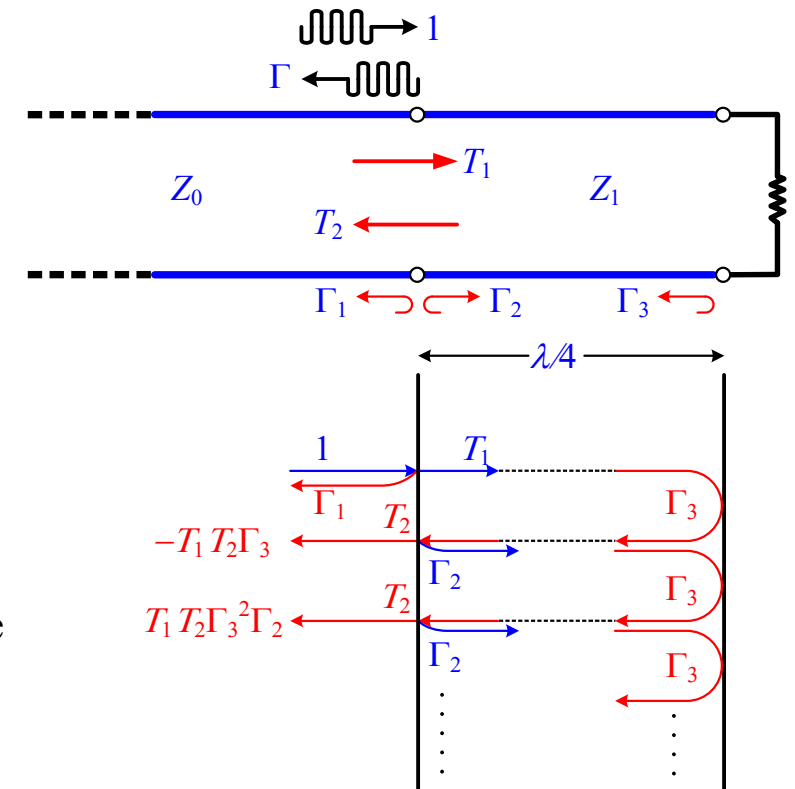
$$T_1 = 1 + \Gamma_1 = \frac{2Z_1}{Z_1 + Z_0}, \quad T_2 = 1 + \Gamma_2 = \frac{2Z_0}{Z_1 + Z_0}$$



3 Multiple reflection Viewpoint for $\lambda/4$ Impedance Transformer

- Total reflection coefficient

$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 + T_1 T_2 \Gamma_2 \Gamma_3^2 - T_1 T_2 \Gamma_2^2 \Gamma_3^3 + \dots \leftarrow 180^\circ \text{ phase shift}$$

$$= \Gamma_1 - T_1 T_2 \Gamma_3 \sum_{n=0}^{\infty} (-\Gamma_2 \Gamma_3)^n$$

- Since $|\Gamma_3| < 1$ and $|\Gamma_2| < 1$,

$$\Gamma = \Gamma_1 - \frac{T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3} \leftarrow \sum_{n=0}^{\infty} x^n = \frac{1}{1-x} \text{ for } |x| < 1$$


$$= \frac{\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3} = \frac{\Gamma_1 - \Gamma_1^2 \Gamma_3 - T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3}$$

- Simplified numerator: $\Gamma_1 - \Gamma_3(\Gamma_1^2 + T_1 T_2) = \Gamma_1 - \Gamma_3 \left[\frac{(Z_1 - Z_0)^2}{(Z_1 + Z_0)^2} + \frac{4Z_1 Z_0}{(Z_1 + Z_0)^2} \right] = \Gamma_1 - \Gamma_3$

$$= \frac{(Z_1 - Z_0)}{(Z_1 + Z_0)} - \frac{(R_L - Z_1)}{(R_L + Z_1)} = \frac{(Z_1 - Z_0)(R_L + Z_1) - (R_L - Z_1)(Z_1 + Z_0)}{(Z_1 + Z_0)(R_L + Z_1)}$$

$$= \frac{(Z_1 R_L + Z_1^2 - Z_0 R_L - Z_0 Z_1) - (Z_1 R_L + Z_0 R_L - Z_1^2 - Z_0 Z_1)}{(Z_1 + Z_0)(R_L + Z_1)} = \frac{2(Z_1^2 - Z_0 R_L)}{(Z_1 + Z_0)(R_L + Z_1)}$$

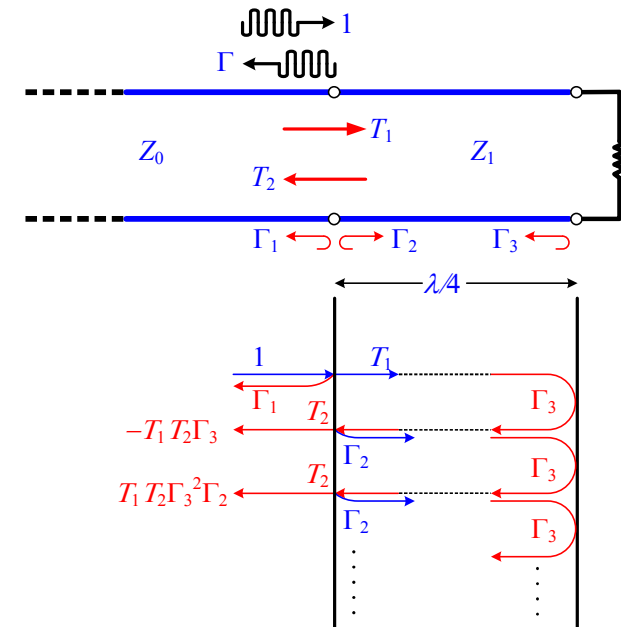- If $Z_1 = \sqrt{Z_0 R_L}$, then $\Gamma = 0$ and the transmission line is matched.



4 Impedance Matchings

- Lossless transmission line circuit with arbitrary generator and load impedances


- Input impedance looking into terminated transmission line from generator:

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{(V_0^+ e^{-j\beta l} + V_0^- e^{-j\beta l})}{(V_0^+ e^{-j\beta l} + V_0^- e^{-j\beta l}) / Z_0} = Z_0 \frac{1 + \Gamma_l e^{-j2\beta l}}{1 - \Gamma_l e^{-j2\beta l}}$$

$$= Z_0 \frac{Z_l + jZ_0 \tan \beta l}{Z_0 + jZ_l \tan \beta l}$$

where Γ_l : reflection coefficient at load

l : length from load

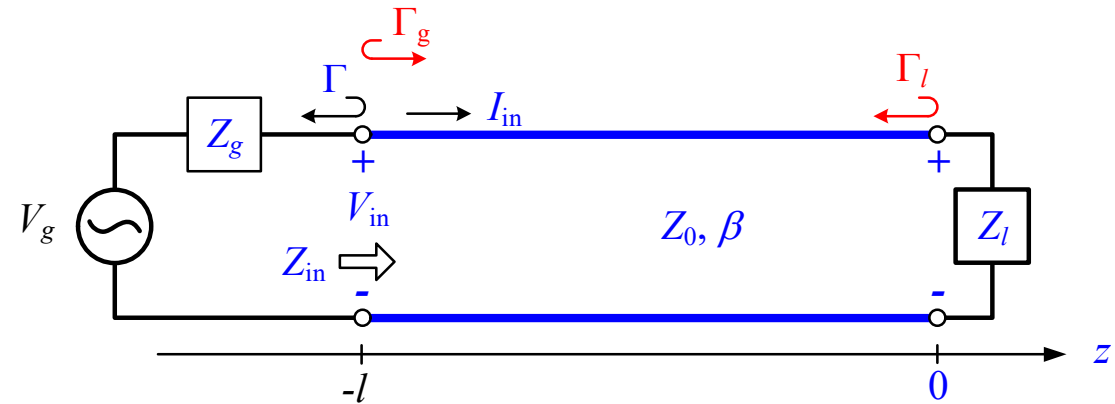

- Voltage wave at arbitrary location of transmission line:

$$V(z) = (V_0^+ e^{-j\beta z} + V_0^- e^{-j\beta z}) = V_0^+ (e^{-j\beta z} + \Gamma_l e^{j\beta z}) \quad \leftarrow \quad \Gamma_l = \frac{Z_l - Z_0}{Z_l + Z_0}$$

- Voltage at generator end (@ $z = -l$)

$$V(-l) = V_g \frac{Z_{in}}{Z_g + Z_{in}} = V_0^+ (e^{j\beta l} + \Gamma_l e^{-j\beta l})$$

$$V_0^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{(e^{j\beta l} + \Gamma_l e^{-j\beta l})}$$

4 Impedance Matchings

- Voltage at generator end (@ $z = -l$ (V_0^+))

$$V_0^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{(e^{j\beta l} + \Gamma_l e^{-j\beta l})} \leftarrow Z_{in} = Z_0 \frac{1 + \Gamma_l e^{-j2\beta l}}{1 - \Gamma_l e^{-j2\beta l}}$$


$$= V_g \frac{Z_0 \frac{1 + \Gamma_l e^{-2j\beta l}}{1 - \Gamma_l e^{-2j\beta l}}}{Z_0 \frac{1 + \Gamma_l e^{-2j\beta l}}{1 - \Gamma_l e^{-2j\beta l}} + Z_g} \frac{1}{e^{j\beta l} + \Gamma_l e^{-j\beta l}}$$

$$= V_g \frac{Z_0}{Z_0 + Z_g} \frac{1}{\frac{1 - \Gamma_l e^{-2j\beta l}}{1 + \Gamma_l e^{-2j\beta l}} e^{j\beta l} + \Gamma_l e^{-j\beta l}} = V_g \frac{Z_0}{Z_0 + Z_g} \frac{1}{\frac{e^{j\beta l} - \Gamma_l e^{-j\beta l}}{e^{j\beta l} + \Gamma_l e^{-j\beta l}} e^{j\beta l} + \Gamma_l e^{-j\beta l}} = V_g \frac{Z_0}{Z_0(e^{j\beta l} + \Gamma_l e^{-j\beta l}) + Z_g(e^{j\beta l} - \Gamma_l e^{-j\beta l})}$$

$$= V_g \frac{Z_0}{e^{j\beta l}(Z_0 + Z_g) + \Gamma_l e^{-j\beta l}(Z_0 - Z_g)} = V_g \frac{Z_0}{Z_0 + Z_g} \frac{1}{e^{j\beta l} + \Gamma_l e^{-j\beta l} \frac{Z_0 - Z_g}{Z_0 + Z_g}} = V_g \frac{Z_0}{Z_0 + Z_g} \frac{1}{e^{j\beta l} - \Gamma_l e^{-j\beta l} \frac{Z_g - Z_0}{Z_g + Z_0}}$$

$$= V_g \frac{Z_0}{Z_0 + Z_g} \frac{1}{e^{j\beta l} - \Gamma_l \Gamma_g e^{-j\beta l}} = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-j\beta l}}{1 - \Gamma_l \Gamma_g e^{-2j\beta l}}$$

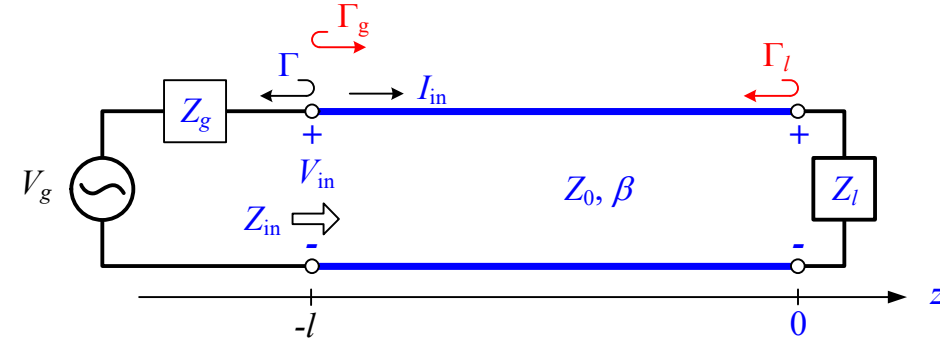where Γ_g : reflection coefficient seen looking into generator $\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}$




4 Impedance Matchings

- (Averaging) Power delivered to load:

$$P = \operatorname{Re}\left[\frac{V_{\text{in}}}{\sqrt{2}} \frac{I_{\text{in}}^*}{\sqrt{2}}\right] = \frac{1}{2} \operatorname{Re}[V_{\text{in}} I_{\text{in}}^*] = \frac{1}{2} |V_{\text{in}}|^2 \operatorname{Re}\left[\frac{1}{Z_{\text{in}}^*}\right]$$

$$= \frac{1}{2} |V_g|^2 \left| \frac{Z_{\text{in}}}{Z_{\text{in}} + Z_g} \right|^2 \operatorname{Re}\left[\frac{1}{Z_{\text{in}}^*}\right]$$

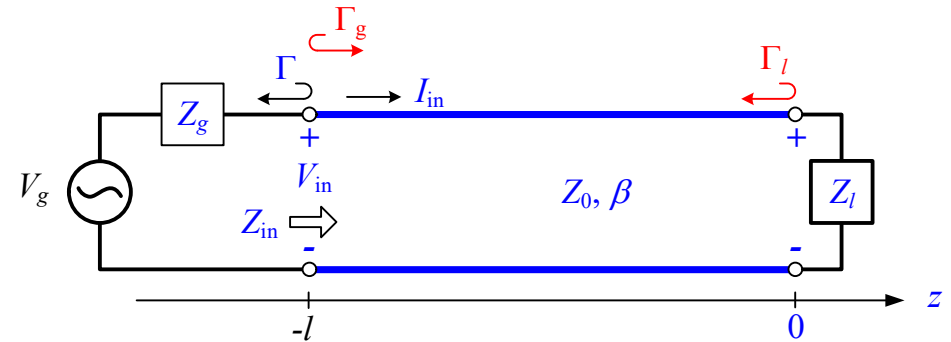

- Let assume general source and load conditions: $Z_{\text{in}} = R_{\text{in}} + jX_{\text{in}}$ and $Z_g = R_g + jX_g$

$$P = \frac{1}{2} |V_g|^2 \frac{|Z_{\text{in}}|^2}{(R_{\text{in}} + R_g)^2 + (X_{\text{in}} + X_g)^2} \operatorname{Re}\left[\frac{1}{Z_{\text{in}}^*}\right] = \frac{1}{2} |V_g|^2 \frac{|Z_{\text{in}}|^2}{(R_{\text{in}} + R_g)^2 + (X_{\text{in}} + X_g)^2} \operatorname{Re}\left[\frac{Z_{\text{in}}}{|Z_{\text{in}}|^2}\right]$$

$$= \frac{1}{2} |V_g|^2 \frac{|Z_{\text{in}}|^2}{(R_{\text{in}} + R_g)^2 + (X_{\text{in}} + X_g)^2} \frac{\operatorname{Re}(Z_{\text{in}})}{|Z_{\text{in}}|^2} = \frac{1}{2} |V_g|^2 \frac{R_{\text{in}}}{(R_{\text{in}} + R_g)^2 + (X_{\text{in}} + X_g)^2}$$

- Assume that the generator impedance (Z_g) is fixed and consider three cases according to load impedance.

4 Impedance Matchings

- Case study 1: load matched to transmission line

- $Z_l = Z_0 \rightarrow \Gamma_l = 0$ & (V)SWR = 1.

- $Z_{in} = Z_0 \neq Z_g$

- Power delivered to load:

$$P = \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \Big|_{Z_l=Z_0=R_{in}} = \frac{1}{2} |V_g|^2 \frac{Z_0}{(Z_0 + R_g)^2 + X_g^2}$$


- Case study 2: generator matched to transmission line

- $Z_{in} = Z_g \rightarrow \Gamma_l = 0$ & (V)SWR = 1.

- Overall reflection coefficient: $\Gamma = \frac{Z_{in} - Z_g}{Z_{in} + Z_g} = 0$

- Power delivered to load: $P = \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \Big|_{Z_g=Z_{in}} = \frac{1}{2} |V_g|^2 \frac{R_g}{(R_g + R_g)^2 + (X_g + X_g)^2}$

$$= \frac{1}{2} |V_g|^2 \frac{R_g}{4(R_g^2 + X_g^2)} = \frac{1}{8} |V_g|^2 \frac{R_g}{R_g^2 + X_g^2}$$

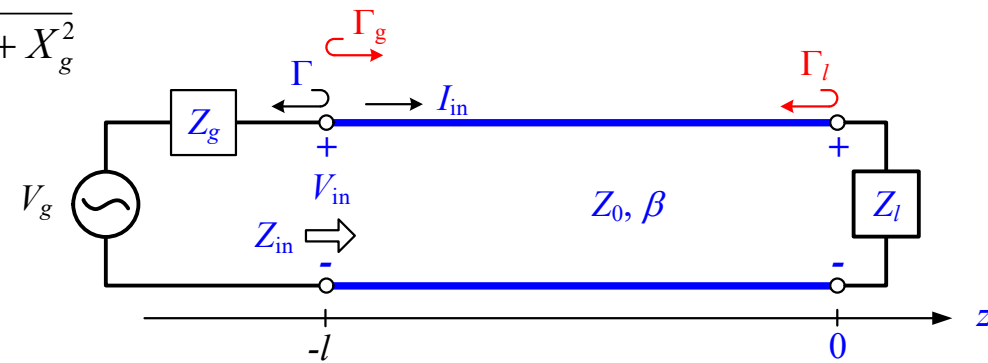

4 Impedance Matchings

Case study 3: *conjugate matching*

- Assumption: fixed generator impedance (Z_g)
- Variable input impedance (Z_{in}) due to unknown load impedance (Z_l) and length of transmission line
- Conditions for maximum power delivered to load:

$$\text{Condition 1: } \frac{\partial P}{\partial R_{in}} = \frac{\partial}{\partial R_{in}} \left[\frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \right] = 0 \leftarrow \frac{d}{dx} \left(\frac{f}{g} \right) = \frac{f'g - fg'}{g^2}$$


$$\rightarrow \frac{1}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} + \frac{-2R_{in}(R_{in} + R_g)}{[(R_{in} + R_g)^2 + (X_{in} + X_g)^2]^2} = 0$$

$$(R_{in} + R_g)^2 + (X_{in} + X_g)^2 - 2R_{in}(R_{in} + R_g) = 0$$

$$R_g^2 - R_{in}^2 + (X_{in} + X_g)^2 = 0 \quad (*)$$

$$\text{Condition 2: } \frac{\partial P}{\partial X_{in}} = 0 \rightarrow \frac{-2R_{in}(X_{in} + X_g)}{[(R_{in} + R_g)^2 + (X_{in} + X_g)^2]^2} = 0$$

$$R_{in}(X_{in} + X_g) = 0 \quad (**)$$

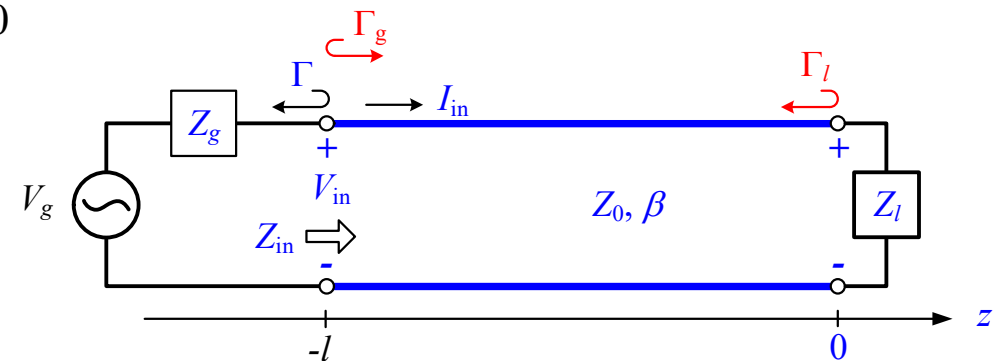

4 Impedance Matchings


- Solving (*) and (**) simultaneously for $R_{in} (\neq 0)$ and X_{in}

$$(R_{in} = R_g \text{ and } X_{in} = -X_g) \leftrightarrow Z_{in} = Z_g^*$$

- Maximum power delivered to load:

$$P = \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \Big|_{R_{in}=R_g \text{ \& } X_{in}=-X_g}$$

$$= \frac{1}{2} |V_g|^2 \frac{R_g}{(R_g + R_g)^2 + (-X_g + X_g)^2} = \frac{1}{2} |V_g|^2 \frac{1}{4R_g}$$

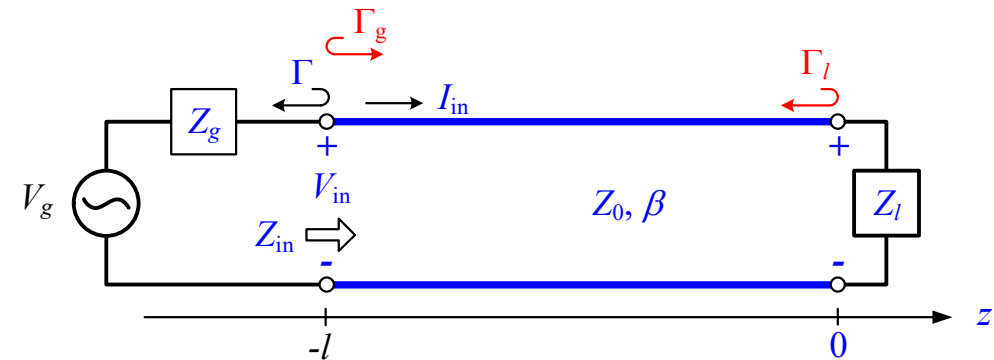

→ **Conjugate matching**

→ **Maximum power transfer** to load for fixed generator impedance

$$\text{cf.) } P = \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \Big|_{Z_l=Z_0=R_{in}} = \frac{1}{2} |V_g|^2 \frac{Z_0}{(Z_0 + R_g)^2 + X_g^2} \quad (\text{case study \#1})$$

$$P = \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \Big|_{Z_g=Z_{in}} = \frac{1}{2} |V_g|^2 \frac{R_g}{4(R_g^2 + X_g^2)} \quad (\text{case study \#2})$$

5 Review

- Network analyzer
 - General and widely used circuit measurement system
 - 1 ~ n ports network measurement
 - Magnitude and phase
 - S -parameters, RL, IL, GD, etc
- $\lambda/4$ Impedance Transformer
- Impedance matching
 - $Z_{in} = Z_g^*$ or $Z_g = Z_{in}^*$
 $\Leftrightarrow Z_{in} = R_{in} + jX_{in} = R_g - jX_g^*$
 - At any reference plane