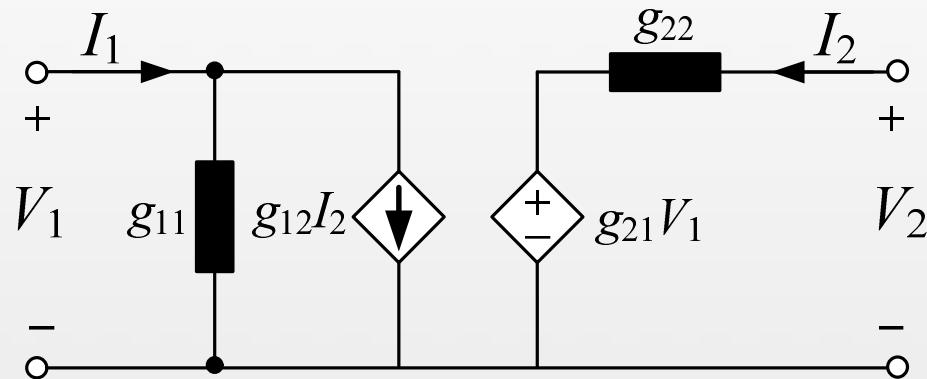


Chapter 4

Microwave Network Analysis

Prof. Jeong, Yongchae



Learning Objectives



- Know about impedance parameters (or Z-parameters)
- Know about admittance parameters (or Y-parameters)
- Know about hybrid and inverse hybrid parameters (or h - and g -parameters)

Learning contents

- Impedance Parameters
- Admittance parameters
- Hybrid and Inverse Hybrid Parameters

Impedance Parameters

- **Impedance parameter (Z-parameters)**
 - Z-parameters describe the interactions between voltages and currents in 2-port network under open-circuited condition.
 - By setting input or output ports to be open-circuited, the Z-parameter of input and output ports can be calculated.
 - The input and output of a 2-port network can be either voltage or current.
 - Network driven by voltages
 - Network driven by currents

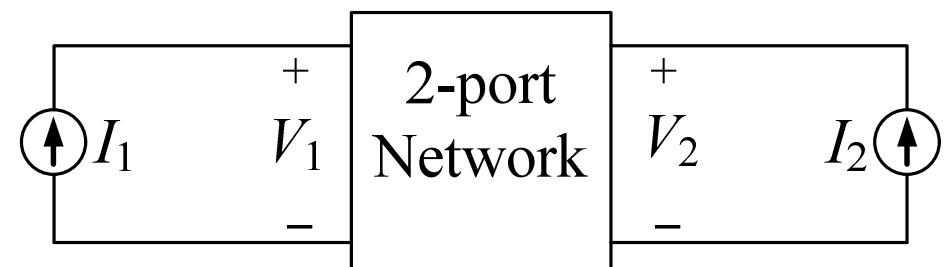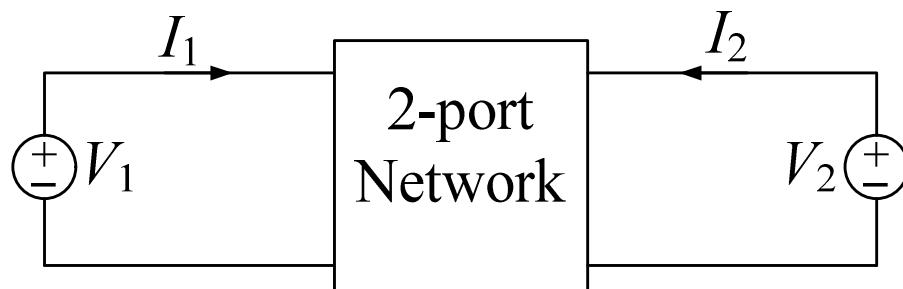

1

Impedance Parameters

- The ratios of voltage to current can be defined as:


$$\frac{V_1}{I_1}, \frac{V_1}{I_2}, \frac{V_2}{I_1}, \text{ and } \frac{V_2}{I_2}$$

- These four ratios are considered as input, output, trans-impedance of the network:



$$Z_{ij} = \frac{V_i}{I_j}$$

@ $i = j$, input and output impedance

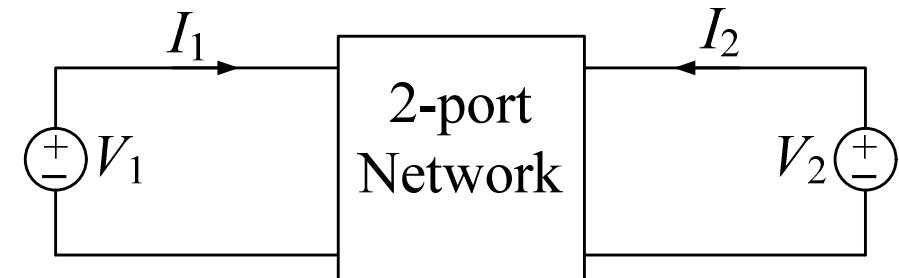@ $i \neq j$, forward or reverse trans-impedance



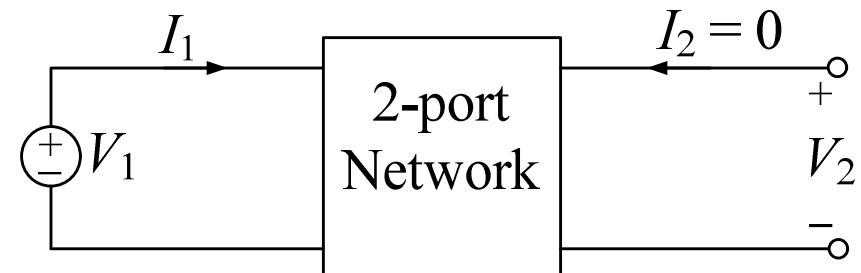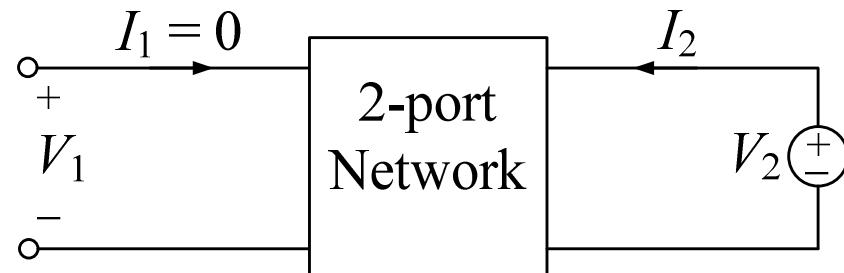- The values of Z-parameters in a 2-port network can be determined with the condition of $I_1 = 0$ or $I_2 = 0$.
→ Open conditions




1

Impedance Parameters

- For $I_2 = 0$ or output port is open-circuited:

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad : \text{Open-circuited input impedance}$$


$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad : \text{Open-circuited trans-impedance from input port to output port}$$

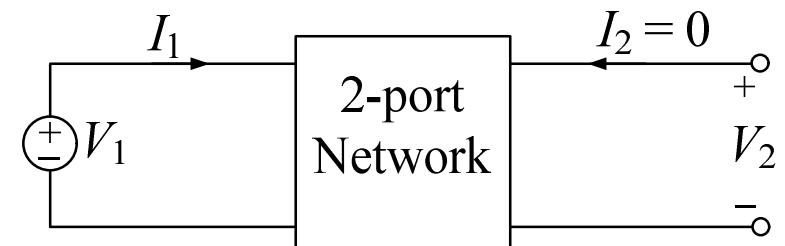

- For $I_1 = 0$ or input port is open-circuited:

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad : \text{Open-circuited output impedance}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad : \text{Open-circuited trans-impedance from output port to input port}$$

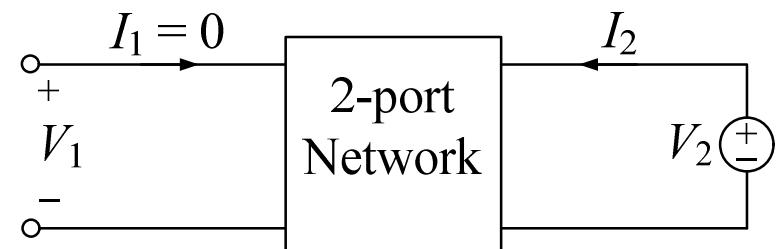

Impedance Parameters

- Relation between voltage and current of 2-port network with Z -parameters:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad (1)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad (2)$$

- Matrix form of Z -parameters :



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

- For a symmetrical network: $Z_{11} = Z_{22}$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

- For reciprocal network: $Z_{21} = Z_{12}$


$$\left. \frac{V_2}{I_1} \right|_{I_2=0} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

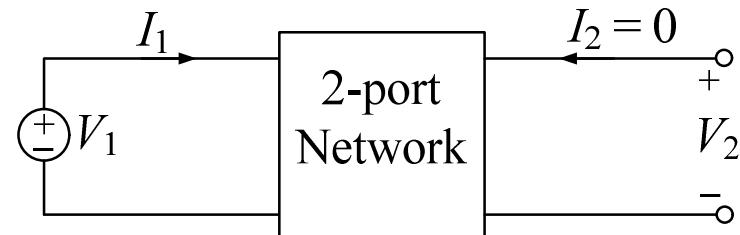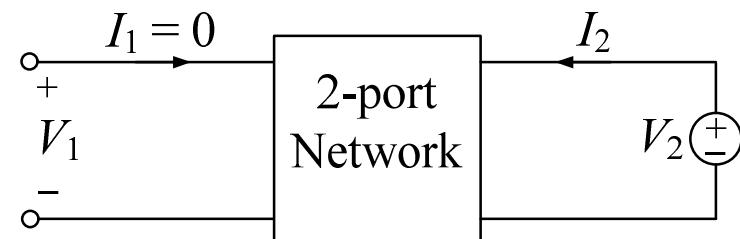


1

Impedance Parameters

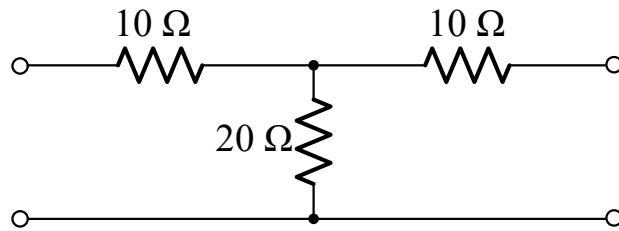
- Example: Calculate the values of Z-parameter of the following circuit.



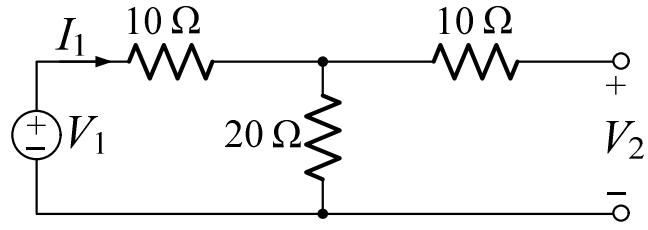- Solution: The values of Z-parameter can be calculated as the following:



$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{(10+20)I_1}{I_1} = 30 \Omega$$

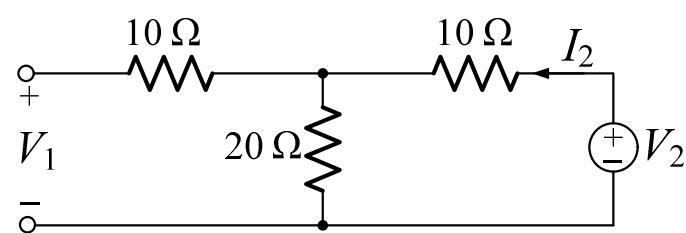


$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{20I_1}{I_1} = 20 \Omega$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{(10+20)I_2}{I_2} = 30 \Omega$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{20I_2}{I_2} = 20 \Omega$$

2 Admittance Parameters

- **Admittance parameters (Y -parameters)**
 - Y -parameters describe the interactions between voltages and currents in 2-port network under short-circuited condition.
 - By setting input or output port to short-circuited, the Y -parameter of input and output ports can be calculated.
 - The input and output of a 2-port network can be either voltage or current.
 - Network driven by current at input port and short-circuited at output port
 - Network driven by currents by current at output port and short-circuited at input port

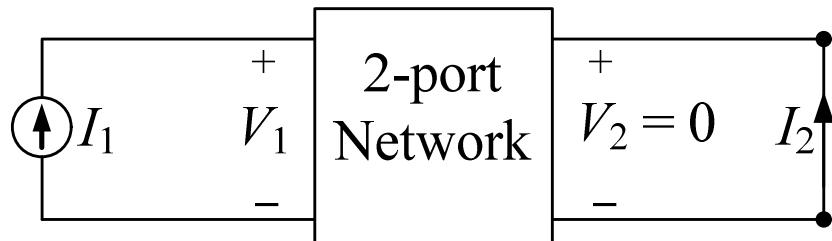

2 Admittance Parameters

- The ratio of current to voltage can be defined as:




$$\frac{I_1}{V_1}, \frac{I_1}{V_2}, \frac{I_2}{V_1}, \text{ and } \frac{I_2}{V_2}$$

- These four ratios are considered as input, output, trans-admittance of the network:

$$Y_{ij} = \frac{I_i}{V_j}$$

- The values of Y -parameters in a 2-port network can be determined with the condition of $V_1 = 0$ or $V_2 = 0$.

→ Short conditions

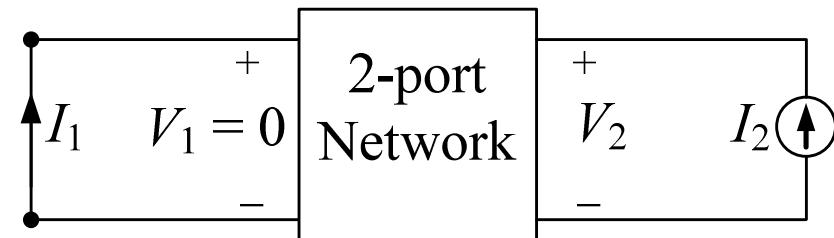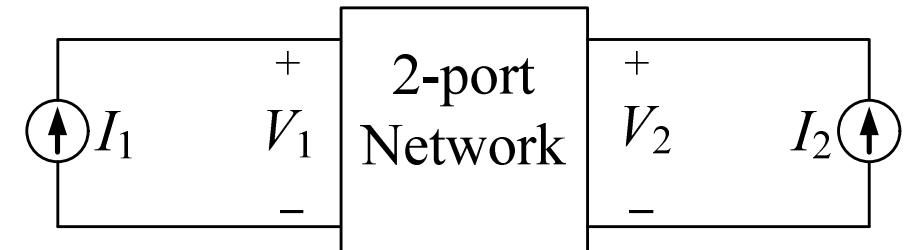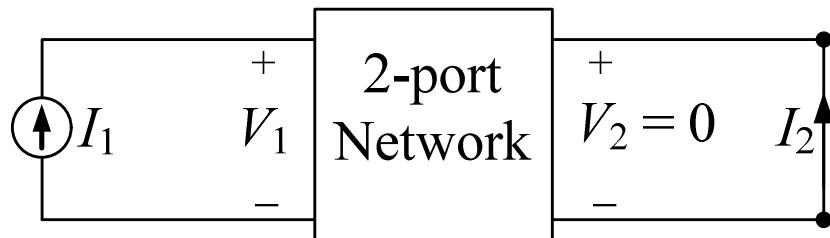


2 Admittance Parameters

- For $V_2 = 0$ or output port is short-circuited:

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad : \text{Short-circuited input admittance}$$


$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad : \text{Short-circuited trans-admittance from input port to output port}$$

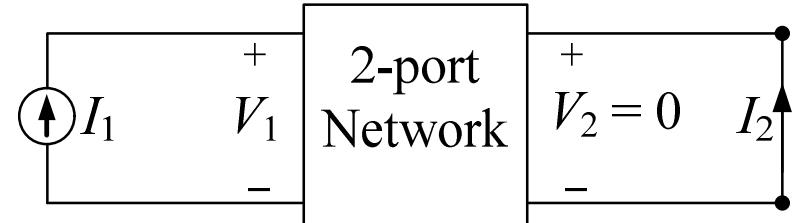

- For $V_1 = 0$ or input port is short-circuited:

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \quad : \text{Short-circuited output admittance}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad : \text{Short-circuited trans-admittance from output port to input port}$$

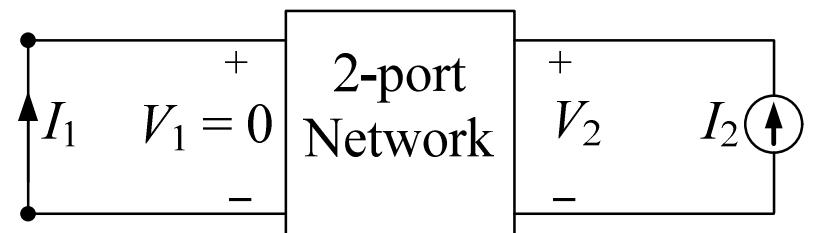

2 Admittance Parameters

- Relation between current and voltage of 2-port network with Y -parameters:

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad (3)$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad (4)$$

- Matrix form of Y -parameters:



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- For a symmetrical network: $Y_{11} = Y_{22}$

$$\left. \frac{I_1}{V_1} \right|_{V_2=0} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

- For reciprocal network: $Y_{21} = Y_{12}$

$$\left. \frac{I_2}{V_1} \right|_{V_2=0} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

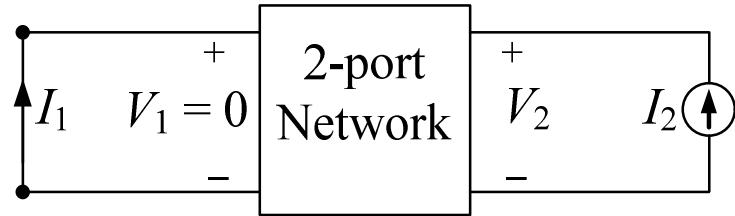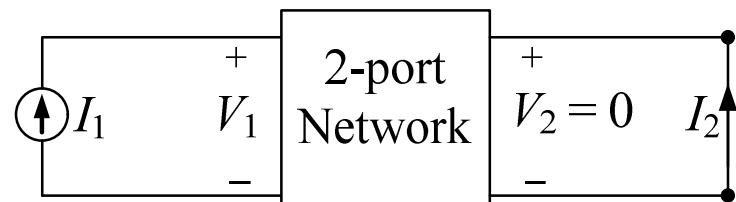

2 Admittance Parameters

- Example: Calculate Y -parameter of given network.

- Solution:

Applying Kirchoff's current law at node “ a ”:

$$I_1 = I_3 + I_4 = V_1 Y_A + (V_1 - V_2) Y_B = (Y_A + Y_B) V_1 - Y_B V_2 \quad (5)$$

Apply Kirchoff's current law at node “ b ”:


$$I_2 = I_5 - I_4 = V_2 Y_C - (V_1 - V_2) Y_B = -Y_B V_1 + (Y_B + Y_C) V_2 \quad (6)$$

Comparing equations (3) and (5):

$$Y_{11} V_1 + Y_{12} V_2 = (Y_A + Y_B) V_1 - Y_B V_2$$

$$\Rightarrow Y_{11} = Y_A + Y_B$$

$$\Rightarrow Y_{12} = -Y_B$$

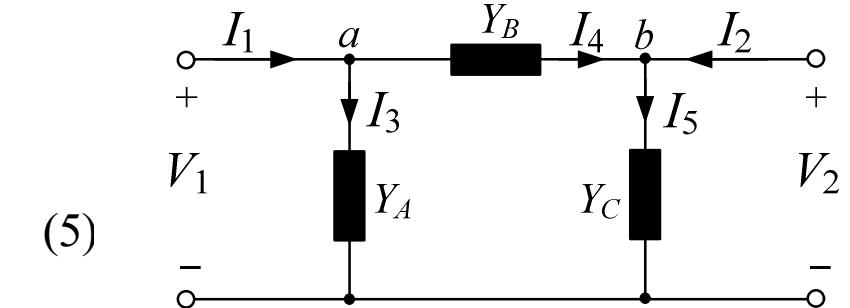

Comparing equation (4) and (6):

$$Y_{21} V_1 + Y_{22} V_2 = -Y_B V_1 + (Y_B + Y_C) V_2$$



$$\Rightarrow Y_{21} = -Y_B$$

$$\Rightarrow Y_{22} = Y_B + Y_C$$

Hybrid Parameters

- **Hybrid parameters (*h*-parameters)**

- *h*-parameters includes short-circuited input impedance and open-circuited output admittance for comprehensive network analysis.
- *h*-parameters use *Z*-parameter, voltage ratios, *Y*-parameter, and current ratios to shows the relationship between voltage and current in a 2-port network.
- In cases where *Z*-parameters are impractical such as with the ideal transformer, *h*-parameter provides a viable solution for circuit analysis.
- Network driven by voltage at input port and short-circuited at output port
- Network driven by voltage at output port and open-circuited at input port

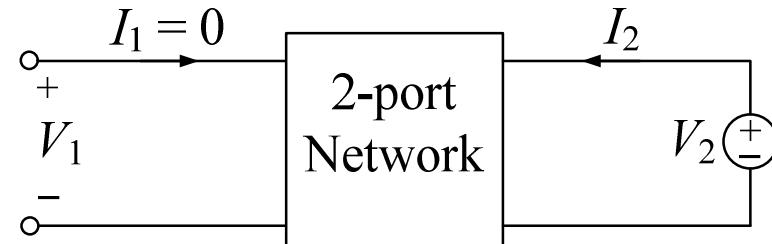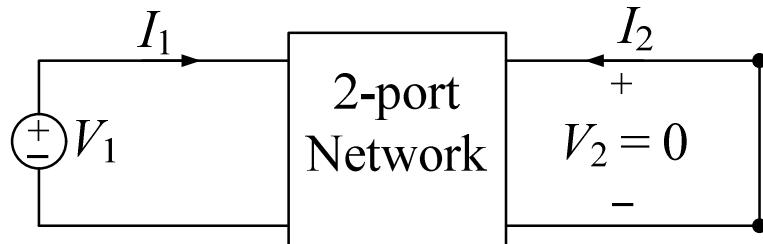

3

Hybrid Parameters

- Relation between current and voltage of 2-port network with h -parameters:

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad (7)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad (8)$$


- Matrix form of h -parameters:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

- For $V_2 = 0$ or output port is short-circuited:

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad : \text{Short-circuited input impedance}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad : \text{Short-circuited current gain}$$

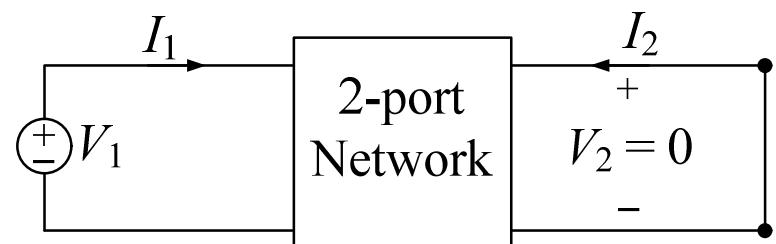


3

Hybrid Parameters


- For $I_1 = 0$ or input port is open-circuited:

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad : \text{Open-circuited output admittance}$$

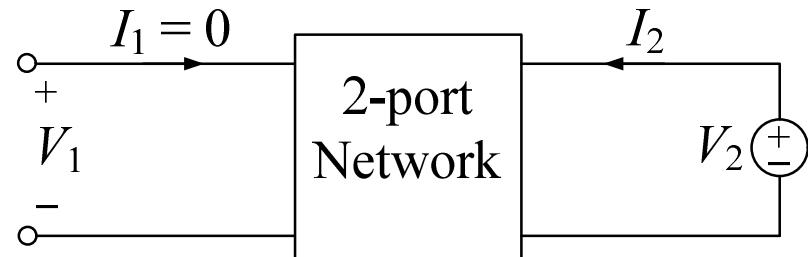

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad : \text{Open-circuited reverse voltage gain}$$

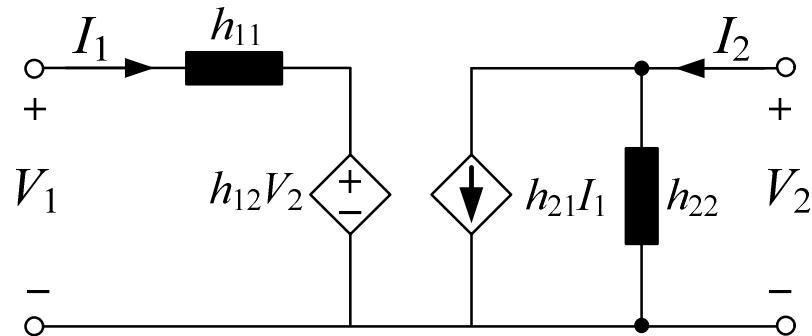- h -parameter are crucial for analyzing bipolar junction transistors (BJTs).





4 Inverse Hybrid Parameters

- **Inverse hybrid parameters (g -parameters)**

- g -parameters can be obtained in a similar way to h -parameters.
- The port termination conditions of g -parameters are inverse to h -parameters.

- Network driven by voltage at input port and open-circuited at output port

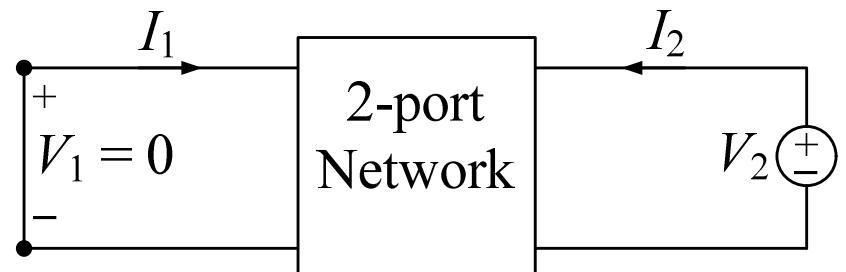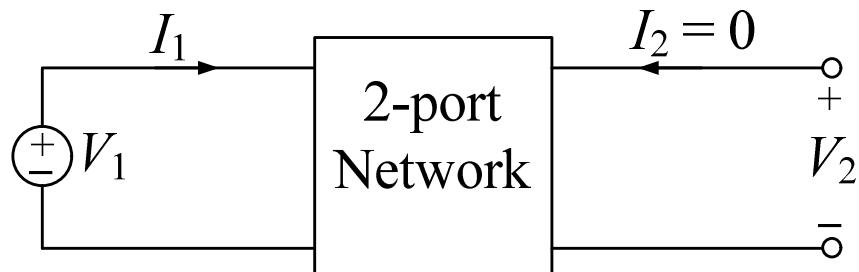- Network driven by voltage at output port and short-circuited at input port



4 Inverse Hybrid Parameters

- Relation between current and voltage of 2-port network with g -parameters:

$$I_1 = g_{11}V_1 + g_{12}I_2 \quad (9)$$

$$V_2 = g_{21}V_1 + g_{22}I_2 \quad (10)$$


- Matrix form of g -parameters:

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

- For $I_2 = 0$ or output port is open-circuited:

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \quad : \text{Open-circuited input admittance}$$


$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad : \text{Open-circuited voltage gain}$$

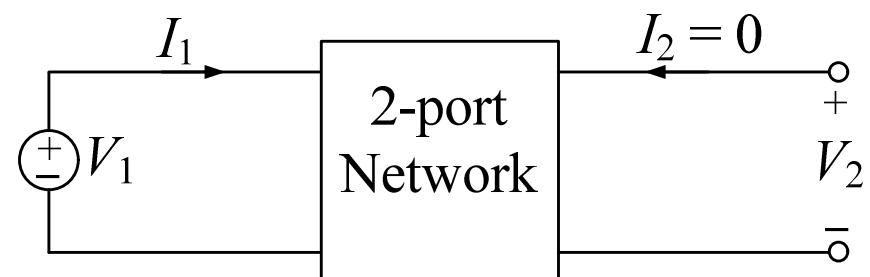

4 Inverse Hybrid Parameters


- For $V_1 = 0$ or input port is short-circuited:

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} \quad : \text{Short-circuited output impedance}$$

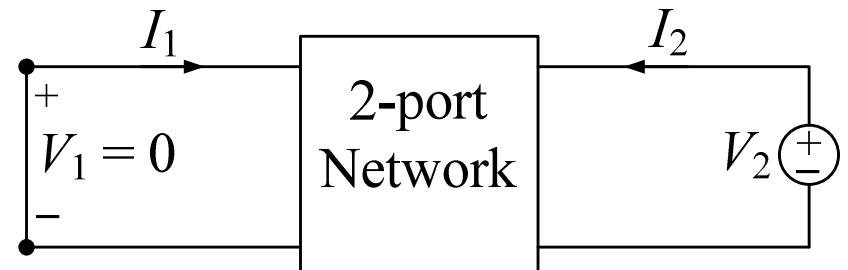

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} \quad : \text{Short-circuited reverse current gain}$$

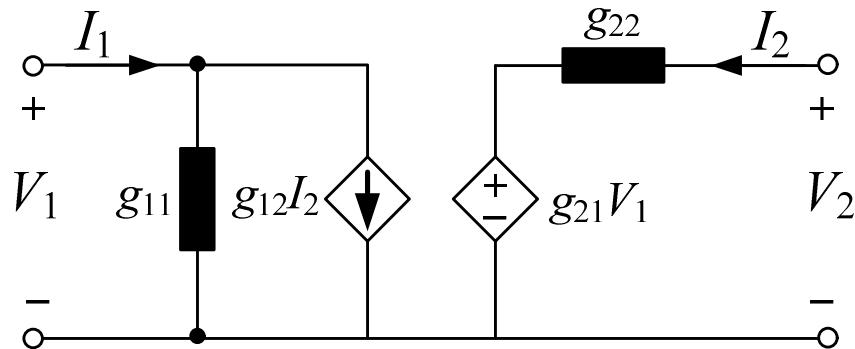- g -parameter are crucial for analyzing junction field effect transistors (JFETs).



- Impedance parameters or Z -parameters
- Admittance parameters or Y -parameters
- Hybrid parameters or h -parameters
- Inverse hybrid parameters or g -parameters