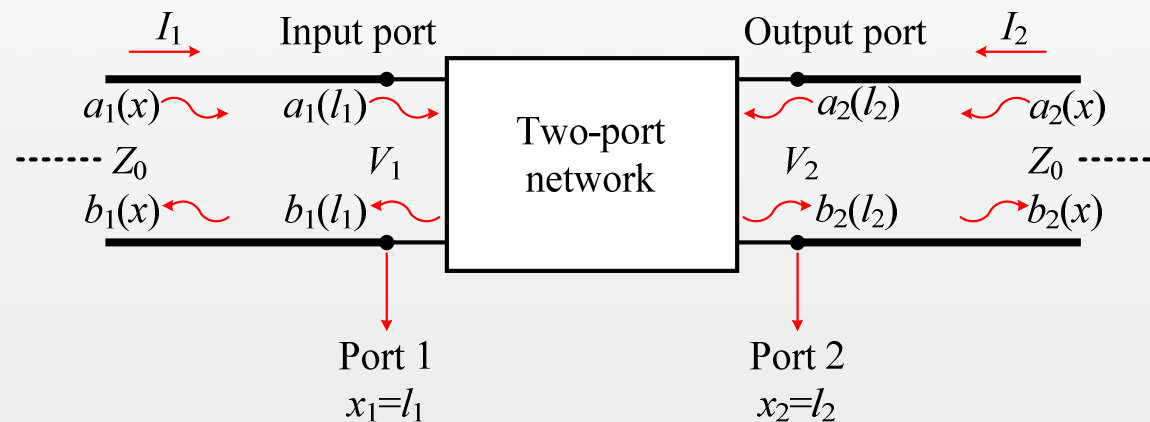


# Chapter 4

## Microwave Network Analysis

Prof. Jeong, Yongchae



## Learning Objectives

- Learn Scattering-parameters ( $S$ -parameters)
- Learn how to obtain  $S$ -parameters of 1-port network
- Learn how to obtain  $S$ -parameters of 2-port network
- Accustomed to parameter conversion

## Learning contents

- Why  $S$ -parameters?
- $S$ -parameters of 1-port network
- $S$ -parameters of 2-port network
- Parameters Conversion and Examples

# 1 Why S-Parameters?

- **Scattering parameter** is also called **S-parameters**.
  - S-parameters denote the working of an electrical network or circuit when stimulated with signals.
  - The previous (Z-, Y-, h-, g-) parameters are useful for low frequency circuit designs.
  - At microwave frequency, it is not easy to measure the voltage and current.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad @ \text{ output port: open}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad @ \text{ input port: open}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad @ \text{ output port: open}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad @ \text{ input port: open}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad @ \text{ output port: shorted}$$



$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad @ \text{ input port: shorted}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad @ \text{ output port: shorted}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \quad @ \text{ input port: shorted}$$
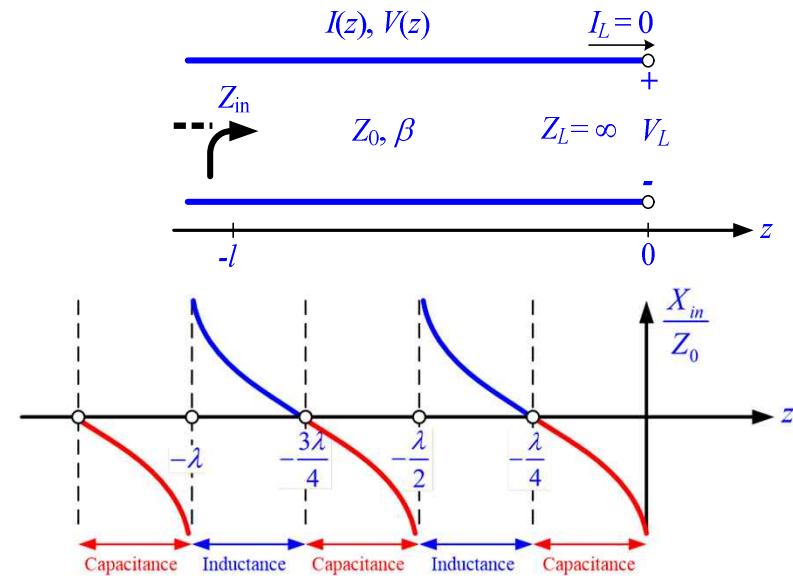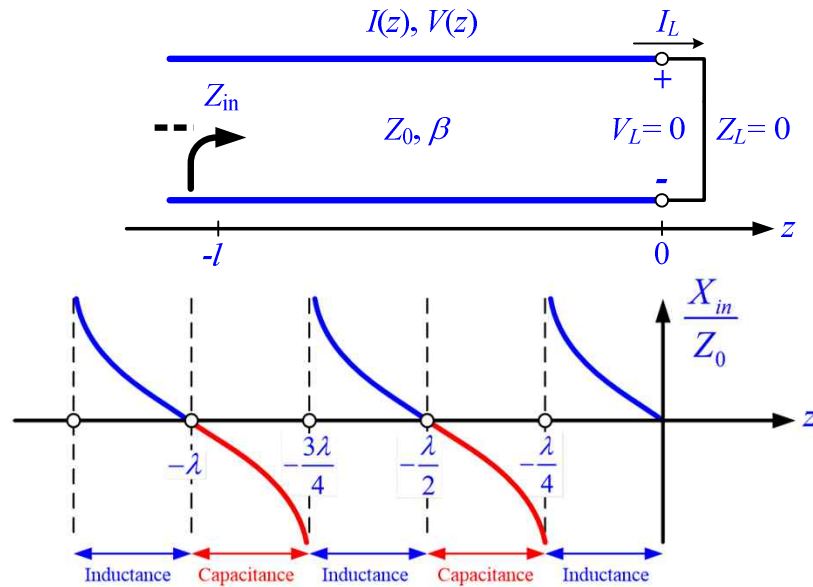
# 1 Why S-Parameters?

- Short ( $Z = 0 + j0$ ) and open ( $Z = \infty + j\infty$ ) conditions are also difficult to achieve at microwave frequency, whereas these conditions are easy at low frequency to realize due to long wavelength.



$$Z = 0 + j0 \neq 0 \pm jX \quad : \text{short condition}$$

$$Z = \infty + j\infty \neq 0 \pm jX \quad : \text{open condition}$$

- Matching condition is easier to achieve than short- or open-circuited conditions.

→ **Define new parameter based on the reflection and transmission characteristics: S-parameters**

## 2 S-Parameters of 1-port Network

- A 1-port network has one S-parameter called  $S_{11}$ .
  - $S_{11}$  is the ratio of the incident voltage wave to the reflected voltage wave at the input port of the network or circuit.
  - $S_{11}$  is also known as return loss, a measure of the voltage reflection ratio at the input port.
  - Assuming:

$$V^+(x) = Ae^{-j\beta x} \quad \text{: incident voltage wave}$$

$$V^-(x) = Be^{j\beta x} \quad \text{: reflected voltage wave}$$


- Total voltage and current waves:

$$V(x) = V^+(x) + V^-(x)$$

$$I(x) = I^+(x) + I^-(x) = \frac{V^+(x)}{Z_0} - \frac{V^-(x)}{Z_0}$$

- Reflection coefficient:

$$\Gamma(x) = \frac{V^-(x)}{V^+(x)}$$

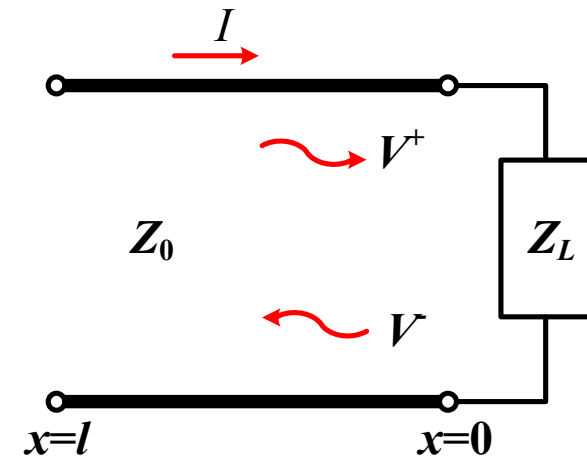

## 2 S-Parameters of 1-port Network

- Normalized voltage and current waves:  $v(x) = \frac{V(x)}{\sqrt{Z_0}} = \frac{V^+(x)}{\sqrt{Z_0}} + \frac{V^-(x)}{\sqrt{Z_0}} = a(x) + b(x)$ ,

$$i(x) = \sqrt{Z_0} I(x) = \frac{V^+(x)}{\sqrt{Z_0}} - \frac{V^-(x)}{\sqrt{Z_0}} = a(x) - b(x)$$

- Normalized incident and reflected voltage waves:

$$a(x) = \frac{V^+(x)}{\sqrt{Z_0}}, \quad b(x) = \frac{V^-(x)}{\sqrt{Z_0}}$$

- Overall normalized voltage and current waves:


$$v(x) = a(x) + b(x), \quad i(x) = a(x) - b(x)$$

- Normalized incident and reflected voltage waves in terms of  $V(x)$  and  $I(x)$ :

$$a(x) \equiv \frac{1}{2} \left[ \frac{V(x)}{\sqrt{Z_0}} + \sqrt{Z_0} I(x) \right] = \frac{1}{2} [v(x) + i(x)] \quad [\sqrt{\text{VA}}], \quad b(x) \equiv \frac{1}{2} \left[ \frac{V(x)}{\sqrt{Z_0}} - \sqrt{Z_0} I(x) \right] = \frac{1}{2} [v(x) - i(x)] \quad [\sqrt{\text{VA}}]$$

→ Conceptual unit  $[\sqrt{\text{VA}}]$  is meaningless.

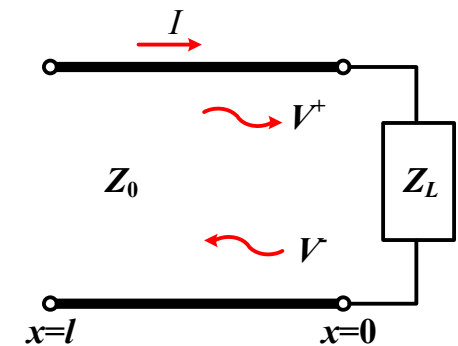→  $a^2(x)$  and  $b^2(x)$  have a unit of  $[\text{VA}]$  (or  $[\text{W}]$ ), and it's power!!!



## 2 S-Parameters of 1-port Network

- Normalized network impedance:

$$z(x) = \frac{v(x)}{i(x)} = \frac{V(x) / \sqrt{Z_0}}{\sqrt{Z_0} I(x)} = \frac{1}{Z_0} \frac{V(x)}{I(x)} = \frac{Z_L}{Z_0} = z_L$$

- Power:

$$v(x)i(x) = \frac{V(x)}{\sqrt{Z_0}} \cdot \sqrt{Z_0} I = V(x)I(x)$$

- Definition of  $S_{11}$ :

$$S_{11} = \frac{b(x)}{a(x)} = \frac{v(x) - i(x)}{v(x) + i(x)} = \frac{v(x) / i(x) - 1}{v(x) / i(x) + 1}$$

$$= \frac{z - 1}{z + 1} = \frac{\frac{Z_L}{Z_0} - 1}{\frac{Z_L}{Z_0} + 1} = \frac{Z_L - Z_0}{Z_L + Z_0} = \Gamma_L$$

- Define power:

$$P(x) = \frac{1}{2} \operatorname{Re} [V(x) I^*(x)] = \frac{1}{2} \operatorname{Re} [v(x) i(x)^*]$$

$$= \frac{1}{2} \operatorname{Re} \left\{ [a(x) + b(x)] [a(x) - b(x)^*] \right\}$$

$$= \frac{1}{2} [ |a(x)|^2 - |b(x)|^2 ]$$


- If  $Z_L = Z_0$ ,  $S_{11} = 0$  and  $b = 0$

$$P_i = \frac{1}{2} |a|^2 : \text{incident power}$$

- If  $b \neq 0$

$$P = \frac{1}{2} [ |a|^2 - |b|^2 ] = P_i - P_r$$

: real incident power

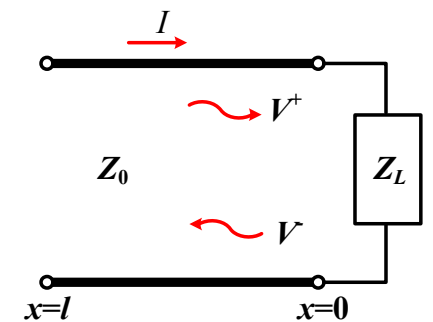

## 2 S-Parameters of 1-port Network


- **Example 1:** Calculate the  $S_{11}$  of following network.

- Input impedance:

$$\begin{aligned}Z_{in} &= 100 \parallel [20 + (50 \parallel 50)] \\ &= 100 \parallel [20 + 25] \\ &= 100 \parallel 45 = 31.03\end{aligned}$$

- Reflection coefficient:
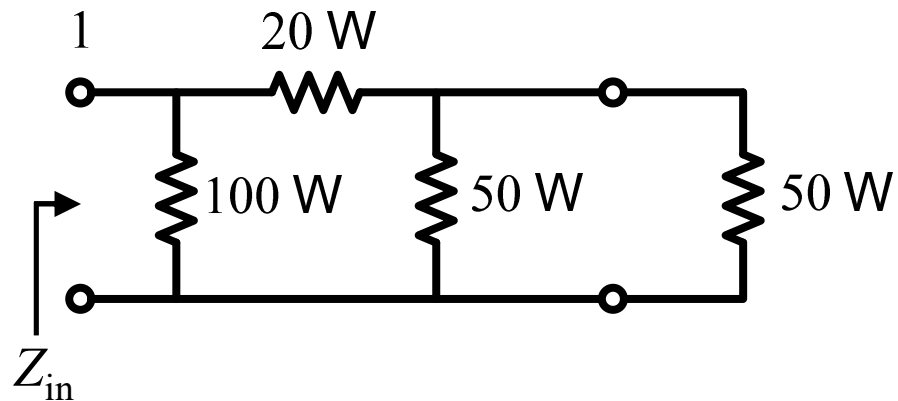
$$\begin{aligned}S_{11} &= \Gamma_{IN} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \\ &= \frac{31.03 - 50}{31.03 + 50} = -0.23 \text{ or } 0.23 \angle \pi\end{aligned}$$





### 3 S-Parameters of 2-port Network

- 2-port network

- S-parameters of network in view of incident and reflected voltage waves

$$b_1(l_1) = S_{11}a_1(l_1) + S_{12}a_2(l_2)$$

$$b_2(l_2) = S_{21}a_1(l_1) + S_{22}a_2(l_2)$$

- In matrix form:


$$\begin{bmatrix} b_1(l_1) \\ b_2(l_2) \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1(l_1) \\ a_2(l_2) \end{bmatrix} \Rightarrow [b] = [S][a]$$

where  $S_{11}a_1(l_1)$ : contribution to reflected wave  $b_1(l_1)$  due to incident wave  $a_1(l_1)$  at port 1.

$S_{12}a_2(l_2)$ : contribution to reflected wave  $b_1(l_1)$  due to incident wave  $a_2(l_2)$  at port 2,

- S-parameter matrix of 2-port network measured at input and output ports:
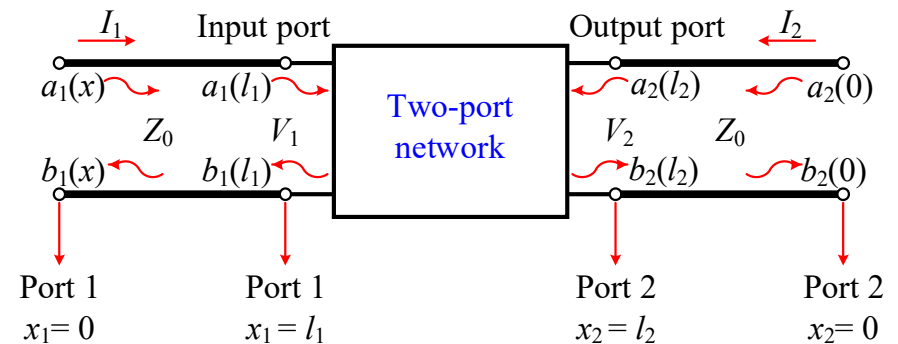
$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$



### 3 S-Parameters of 2-port Network

- S-parameters are reflection and transmission coefficients.
- S-parameter at a specific port of network is measured when the other port is properly terminated or matched.

$$S_{11} = \left. \frac{b_1(l_1)}{a_1(l_1)} \right|_{a_2(l_2)=0} \quad \text{: input reflection coefficient with output port properly terminated}$$

$$S_{21} = \left. \frac{b_2(l_2)}{a_1(l_1)} \right|_{a_2(l_2)=0} \quad \text{: forward transmission coefficient with output port properly terminated}$$

$$S_{22} = \left. \frac{b_2(l_2)}{a_2(l_2)} \right|_{a_1(l_1)=0} \quad \text{: output reflection coefficient with input port properly terminated}$$

$$S_{12} = \left. \frac{b_1(l_1)}{a_2(l_2)} \right|_{a_1(l_1)=0} \quad \text{: reverse transmission coefficient with input port properly terminated}$$

- What are  $a_2(l_2) = 0$  and  $a_1(l_1) = 0$  ?

- 2-port network combined with 1-port load


- At port 2,  $a_L = b_2(0)$  and  $b_L = a_2(0)$

- Reflection condition in cases of  $Z_L = Z_0 = Z_s$

$$\Gamma_L = \left. \frac{Z_L - Z_0}{Z_L + Z_0} \right|_{Z_L=Z_0} = 0 = \frac{b_L}{a_L} = \frac{a_2(0)}{b_2(0)} \rightarrow b_L = a_2(0) = a_2(l_2) = 0$$

- Source and load matched conditions guarantee  $a_2(l_2) = 0$  and  $a_1(l_1) = 0$  !!!

- Calibration of network analyzer

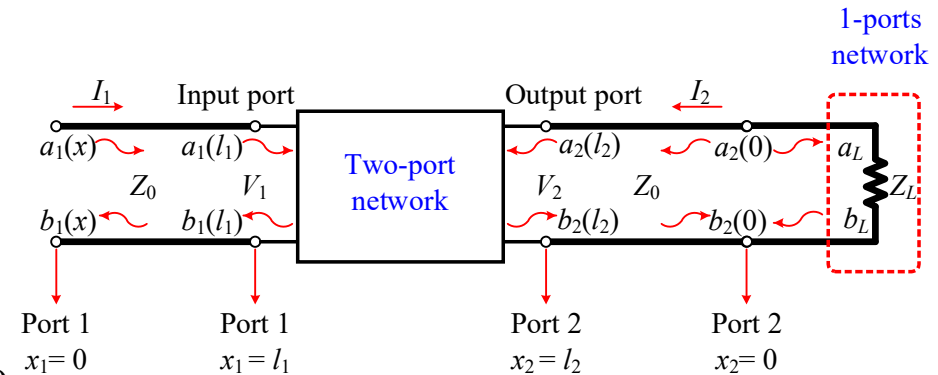

### 3 Parameters Conversion and Examples

- Relation between  $[S]$  and  $[Z]$

$$V_1(x_1) = \sqrt{Z_0} v_1(x_1), \quad V_2(x_2) = \sqrt{Z_0} v_2(x_2)$$

$$I_1(x_1) = i_1(x_1) / \sqrt{Z_0}, \quad I_2(x_2) = i_2(x_2) / \sqrt{Z_0}$$


$$\begin{bmatrix} V_1(x_1) \\ V_2(x_2) \end{bmatrix} = \begin{bmatrix} \sqrt{Z_0} v_1(x_1) \\ \sqrt{Z_0} v_2(x_2) \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1(x_1) \\ I_2(x_2) \end{bmatrix}$$

$$= \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} i_1(x_1) / \sqrt{Z_0} \\ i_2(x_2) / \sqrt{Z_0} \end{bmatrix}$$

$$\Rightarrow \sqrt{Z_0} \begin{bmatrix} v_1(x_1) \\ v_2(x_2) \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} i_1(x_1) \\ i_2(x_2) \end{bmatrix} / \sqrt{Z_0}$$

$$\Leftrightarrow Z_0 [v(x)] = [Z][i(x)]$$
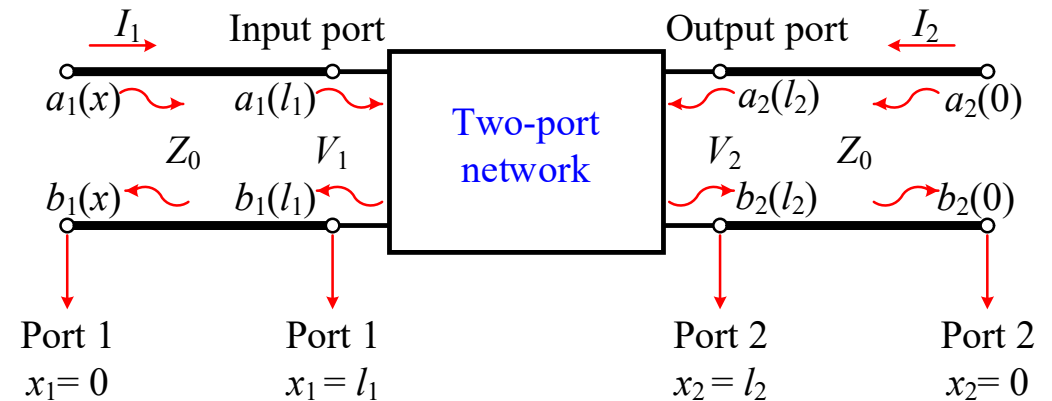
$$\Leftrightarrow [\zeta] = \frac{[Z]}{Z_0} \quad : \text{normalized impedance matrix}$$



$$\begin{aligned} \circ [v(x)] &= [a(x)] + [b(x)] = [a(x)] + [S][a(x)] \\ &= ([U] + [S])[a(x)] \end{aligned}$$

$$\begin{aligned} \circ [i(x)] &= [a(x)] - [b(x)] = [a(x)] - [S][a(x)] \\ &= ([U] - [S])[a(x)] \end{aligned}$$


### 3 Parameters Conversion and Examples

- Since  $[v(x)] = [\zeta][i(x)]$ , the following equation can be obtained.

$$\begin{aligned}
 [a(x)] + [b(x)] &= [\zeta]([a(x)] - [b(x)]) \\
 ([\zeta] + [U])[b(x)] &= ([\zeta] - [U])[a(x)] \\
 [b(x)] &= ([\zeta] + [U])^{-1}([\zeta] - [U])[a(x)] = [S][a(x)] \\
 \therefore [S] &= ([\zeta] + [U])^{-1}([\zeta] - [U]) \rightarrow [S] = f([\zeta])
 \end{aligned}$$

or
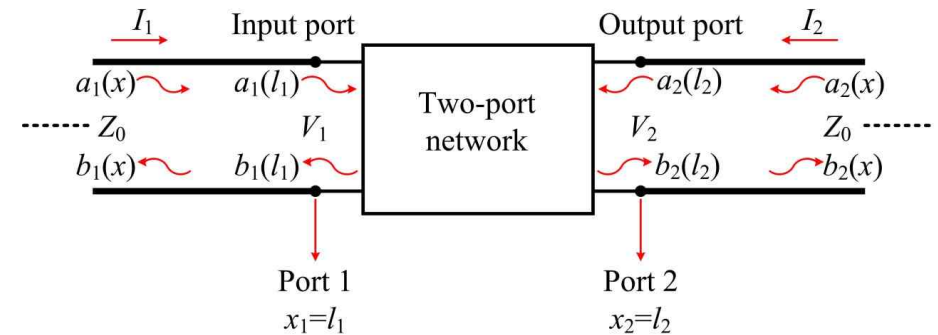
$$\begin{aligned}
 [v(x)] &= [\zeta][i(x)] \\
 [a(x)] + [b(x)] &= [\zeta]([a(x)] - [b(x)]) \\
 ([U] + [S])[a(x)] &= [\zeta]([U] - [S])[a(x)] \\
 \therefore [\zeta] &= ([U] + [S])([U] - [S])^{-1} \\
 &\rightarrow [\zeta] = g([S])
 \end{aligned}$$




- For  $[b(x)] = [S][a(x)]$ ,  $[v(x)] = [\zeta][i(x)]$ ,  
 $[b(x)] = ([v] - [i(x)])/2$ , and  
 $[a(x)] = ([v(x)] + [i(x)])/2$   
 $\rightarrow ([\zeta] - [U])[i(x)] = [S]([\zeta] + [U])[i(x)]$   
 $\therefore [S] = ([\zeta] - [U])([\zeta] + [U])^{-1}$   
or  $[\zeta] = ([U] - [S])^{-1}([U] + [S])$

### 3 Parameters Conversion and Examples

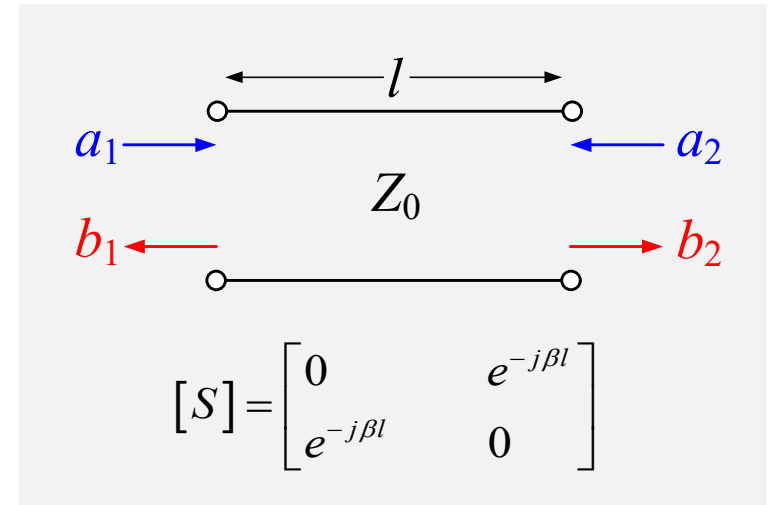- **Example 2:** Determine  $[Z]$  of transmission line from  $[S]$  of transmission line

Solution:

$$\begin{aligned}
 [\zeta] &= ([U] + [S])([U] - [S])^{-1} \\
 &= \begin{bmatrix} 1 & e^{-j\beta l} \\ e^{-j\beta l} & 1 \end{bmatrix} \begin{bmatrix} 1 & -e^{-j\beta l} \\ -e^{-j\beta l} & 1 \end{bmatrix}^{-1} \\
 &= \frac{1}{1 - e^{-j2\beta l}} \begin{bmatrix} 1 & e^{-j\beta l} \\ e^{-j\beta l} & 1 \end{bmatrix} \begin{bmatrix} 1 & e^{-j\beta l} \\ e^{-j\beta l} & 1 \end{bmatrix} = \begin{bmatrix} \frac{1 + e^{-j2\beta l}}{1 - e^{-j2\beta l}} & \frac{2e^{-j\beta l}}{1 - e^{-j2\beta l}} \\ \frac{2e^{-j\beta l}}{1 - e^{-j2\beta l}} & \frac{1 + e^{-j2\beta l}}{1 - e^{-j2\beta l}} \end{bmatrix} \\
 &= \begin{bmatrix} -j \frac{(e^{j\beta l} + e^{-j\beta l})/2}{(e^{j\beta l} - e^{-j\beta l})/2j} & -j \frac{1}{(e^{j\beta l} - e^{-j\beta l})/2j} \\ -j \frac{1}{(e^{j\beta l} - e^{-j\beta l})/2j} & -j \frac{(e^{j\beta l} + e^{-j\beta l})/2}{(e^{j\beta l} - e^{-j\beta l})/2j} \end{bmatrix} = \begin{bmatrix} -j \cot \beta l & -j \csc \beta l \\ -j \csc \beta l & -j \cot \beta l \end{bmatrix} \Rightarrow [Z] = \begin{bmatrix} -jZ_0 \cot \beta l & -jZ_0 \csc \beta l \\ -jZ_0 \csc \beta l & -jZ_0 \cot \beta l \end{bmatrix}
 \end{aligned}$$



### 3 Parameters Conversion and Examples

- **Example 3:** Determine the Z-parameters of transmission line with open- and short-circuited conditions.

Solution:

$$\begin{cases} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{12}I_1 + Z_{11}I_2 \end{cases} \quad \text{@symmetric network}$$


- Output open :  $I_2 = 0$ ,  $Z_{11} = \frac{V_1}{I_1} = Z_0 \frac{Z_L + jZ_0 \tan \theta}{Z_0 + jZ_L \tan \theta}$   
 $= -jZ_0 \cot \beta l$

- Output short :  $V_2 = 0$ ,  $0 = Z_{12}I_1 + Z_{11}I_2 \Rightarrow I_2 = -\frac{Z_{12}}{Z_{11}} I_1$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 = \left( Z_{11} - \frac{Z_{12}^2}{Z_{11}} \right) I_1$$

$$Z_{in} = \frac{V_1}{I_1} = Z_{11} - \frac{Z_{12}^2}{Z_{11}} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$
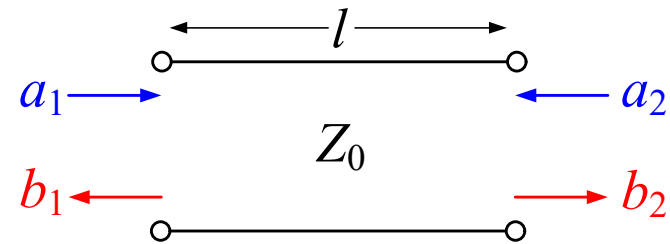
$$= jZ_0 \tan \beta l \quad \text{: short-circuited}$$



$$Z_{12}^2 = Z_{11}^2 - Z_{11} (jZ_0 \tan \beta l) = -Z_0^2 \cot^2 \beta l - Z_0^2$$

$$= -Z_0^2 \csc^2 \beta l$$

$$\therefore Z_{12} = \pm jZ_0 \csc \beta l$$

### 3 Parameters Conversion and Examples

- **Example 4:** Determine the  $S$ -parameter of the given network.


Solution:

$$- \begin{cases} b_1 = S_{11}a_1 + S_{12}a_2 \\ b_2 = S_{21}a_1 + S_{22}a_2 \end{cases}$$

$$- Y_{\text{in}} = Y_0 + jB \quad (\text{In case port 2 is matched})$$

$$- S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad \leftarrow \text{Reflection coefficient}$$
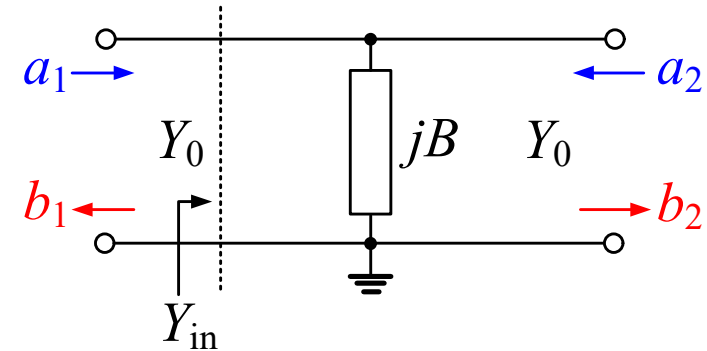
$$= \frac{Y_0 - Y_{\text{in}}}{Y_0 + Y_{\text{in}}} = \frac{-jB}{2Y_0 + jB}$$



$$- S_{21} = 1 + S_{11} = \frac{2Y_0}{2Y_0 + jB}$$

$$- \text{From symmetry, } S_{11} = S_{22} \text{ and } S_{12} = S_{21}.$$

### 3 Parameters Conversion and Examples

- **Example 5:** Determine the  $S$ -parameter of the given network.

Solution:

- reciprocal network.


$$Z_{in} = Z_0 + jX \quad (\text{In case port 2 is matched})$$

- Use normalized voltage:

$$\begin{cases} a_1 = \overline{V_1^+} = V_1^+ / \sqrt{Z_c} \\ a_2 = \overline{V_2^+} = V_2^+ / \sqrt{Z_c} \\ b_1 = \overline{V_1^-} = V_1^- / \sqrt{Z_c} \\ b_2 = \overline{V_2^-} = V_2^- / \sqrt{Z_c} \end{cases}$$

- Overall input voltage and current:
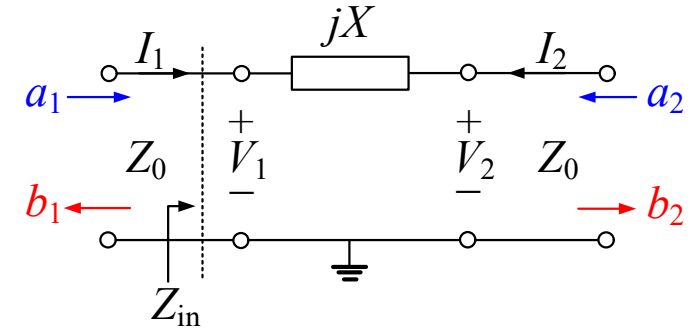
$$\begin{cases} V_1 = V_1^+ + V_1^- = V_1^+ \left( 1 + \frac{V_1^-}{V_1^+} \right) = V_1^+ (1 + S_{11}) \\ I_1 = Y_0 (V_1^+ - V_1^-) = Y_0 V_1^+ \left( 1 - \frac{V_1^-}{V_1^+} \right) = Y_0 V_1^+ (1 - S_{11}) \end{cases}$$



- Apply KCL for incidence from port 1:

$$-I_2 = I_2^- = I_1$$

$$= Y_0 V_1^+ (1 - S_{11})$$

$$\Rightarrow I_2^- = Y_0 V_2^- = Y_0 V_1^+ S_{21} = Y_0 V_1^+ (1 - S_{11})$$

$$S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{jX}{2Z_0 + jX}$$

$$S_{21} = \frac{b_2}{a_1} = \frac{\overline{V_2^-}}{V_1^+} = \frac{V_2^- / \sqrt{Z_c}}{V_1^+ / \sqrt{Z_c}} = \frac{V_2^-}{V_1^+}$$

$$= 1 - S_{11} = \frac{2Z_0}{2Z_0 + jX}$$



## 4 Review

- Why  $S$ -parameter?
- $S$ -parameter of 1-port network
- $S$ -parameter of 2-port network
- Relation between  $[S]$  and  $[Z]$