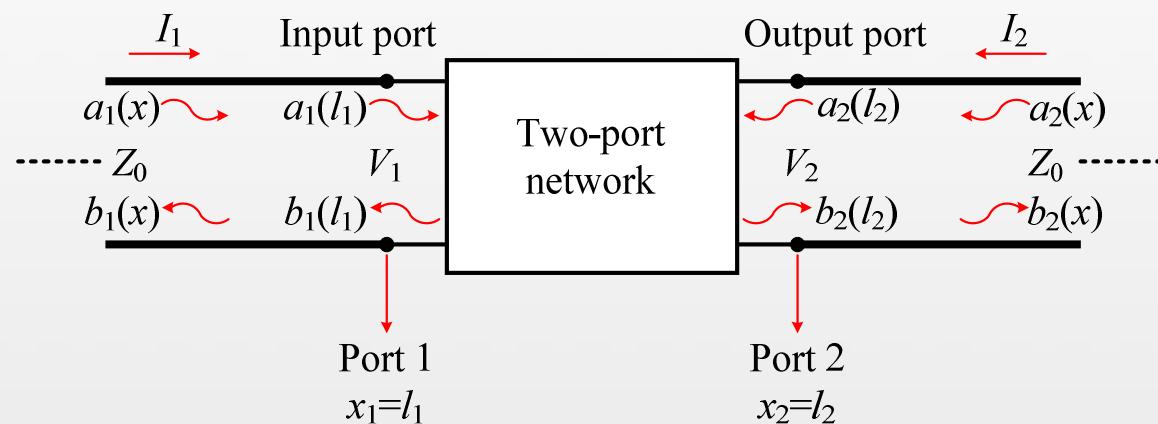


Chapter 4

Microwave Network Analysis

Prof. Jeong, Yongchae



Learning Objectives

- Know about properties of Scattering matrix
- Know about $ABCD$ -parameters
- Know about conversion relation between 2-port network parameters

Learning contents

- Properties of Scattering Matrix
- $ABCD$ -Parameters
- Conversion between 2-port Network Parameters

Properties of Scattering Matrix

- Symmetric matrix: $\mathbf{S}_{ij} = \mathbf{S}_{ji}$ (reciprocal network)

$$[S] = ([Z] + [U])^{-1} ([Z] - [U]) \quad \leftarrow ([A][B])^{-1} = [B]^{-1}[A]^{-1}$$

$$\begin{aligned} [S]^t &= ([Z] - [U])^t \left[([Z] + [U])^{-1} \right]^t = ([Z] - [U])^t \left[([Z] + [U])^t \right]^{-1} \\ &= ([Z] - [U])([Z] + [U])^{-1} = [S] \end{aligned}$$

- Unitary matrix:** Lossless n -port network conservation of energy

Sum of all incident power = Sum of all exiting powers

$$\sum_n |b_i|^2 = [b]^t [b]^* = \sum_n |a_i|^2 = [a]^t [a]^*$$

$$\begin{aligned} \sum_n |b_i|^2 &= [b]^t [b]^* = ([S][a])^t ([S][a])^* = [a]^t [S]^t [S]^*[a]^* \\ &= [a]^t [a]^* = [a]^t [a]^* = \sum_n |a_i|^2 \end{aligned}$$

$$\therefore [S]^t [S]^* = [U]$$

Ex.] For 2-port network,

$$\begin{pmatrix} b_1 \\ b_2 \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix} \Rightarrow [b] = [S][a]$$

$$\sum_{i=1}^2 |b_i|^2 = (b_1 \quad b_2) \begin{pmatrix} b_1^* \\ b_2^* \end{pmatrix} = |b_1|^2 + |b_2|^2$$

Properties of Scattering Matrix

- Otherwise

$$\sum_n |b_i|^2 = [b]^{t*}[b] = \sum_n |a_i|^2 = [a]$$

$$\begin{aligned} |b_i|^2 &= [b]^{t*}[b] = ([S][a])^{t*}([S][a]) = ([a]^t[S]^t)^* [S][a] = [a]^{t*}[S]^{t*}[S][a] \\ &= [a]^{t*}[a] = \sum_n |a_i|^2 \end{aligned}$$

$$\therefore [S]^{t*}[S] = [U]$$

$$\Leftrightarrow \begin{bmatrix} S_{11}^* & S_{21}^* \\ S_{12}^* & S_{22}^* \end{bmatrix} \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$\Rightarrow \begin{cases} S_{11}^*S_{11} + S_{21}^*S_{21} = |S_{11}|^2 + |S_{21}|^2 = 1 & \text{----- (1)} \\ S_{12}^*S_{12} + S_{22}^*S_{22} = |S_{12}|^2 + |S_{22}|^2 = 1 & \text{----- (2)} \\ S_{11}^*S_{12} + S_{21}^*S_{22} = 0 & \text{----- (3)} \\ S_{12}^*S_{11} + S_{22}^*S_{21} = 0 & \text{----- (4)} \end{cases}$$

Properties of Scattering Matrix

$$|b_1|^2 = b_1^* b_1 = (S_{11}^* a_1^* + S_{12}^* a_2^*) (S_{11} a_1 + S_{12} a_2)$$

$$|b_2|^2 = b_2^* b_2 = (S_{21}^* a_1^* + S_{22}^* a_2^*) (S_{21} a_1 + S_{22} a_2)$$

$$\begin{aligned} \Rightarrow |b_1|^2 + |b_2|^2 &= \left(|S_{11}|^2 |a_1|^2 + |S_{12}|^2 |a_2|^2 + S_{11}^* S_{12} a_1^* a_2 + S_{11} S_{12}^* a_1 a_2^* \right) \\ &\quad + \left(|S_{21}|^2 |a_1|^2 + |S_{22}|^2 |a_2|^2 + S_{21}^* S_{22} a_1^* a_2 + S_{21} S_{22}^* a_1 a_2^* \right) \\ &= \left(|S_{11}|^2 + |S_{21}|^2 \right) |a_1|^2 + \left(|S_{12}|^2 + |S_{22}|^2 \right) |a_2|^2 \quad \leftarrow (1) \& (2) \\ &\quad + (S_{11}^* S_{12} + S_{21}^* S_{22}) a_1^* a_2 + (S_{11} S_{12}^* + S_{21} S_{22}^*) a_1 a_2^* \quad \leftarrow (3) \& (4) \\ &= |a_1|^2 + |a_2|^2 \quad : \text{Conservation of energy} \end{aligned}$$

Properties of Scattering Matrix

- S-parameter variation due to change of reference plane

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$\begin{bmatrix} a_1 \\ a_2 \end{bmatrix} = \begin{bmatrix} a'_1 e^{-j\beta l_1} \\ a'_2 e^{-j\beta l_2} \end{bmatrix} = \begin{bmatrix} e^{-j\beta l_1} & 0 \\ 0 & e^{-j\beta l_2} \end{bmatrix} \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix}$$

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} b'_1 e^{j\beta l_1} \\ b'_2 e^{j\beta l_2} \end{bmatrix} = \begin{bmatrix} e^{j\beta l_1} & 0 \\ 0 & e^{j\beta l_2} \end{bmatrix} \begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix}$$

$$\begin{bmatrix} e^{j\beta l_1} & 0 \\ 0 & e^{j\beta l_2} \end{bmatrix} \begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} e^{-j\beta l_1} & 0 \\ 0 & e^{-j\beta l_2} \end{bmatrix} \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix}$$

$$\begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix} = \begin{bmatrix} e^{j\beta l_1} & 0 \\ 0 & e^{j\beta l_2} \end{bmatrix}^{-1} \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} e^{-j\beta l_1} & 0 \\ 0 & e^{-j\beta l_2} \end{bmatrix} \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix}$$
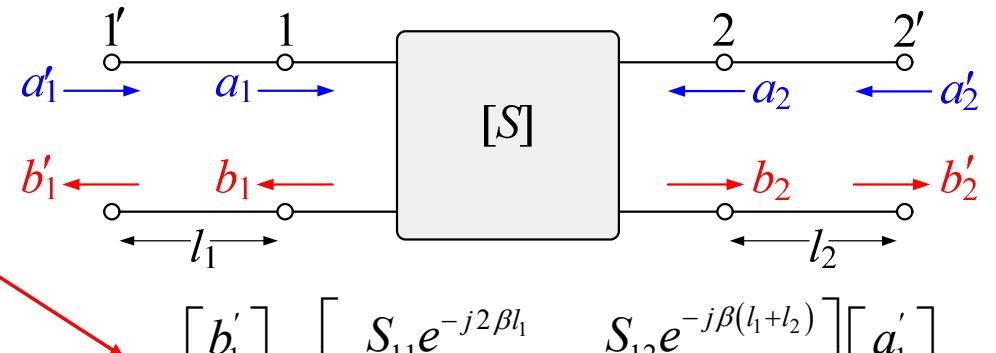
$$= \begin{bmatrix} e^{-j\beta l_1} & 0 \\ 0 & e^{-j\beta l_2} \end{bmatrix} \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} e^{-j\beta l_1} & 0 \\ 0 & e^{-j\beta l_2} \end{bmatrix} \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix}$$



$$\begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix} = \begin{bmatrix} S_{11} e^{-j2\beta l_1} & S_{12} e^{-j\beta(l_1+l_2)} \\ S_{21} e^{-j\beta(l_1+l_2)} & S_{22} e^{-j2\beta l_2} \end{bmatrix} \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix}$$

$$= [S'] \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix}$$

$$[S'] = \begin{bmatrix} S_{11} e^{-j2\beta l_1} & S_{12} e^{-j\beta(l_1+l_2)} \\ S_{21} e^{-j\beta(l_1+l_2)} & S_{22} e^{-j2\beta l_2} \end{bmatrix}$$

New S-parameters: **only phase shift**

2


ABCD-Parameters

- *ABCD*-parameters are used to model two-port network, linking input and output voltages and currents.
- Relation between voltages and currents as the function of *ABCD*-parameters:

$$\begin{cases} V_1 = AV_2 + BI_2 \\ V_2 = CV_2 + DI_2 \end{cases}$$

- Matrix form:
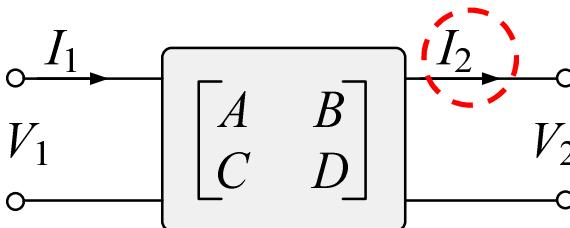
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$



- Define for *ABCD*-parameters:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} : \text{Open circuit reverse voltage gain}$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} : \text{Short-circuited reverse trans-impedance}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} : \text{Open-circuited reverse trans-admittance}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} : \text{Short-circuited reverse current gain}$$

ABCD-Parameters

- Relation to impedance matrix $[Z]$:

$$\begin{cases} V_1 = Z_{11}I_1 - Z_{12}I_2 \\ V_2 = Z_{21}I_1 - Z_{22}I_2 \end{cases} \Rightarrow \begin{cases} I_1 = \frac{1}{Z_{21}}V_2 + \frac{Z_{22}}{Z_{21}}I_2 \\ V_1 = Z_{11}\left(\frac{1}{Z_{21}}V_2 + \frac{Z_{22}}{Z_{21}}I_2\right) - Z_{12}I_2 = \frac{Z_{11}}{Z_{21}}V_2 + \left(\frac{Z_{11}Z_{22}}{Z_{21}} - Z_{12}\right)I_2 \end{cases}$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{Z_{11}I_1}{Z_{21}I_1} = \frac{Z_{11}}{Z_{21}} \quad B = \frac{V_1}{I_2} \Big|_{V_2=0} = \frac{Z_{11}I_1 - Z_{12}I_2}{I_2} \Big|_{V_2=0} = Z_{11} \frac{I_1}{I_2} \Big|_{V_2=0} - Z_{12} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{I_1}{Z_{21}I_1} = \frac{1}{Z_{21}} \quad D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{Z_{22}}{Z_{21}}$$

- $Z_{12} = Z_{21}$ for reciprocal network:


$$\Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} Z_{11}/Z_{12} & (Z_{11}Z_{22} - Z_{12}^2)/Z_{12} \\ 1/Z_{12} & Z_{22}/Z_{12} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \quad \rightarrow \text{Reciprocal circuit: } AD - BC = 1$$

ABCD-Parameters

- In practice, many microwave networks consist of a cascade connection of two or more 2-port networks.
- Convenient to analyze cascade connection of two or more 2-port networks by using *ABCD*-parameters

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \quad \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix} = \begin{bmatrix} A_1 A_2 + B_1 C_2 & A_1 B_2 + B_1 D_2 \\ C_1 A_2 + D_1 C_2 & C_1 B_2 + D_1 D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

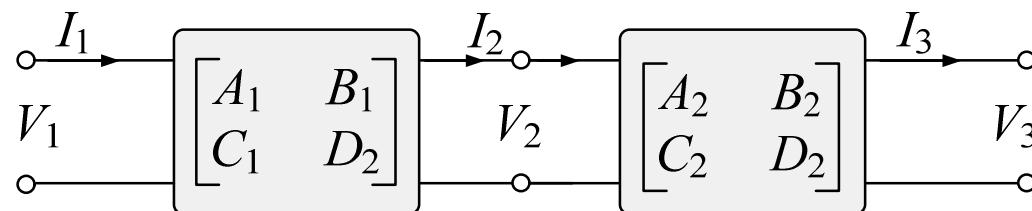

ABCD-Parameters

- ABCD-parameters of transmission line:


$$\begin{cases} V_1 = AV_2 + BI_2 \\ I_1 = CV_2 + DI_2 \end{cases}$$

$$\begin{cases} V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}, & V(0) = V_2, \quad V(-l) = V_1 \\ I(z) = \frac{1}{Z_0} (V^+ e^{-\gamma z} - V^- e^{\gamma z}), & I(0) = I_2, \quad I(-l) = I_1 \end{cases}$$

- $\gamma = \alpha + j\beta = j\beta$:for lossless condition

$$\begin{cases} V(0) = V_2 = V^+ + V^- \\ Z_0 I(0) = Z_0 I_2 = V^+ - V^- \end{cases} \Rightarrow \begin{cases} V^+ = \frac{1}{2} (V_2 + Z_0 I_2) \\ V^- = \frac{1}{2} (V_2 - Z_0 I_2) \end{cases}$$

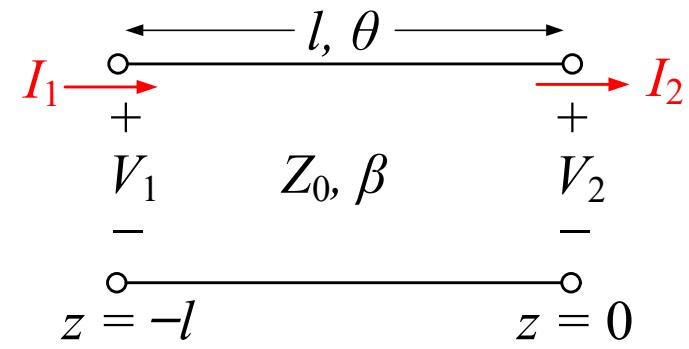cf.)
$$\begin{cases} \cosh \gamma z = \frac{e^{j\beta z} + e^{-j\beta z}}{2} = \cos \beta z \\ \sinh \gamma z = \frac{e^{j\beta z} - e^{-j\beta z}}{2} = j \sin \beta z \end{cases}$$



$$\begin{aligned} \Rightarrow V(z) &= V^+ e^{-\gamma z} + V^- e^{\gamma z} \\ &= \frac{1}{2} (V_2 + Z_0 I_2) e^{-\gamma z} + \frac{1}{2} (V_2 - Z_0 I_2) e^{\gamma z} \\ &= V_2 \left(\frac{e^{\gamma z} + e^{-\gamma z}}{2} \right) + I_2 Z_0 \left(\frac{e^{-\gamma z} - e^{\gamma z}}{2} \right) \\ &= V_2 \cosh \gamma z - I_2 Z_0 \sinh \gamma z \\ &= V_2 \cos \beta z - j I_2 Z_0 \sin \beta z \end{aligned}$$

2


ABCD-Parameters

$$\begin{aligned}\Rightarrow I(z) &= \frac{V^+ e^{-\gamma z} - V^- e^{\gamma z}}{Z_0} \\ &= \frac{1}{Z_0} \left(\frac{V_2 + Z_0 I_2}{2} \right) e^{-\gamma z} - \frac{1}{Z_0} \left(\frac{V_2 - Z_0 I_2}{2} \right) e^{\gamma z} \\ &= \frac{V_2}{Z_0} \left(\frac{e^{-\gamma z} - e^{\gamma z}}{2} \right) + I_2 \left(\frac{e^{\gamma z} + e^{-\gamma z}}{2} \right) \\ &= -\frac{V_2}{Z_0} \sinh \gamma z + I_2 \cosh \gamma z\end{aligned}$$

$$= -j \frac{V_2}{Z_0} \sin \beta z + I_2 \cos \beta z$$

$$\begin{cases} V(-l) = V_1 = V_2 \cos \beta l + j I_2 Z_0 \sin \beta l \\ I(-l) = I_1 = j \frac{V_2}{Z_0} \sin \beta l + I_2 \cos \beta l \end{cases}$$
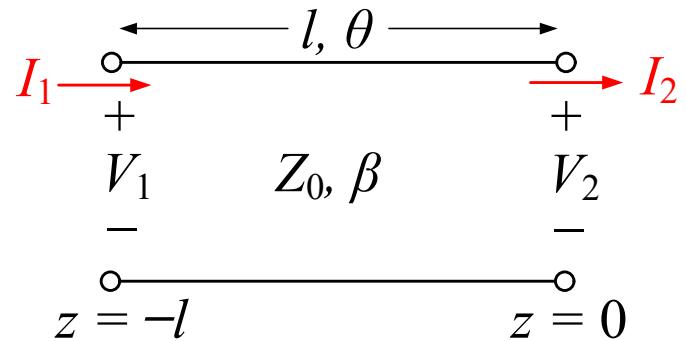
$$\Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \cos \theta & j Z_0 \sin \theta \\ j Y_0 \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \leftarrow \theta = \beta l$$




$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \theta & j Z_0 \sin \theta \\ j Y_0 \sin \theta & \cos \theta \end{bmatrix}$$

- For lossless case: $AD - BC = 1$

ABCD-Parameters

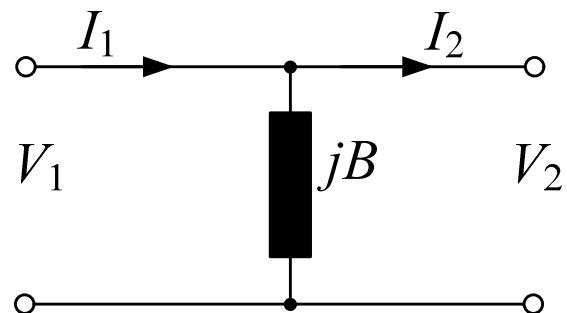- ABCD-parameters of 2-port network consisting of a shunt susceptance between ports 1 and 2:



$$\begin{cases} V_1 = AV_2 + BI_2 \\ I_1 = CV_2 + DI_2 \end{cases}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1 \quad (\text{Voltage ratio})$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = 0 \quad (\text{Resistive})$$


$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \left. \frac{I_1}{V_1} \right|_{I_2=0} = jB \quad (\text{Conductive})$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = 1 \quad (\text{Current ratio})$$

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ jB & 1 \end{bmatrix}$$

ABCD-Parameters

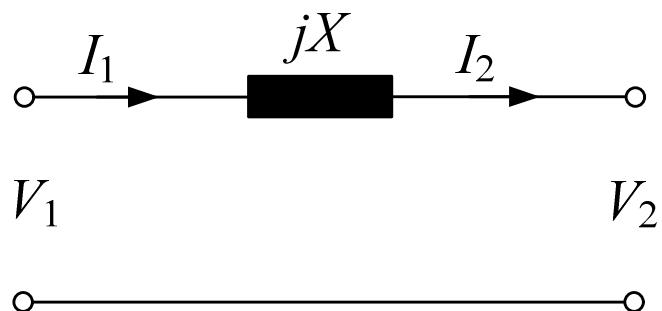- ABCD-parameters of 2-port network consisting of a series reactance between ports 1 and 2:



$$\begin{cases} V_1 = AV_2 + BI_2 \\ I_1 = CV_2 + DI_2 \end{cases}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$

$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = jX$$







$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \left. \frac{I_1}{V_1} \right|_{I_2=0} = 0$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = 1$$

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & jX \\ 0 & 1 \end{bmatrix}$$

ABCD-Parameters

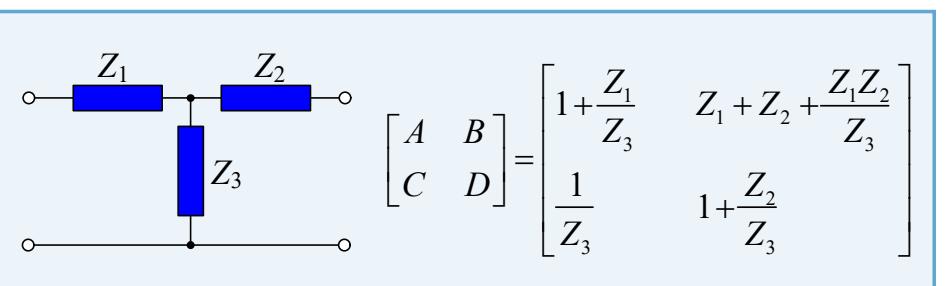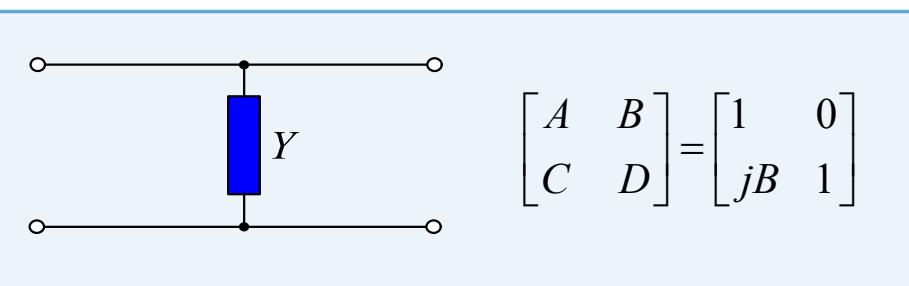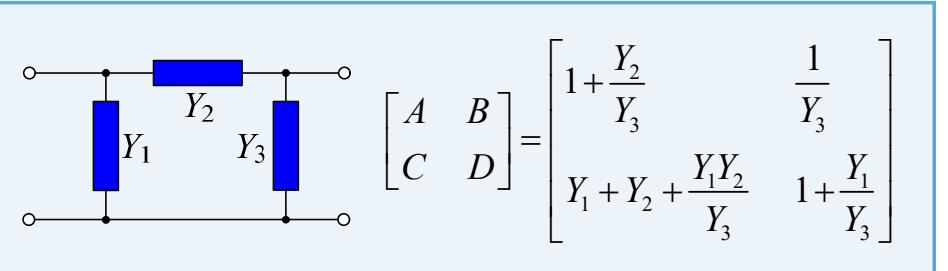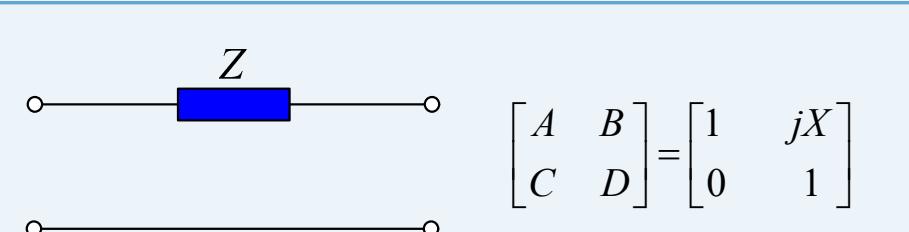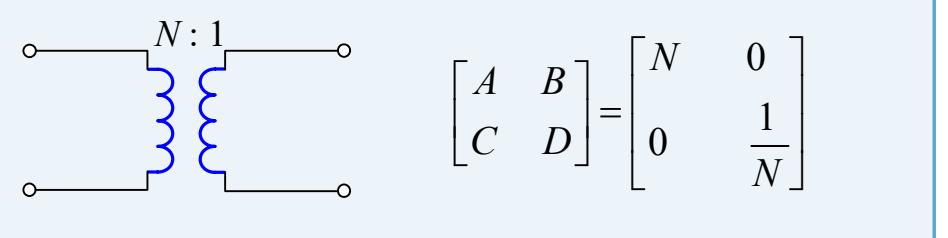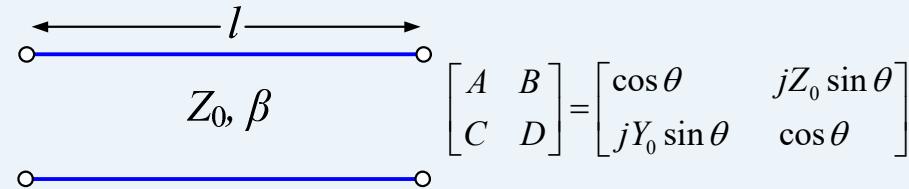- ABCD-parameters of some useful 2-port networks



Conversion between 2-port Network Parameters

	S	Z	Y	ABCD
S_{11}	S_{11}	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
S_{12}	S_{12}	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
S_{21}	S_{21}	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Z}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
S_{22}	S_{22}	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
Z_{11}	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{11}	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
Z_{12}	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{12}	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
Z_{21}	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{21}	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
Z_{22}	$Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{22}	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$

$$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}, \quad |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}, \quad \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}, \quad \Delta Y = (Y_{11} + Z_0)(Y_{22} + Z_0) - Y_{12}Y_{21}, \quad Y_0 = 1/Z_0$$

Conversion between 2-port Network Parameters

	S	Z	Y	ABCD
Y_{11}	$Y_0 \frac{(1-S_{11})(1+S_{22})+S_{12}S_{21}}{(1+S_{11})(1+S_{22})-S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	Y_{11}	$\frac{D}{B}$
Y_{12}	$Y_0 \frac{-2S_{12}}{(1+S_{11})(1+S_{22})-S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	Y_{12}	$\frac{BC-AD}{B}$
Y_{21}	$Y_0 \frac{-2S_{21}}{(1+S_{11})(1+S_{22})-S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	Y_{21}	$\frac{-1}{B}$
Y_{22}	$Y_0 \frac{(1+S_{11})(1-S_{22})+S_{12}S_{21}}{(1+S_{11})(1+S_{22})-S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	Y_{22}	$\frac{A}{B}$
A	$\frac{(1+S_{11})(1-S_{22})+S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	A
B	$Z_0 \frac{(1+S_{11})(1+S_{22})-S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	$\frac{-1}{Y_{21}}$	B
C	$\frac{1}{Z_0} \frac{(1-S_{11})(1-S_{22})-S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_{21}}$	$\frac{- Y }{Y_{21}}$	C
D	$\frac{(1-S_{11})(1+S_{22})+S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{-Y_{11}}{Y_{21}}$	D

$$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}, \quad |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}, \quad \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}, \quad \Delta Y = (Y_{11} + Z_0)(Y_{22} + Z_0) - Y_{12}Y_{21}, \quad Y_0 = 1/Z_0$$

- Properties of Scattering matrix
- $ABCD$ -parameters
- Conversion between 2-port network different parameters