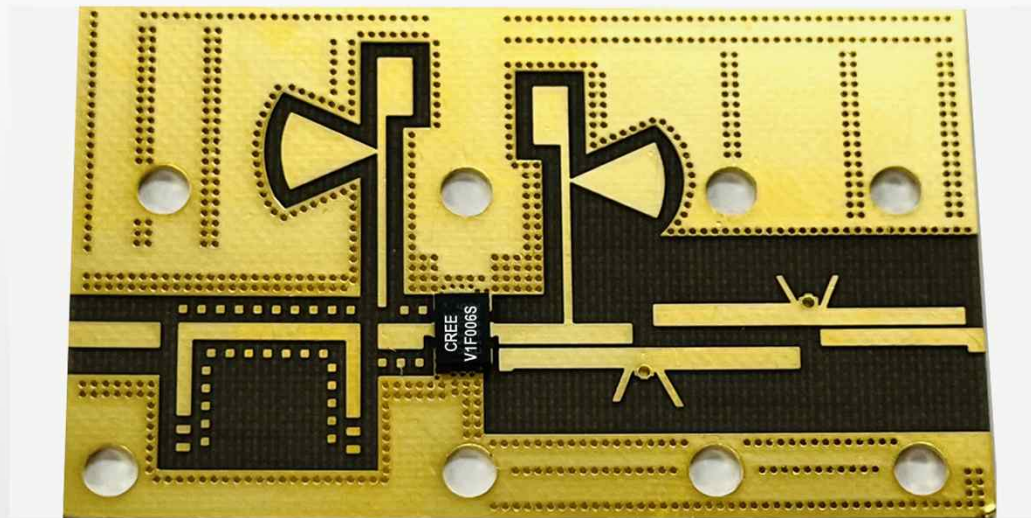


Chapter 5

Impedance Matching

Prof. Jeong, Yongchae



Learning Objectives

- Understanding what is theory of small reflection
- Learn about impedance transformation using single-section
- Learn about impedance transformation using multi-Section

Learning contents

- Introduction about Theory of Small Reflections
- Single-Section Transformer
- Multi-Section Transformer

1 Introduction about Theory of Small Reflection

- An important and useful approximation when considering multi-section matching networks is the ‘**Theory of Small Reflections**’.
- Theory of small reflections provides a simple mathematical form for analyzing the frequency response of many microwave circuits. → **Total reflection coefficient can be obtained from the partial reflections from several small discontinuities.**
- For applications requiring **more bandwidth** than single quarter-wave section, **multi-section transformers can be used.**
- Applications:
 - **Engineering and Telecommunications**: improving the performances on transmission lines, circuits, and antennas by reducing signal reflections.
 - **Optics**: designing anti-reflective coatings for lenses, glasses, and screens to reduce glare and increase transparency.
 - **Acoustics**: developing materials and structures for soundproofing and acoustic treatment to minimize reflected sound waves and enhance sound quality.

2 Single-Section Transformer

- Derivation an approximate expression for overall reflection coefficient Γ


$$\Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

$$\Gamma_2 = -\Gamma_1$$

$$\Gamma_3 = \frac{R_L - Z_2}{R_L + Z_2}$$

$$T_{21} = 1 + \Gamma_1 = \frac{2Z_2}{Z_1 + Z_2}$$
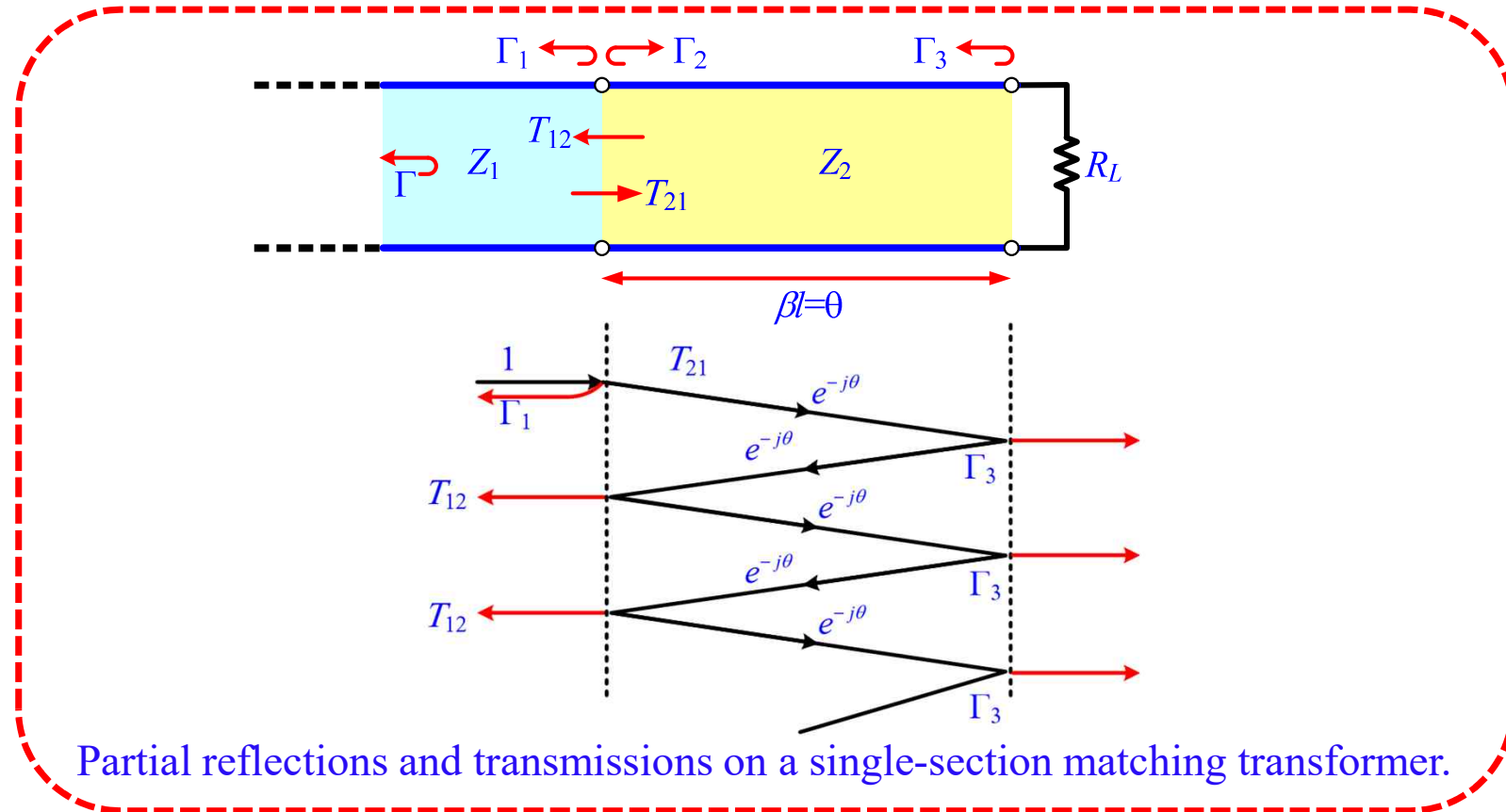
$$T_{12} = 1 + \Gamma_2 = \frac{2Z_1}{Z_1 + Z_2}$$



2 Single-Section Transformer



- Expression of total reflection as an infinite sum of partial reflections and transmissions:

$$\begin{aligned}\Gamma &= \Gamma_1 + T_{12}T_{21}\Gamma_3 e^{-j2\theta} + T_{12}T_{21}\Gamma_3^2\Gamma_2 e^{-j4\theta} + \dots \\ &= \Gamma_1 + T_{12}T_{21}\Gamma_3 e^{-j2\theta} \sum_{n=0}^{\infty} \Gamma_2^n \Gamma_3^n e^{-j2n\theta}\end{aligned}$$

- Using the geometric series and small reflection condition,

$$\sum_{n=0}^{\infty} x^n = \frac{1}{1-x}, \text{ for } |x| < 1$$
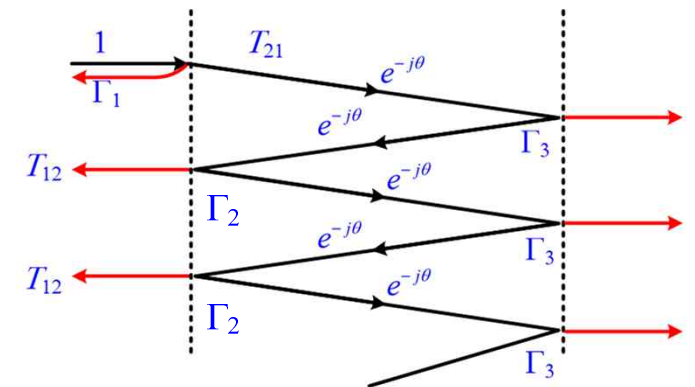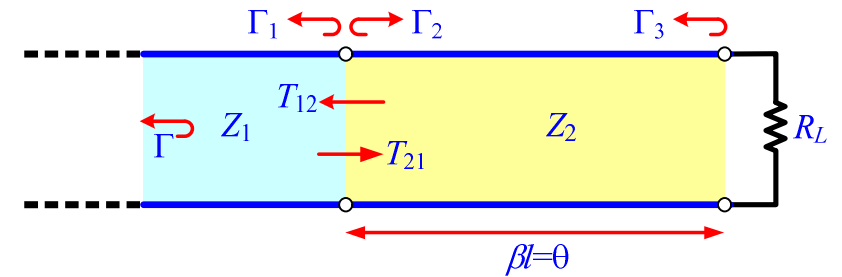
$$\begin{aligned}\Gamma &= \Gamma_1 + \frac{T_{12}T_{21}\Gamma_3 e^{-j2\theta}}{1 - \Gamma_2\Gamma_3 e^{-j2\theta}} \leftarrow \Gamma_2 = -\Gamma_1, T_{21} = 1 + \Gamma_1, T_{12} = 1 + \Gamma_2 = 1 - \Gamma_1 \\ &= \frac{\Gamma_1 - \Gamma_1\Gamma_2\Gamma_3 e^{-j2\theta} + (1 - \Gamma_1)(1 + \Gamma_1)\Gamma_3 e^{-j2\theta}}{1 + \Gamma_1\Gamma_3 e^{-j2\theta}}\end{aligned}$$



2 Single-Section Transformer

- (continue)

$$\begin{aligned} &= \frac{\Gamma_1 - \Gamma_1 \Gamma_2 \Gamma_3 e^{-j2\theta} + (1 - \Gamma_1^2) \Gamma_3 e^{-j2\theta}}{1 + \Gamma_1 \Gamma_3 e^{-j2\theta}} \\ &\cong \frac{\Gamma_1 + \Gamma_3 e^{-j2\theta}}{1 + \Gamma_1 \Gamma_3 e^{-j2\theta}} \quad (1) \end{aligned}$$

$$\Gamma \cong \Gamma_1 + \Gamma_3 e^{-j2\theta} \quad (2)$$

$\Gamma_1 \Gamma_2 \Gamma_3 e^{-2j\theta} \approx 0$ because $\Gamma_1, \Gamma_2, \Gamma_3$ are small
 $(1 - \Gamma_1^2) \approx 1$ because $\Gamma_1^2 \approx 0$


$1 + \Gamma_1 \Gamma_3 e^{-2j\theta} \approx 1$ because $\Gamma_1 \Gamma_3 \approx 0$

■ Intuitive ideas:

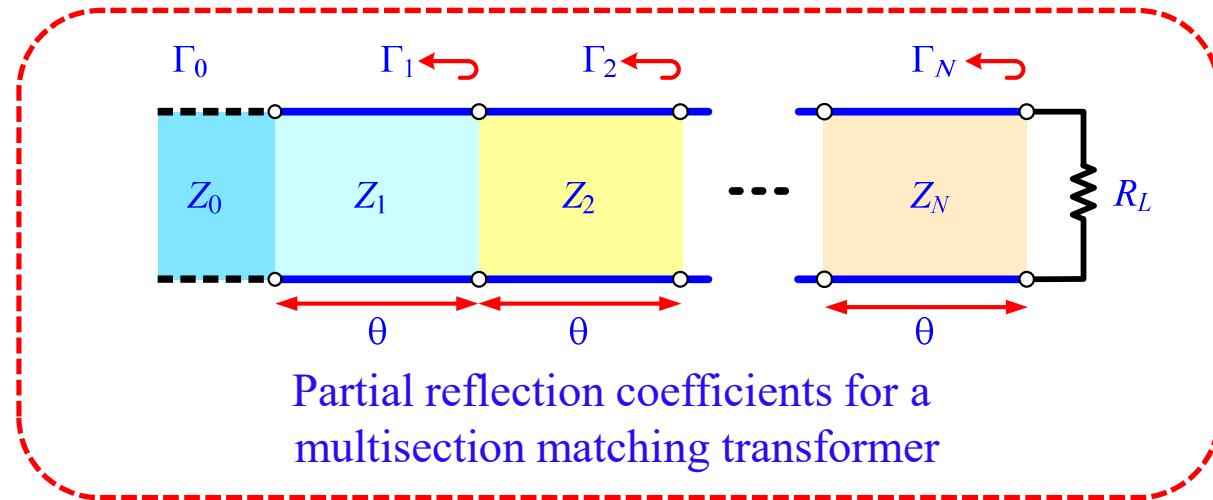- 1) The total reflection is dominated by the reflection from the initial discontinuity between Z_1 and Z_2 (Γ_1), and the first reflection from the discontinuity between Z_2 and Z_L (Γ_3).
- 2) The $e^{-j2\theta}$ term accounts for the round-trip phase delay when the incident wave travels up and down the line.

3 Multi-Section Transformer

- Consider a sequence of N transmission line sections and each section has **equal length** θ , but **dissimilar characteristic impedances**:



- Derivation an approximate expression for the total reflection coefficient Γ .

$$\Gamma_0 = \frac{Z_1 - Z_0}{Z_1 + Z_0}, \dots, \Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \quad (@1 < n < N), \dots, \Gamma_N = \frac{Z_L - Z_N}{Z_L + Z_N}$$


- Assumptions:

- 1) All Z_n increase or decrease monotonically across the transformer.
- 2) R_L is real.

3 Multi-Section Transformer


- If $R_L < Z_0$,
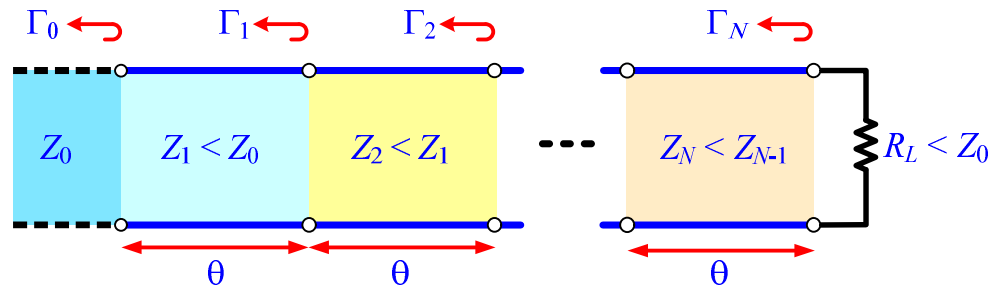
$$Z_0 > Z_1 > Z_2 \dots > Z_N > R_L \quad \Rightarrow \quad \Gamma_n < 0$$



- If $R_L > Z_0$,
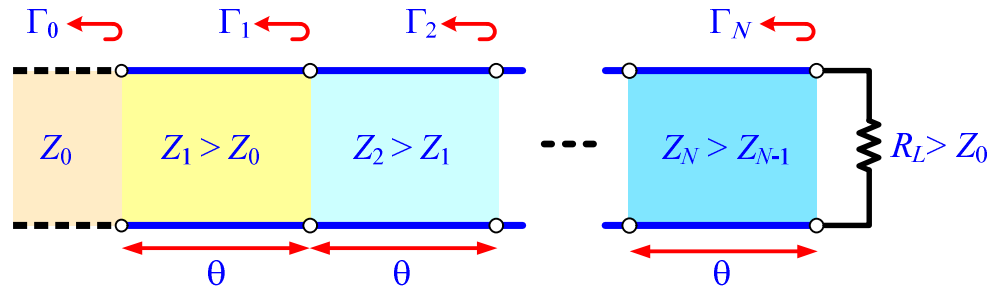
$$Z_0 < Z_1 < Z_2 \dots < Z_N < R_L \quad \Rightarrow \quad \Gamma_n > 0$$




3 Multi-Section Transformer

- Since R_L is real and lossless transmission lines are assumed, all Γ_n will be real.
 - Due to gradually impedance transition from one section to another, ' $Z_{n+1} - Z_n$ ' will be **small**.
 - \Rightarrow Each marginal reflection coefficient Γ_n will be **real** and have a **small** magnitude.
 - \Rightarrow **Theory of Small Reflections**
 - Input reflection coefficient of multi-section impedance transformer

$$\frac{b_0}{a_0} = \Gamma(\theta)$$

$$\Gamma_{in}(\theta) \cong \Gamma_0 + \Gamma_1 e^{-j2\theta} + \Gamma_2 e^{-j4\theta} + \dots + \Gamma_N e^{-j2N\theta} \quad (3)$$
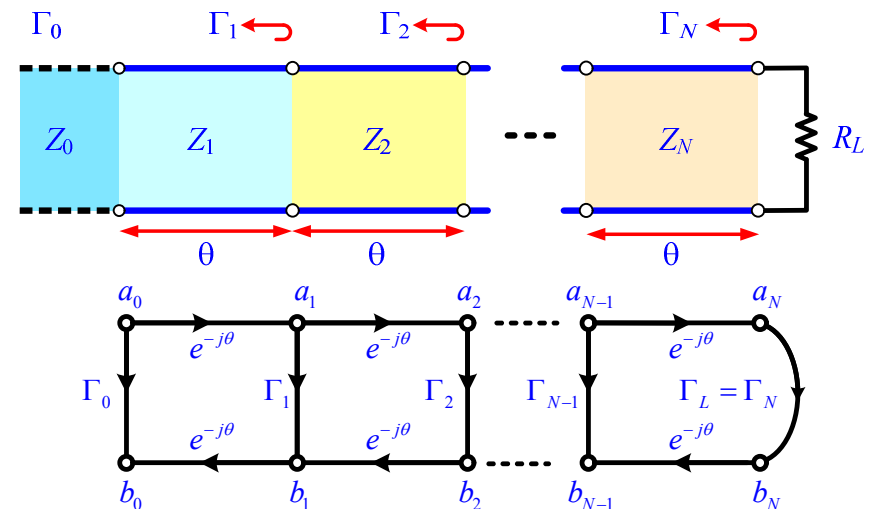
$$= \sum_{n=0}^N \Gamma_n e^{-j2N\theta}$$



3 Multi-Section Transformer

- To simplify this process, transformer is **symmetrical**,

$$\Gamma_0 = \Gamma_N, \Gamma_1 = \Gamma_{N-1}, \Gamma_2 = \Gamma_{N-2}, \dots$$

→ This does not mean that $Z_0 = Z_N, Z_1 = Z_{N-1}, Z_2 = Z_{N-2}, \dots$

- (3) can be re-written as:

$$\Gamma_{in}(\theta) \cong \Gamma_0 + \Gamma_1 e^{-j2\theta} + \Gamma_2 e^{-j4\theta} + \dots + \Gamma_N e^{-j2N\theta} \quad (2)$$

$$= (\Gamma_0 + \Gamma_N e^{-j2N\theta}) + (\Gamma_1 e^{-j2\theta} + \Gamma_{N-1} e^{-j2(N-1)\theta}) + (\Gamma_2 e^{-j4\theta} + \Gamma_{N-2} e^{-j2(N-2)\theta}) + \dots +$$

$$= e^{-jN\theta} \{ \Gamma_0 [e^{jN\theta} + e^{-jN\theta}] + \Gamma_1 [e^{j(N-2)\theta} + e^{-j(N-2)\theta}] + \dots \}$$

$$= 2e^{-jN\theta} \{ \Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots \} \leftarrow e^{jx} + e^{-jx} = 2\cos(x)$$

$$\Gamma_0 = \Gamma_N, \Gamma_1 = \Gamma_{N-1}, \Gamma_2 = \Gamma_{N-2}, \text{ etc.}$$

- For **odd N**, the last term is $\Gamma_{(N-1)/2} (e^{j\theta} + e^{-j\theta})$ as

$$\Gamma(\theta) = 2e^{-jN\theta} [\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots + \Gamma_{(N-1)/2} \cos \theta]$$

3 Multi-Section Transformer

- For even N , the last term is $\Gamma_{N/2}$ as

$$\Gamma(\theta) = 2e^{-jN\theta} [\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots + \frac{1}{2} \Gamma_{N/2}]$$

➔ *Above result imply that the desired reflection coefficient responds a function of θ by using enough sections N and properly choosing Γ_n .*

▪ Questions

- How to determine the necessary number of sections N ?

- How do determine the values of all reflection coefficients Γ_n ?

Answer: Answers will be clear if the design multi-section transformers for a small reflection is designed with two of the most commonly used passband responses:

- Binomial (maximally flat) response

- Chebyshev (equal-ripple) response.

4 Example

- Ex.] Consider the 2-stage quarter-wave transformer of below figure with $Z_1 = 75 \Omega$, $Z_2 = 125 \Omega$, and $R_L = 200 \Omega$. Evaluate the worst-case percent error in computing $|\Gamma|$ from the approximate small reflection theory and the almost exact result.

Solution

- Reflection coefficient between transmission lines

$$\Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1} = \frac{125 - 75}{125 + 75} = 0.25, \quad \Gamma_3 = \frac{R_L - Z_2}{R_L + Z_2} = \frac{200 - 125}{200 + 125} = 0.23$$

- Compare Γ the approximate and exact expressions

$$\Gamma = \frac{\Gamma_1 + \Gamma_3 e^{-j2\theta}}{1 + \Gamma_1 \Gamma_3 e^{-j2\theta}} \cong \Gamma_1 + \Gamma_3 e^{-j2\theta}$$

→ The greatest error will occur depend on denominator.
The worst error will be occurred in conditions of $\theta = 0^\circ$ or $\theta = 180^\circ$.


- Almost exact Γ

$$\Gamma \cong \frac{\Gamma_1 + \Gamma_3 e^{-j2\theta}}{1 + \Gamma_1 \Gamma_3 e^{-j2\theta}} = \frac{0.25 + 0.23e^{j0}}{1 + 0.25 \times 0.23e^{j0}} = 0.454$$

- Γ using small reflection theory

$$\Gamma \cong \Gamma_1 + \Gamma_3 e^{-j2\theta} = 0.25 + 0.23e^{j0} = 0.48$$


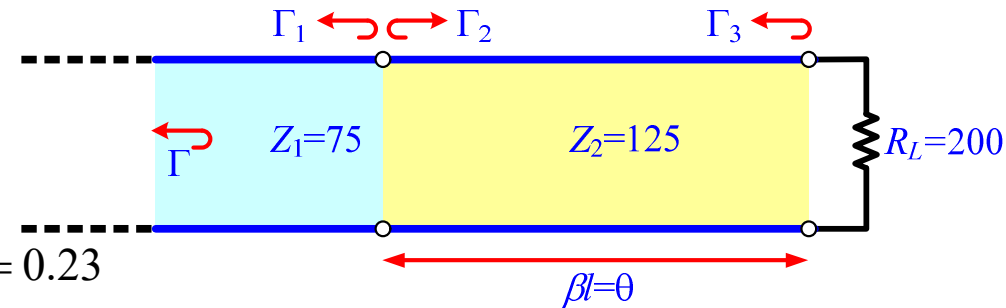
- Thus, the worst-case percent error is about 0.026 or 5.7% .



5 Review

- Single-section transformer
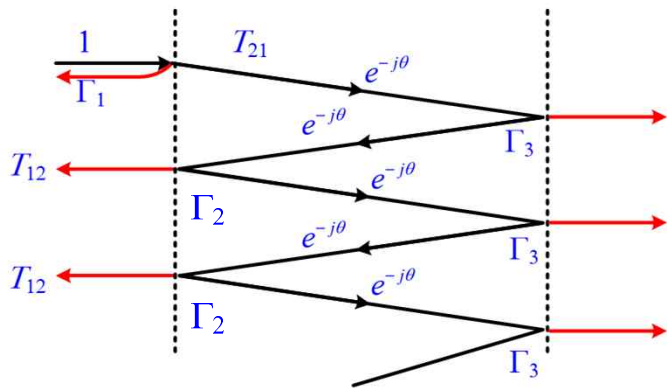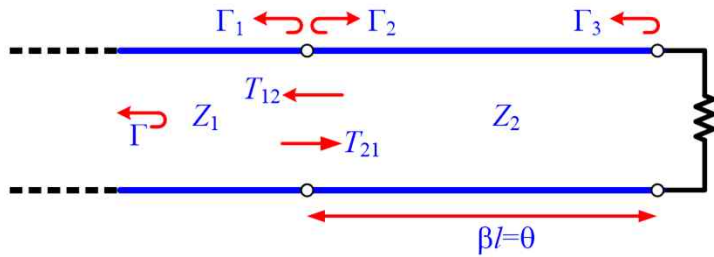
$$\Gamma \cong \Gamma_1 + \Gamma_3 e^{-2j\theta}$$



- Multi-section transformer

$$\Gamma_{in}(\theta) \cong \Gamma_0 + \Gamma_1 e^{-2j\theta} + \Gamma_2 e^{-4j\theta} + \dots + \Gamma_N e^{-2jN\theta}$$

