
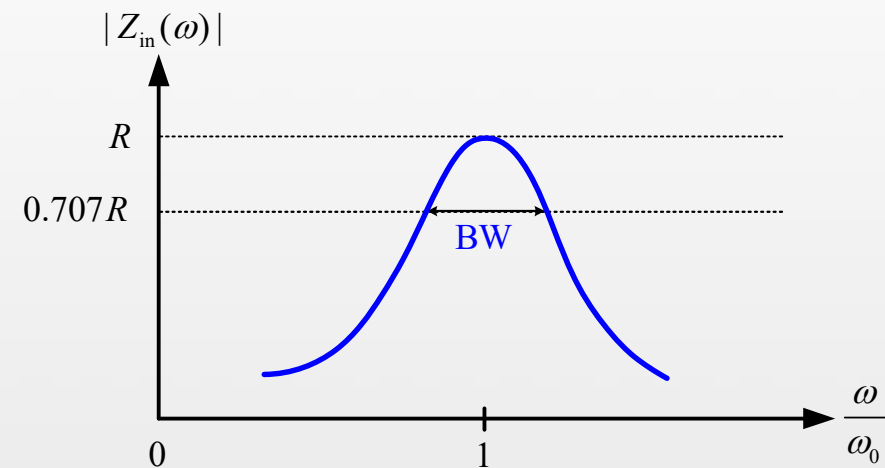


Chapter 6

Microwave Resonators

Prof. Jeong, Yongchae

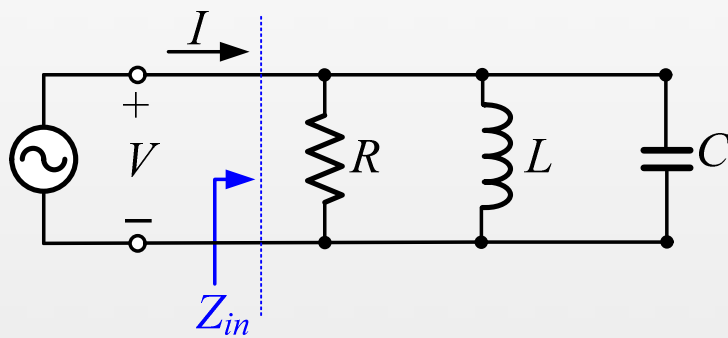

Learning Objectives

- Understanding overview of resonators
- Understanding parallel LC resonant circuit
- Understanding series LC resonant circuit

Learning contents

- Introduction to Microwave Resonators
- Parallel LC Resonant Circuit
- Series LC Resonant Circuit

1 Introduction To Microwave Resonators

- Microwave resonators are used in a variety of applications such as:
 - Filters
 - Oscillators
 - Frequency meters
 - Tuned amplifiers
 - etc.
- The operation of microwave resonators has a similar circuit theory to that of the lumped-element resonators, thus the basic of series and parallel RLC resonant circuits will be reviewed firstly and shortly.
- Types of resonator:
 - Lumped resonator or RLC resonator → Used for low frequency
 - Transmission line resonator → Used for microwave frequency
 - Cavity resonator → Used for RF frequency and high power handling application due to high quality factor.

2 Parallel LC Resonant Circuit

- As its name, a parallel LC resonant circuit (or LC -tank) is an electrical circuit consisting of an inductor (L) and a capacitor (C) connected in parallel, which maintain the same voltage across the components.

- Input impedance

$$Z_{\text{in}} = \left(\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right)^{-1}$$


- Complex power delivered to resonator

$$P_{\text{in}} = \frac{1}{2}VI^* = \frac{1}{2}Z_{\text{in}} |I|^2 = \frac{1}{2}|V|^2 \frac{1}{Z_{\text{in}}^*} = \frac{1}{2}|V|^2 Y_{\text{in}}^*$$

$$= \frac{1}{2}|V|^2 \left(\frac{1}{R} - \frac{1}{j\omega L} - j\omega C \right)$$

$$= \frac{1}{2} \frac{|V|^2}{R} + j2\omega \left(\frac{1}{4} \frac{|V|^2}{\omega^2 L} - \frac{1}{4} |V|^2 C \right)$$

$$= P_l + j2\omega(W_m - W_e)$$

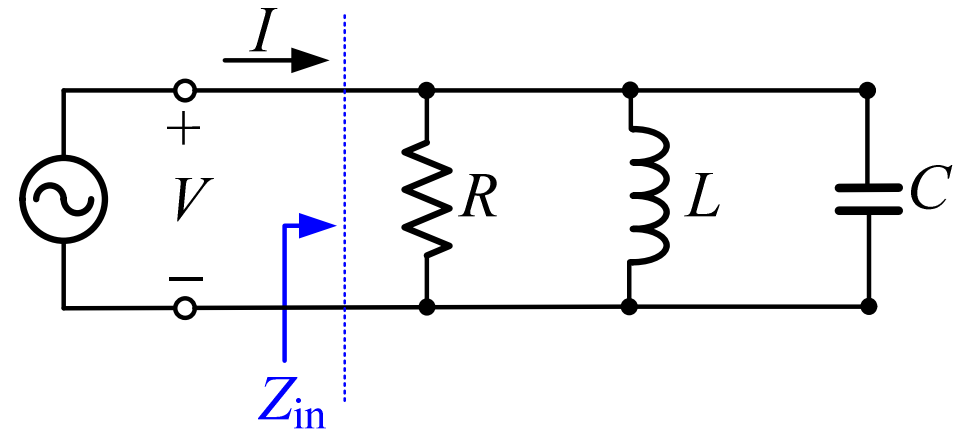

2 Parallel LC Resonant Circuit

- Power dissipated by resistor R

$$P_l = \frac{1}{2} \frac{|V|^2}{R} = \frac{1}{2} G |V|^2$$

- Average electric energy stored in capacitor C

$$W_e = \frac{1}{4} |V|^2 C = \frac{1}{4} V V^* C$$


- Average magnetic energy stored in inductor L

$$W_m = \frac{1}{4} |I_L|^2 L = \frac{1}{4} I_L I_L^* L = \frac{1}{4} \left| \frac{V}{\omega L} \right|^2 L = \frac{1}{4\omega^2 L} V V^*$$

- Input impedance

$$P_{in} = \frac{1}{2} V I^* = \frac{1}{2} Z_{in} |I|^2$$

$$\rightarrow Z_{in} = \frac{P_{in}}{\frac{1}{2} |I|^2} = \frac{P_l + j2\omega(W_m - W_e)}{\frac{1}{2} |I|^2}$$

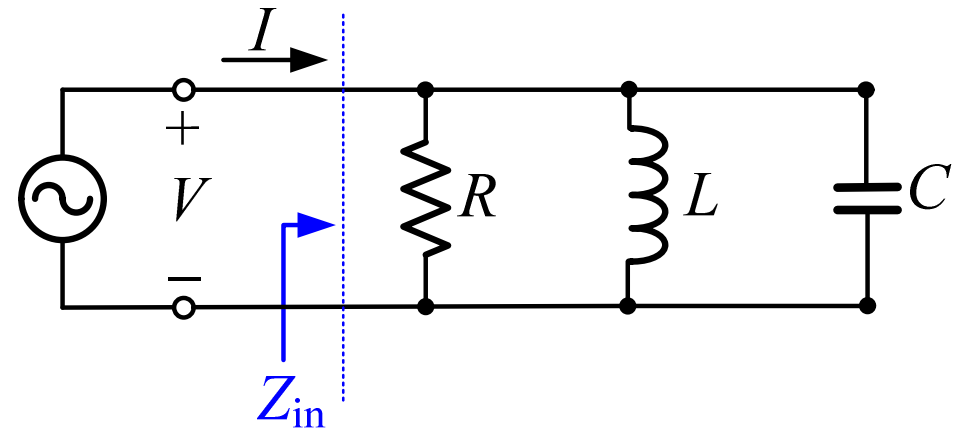

2 Parallel LC Resonant Circuit

- If $W_e = W_m$

$$\frac{1}{4}VV^*C = \frac{1}{4\omega_0^2L}VV^* \rightarrow C = \frac{1}{\omega_0^2L}$$

$$\therefore \omega = \omega_0 = \sqrt{\frac{1}{LC}}$$

- Quality factor (Q -factor)


$$Q = \omega_0 \frac{\text{average stored energy}}{\text{dissipated power loss}}$$

- Stored time average energy

$$W = W_m + W_e = 2W_m = 2W_e = \frac{1}{2}CVV^*$$

- Dissipated power: $P_l = \frac{1}{2}GVV^*$
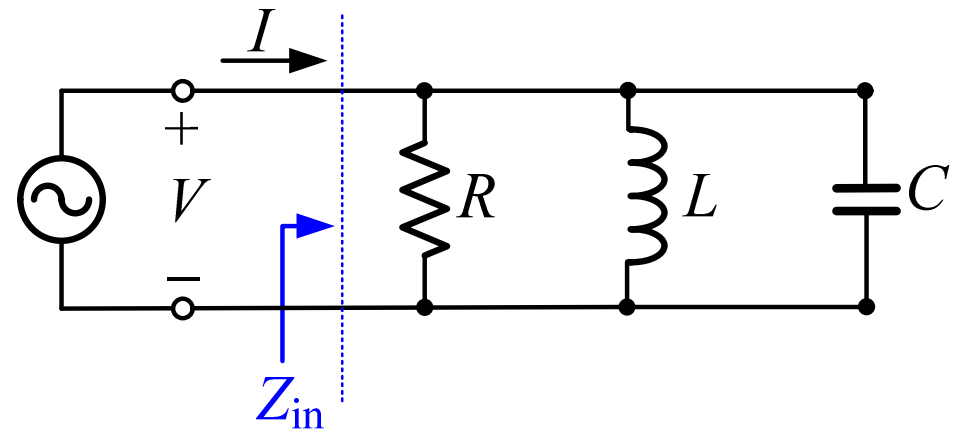
$$\Rightarrow Q = \omega_0 \frac{\frac{1}{2}CVV^*}{\frac{1}{2}GVV^*} = \frac{\omega_0 C}{G} = \omega_0 RC = \frac{R}{\omega_0 L} \quad (\text{in parallel RLC network})$$



2 Parallel LC Resonant Circuit

- Impedance at around resonate frequency (@ $\omega = \omega_0 \pm \Delta\omega$)

$$Z_{in} = \left[\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right]^{-1} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C}$$



$$= \frac{R}{1 + j\omega_0 RC \left(\frac{\omega}{\omega_0} - \frac{1}{\omega_0 \omega LC} \right)} = \frac{R}{1 + jQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$

$$= \frac{R}{1 + jQ \frac{(\omega + \omega_0)(\omega - \omega_0)}{\omega\omega_0}} \approx \frac{R}{1 \pm j2Q \frac{\Delta\omega}{\omega_0}}$$

- $|Z_{in}|_{\max} = R$ @ $\omega = \omega_0$

- If $2Q \frac{\Delta\omega}{\omega_0} = 1$, $Q = \frac{\omega_0}{2\Delta\omega}$ and $|Z_{in}| = \frac{1}{\sqrt{2}} |Z_{in}|_{\max}$

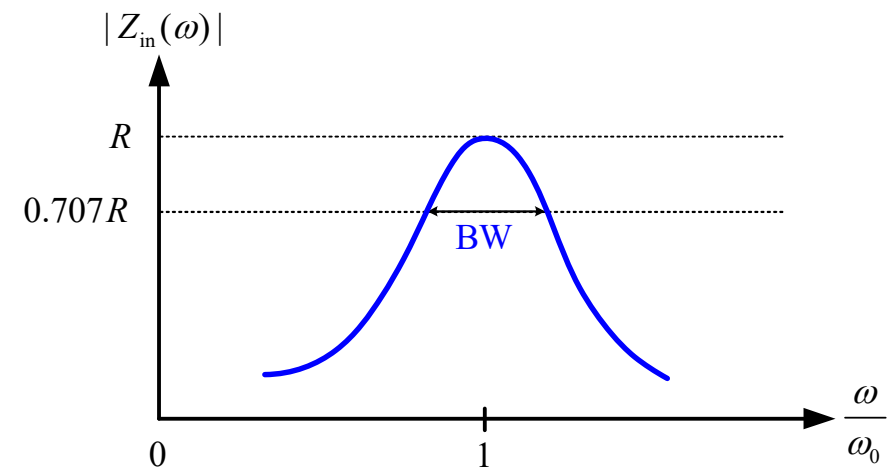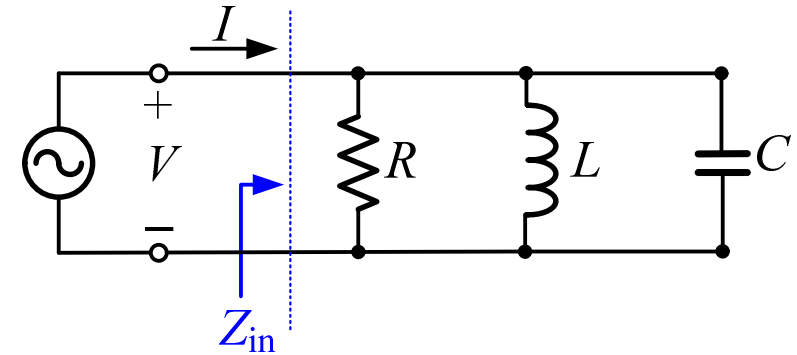where $2\Delta\omega$: bandwidth, $2\Delta\omega / \omega_0$: fractional bandwidth (FBW)



2 Parallel LC Resonant Circuit

- Quality factor (Q -factor, unloaded Q)

$$Q = \frac{\omega_0}{2\Delta\omega} = \frac{1}{\text{FBW}}$$

- Q including load or source resistance: Q_L (loaded Q)



$$Q_L = \frac{R // R_L}{\omega_0 L} = \frac{RR_L / (R + R_L)}{\omega_0 L}$$

- If $R = \infty$, the external Q can be calculated as

$$Q_{ex} = \frac{R_L}{\omega_0 L}$$

- If $R_L = \infty$, the internal Q or unloaded Q is

$$Q_{in} = Q_u = \frac{R}{\omega_0 L}$$

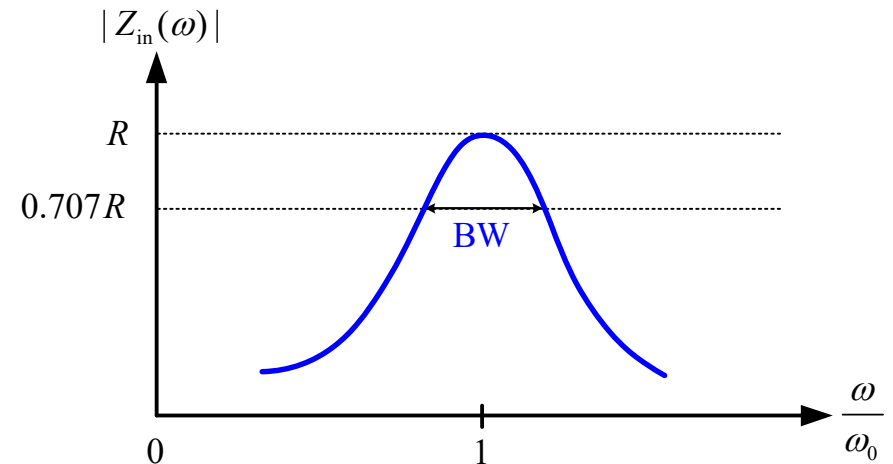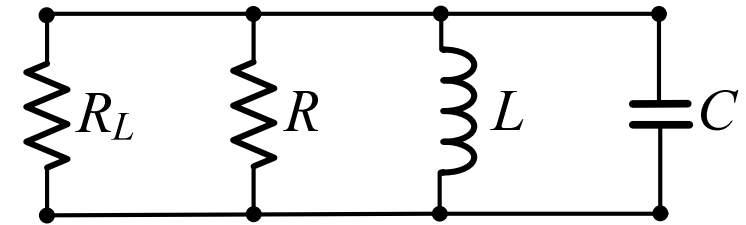


2 Parallel LC Resonant Circuit

- General relationship among Q -factors

$$Q_L = \frac{R // R_L}{\omega_0 L} = \frac{RR_L / (R + R_L)}{\omega_0 L}$$

$$\frac{1}{Q_L} = \frac{\omega_0 L}{RR_L} = \omega_0 L \frac{R + R_L}{RR_L} = \omega_0 L \left(\frac{1}{R} + \frac{1}{R_L} \right)$$
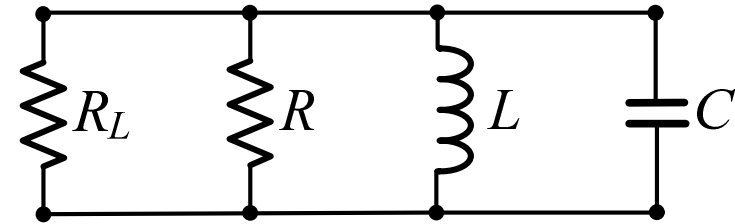
$$= \frac{\omega_0 L}{R} + \frac{\omega_0 L}{R_L} = \frac{1}{Q_u} + \frac{1}{Q_{ex}} \Rightarrow Q_L < Q_u \text{ \& } Q_{ex}$$



- Energy damping factor (δ)** : Decaying ratio of oscillation amplitude in case of drop of external energy

$$W = W_0 e^{-2\delta t}$$

$$-\frac{dW}{dt} = P_l = 2\delta W$$

$$\delta = \frac{P_l}{2W} = \frac{\omega_0}{2} \frac{P_l}{\omega_0 W} = \frac{\omega_0}{2Q}$$

$$W = W_0 e^{-\omega_0 t / Q} \rightarrow \text{Higher } Q\text{-factor guarantees longer energy conservation!}$$

3 Series LC Resonant Circuit



- In series LC circuit, the components share the same current but have different voltage across each, showing voltage summation.

- Input impedance

$$Z_{in} = R + j\omega L - j\frac{1}{\omega C}$$

- Complex power delivered to the resonator

$$\begin{aligned} P_{in} &= \frac{1}{2}VI^* = \frac{1}{2}Z_{in}|I|^2 = \frac{1}{2}|V|^2 \frac{1}{Z_{in}^*} \\ &= \frac{1}{2}|I|^2 \left(R + j\omega L - j\frac{1}{\omega C} \right) \\ &= \frac{1}{2}|I|^2 R + j2\omega \left(\frac{1}{4}|I|^2 L - \frac{1}{4}\frac{|I|^2}{\omega^2 C} \right) \\ &= P_l + j2\omega(W_m - W_e) \end{aligned}$$

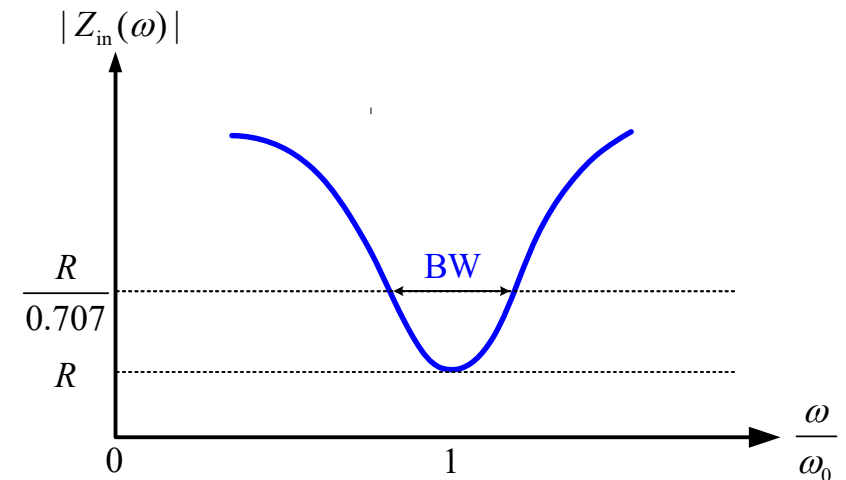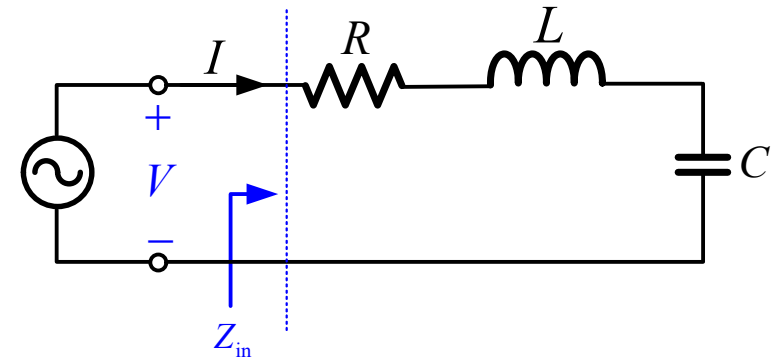

3 Series LC Resonant Circuit

- Power dissipated by resistor (R)

$$P_l = \frac{1}{2} |I|^2 R$$

- Average electric energy stored in capacitor (C)

$$W_e = \frac{1}{4} |V_C|^2 C = \frac{1}{4} |I|^2 \frac{1}{\omega^2 C}$$


where V_C : voltage across capacitor

- Average magnetic energy stored in the inductor (L)

$$W_m = \frac{1}{4} |I|^2 L$$

- Input impedance

$$Z_{in} = \frac{P_{in}}{\frac{1}{2} |I|^2} = \frac{P_l + 2j\omega(W_m - W_e)}{\frac{1}{2} |I|^2}$$

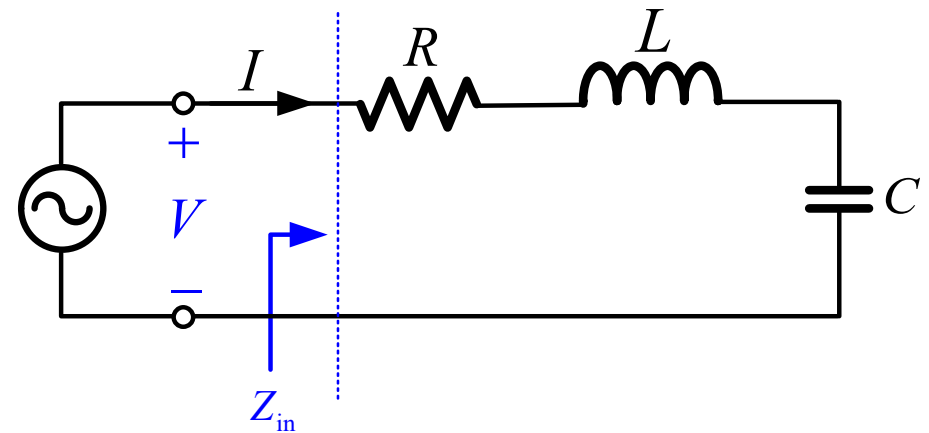

3 Lumped Resonant Circuit: LC Series Resonant Circuit

- At the resonant frequency, $W_m = W_e$

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

- Quality factor (Q -factor)

$$Q = \omega_0 \frac{\text{average stored energy}}{\text{dissipated power loss}} = \omega_0 \frac{W_m + W_e}{P_l}$$



- Unloaded Q can be evaluated at resonance: $W_m = W_e$

$$Q_u = \omega_0 \frac{2W_m}{P_l} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

→ Q is increased as R decreases

- Impedance near the resonant frequency: $\omega = \omega_0 \pm \Delta\omega$
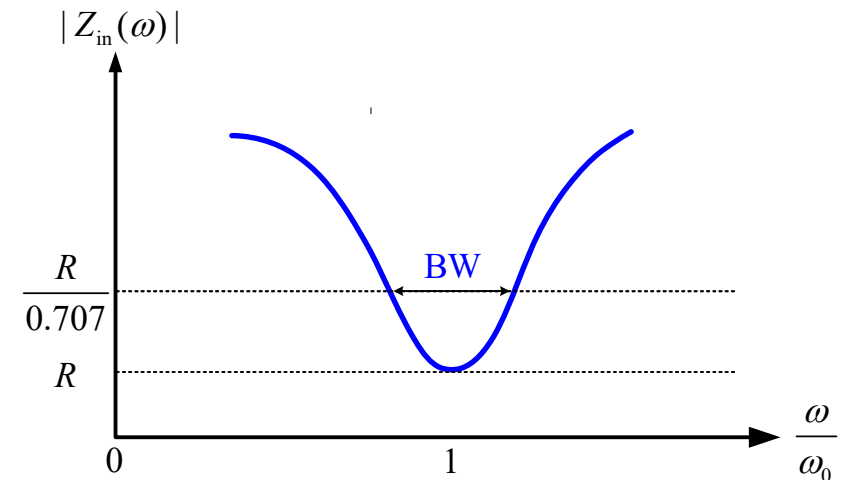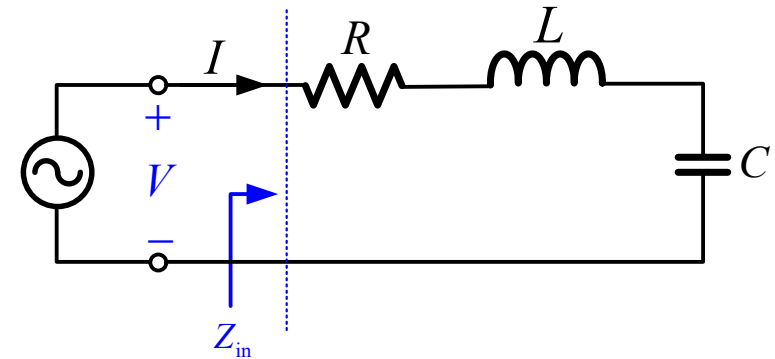
$$Z_{in} = R + j\omega_0 L \left(\frac{\omega}{\omega_0} - \frac{1}{\omega\omega_0 LC} \right) = R + j\omega_0 L \left(\frac{\omega^2 - \omega_0^2}{\omega_0 \omega} \right)$$





3 Lumped Resonant Circuit: LC Series Resonant Circuit

- Due to $\omega^2 - \omega_0^2 = (\omega - \omega_0)(\omega + \omega_0)$
 $= \Delta\omega(2\omega - \Delta\omega)$
 $\approx 2\omega\Delta\omega$ for small $\Delta\omega$

- Relation between Z_{in} and Q_u

$$Z_{in} = R + j\omega_0 L \left(\frac{\omega^2 - \omega_0^2}{\omega_0 \omega} \right)$$
$$\approx R \left\{ 1 + j \frac{\omega_0 L}{R} \left(\frac{2\omega\Delta\omega}{\omega_0 \omega} \right) \right\}$$
$$= R \left(1 + j2Q \frac{\Delta\omega}{\omega_0} \right)$$

(in series RLC network)

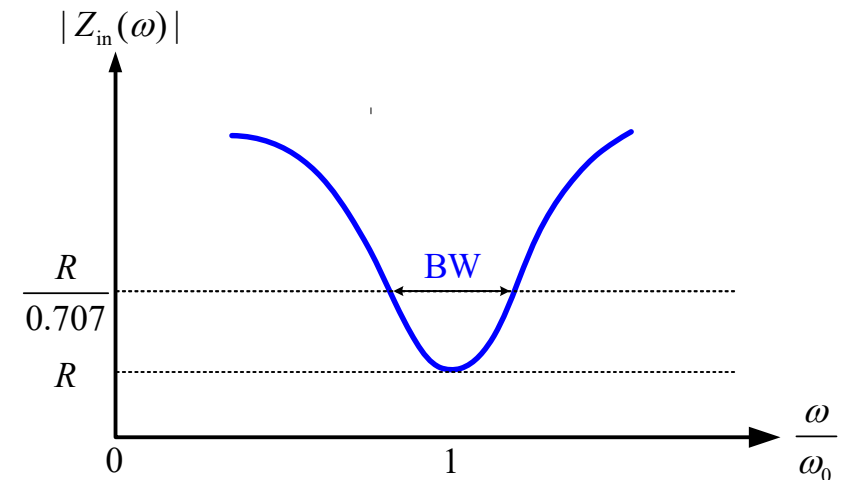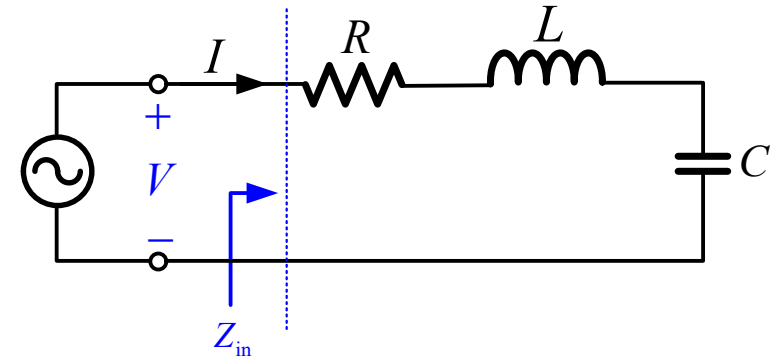


3 Lumped Resonant Circuit: LC Series Resonant Circuit

- **Example:** A series resonant network consisting of a resistor of $30\ \Omega$, a capacitor of $2\ \mu\text{F}$, and an inductor of $2\ \text{mH}$ is connected across a sinusoidal supply voltage which has a constant output of $9\ \text{V}$ at all frequencies.
 - a) Determine resonant frequency
 - b) Determine current at resonance
 - c) Determine voltage magnitude across inductor
 - d) Determine unloaded Q of circuit at resonance

Solution:

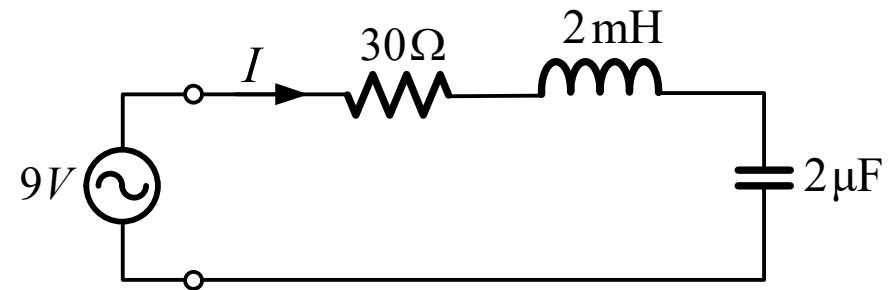- a) Resonant frequency:

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.002 \times 2 \times 10^{-6}}} = 2,516\ \text{Hz}$$



3 Lumped Resonant Circuit: LC Series Resonant Circuit

b) Current at resonant


$$I = \frac{V}{R} = \frac{9}{30} = 0.3 \text{ A}$$

c) Voltage across inductor

$$\begin{aligned} |V_L| &= I \times X_L = 0.3 \times (2\pi fL) \\ &= 0.3 \times (2\pi \times 2516 \times 0.002) = 9.48 \text{ V} \end{aligned}$$

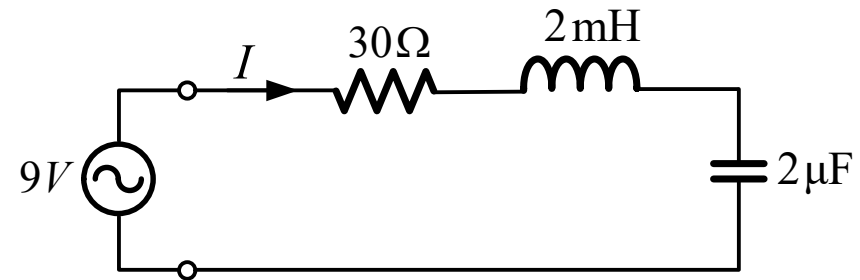
d) Determine unloaded Q :

$$\begin{aligned} Q_u &= \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} \\ &= \frac{2\pi fL}{R} = \frac{2\pi \times 2516 \times 0.002}{30} = 1.05 \quad \text{: not good } Q\text{-factor} \end{aligned}$$



4 Review

Quantity	Parallel Resonator	Series Resonator
Input impedance/admittance	$Y_{in} = \frac{1}{R} + j\omega C - j\frac{1}{\omega L}$ $\approx \frac{1}{R} + j\frac{2Q_u\Delta\omega}{R\omega_0}$	$Z_{in} = R + j\omega L - j\frac{1}{\omega C}$ $\approx R + j\frac{2RQ_u\Delta\omega}{\omega_0}$
Power loss	$P_l = \frac{1}{2} \frac{ V ^2}{R}$	$P_l = \frac{1}{2} I ^2 R$
Stored magnetic energy	$W_m = \frac{1}{4} V ^2 \frac{1}{\omega^2 L}$	$W_m = \frac{1}{4} I ^2 L$
Stored electric energy	$W_e = \frac{1}{4} V ^2 C$	$W_e = \frac{1}{4} I ^2 \frac{1}{\omega^2 C}$
Resonant frequency	$\omega_0 = \frac{1}{\sqrt{LC}}$	$\omega_0 = \frac{1}{\sqrt{LC}}$
Unloaded Q	$Q_u = \omega_0 RC = \frac{R}{\omega_0 L}$	$Q_u = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$
External Q	$Q_{ex} = \frac{R_L}{\omega_0 L}$	$Q_{ex} = \frac{\omega_0 L}{R_L}$

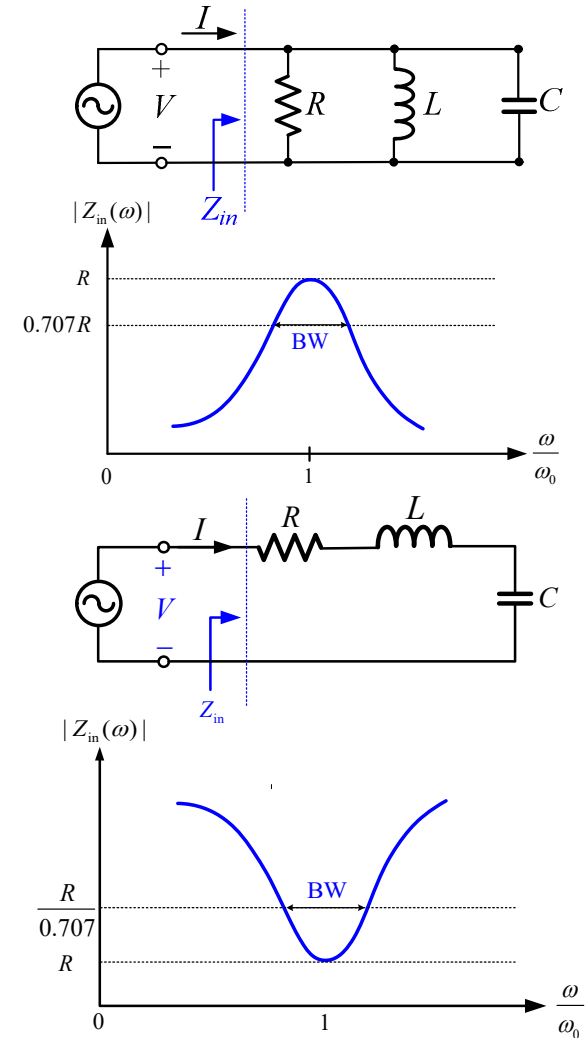

4 Review

Why the *LC* circuit (or *LC*-tank) is called a tuned circuit or tank circuit?

- The charge flows back and forth between the plates of the capacitor and through the inductor. The energy oscillates between a capacitor and an inductor until the internal resistance of the components and connecting wires makes the oscillations to die-out.
- The LC circuit behaves like a harmonic oscillator, akin to a pendulum swinging or water sloshing in a tank, which is why it's called a tuned or tank circuit.
- The LC circuit can act as an electrical resonator and storing energy oscillates between the electric field and magnetic field at the frequency called a resonant frequency.