
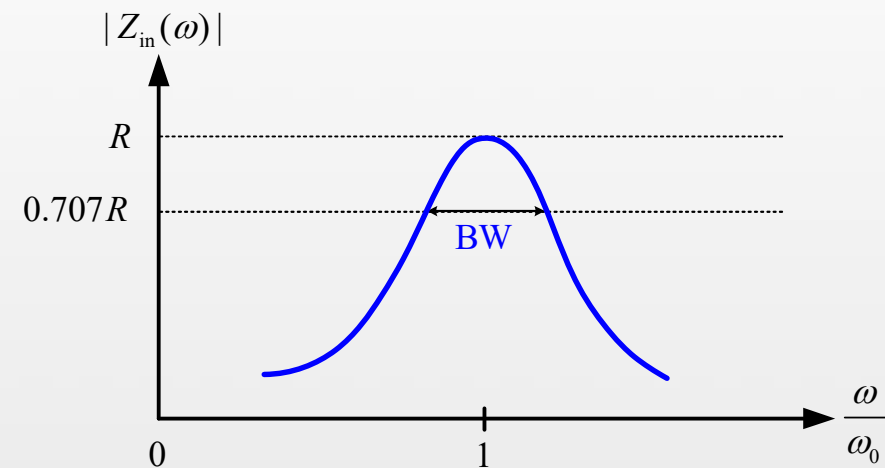


Chapter 6

Microwave Resonant Circuit

Prof. Jeong, Yongchae

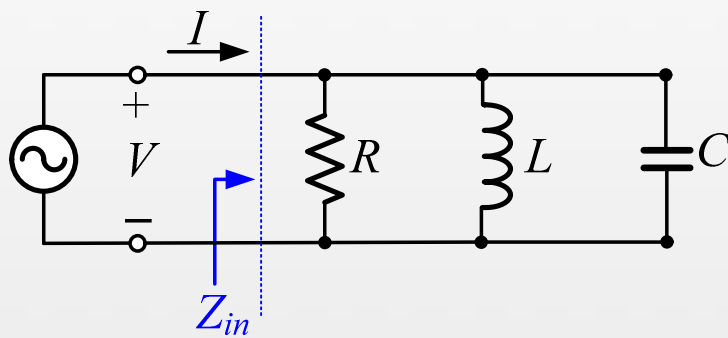

Learning Objectives

- Understanding about transmission line resonator
- Understanding about coaxial resonator
- Understand Q -factor of transmission line resonator

Learning contents

- Transmission Line Resonator
- Coaxial Resonator
- Q of transmission line resonator

1 Transmission Line Resonator

▪ Shorted transmission line resonator

- Input impedance

$$Y_{\text{in}} = -jY_0 \cot[\beta(\omega)d] \leftarrow \beta = \frac{2\pi}{\lambda} = \frac{\omega}{c} = f(\beta), @ \beta(\omega_0)d = (2n-1) \cdot \frac{\pi}{2}$$

$$\Rightarrow Y_{\text{in}} = 0$$

- For parallel LC resonant circuit:


$$Y = j\left(\omega C - \frac{1}{\omega L}\right) \leftarrow @ \omega_0 = \frac{1}{\sqrt{LC}}$$

$$= 0$$

- In order to have the same frequency characteristics:

$$(1) \quad Y_{\text{in}} = Y = 0 \quad @ \quad \omega = \omega_0$$

$$(2) \quad \left. \frac{\partial Y_{\text{in}}}{\partial \omega} \right|_{\omega_0} = \left. \frac{\partial Y}{\partial \omega} \right|_{\omega_0}$$

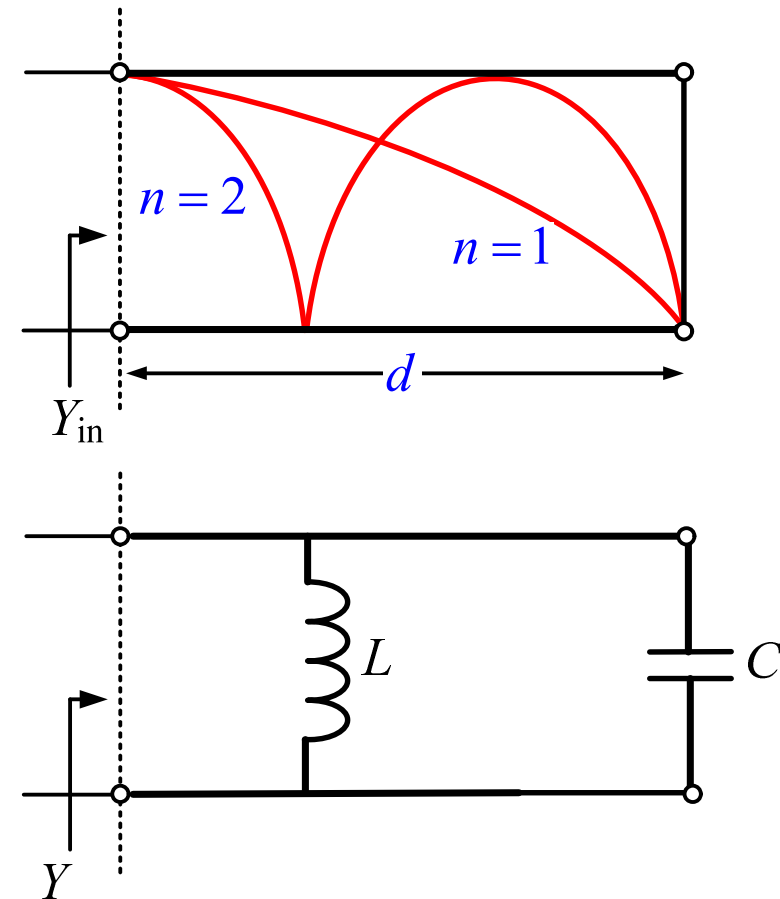

1 Transmission Line Resonator


- In order to have the same frequency characteristics (continued)

$$\left. \frac{\partial Y_{\text{in}}}{\partial \omega} \right|_{\omega_0} = -jY_0 \frac{-1}{\sin^2 \beta(\omega)d} \cdot d \cdot \left. \frac{d\beta}{d\omega} \right|_{\omega_0} = jY_0 \frac{\beta'(\omega_0)}{\sin^2 \beta(\omega_0)d} d \quad \leftarrow Y_{\text{in}} = -jY_0 \cot[\beta(\omega)d], \beta(\omega_0)d = (2n-1) \cdot \frac{\pi}{2}$$

$$= jY_0 \beta'(\omega_0)d = jY_0 \frac{\beta'(\omega_0)}{\beta(\omega_0)} \frac{(2n-1)\pi}{2}$$

$$\left. \frac{\partial Y}{\partial \omega} \right|_{\omega_0} = j \left(C + \frac{1}{\omega^2 L} \right) \Big|_{\omega_0} = j2C \quad \leftarrow Y = j \left(\omega C - \frac{1}{\omega L} \right), @ \omega_0 = \frac{1}{\sqrt{LC}}$$
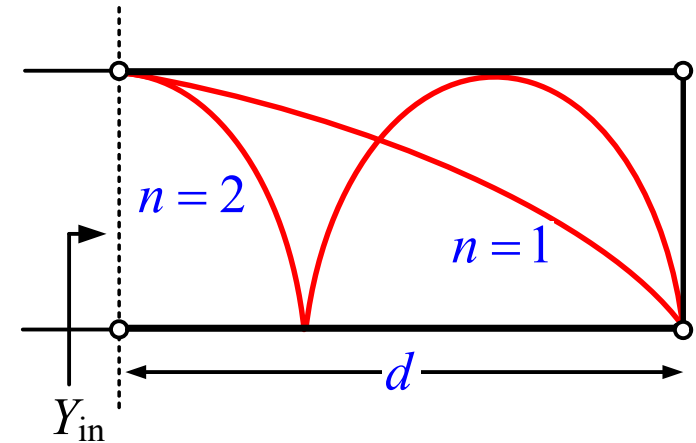
$$\Rightarrow C = \frac{Y_0 \beta'(\omega_0)}{2\beta(\omega_0)} \frac{(2n-1)\pi}{2}, \quad L = \frac{1}{\omega_0^2 C}$$



- For the coaxial transmission line: $\beta = \omega\sqrt{LC}$

$$C = \frac{Y_0 \beta'(\omega_0)}{2\beta(\omega_0)} \frac{(2n-1)\pi}{2} \Big|_{\beta=\omega\sqrt{LC}} = \frac{Y_0 \sqrt{LC}}{2\omega_0 \sqrt{LC}} \frac{(2n-1)\pi}{2} = \frac{Y_0}{2\omega_0} \frac{(2n-1)\pi}{2}, \quad L = \frac{1}{\omega_0^2 C}$$

1 Transmission Line Resonator

▪ Loaded Transmission Line

- Insert susceptance “ jB ” on **real** transmission line;

- Consider

$$\gamma = \alpha + j\beta = j(\beta - j\alpha)$$

where α : attenuation constant of transmission line

β : phase constant of transmission line

- Input Admittance


$$Y_{in} = jB - jY_0 \coth \gamma d = jB - jY_0 \cot(\beta - j\alpha)d$$

- At the resonant frequency ω_0 with small α , $Y_{in} = 0$

$$0 = jB - jY_0 \cot(\beta(\omega_0)d)$$

- For $|B| \gg Y_0$
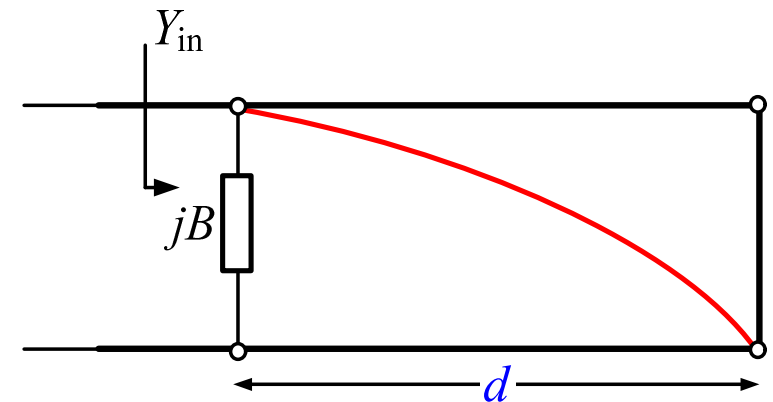
$$\therefore \beta(\omega_0)d = \cot^{-1}\left(\frac{B}{Y_0}\right) \approx n\pi$$



2 Coaxial Resonator

- Coaxial resonator

- TEM mode resonator at VHF and UHF

$$l \approx \frac{n\lambda}{4}, \quad n = 1, 2, 3, \dots$$

- @ $z = d_1$


$$Z_l = jZ_0 \tan\left(\frac{2\pi}{\lambda}d_1\right)$$

- @ resonant frequency (ω_0)

$$Z_0 \tan\left(\frac{2\pi}{\lambda}d_1\right) - \frac{1}{\omega_0 C} = 0$$

- Resonant frequency is determined by Z_0 , d_1 , and C .

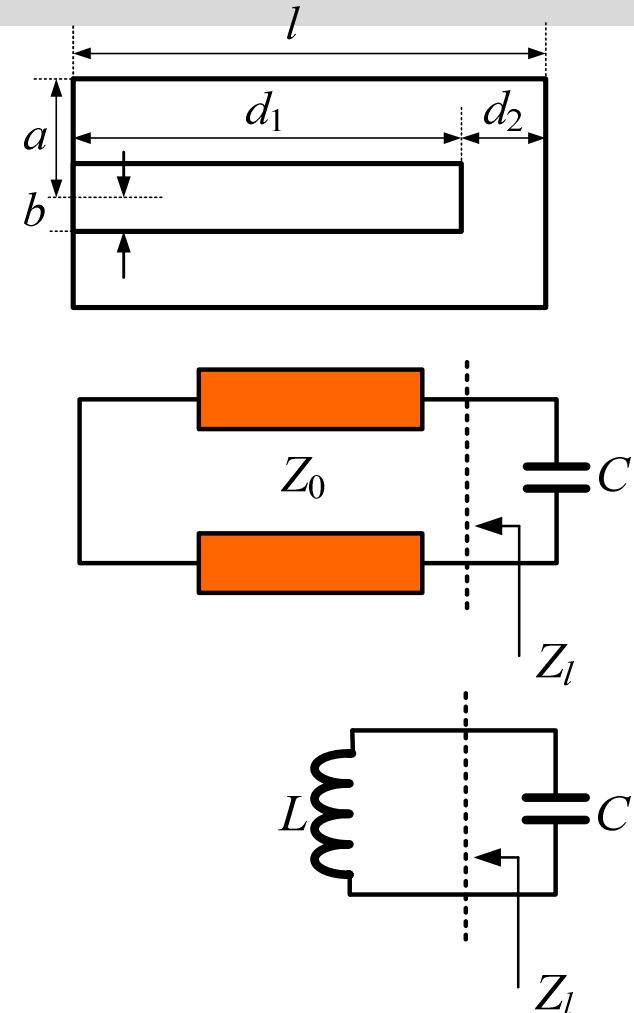- **Low Q -factor** but **simple** and **single mode (TEM mode)** operation for variable resonant frequency.



3 Q of Transmission Line Resonator

- Real transmission line resonator
 - Q -factor of **real** ($\gamma = \alpha + j\beta$) transmission line resonator

- Length of transmission line: $d = \frac{\lambda}{4}$ at f_0

- Near the resonant frequency ($\omega = \omega_0 + \Delta\omega$)

$$\beta d = \omega\sqrt{LC}d = \omega_0\sqrt{LC}d + \Delta\omega\sqrt{LC}d$$


- Since

$$\tan \beta d = \tan\left(\omega_0\sqrt{LC}d + \Delta\omega\sqrt{LC}d\right) = \tan\left(\frac{\pi}{2} + \Delta\omega\sqrt{LC}d\right)$$

$$= -\cot(\Delta\omega\sqrt{LC}d)$$

$$\approx \frac{-1}{\Delta\omega\sqrt{LC}d}$$


$$\tanh \alpha d \approx \alpha d \quad (@ |\alpha d| \ll 1),$$

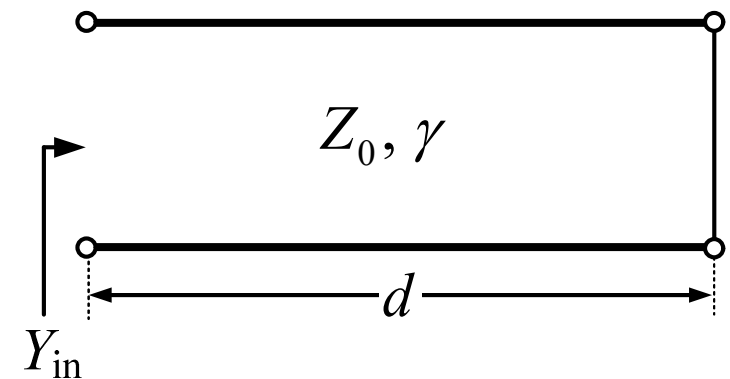

3 Q of Transmission Line Resonator

- Normalized input admittance at around resonant frequency

$$\begin{aligned}\bar{Y}_{\text{in}} &= \frac{Y_{\text{in}}}{Y_0} = \coth \gamma d = \coth(\alpha + j\beta)d = \frac{1}{\tanh(\alpha + j\beta)d} \\ &= \frac{1 + j \tan \beta d \tanh \alpha d}{\tanh \alpha d + j \tan \beta d} \approx \frac{1 - j\alpha d / \Delta\omega \sqrt{LCd}}{\alpha d - j / \Delta\omega \sqrt{LCd}} \\ &= \frac{\Delta\omega \sqrt{LCd} - j\alpha d}{\Delta\omega \sqrt{LC} \alpha d^2 - j} = \frac{\alpha d + j\Delta\omega \sqrt{LCd}}{1 + j\Delta\omega \sqrt{LC} \alpha d^2}\end{aligned}$$

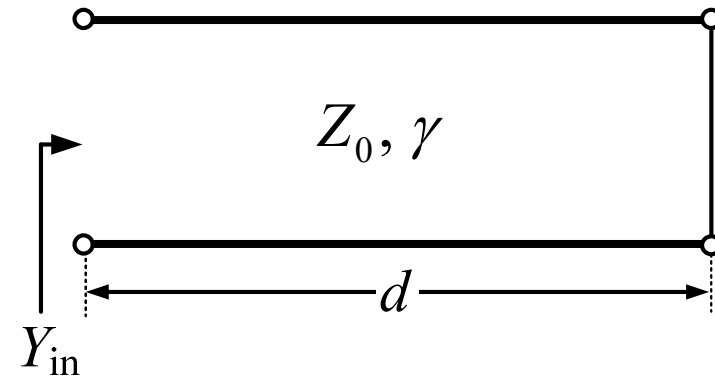

- Further approximation:

$$\bar{Y}_{\text{in}} = \frac{\alpha d + j\Delta\omega \sqrt{LCd}}{1 + j\Delta\omega \alpha d^2 \sqrt{LC}} \approx \alpha d + j\Delta\omega \sqrt{LCd} \leftarrow \alpha \text{ and } \Delta\omega: \text{ too small values}$$

- Using $Y_0 = \sqrt{\frac{C}{L}}$ and $\alpha = \frac{Y_0 R}{2}$,

$$Y_{\text{in}} = \bar{Y}_{\text{in}} Y_0 = (\alpha d + j\Delta\omega \sqrt{LCd}) Y_0 = \frac{R}{2} Y_0^2 d + j\Delta\omega \sqrt{LCd} Y_0 = \frac{RC}{2L} d + j\Delta\omega Cd$$

3 Q of Transmission Line Resonator


- Equivalent circuit of real transmission line resonator

- Input admittance:

$$\begin{aligned}
 Y'_{\text{in}} &= \frac{1}{R_0 + j\omega L_0} + j\omega C_0 \leftarrow R_0: \text{ parasitic resistance of inductor} \\
 &= \frac{j\omega C_0 (R_0 + j\omega L_0) + 1}{R_0 + j\omega L_0} \\
 &\approx \frac{j\omega C_0 R_0 - \omega^2 L_0 C_0 + 1}{j\omega L_0} \quad \leftarrow R_0 \ll \omega L_0 \text{ assumed}
 \end{aligned}$$

- @ resonant frequency, $\omega_0^2 L_0 C_0 = 1$
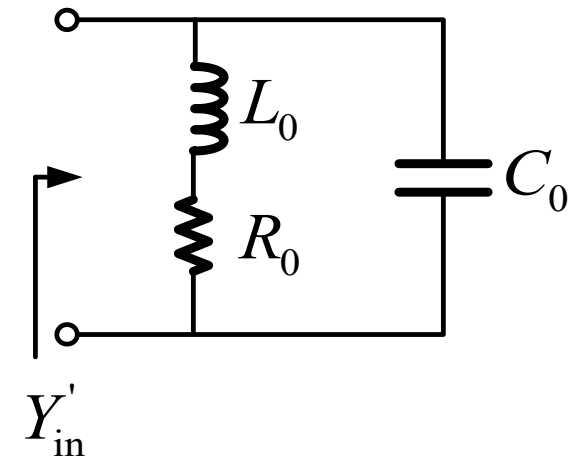
$$\begin{aligned}
 Y'_{\text{in}} &= \frac{C_0 R_0}{L_0} + \frac{\omega_0^2 L_0 C_0 - \omega^2 L_0 C_0}{j\omega L_0} \\
 &= R_0 \frac{C_0}{L_0} - jL_0 C_0 \frac{(\omega_0 - \omega)(\omega_0 + \omega)}{\omega L_0} \approx R_0 \frac{C_0}{L_0} + jC_0 2\Delta\omega
 \end{aligned}$$



3 Q of Transmission Line Resonator

- Comparison to obtain equivalent circuit element values

$$Y_{\text{in}} = \frac{RC}{2L}d + j\Delta\omega Cd$$

$$Y'_{\text{in}} = R_0 \frac{C_0}{L_0} + j2\Delta\omega C_0$$



$$\Rightarrow R_0 \frac{C_0}{L_0} = \frac{RC}{2L}d = \frac{RC_0}{L} \leftarrow Cd = 2C_0$$

$$\Rightarrow \frac{R_0}{L_0} = \frac{R}{L}$$

- Q -factor of equivalent circuit

$$Q = \frac{\omega L_0}{R_0} \leftarrow \text{Assuning lossless } C_0$$
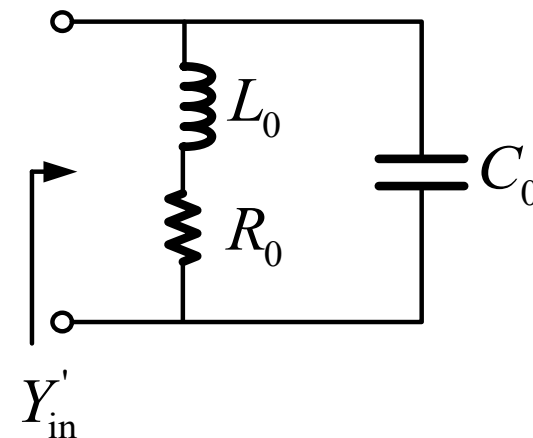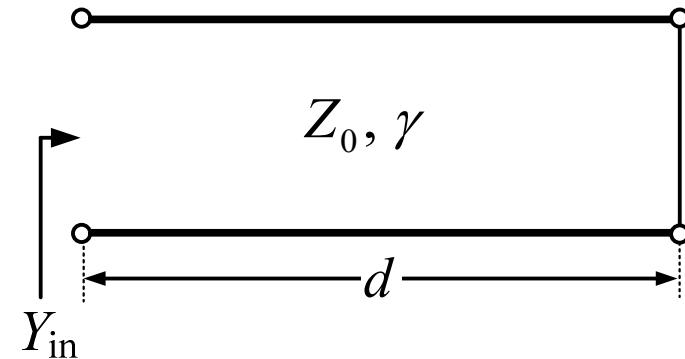
$$= \frac{\omega L}{R} = \frac{\omega L}{2\alpha} = \frac{\omega L}{2\alpha} \sqrt{\frac{C}{L}} = \frac{\omega \sqrt{LC}}{2\alpha} = \frac{\beta}{2\alpha}$$



3 Q of Transmission Line Resonator

▪ Example 1

- Open circuited $\lambda/2$ microstrip line resonator of 50Ω
- Teflon substrate ($\epsilon_r = 2.08$, $\tan \delta = 0.0004$, and $h(\text{thickness}) = 0.159 \text{ cm}$) with copper conductors
- Ignore fringing fields at the end of the line.
- $W = 0.508 \text{ cm}$ (50Ω line width), $\epsilon_e = 1.8$ (effective permittivity), and $R_s = 1.84 \text{ p}\Omega$ (surface resistivity)
- Compute required length of line for resonance at 5 GHz and unloaded Q of resonator.


Solution:

- Resonant length with effective dielectric constant (ϵ_e)

$$l = \frac{\lambda}{2} = \frac{v_p}{2f} = \frac{c}{2f\sqrt{\epsilon_e}} = \frac{3 \times 10^8}{2(5 \times 10^9)\sqrt{1.8}} = 2.24 \text{ cm}$$

- Propagation constant
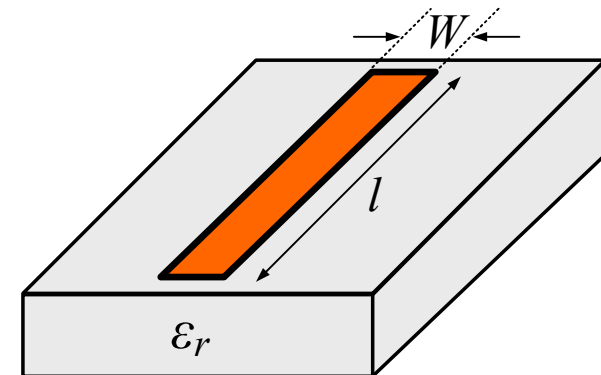
$$\beta = \frac{2\pi f}{v_p} = \frac{2\pi f\sqrt{\epsilon_e}}{c} = \frac{2\pi(5 \times 10^9)\sqrt{1.8}}{3 \times 10^8} = 151 \text{ rad/m}$$



3 Q of Transmission Line Resonator

Solution (continued)

- Approximate attenuation due to conductor loss

$$\alpha_c = \frac{Y_0 R_s}{2 W} = \frac{R_s}{Z_0 W} = \frac{1.84 \times 10^{-12}}{2 \times 50 \times 0.00508} = 0.0362 \text{ Np/m}$$

← $R_s [\Omega / \text{m}^2]$, $\text{m}^2 = \text{width} \times \text{length} [1 \text{ m}] = \text{width}(W)$

- Approximate attenuation due to dielectric loss


$$\alpha_d = \frac{k_0 \epsilon_r (\epsilon_e - 1) \tan \delta}{2 \sqrt{\epsilon_e} (\epsilon_r - 1)} = \frac{104.7 \times 2.08 \times (1.8 - 1) \times 0.0004}{2 \sqrt{1.8} \times (2.08 - 1)} = 0.024 \text{ Np/m}$$

- Total attenuation with ignoring radiation loss

$$\alpha = \alpha_c + \alpha_d = 0.0362 + 0.024 = 0.0604 \text{ Np/m}$$

- Unloaded Q of the microstrip resonator
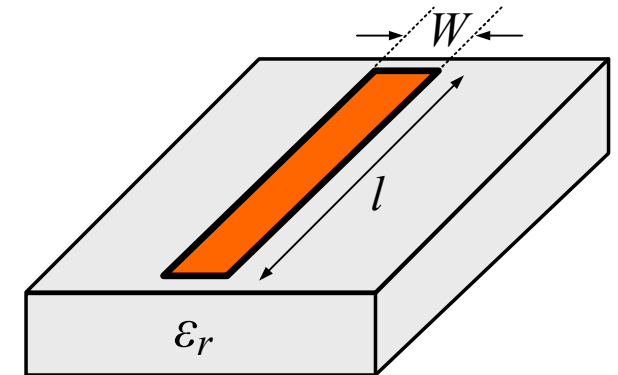
$$Q_0 = \frac{\beta}{2\alpha} = \frac{151}{2 \times 0.0604} = 1,250$$



3 Q of Transmission Line Resonator

▪ Example 2


- A $\lambda/2$ copper coaxial line with $a = 1$ mm , $b = 4$ mm, $\epsilon_r = 2.08$, and $\tan \delta = 0.0004$.
- Conductivity of copper $\sigma = 5.813 \times 10^7$ S/m
- Intrinsic impedance of electric material filled coaxial line: $\eta = 377$ and surface resistivity $R_s = 1.84 \times 10^{-2} \Omega$.
- Resonant frequency: 5 GHz
- Compare the unloaded Q of an air-filled coaxial line resonator to Teflon-filled coaxial line resonator.

Solution:

- Propagation constants of each dielectric material (symmetrical & homogenous materials)

$$\beta_{\text{air}} = \frac{2\pi f}{v_p} = \frac{2\pi f \sqrt{\epsilon_0}}{c} = \frac{2\pi(5 \times 10^9) \sqrt{1}}{3 \times 10^8} = 104.7 \text{ rad/m}$$
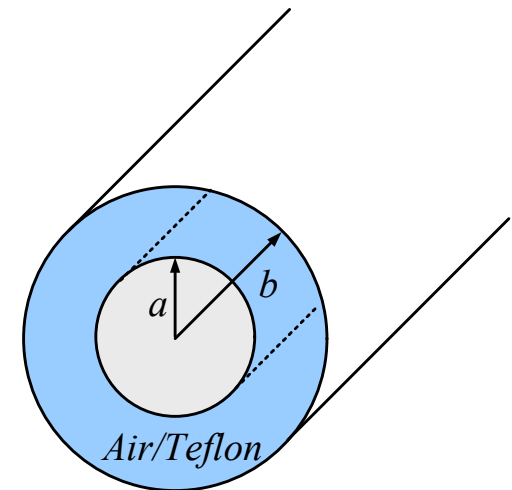
$$\beta_{\text{Teflon}} = \frac{2\pi f}{v_p} = \frac{2\pi f \sqrt{\epsilon_r}}{c} = \frac{2\pi(5 \times 10^9) \sqrt{2.08}}{3 \times 10^8} = 151.02 \text{ rad/m}$$



3 Q of Transmission Line Resonator

Solution (continued)

- Attenuation due to conductor loss for the air-filled line

$$\alpha_{c_air} = \frac{R_s}{2\eta \ln\left(\frac{b}{a}\right)} \left(\frac{1}{a} + \frac{1}{b}\right) = \frac{1.84 \times 10^{-2}}{2 \times 377 \times \ln\left(\frac{0.004}{0.001}\right)} \left(\frac{1}{0.001} + \frac{1}{0.004}\right) = 0.022 \text{ Np/m}$$


- Attenuation due to conductor loss for teflon-filled line

$$\alpha_{c_Teflon} = \frac{R_s \sqrt{\epsilon_r}}{2\eta \ln\left(\frac{b}{a}\right)} = \frac{1.84 \times 10^{-12} \times \sqrt{2.08}}{2 \times \ln\left(\frac{0.004}{0.001}\right)} \left(\frac{1}{0.001} + \frac{1}{0.004}\right) = 0.032 \text{ Np/m}$$

- Dielectric loss of air-filled line: $\alpha_{d_air} = 0$.

- Dielectric loss of teflon-filled line
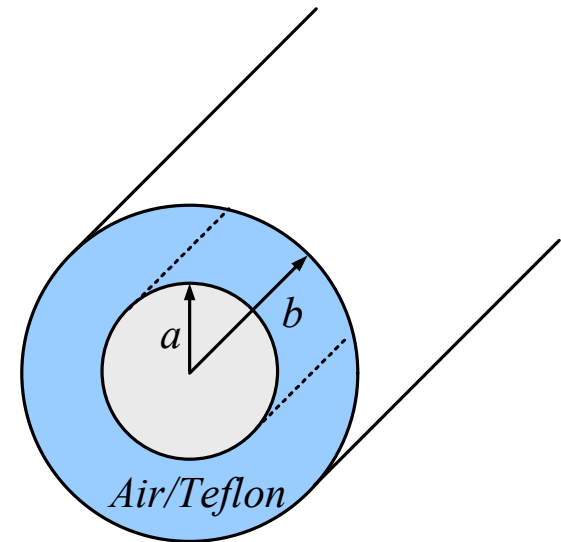
$$\alpha_{d_Teflon} = k_0 \frac{\sqrt{\epsilon_r}}{2} \tan \delta = \frac{104.7 \times \sqrt{2.08} \times 0.0004}{2} = 0.03 \text{ Np/m}$$



3 Q of Transmission Line Resonator

Solution (continued)


- Unloaded Q of air-filled coaxial transmission line resonator

$$Q_{\text{air}} = \frac{\beta_{\text{air}}}{2(\alpha_{c_{\text{air}}} + \alpha_{d_{\text{air}}})} = \frac{104.7}{2 \times (0.022 + 0)} = 2,379.5$$

- Unloaded Q of teflon-filled coaxial transmission line resonator

$$Q_{\text{Teflon}} = \frac{\beta_{\text{Teflon}}}{2(\alpha_{c_{\text{Teflon}}} + \alpha_{d_{\text{Teflon}}})} = \frac{151.02}{2 \times (0.032 + 0.03)} = 1,218$$

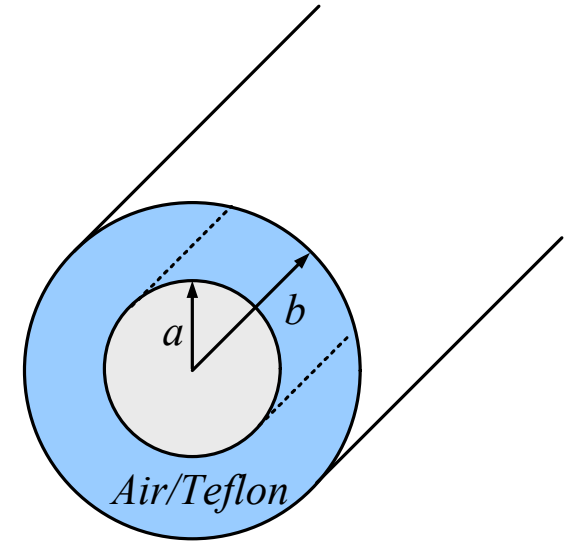- Thus, it is seen that the Q of the teflon-filled line is almost half that of the air-filled line .



4 Review

- Transmission line resonator
- Coaxial resonator
- Unloaded Q of transmission line resonator

