
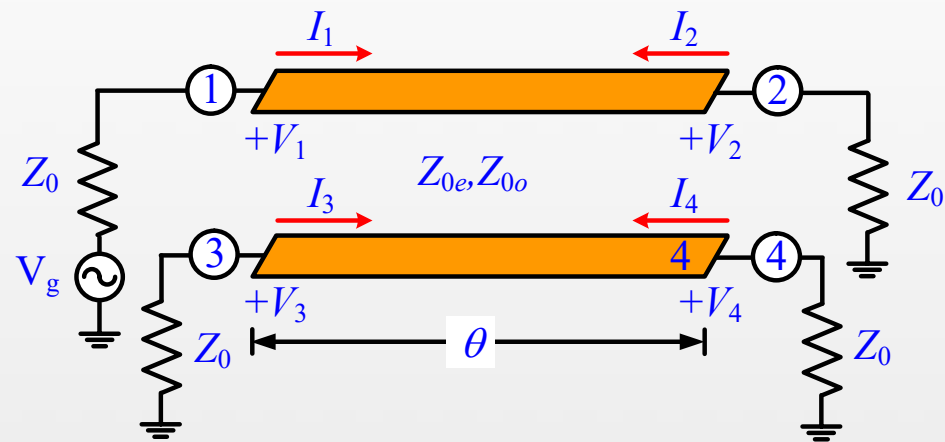


# Chapter 7

## Power Dividers and Couplers

Prof. Jeong, Yongchae

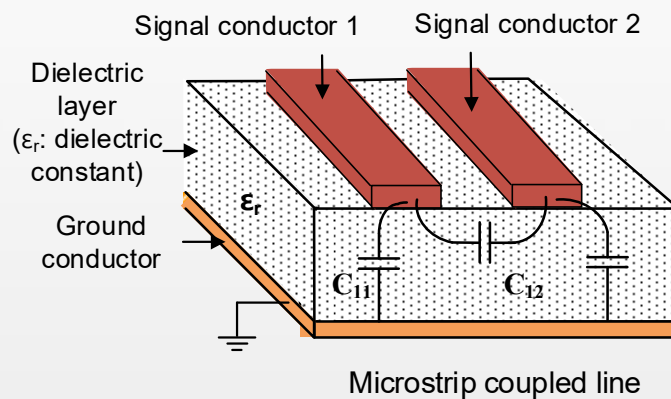

## Learning Objectives



- Understanding what is coupled transmission line.
- Learn about coupled line theory
- Learn what are different configurations of coupled transmission lines.

## Learning contents

- Single and Coupled Transmission Lines
- Coupled line theory
- Different Configurations of Coupled Transmission Lines

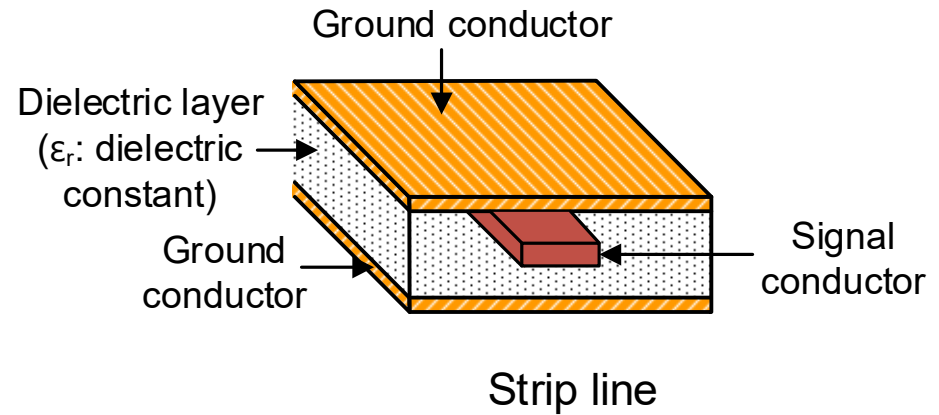
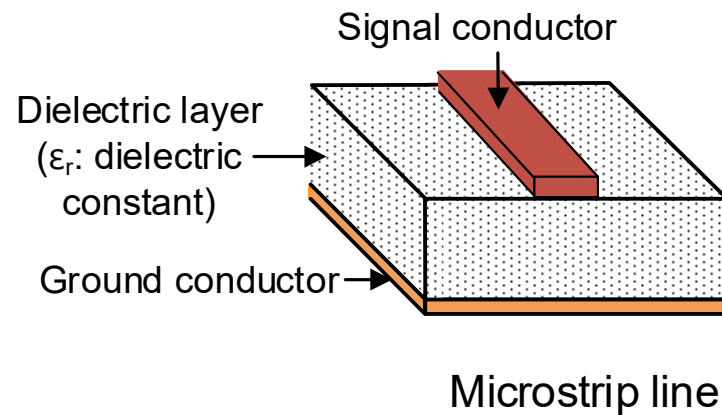
# 1 Single and Coupled Transmission Lines

- Single transmission lines
  - Consists of a pair of conductor (single signal conductor and ground conductor) separated by dielectric layer


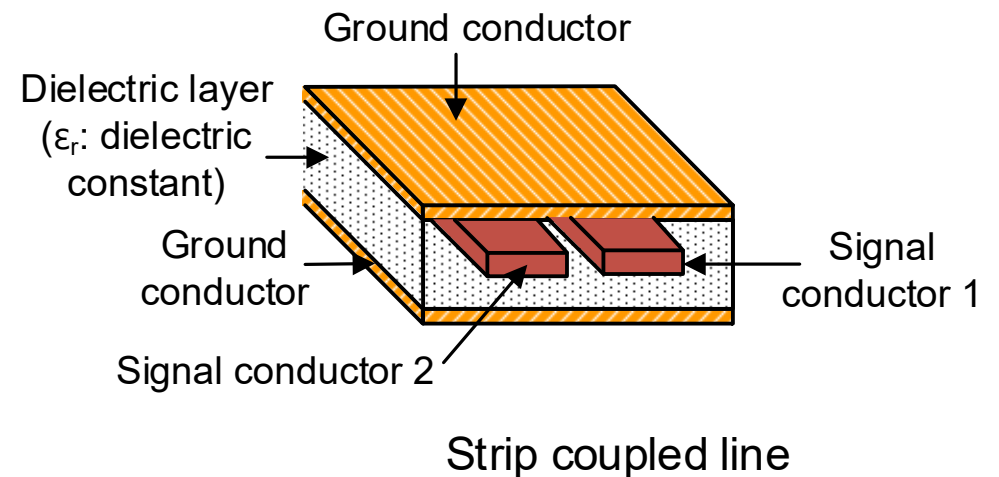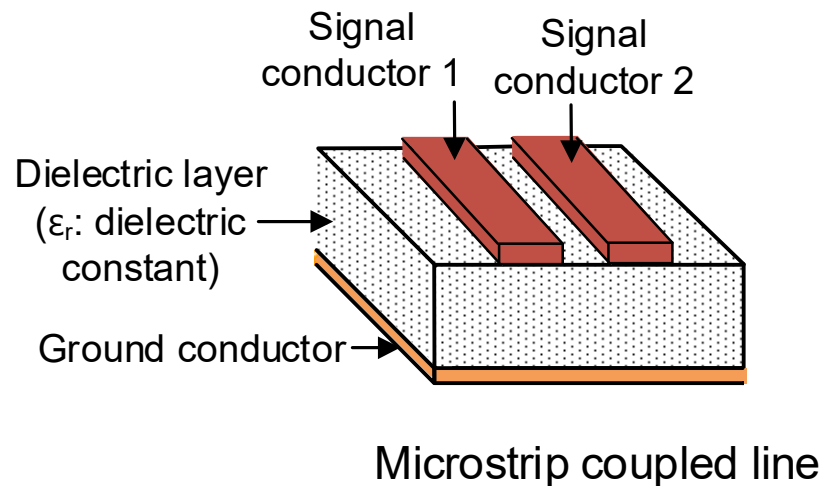
# 1 Single and Coupled Transmission Lines

- Coupled transmission lines
  - Two or more signal lines are placed closely together so that they interact with each other.
  - Power can be coupled between the lines due to the interaction of the electromagnetic fields of each line.
  - TEM mode operation: strip-coupled line ← homogeneous structure
  - Quasi-TEM mode operation: microstrip coupled lines ← inhomogeneous structure





## 2 Coupled Line Theory

### Introduction of coupled line theory

- TEM propagation: The electrical characteristics of the coupled lines can be completely determined from the effective capacitances between the lines and the velocity of propagation on the line.
- $C_{12}$ : capacitance between two strip conductors in absence of ground conductor
- $C_{11}$  and  $C_{22}$ : capacitances between one strip conductor and ground in absence of another strip conductor


- If two transmission lines are identical,

$$C_{11} = C_{22}$$

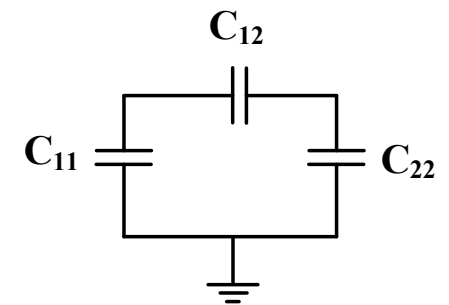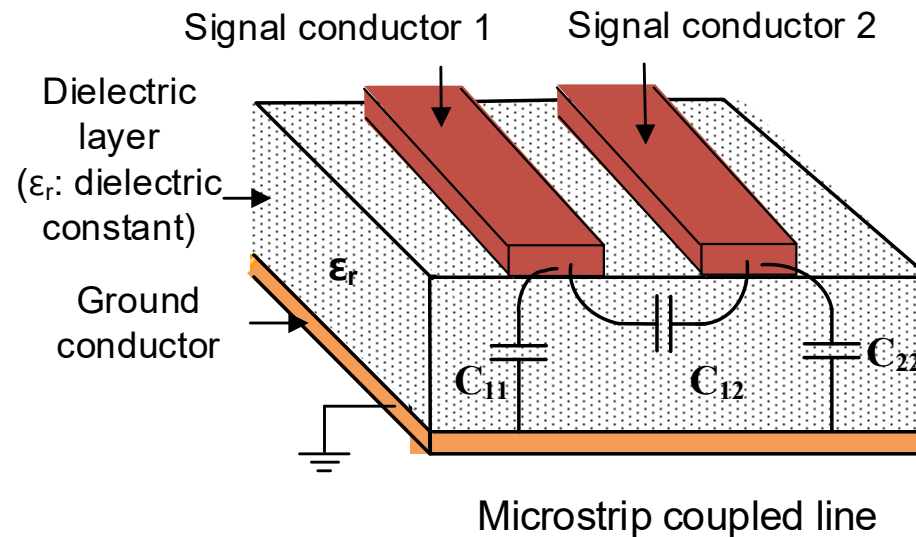
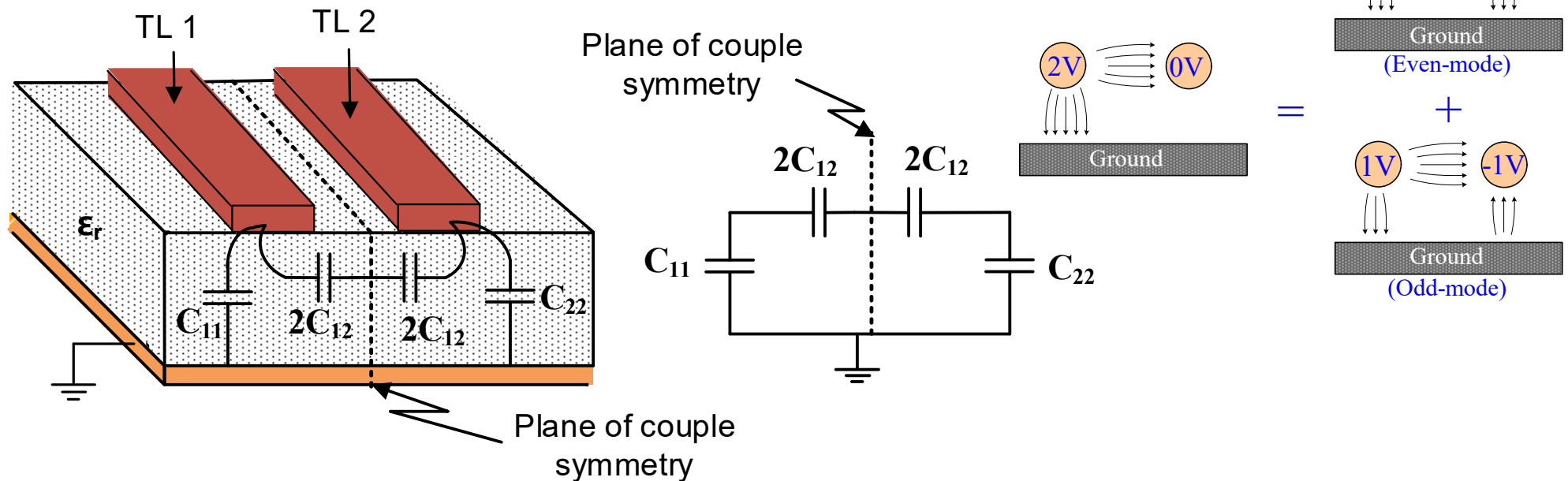
## 2 Coupled Line Theory

- Coupled line theory
  - If two transmission lines are identical, symmetric plane of circuit exists.
  - Even and odd-mode analysis can be used to find even- and odd-mode characteristic impedances of coupled line.



## 2 Coupled Line Theory

### ■ Even-mode characteristic impedance

- If two incident waves along two transmission lines are equal (*i.e.* equal in magnitude and phase), then virtual open plane is created at symmetric center plane of circuit.
- Under even-mode,  $2C_{12}$  capacitors are “*disconnected*”.


- Even-mode capacitance per unit length of each transmission line is given as

$$C_e = C_{11} = C_{22} \quad (1)$$

- Characteristic impedance for even mode

$$Z_{0e} = \sqrt{\frac{L}{C_e}} = \frac{\sqrt{LC_e}}{C_e} = \frac{1}{vC_e} \quad (2) \leftarrow v = \frac{1}{\sqrt{LC}}$$

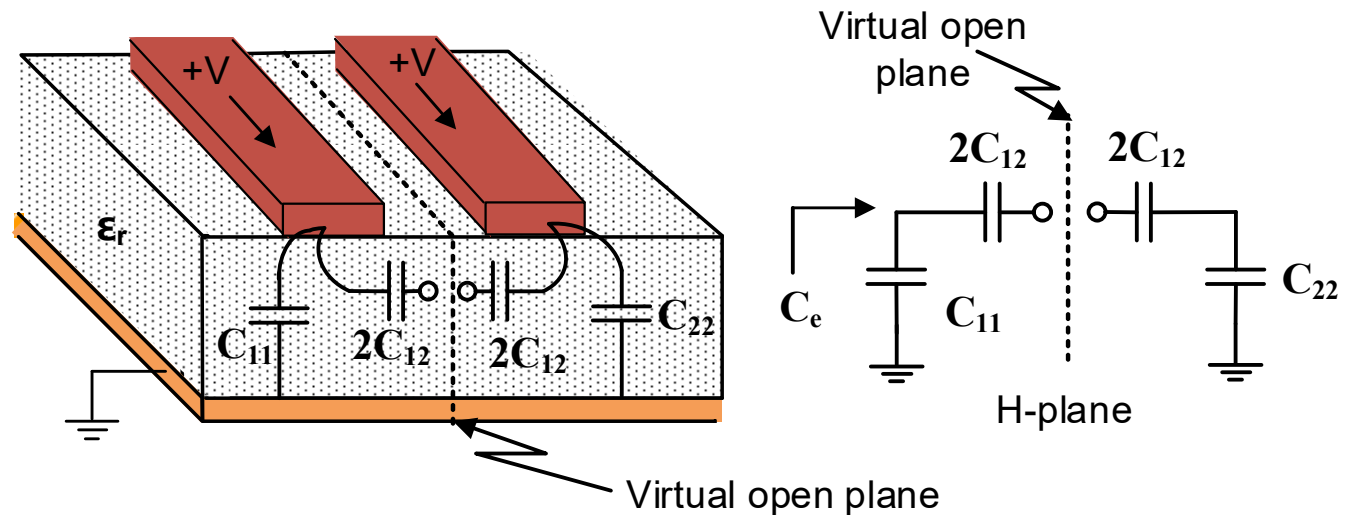$v$ : velocity of propagation on transmission line



## 2 Coupled Line Theory

### ▪ Odd-mode characteristic impedance


- If two incident waves along two transmission lines are opposite (*i.e.* equal in magnitude, but out-of-phased ( $180^\circ$ )), then virtual ground plane is created at symmetric center plane of circuit.
- Under odd-mode, a voltage null exists between the two strip conductors

- Odd-mode capacitance per unit length of each transmission line is given as

$$C_o = C_{11} + 2C_{12} = C_{22} + 2C_{12} \quad (3)$$

- Characteristic impedance for even mode


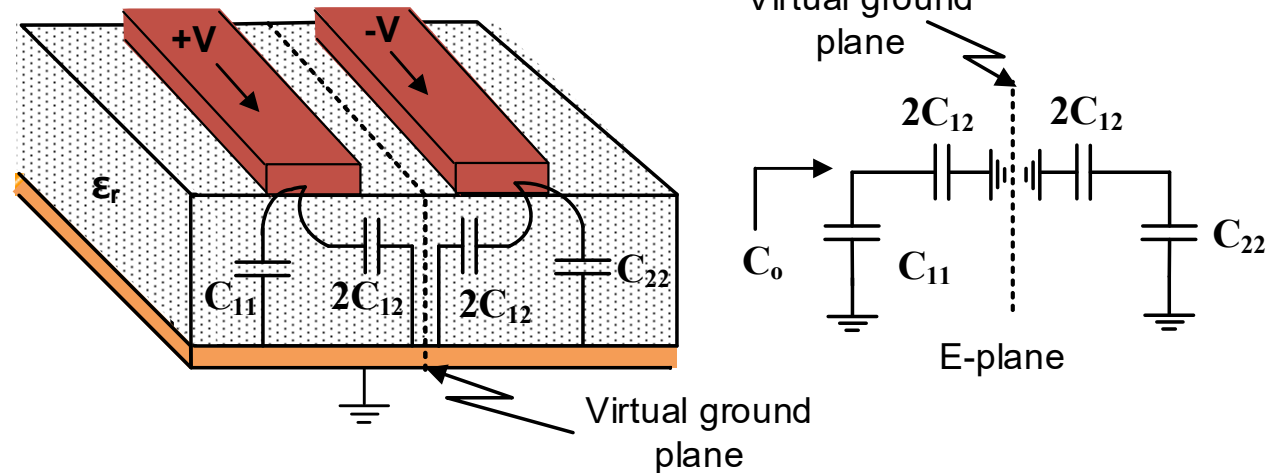
$$Z_{0o} = \sqrt{\frac{L}{C_o}} = \frac{\sqrt{LC_o}}{C_o} = \frac{1}{vC_o} \quad (4) \leftarrow v = \frac{1}{\sqrt{LC}}$$




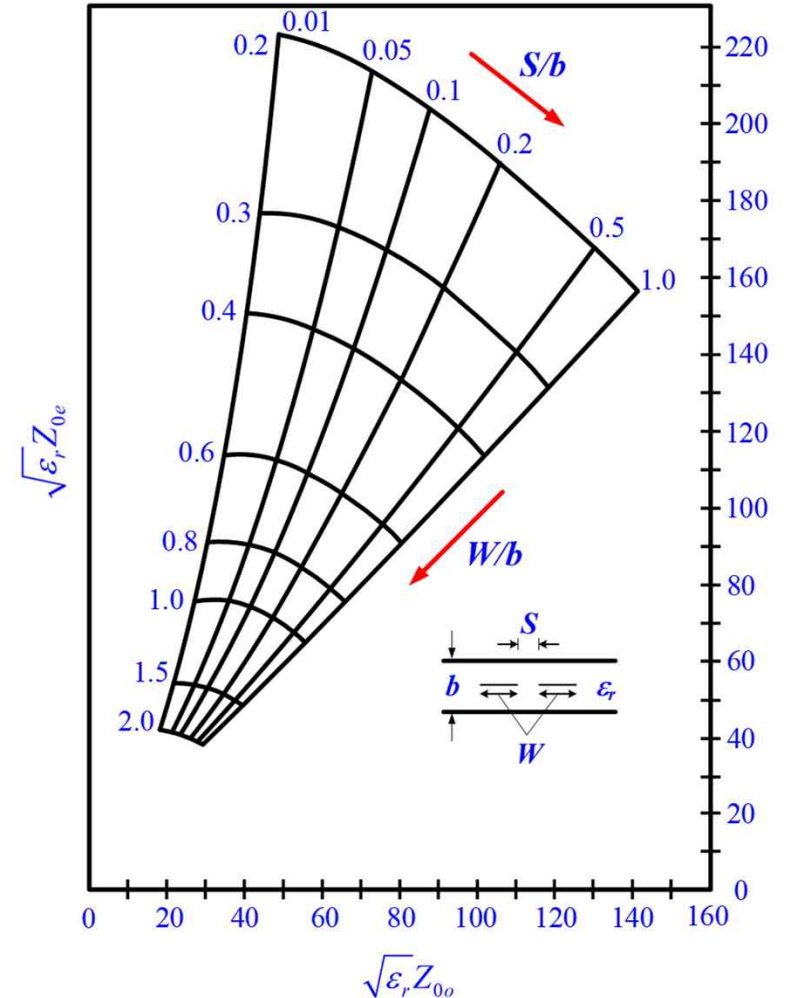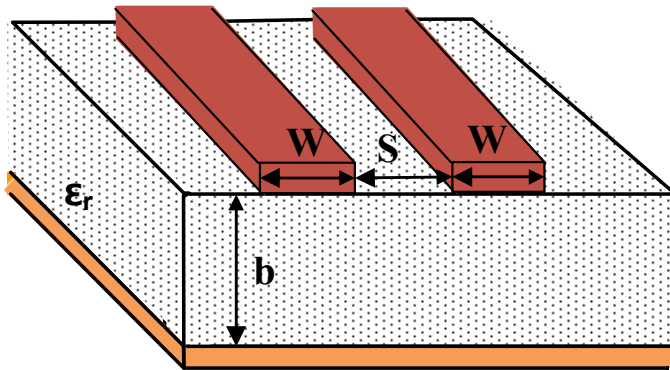
## 2 Coupled Line Theory

- Even- and odd-mode characteristic impedances of coupled line for given dielectric substrate
  - For quasi-TEM lines, characteristic impedances can be calculated numerically or by appropriate quasi-static technique
  - For symmetric coupled line, figure can be used to determine necessary strip line widths and spacing for given set of characteristics impedances → **Educational purpose**



\* *Modern microwave circuits or EM simulators contain physical structure evaluation programs.*

## 2 Coupled Line Theory

- Example: Even- and odd-mode characteristic impedances of coupled line for given dielectric substrate
  - Assuming  $W \gg S$  and  $W \gg b$  *for coupled strip line* so that fringing fields can be ignored and determine the even- and odd-mode characteristic impedances.

### Solution



- Since line is symmetric,  $C_{11} = C_{22}$
- Capacitance of a parallel plate capacitor with plate area,  $S$ , and plate separation  $d$

$$C = \frac{\epsilon S}{d}, \quad \epsilon : \text{permittivity of material between plates}$$

- Capacitance per unit length ( $\rightarrow S = W \times L = W$ )

$$C_{11} = \frac{\epsilon_r \epsilon_0 W}{(b-S)/2} + \frac{\epsilon_r \epsilon_0 W}{b - \frac{(b-S)}{2}} = \frac{\epsilon_r \epsilon_0 W}{(b-S)/2} + \frac{\epsilon_r \epsilon_0 W}{(b+S)/2} = \frac{4b\epsilon_r \epsilon_0 W}{b^2 - S^2} [\text{F/m}]$$

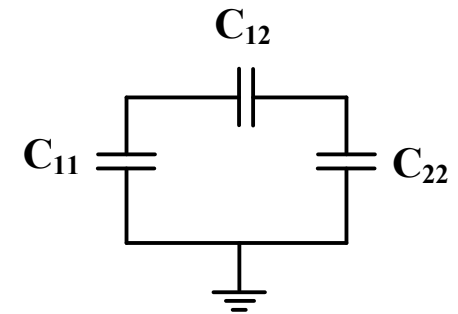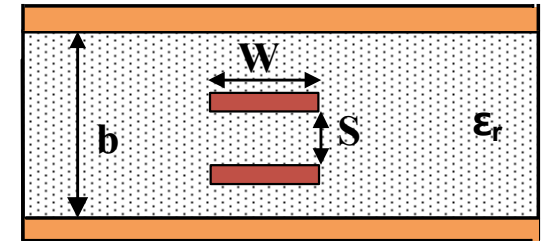Assumption:  $t$  (thickness of metal line)  $\rightarrow 0$



## 2 Coupled Line Theory

- Capacitance between coupled lines per unit length

$$C_{12} = \frac{\epsilon_r \epsilon_0 W}{S} [\text{F/m}]$$

- Even-mode capacitance per unit length

$$C_e = C_{11} = \frac{4b\epsilon_r\epsilon_0 W}{b^2 - S^2} [\text{F/m}]$$

- Odd-mode capacitance per unit length

$$\begin{aligned} C_o &= C_{11} + 2C_{12} \\ &= 2\epsilon_r\epsilon_0 W \left( \frac{2b}{b^2 - S^2} + \frac{1}{S} \right) [\text{F/m}] \end{aligned}$$

- Phase velocity on coupled lines



$$v = 1 / \sqrt{\epsilon_r \epsilon_0 \mu_0}$$

- Even-mode characteristic impedance

$$\begin{aligned} Z_{0e} &= \frac{1}{vC_e} = \sqrt{\epsilon_r \epsilon_0 \mu_0} \frac{b^2 - S^2}{4b\epsilon_r \epsilon_0 W} \\ &= \sqrt{\frac{\mu_0}{\epsilon_0}} \frac{b^2 - S^2}{4bW \sqrt{\epsilon_r}} = Z_0 \frac{b^2 - S^2}{4bW \sqrt{\epsilon_r}} \end{aligned}$$

- Odd-mode characteristic impedance
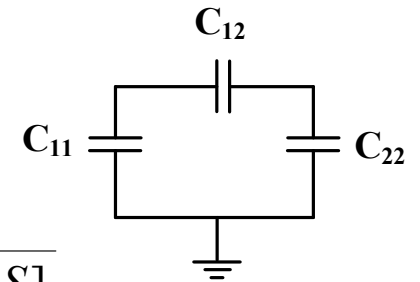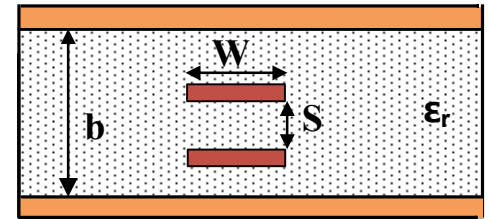
$$\begin{aligned} Z_{0o} &= \frac{1}{vC_o} = \frac{\sqrt{\epsilon_r \epsilon_0 \mu_0}}{2\epsilon_r \epsilon_0 W [2b / (b^2 - S^2) + 1 / S]} \\ &= \sqrt{\frac{\mu_0}{\epsilon_0}} \frac{1}{2W \sqrt{\epsilon_r} [2b / (b^2 - S^2) + 1 / S]} \\ &= \eta_0 \frac{1}{2W \sqrt{\epsilon_r} [2b / (b^2 - S^2) + 1 / S]} \end{aligned}$$



## 2 Coupled Line Theory

- Even- and odd-mode characteristic impedances calculation of microstrip coupled lines by using microwave circuit simulator

**Substrate information** →

**Physical dimensions of coupled transmission lines**

Parameter	Value	Unit
Er	2.200	N/A
Mur	1.000	N/A
H	0.787	mm
Hu	3.9e+34	mil
T	0.035	mm
Cond	4.1e7	N/A
TanD	9.000e-4	N/A
Rough	0.000	mil

Parameter	Value	Unit
W	0.800	mm
S	0.200	mm
L	28.000	mm

Parameter	Value	Unit
ZE	119.232000	Ohm
ZO	54.325100	Ohm
ZO	80.481600	Ohm
C_DB	-8.543030	N/A
E_Eff	87.601300	deg

**Calculated Results**

KE	1.847
KO	1.553
AE_DB	0.021
AO_DB	0.039
SkinDepth	0.001

**Even and odd-mode characteristic impedances**

### 3 Different Coupled Transmission Lines

- 4-port coupled lines impedance matrix (Z-parameters)

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} & Z_{14} \\ Z_{21} & Z_{22} & Z_{23} & Z_{24} \\ Z_{31} & Z_{32} & Z_{33} & Z_{34} \\ Z_{41} & Z_{42} & Z_{43} & Z_{44} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix}, \quad (5)$$


where

$$Z_{11} = Z_{22} = Z_{33} = Z_{44} = -j \frac{Z_{0e} + Z_{0o}}{2} \cot \theta$$

$$Z_{12} = Z_{21} = Z_{34} = Z_{43} = -j \frac{Z_{0e} - Z_{0o}}{2} \cot \theta$$

$$Z_{13} = Z_{31} = Z_{24} = Z_{42} = -j \frac{Z_{0e} - Z_{0o}}{2} \csc \theta$$
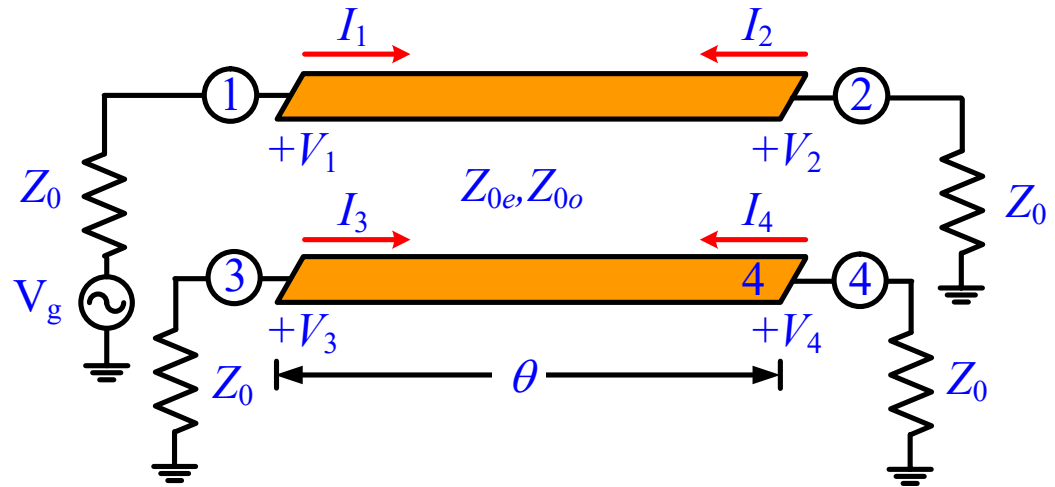
$$Z_{14} = Z_{41} = Z_{23} = Z_{32} = -j \frac{Z_{0e} + Z_{0o}}{2} \csc \theta$$




- $Z_{0e}$ : even-mode characteristic impedance
- $Z_{0o}$ : odd-mode characteristic impedance
- $\theta$ : electrical length of coupled line

### 3 Different Coupled Transmission Lines

- 2-port open-circuited coupled lines
  - Terminating ports 2 and 3 with open of 4-port coupled transmission line
  - Setting  $I_2 = I_3 = 0$  in (5), Z-parameters of two-port coupled line can be found as

$$\begin{bmatrix} Z'_{11} & Z'_{12} \\ Z'_{21} & Z'_{22} \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{24} \\ Z_{42} & Z_{44} \end{bmatrix}$$
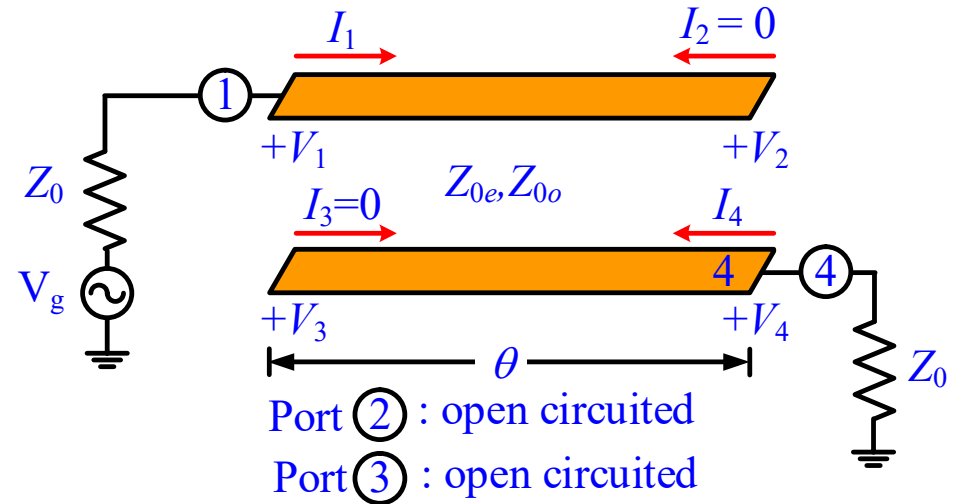
$$= \begin{bmatrix} -j \frac{Z_{0e} + Z_{0o}}{2} \cot \theta & -j \frac{Z_{0e} - Z_{0o}}{2} \csc \theta \\ -j \frac{Z_{0e} - Z_{0o}}{2} \csc \theta & -j \frac{Z_{0e} + Z_{0o}}{2} \cot \theta \end{bmatrix} = -j Z_{0o} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} + j \frac{Z_{0e} - Z_{0o}}{2} \begin{bmatrix} -\cot \theta & -\csc \theta \\ -\csc \theta & -\cot \theta \end{bmatrix}$$



*- Equivalent two open stubs with  $Z_{0o}$  are connected series with ports 1 and 4, and coupled transmission line  $(Z_{0e} - Z_{0o})/2$  with electrical length  $\theta$  is between open stubs.*

### 3 Different Coupled Transmission Lines

- 4-port coupled lines admittance matrix ( $Y$ -parameters)

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}, \quad (6)$$


where

$$Y_{11} = Y_{22} = Y_{33} = Y_{44} = -j \frac{Y_{0e} + Y_{0o}}{2} \cot \theta$$

$$Y_{12} = Y_{21} = Y_{34} = Y_{43} = -j \frac{Y_{0o} - Y_{0e}}{2} \cot \theta$$

$$Y_{13} = Y_{31} = Y_{24} = Y_{42} = -j \frac{Y_{0o} - Y_{0e}}{2} \csc \theta$$
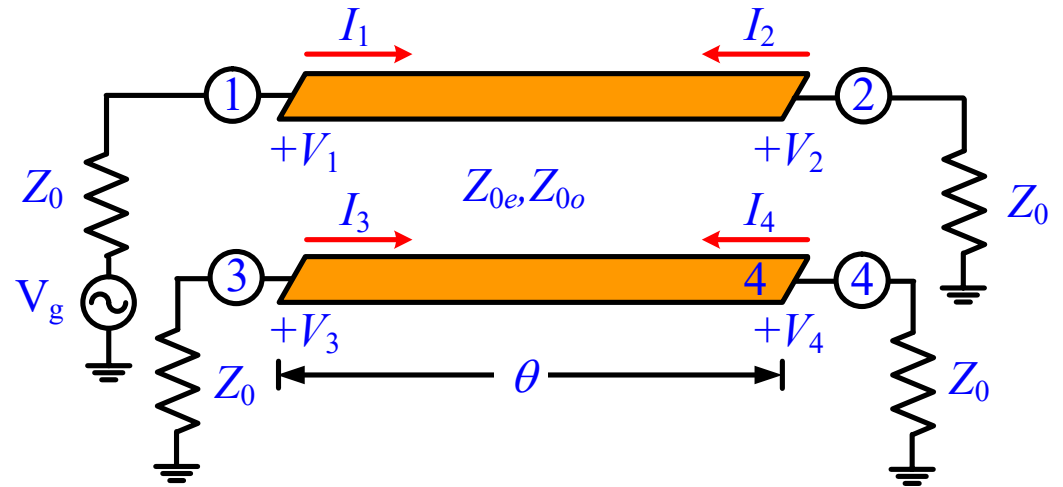
$$Y_{14} = Y_{41} = Y_{23} = Y_{32} = -j \frac{Y_{0e} + Y_{0o}}{2} \csc \theta$$



- $Y_{0e} = 1 / Z_{0e}$ : even-mode characteristic admittance
- $Y_{0o} = 1 / Z_{0o}$ : odd-mode characteristic admittance
- $\theta$ : electrical length of coupled line

### 3 Different Coupled Transmission Lines


- 2-port short-circuited coupled lines

- Terminating ports 2 and 3 with short of 4-port coupled transmission line
- Setting  $V_2 = V_3 = 0$  in (6), Y-parameters of two-port coupled line can be found as

$$\begin{bmatrix} Y'_{11} & Y'_{12} \\ Z'_{21} & Z'_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{24} \\ Y_{42} & Y_{44} \end{bmatrix}$$

$$= \begin{bmatrix} -j \frac{Y_{0e} + Y_{0o}}{2} \cot \theta & -j \frac{Y_{0o} - Y_{0e}}{2} \csc \theta \\ -j \frac{Y_{0o} - Y_{0e}}{2} \csc \theta & -j \frac{Y_{0e} + Y_{0o}}{2} \cot \theta \end{bmatrix} = -j Y_{0e} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} + j \frac{(Y_{0o} - Y_{0e})}{2} \begin{bmatrix} -\cot(\pi + \theta) & \csc(\pi + \theta) \\ \csc(\pi + \theta) & -\cot(\pi + \theta) \end{bmatrix}$$

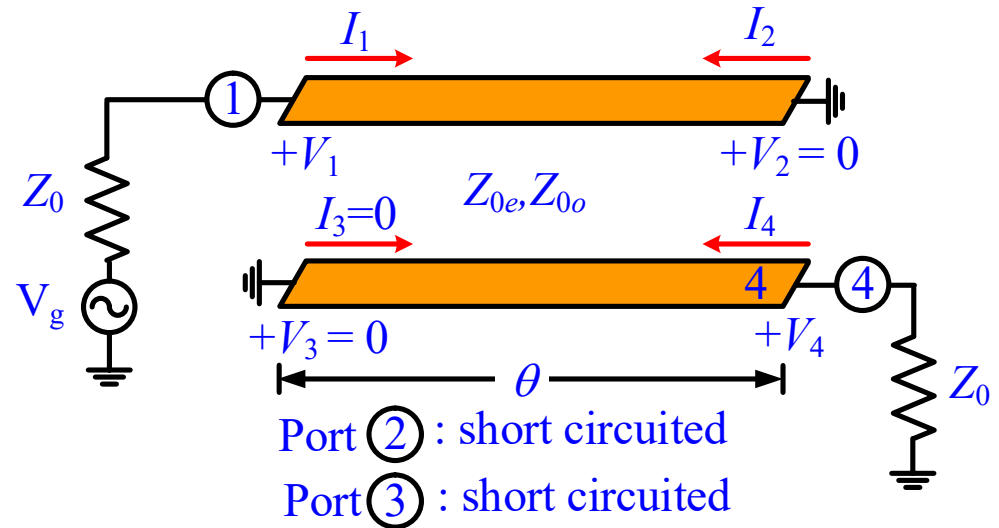
*- Equivalent two short stubs with characteristic admittance of  $Y_{0e}$  are connected in parallel with ports 1 and 4, and that transmission line  $(Y_{0o} - Y_{0e})/2$  with electrical length of  $(\theta + \pi)$  is between short stubs.*




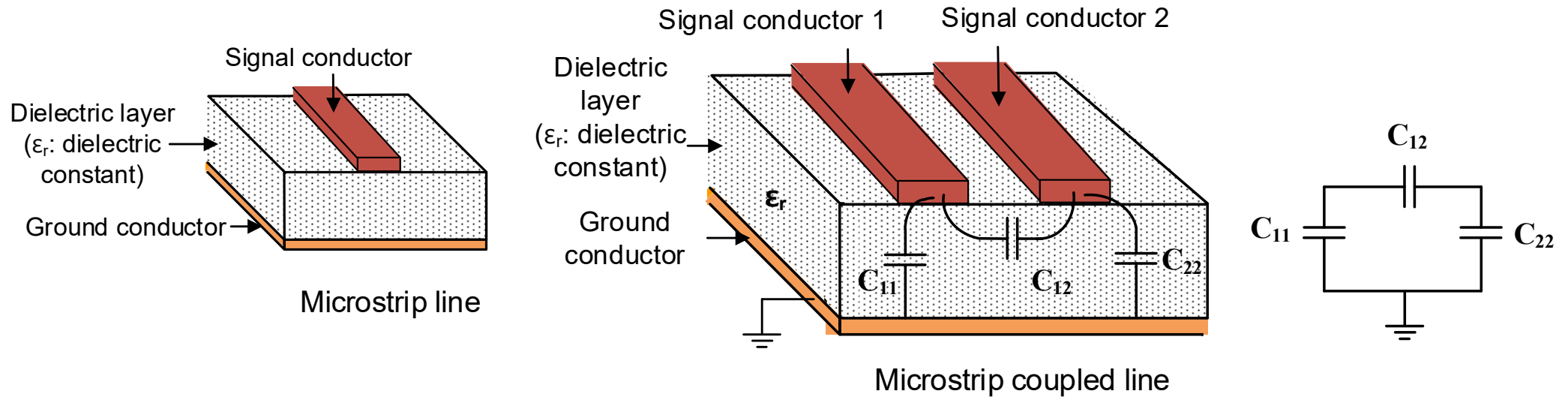
## 4 Review

- Single transmission line and coupled lines



- Coupled line theory
  - Even- and odd-mode characteristic impedances