
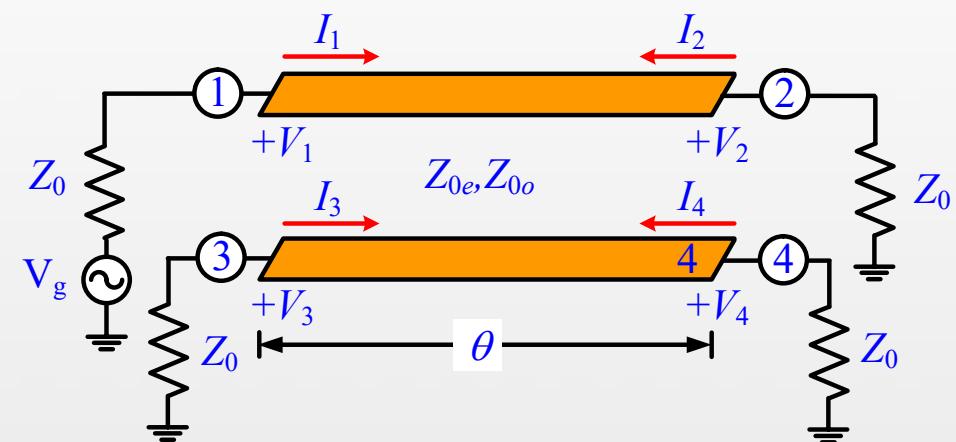


# Chapter 7

## Power Dividers and Couplers

Prof. Jeong, Yongchae

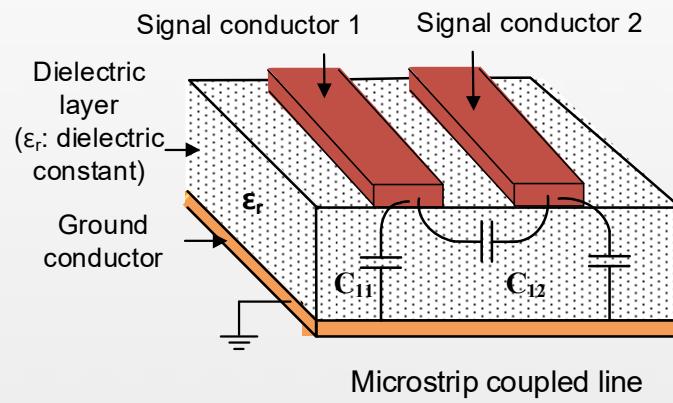

## Learning Objectives


- Learn what is coupled line directional coupler.
- Learn how to find design equations of directional coupler.

## Learning contents

- Brief Introduction of Directional Coupler
- Design Equations of Coupled Line Coupler
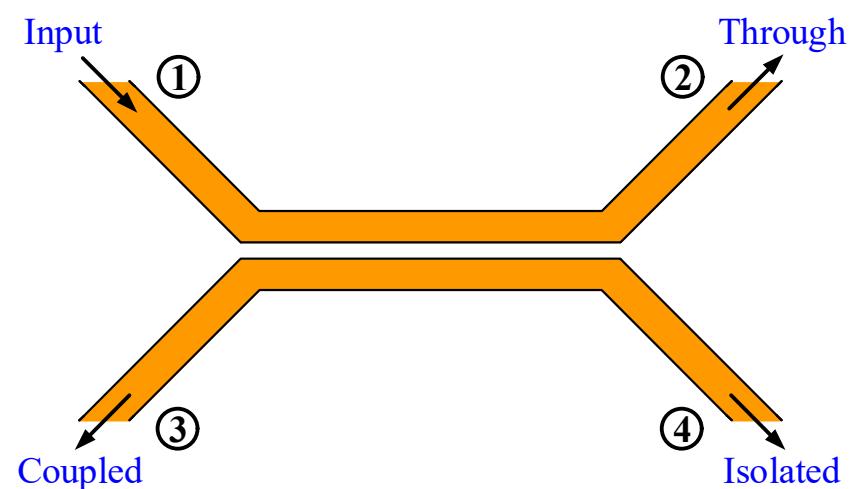
# Brief Introduction of Directional Coupler

- What is directional coupler?
  - One of fundamental components in microwave and RF engineering
  - Four-port passive circuit
  - **Input port (port 1):** signal entering port
  - **Through port (port 2):** signal exiting port with minimum insertion loss
  - **Coupled port (port 3):** A small fraction coupling port of input signal
  - **Isolated port (port 4):** Ideally, no signal appearing port




## 2
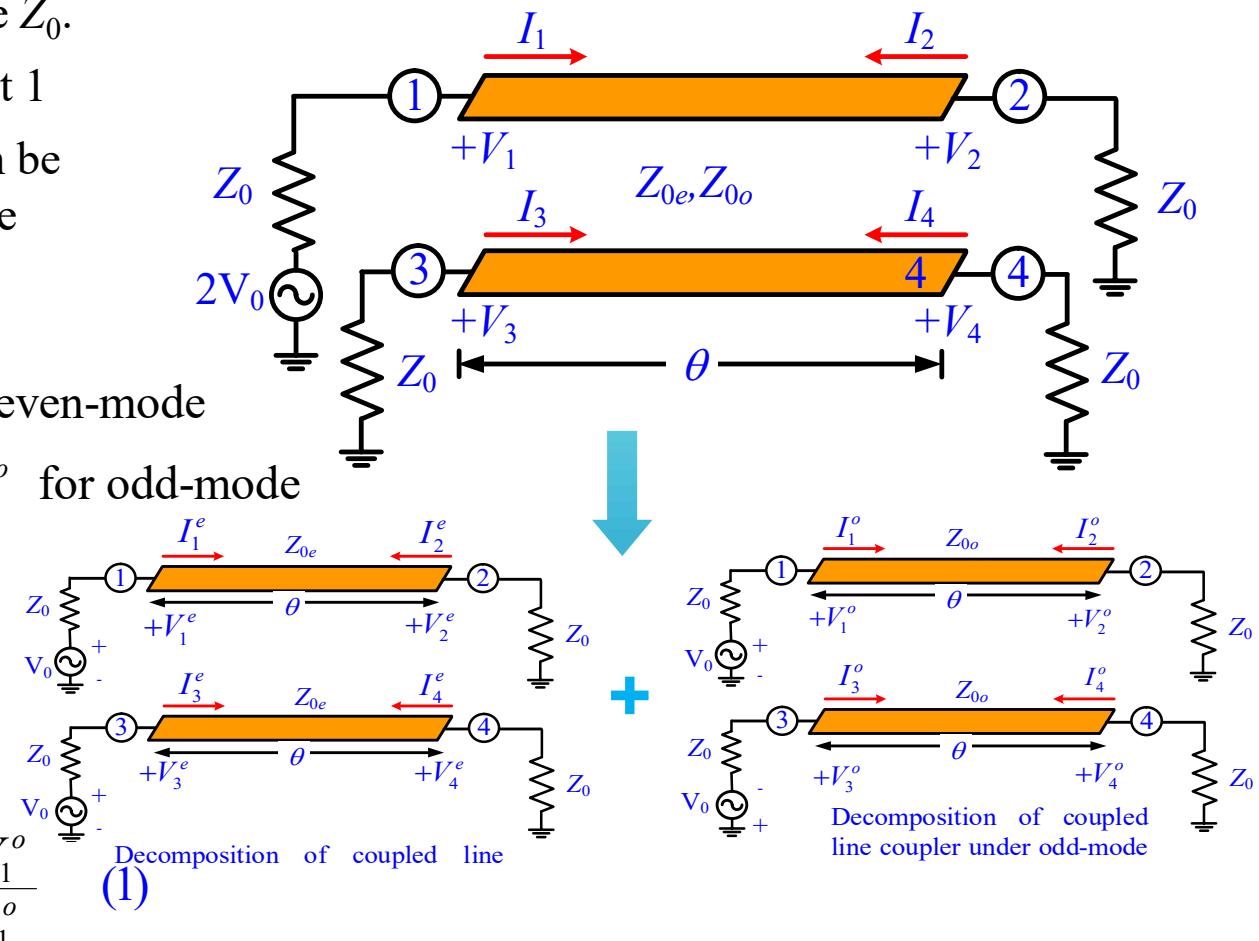
## Design Equations of Coupled Line Coupler

- 4-port coupled line coupler
- 4-port network is terminated with impedance  $Z_0$ .
- Driven with a voltage generator of 2V at port 1
- By superposition, the excitation at port 1 can be treated as the sum of the even- and odd-mode excitations.
- From symmetry
 
$$I_1^e = I_3^e, I_4^e = I_2^e, V_1^e = V_3^e, \text{ and } V_4^e = V_2^e \quad \text{for even-mode}$$

$$I_1^o = -I_3^o, I_4^o = -I_2^o, V_1^o = -V_3^o, \text{ and } V_4^o = -V_2^o \quad \text{for odd-mode}$$
- $P_{i,i=1,2,3,4} = f(V_1, I_1, V_2, I_2, V_3, I_3, V_4, I_4)$   
 $= g(V_1^e, V_1^o, I_1^e, I_1^o, V_2^e, V_2^o, I_2^e, I_2^o,$   
 $V_3^e, V_3^o, I_3^e, I_3^o, V_4^e, V_4^o, I_4^e, I_4^o)$   
 $= h(V_1^e, V_1^o, I_1^e, I_1^o, V_2^e, V_2^o, I_2^e, I_2^o)$
- Input impedance at port 1:  $Z_{in} = \frac{V_1}{I_1} = \frac{V_1^e + V_1^o}{I_1^e + I_1^o}$



## Design Equations of Coupled Line Coupler

- Even- and odd-mode input impedances

$Z_{\text{in}}^e$  : input impedance at port 1 for even-mode

$Z_{\text{in}}^o$  : input impedance at port 1 for odd-mode


- Input impedances for even and odd-modes

$$Z_{\text{in}}^e = Z_{0e} \frac{Z_0 + jZ_{0e} \tan \theta}{Z_{0e} + jZ_0 \tan \theta} \quad (2)$$

$$Z_{\text{in}}^o = Z_{0o} \frac{Z_0 + jZ_{0o} \tan \theta}{Z_{0o} + jZ_0 \tan \theta} \quad (3)$$

- By voltage division for even-mode
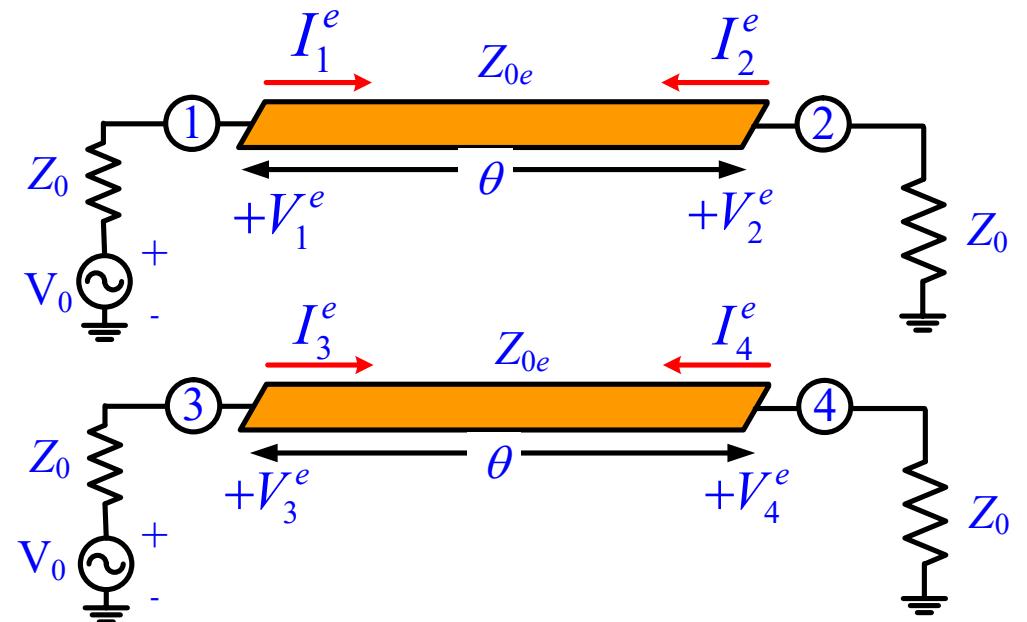
$$V_1^e = V_0 \frac{Z_{\text{in}}^e}{Z_{\text{in}}^e + Z_0} \quad (4) \quad I_1^e = \frac{V_0}{Z_{\text{in}}^e + Z_0} \quad (5)$$



Decomposition of coupled line coupler under even-mode excitation

## Design Equations of Coupled Line Coupler

- By voltage division for odd-mode


$$V_1^o = V_0 \frac{Z_{in}^o}{Z_{in}^o + Z_0} \quad (6)$$

$$I_1^o = \frac{V_0}{Z_{in}^o + Z_0} \quad (7)$$

- Input impedance using (1)

$$Z_{in} = \frac{V_1^e + V_1^o}{I_1^e + I_1^o} = \frac{V_0 \frac{Z_{in}^e}{Z_{in}^e + Z_0} + V_0 \frac{Z_{in}^o}{Z_{in}^o + Z_0}}{\frac{V_0}{Z_{in}^e + Z_0} + \frac{V_0}{Z_{in}^o + Z_0}}$$
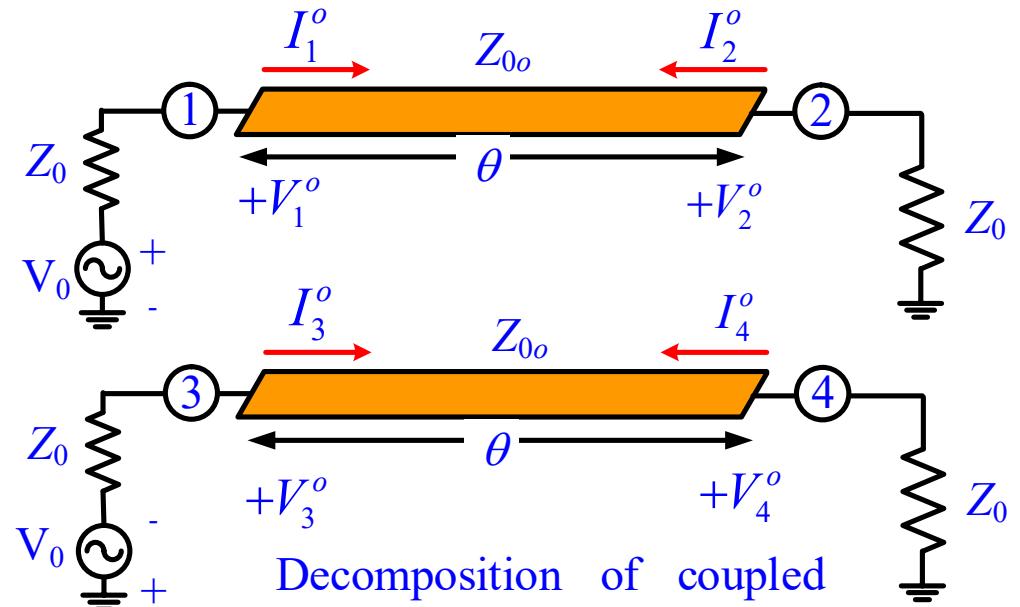
$$= \frac{Z_{in}^e (Z_{in}^o + Z_0) + Z_{in}^o (Z_{in}^e + Z_0)}{Z_{in}^e + Z_{in}^o + 2Z_0} = \frac{2Z_{in}^e Z_{in}^o + Z_0 (Z_{in}^e + Z_{in}^o) + 2Z_0^2 - 2Z_0^2}{Z_{in}^e + Z_{in}^o + 2Z_0} = Z_0 + \frac{2(Z_{in}^o Z_{in}^e - Z_0^2)}{Z_{in}^e + Z_{in}^o + 2Z_0} \quad (8)$$



Decomposition of coupled line coupler under odd-mode excitation

## Design Equations of Coupled Line Coupler

- If let  $Z_0 = \sqrt{Z_{0e}Z_{0o}}$  (9)

- Equations (2) and (3) are reduced as

$$Z_{\text{in}}^e = Z_{0e} \frac{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta}{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta}, \quad Z_{\text{in}}^o = Z_{0o} \frac{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta}{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta}$$

$$Z_{\text{in}}^e = Z_{0e} \frac{Z_0 + jZ_{0e} \tan \theta}{Z_{0e} + jZ_0 \tan \theta} \quad (2)$$

$$Z_{\text{in}}^o = Z_{0o} \frac{Z_0 + jZ_{0o} \tan \theta}{Z_{0o} + jZ_0 \tan \theta} \quad (3)$$

- Then

$$Z_{\text{in}}^e Z_{\text{in}}^o = Z_{0e} \frac{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta}{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta} \times Z_{0o} \frac{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta}{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta} = Z_{0e} Z_{0o} = Z_0^2$$

$$\rightarrow Z_{\text{in}} = Z_0 + \underbrace{\frac{2(Z_{\text{in}}^e Z_{\text{in}}^o - Z_0^2)}{Z_{\text{in}}^e + Z_{\text{in}}^o + 2Z_0}}_{\text{Equation (8)}} = Z_0 + \frac{2(Z_0^2 - Z_0^2)}{Z_{\text{in}}^e + Z_{\text{in}}^o + 2Z_0}$$

$$\rightarrow Z_{\text{in}} = Z_0 \quad (10)$$

❖ As long as equation (10) is satisfied, port 1 (by symmetry, all other ports) will be matched.

## Design Equations of Coupled Line Coupler

- If  $Z_0 = \sqrt{Z_{0e}Z_{0o}}$  is satisfied, so that we have  $V_1 = V_0$ , voltage at port 3 can be written as

$$V_3 = V_3^e + V_3^o = V_1^e - V_1^o = V_0 \left[ \frac{Z_{\text{in}}^e}{Z_{\text{in}}^e + Z_0} - \frac{Z_{\text{in}}^o}{Z_{\text{in}}^o + Z_0} \right] \quad (11)$$

- From (2) and (3),

$$\begin{aligned} \frac{Z_{\text{in}}^e}{Z_{\text{in}}^e + Z_0} &= \underbrace{\frac{Z_{0e} \frac{Z_0 + jZ_{0e} \tan \theta}{Z_{0e} + jZ_0 \tan \theta}}{Z_{0e} \frac{Z_0 + jZ_{0e} \tan \theta}{Z_{0e} + jZ_0 \tan \theta} + Z_0}}_{\text{Equation (2)}} = \frac{Z_{0e}(Z_0 + jZ_{0e} \tan \theta)}{2Z_{0e}Z_0 + j(Z_{0e}^2 + Z_0^2)\tan \theta} = \frac{Z_0 + jZ_{0e} \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o})\tan \theta} \\ \frac{Z_{\text{in}}^o}{Z_{\text{in}}^o + Z_0} &= \underbrace{\frac{Z_{0o} \frac{Z_0 + jZ_{0o} \tan \theta}{Z_{0o} + jZ_0 \tan \theta}}{Z_{0o} \frac{Z_0 + jZ_{0o} \tan \theta}{Z_{0o} + jZ_0 \tan \theta} + Z_0}}_{\text{Equation (3)}} = \frac{Z_{0o}(Z_0 + jZ_{0o} \tan \theta)}{2Z_{0o}Z_0 + j(Z_{0o}^2 + Z_0^2)\tan \theta} = \frac{Z_0 + jZ_{0o} \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o})\tan \theta} \end{aligned}$$

## Design Equations of Coupled Line Coupler

- Equation (11) reduces

$$\begin{aligned}
 V_3 &= V_0 \left\{ \frac{Z_{in}^e}{Z_{in}^e + Z_0} - \frac{Z_{in}^o}{Z_{in}^o + Z_0} \right\} = V_0 \left\{ \frac{Z_0 + jZ_{0e} \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta} - \frac{Z_0 + jZ_{0o} \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta} \right\} \\
 &= V_0 \frac{j(Z_{0e} - Z_{0o}) \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta} \quad (12)
 \end{aligned}$$

- Coupling coefficient:  $C = \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}}$  (13)

- From (13), even and odd-mode characteristic impedances can be derived as

$$Z_{0e} = \frac{Z_{0o}(1+C)}{1-C} = \frac{Z_0^2(1+C)}{Z_{0e}(1-C)} \rightarrow Z_{0e} = Z_0 \sqrt{\frac{1+C}{1-C}}, \quad Z_{0o} = \frac{Z_{0e}(1-C)}{1+C} = \frac{Z_0^2(1-C)}{Z_{0o}(1+C)} \rightarrow Z_{0o} = Z_0 \sqrt{\frac{1-C}{1+C}}$$

- From (13) with  $Z_0^2 = Z_{0e}Z_{0o}$ ,

$$\sqrt{1-C^2} = \sqrt{1 - \left( \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}} \right)^2} = \sqrt{\frac{(Z_{0e} + Z_{0o})^2 - (Z_{0e} - Z_{0o})^2}{(Z_{0e} + Z_{0o})^2}} = \sqrt{\frac{4Z_{0e}Z_{0o}}{(Z_{0e} + Z_{0o})^2}} = \sqrt{\frac{4Z_0^2}{(Z_{0e} + Z_{0o})^2}} = \frac{2Z_0}{Z_{0e} + Z_{0o}}$$

## Design Equations of Coupled Line Coupler

- From (12)



$$V_3 = V_0 \frac{j(Z_{0e} - Z_{0o}) \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta} = V_0 \frac{j(Z_{0e} - Z_{0o})(Z_{0e} + Z_{0o}) \tan \theta}{2Z_0 (Z_{0e} + Z_{0o}) + j \tan \theta} = V_0 \frac{jC \tan \theta}{\sqrt{-C^2} + j \tan \theta} \quad (14)$$

- Design equations of coupled line coupler (*another trial*)

$$\begin{bmatrix} V_1^e \\ I_1^e \end{bmatrix} = \begin{bmatrix} \cos \theta & jZ_{0e} \sin \theta \\ jY_{0e} \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_2^e \\ I_2^e \end{bmatrix} \quad (15a)$$

$$\begin{bmatrix} V_1^o \\ I_1^o \end{bmatrix} = \begin{bmatrix} \cos \theta & jZ_{0o} \sin \theta \\ jY_{0o} \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_2^o \\ I_2^o \end{bmatrix} \quad (15b)$$
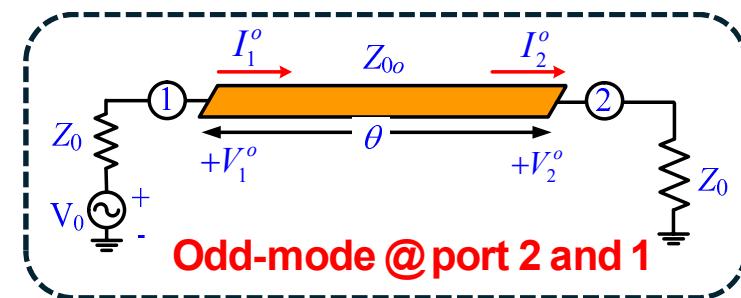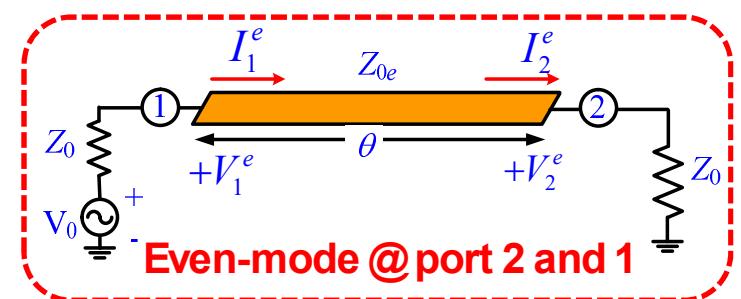
$$\begin{cases} V_2^e = Z_0 I_2^e \\ V_2^o = Z_0 I_2^o \\ V_1^e + Z_0 I_1^e = V_0 \\ V_1^o + Z_0 I_1^o = V_0 \end{cases}$$



- From (15a)

$$\begin{aligned} I_1^e &= jY_{0e} \sin \theta \times V_2^e + \cos \theta \times I_2^e = jY_{0e} \sin \theta \times Z_0 I_2^e + \cos \theta \times I_2^e \\ &= (\cos \theta + jZ_0 Y_{0e} \sin \theta) I_2^e \rightarrow I_2^e = \frac{I_1^e}{(\cos \theta + jZ_0 Y_{0e} \sin \theta)} \end{aligned} \quad (16)$$

## Design Equations of Coupled Line Coupler

$$V_1^e = \cos\theta \times V_2^e + jZ_{0e} \sin\theta \times I_2^e = \cos\theta \times Z_0 I_2^e + jZ_{0e} \sin\theta \times I_2^e \quad \leftarrow V_2^e = Z_0 I_2^e$$

$$\begin{aligned} &= (Z_0 \cos\theta + jZ_{0e} \sin\theta) I_2^e = \frac{Z_0 \cos\theta + jZ_{0e} \sin\theta}{\cos\theta + jZ_0 Y_{0e} \sin\theta} I_1^e = \frac{Z_0 \cos\theta + jZ_{0e} \sin\theta}{\cos\theta + j(Z_0 \sin\theta / Z_{0e})} I_1^e \\ &= \frac{Z_0 Z_{0e} \cos\theta + jZ_{0e}^2 \sin\theta}{Z_{0e} \cos\theta + jZ_0 \sin\theta} I_1^e \rightarrow I_1^e = V_1^e \frac{Z_{0e} \cos\theta + jZ_0 \sin\theta}{Z_0 Z_{0e} \cos\theta + jZ_{0e}^2 \sin\theta} \end{aligned}$$

$$\begin{bmatrix} V_1^e \\ I_1^e \end{bmatrix} = \begin{bmatrix} \cos\theta & jZ_{0e} \sin\theta \\ jY_{0e} \sin\theta & \cos\theta \end{bmatrix} \begin{bmatrix} V_2^e \\ I_2^e \end{bmatrix}$$

$$\begin{bmatrix} V_1^o \\ I_1^o \end{bmatrix} = \begin{bmatrix} \cos\theta & jZ_{0e} \sin\theta \\ jY_{0e} \sin\theta & \cos\theta \end{bmatrix} \begin{bmatrix} V_2^o \\ I_2^o \end{bmatrix}$$

- Even-mode voltage at port 1

$$V_1^e + Z_0 I_1^e = V_0$$

$$V_1^e \left( 1 + Z_0 \frac{I_1^e}{V_1^e} \right) = V_0$$

$$V_1^e \left( 1 + Z_0 \frac{Z_{0e} \cos\theta + jZ_0 \sin\theta}{Z_0 Z_{0e} \cos\theta + jZ_{0e}^2 \sin\theta} \right) = V_0$$



$$V_1^e \left( 1 + \frac{Z_0 Z_{0e} \cos\theta + jZ_0^2 \sin\theta}{Z_0 Z_{0e} \cos\theta + jZ_{0e}^2 \sin\theta} \right) = V_0$$

$$V_1^e \left\{ \frac{2Z_0 Z_{0e} \cos\theta + j(Z_0^2 + Z_{0e}^2) \sin\theta}{Z_0 Z_{0e} \cos\theta + jZ_{0e}^2 \sin\theta} \right\} = V_0$$

$$V_1^e = V_0 \frac{Z_0 Z_{0e} \cos\theta + jZ_{0e}^2 \sin\theta}{2Z_0 Z_{0e} \cos\theta + j(Z_0^2 + Z_{0e}^2) \sin\theta} \quad (17)$$

## 2

## Design Equations of Coupled Line Coupler

- Even-mode current at port 1

$$\begin{aligned} I_1^e &= \frac{Z_{0e} \cos \theta + j Z_0 \sin \theta}{Z_0 Z_{0e} \cos \theta + j Z_{0e}^2 \sin \theta} V_1^e \leftarrow V_1^e \text{ from (17)} \\ &= \frac{Z_{0e} \cos \theta + j Z_0 \sin \theta}{Z_0 Z_{0e} \cos \theta + j Z_{0e}^2 \sin \theta} \times V_0 \frac{Z_0 Z_{0e} \cos \theta + j Z_{0e}^2 \sin \theta}{2 Z_0 Z_{0e} \cos \theta + j(Z_0^2 + Z_{0e}^2) \sin \theta} = V_0 \frac{Z_{0e} \cos \theta + j Z_0 \sin \theta}{2 Z_0 Z_{0e} \cos \theta + j(Z_0^2 + Z_{0e}^2) \sin \theta} \end{aligned}$$

- Even-mode current at port 2

$$\begin{aligned} I_2^e &= \frac{I_1^e}{\cos \theta + j Z_0 Y_{0e} \sin \theta} = \frac{1}{Y_{0e} (Z_{0e} \cos \theta + j Z_0 \sin \theta)} V_0 \frac{Z_{0e} \cos \theta + j Z_0 \sin \theta}{2 Z_0 Z_{0e} \cos \theta + j(Z_0^2 + Z_{0e}^2) \sin \theta} \\ &= \frac{Z_{0e}}{2 Z_0 Z_{0e} \cos \theta + j(Z_0^2 + Z_{0e}^2) \sin \theta} V_0 \end{aligned}$$

- Even-mode voltage at port 2

$$\begin{aligned} V_2^e &= Z_0 I_2^e = \frac{Z_{0e} Z_0 I_1^e}{Z_{0e} \cos \theta + j Z_0 \sin \theta} \\ &= \frac{Z_{0e} Z_0}{Z_{0e} \cos \theta + j Z_0 \sin \theta} \times V_0 \frac{Z_{0e} \cos \theta + j Z_0 \sin \theta}{2 Z_0 Z_{0e} \cos \theta + j(Z_{0e}^2 + Z_0^2) \sin \theta} = V_0 \frac{Z_{0e} Z_0}{2 Z_0 Z_{0e} \cos \theta + j(Z_{0e}^2 + Z_0^2) \sin \theta} \end{aligned}$$

## Design Equations of Coupled Line Coupler

- Odd-mode voltage at ports 1 and 2 using (15b) as like even-mode

$$V_1^o = V_0 \frac{Z_0 Z_{0o} \cos \theta + j Z_{0o}^2 \sin \theta}{2 Z_0 Z_{0o} \cos \theta + j(Z_0^2 + Z_{0o}^2) \sin \theta}, \quad I_1^o = V_0 \frac{Z_{0o} \cos \theta + j Z_0 \sin \theta}{2 Z_0 Z_{0o} \cos \theta + j(Z_0^2 + Z_{0o}^2) \sin \theta}$$

$$V_2^o = Z_0 I_2^o = \frac{Z_0 Z_{0o}}{Z_{0o} \cos \theta + j Z_0 \sin \theta} I_1^o = V_0 \frac{Z_0 Z_{0o}}{Z_0 Z_{0o} \cos \theta + j(Z_0^2 + Z_{0o}^2) \sin \theta}$$

- Total voltage at port 2: combination of even and odd-mode excitations voltages

$$\begin{aligned} V_2 &= V_2^e + V_2^o = V_0 \left\{ \frac{Z_{0e} Z_0}{2 Z_0 Z_{0e} \cos \theta + j(Z_0^2 + Z_{0e}^2) \sin \theta} + \frac{Z_0 Z_{0o}}{Z_0 Z_{0o} \cos \theta + j(Z_0^2 + Z_{0o}^2) \sin \theta} \right\} \\ &= V_0 \left\{ \frac{Z_{0e} Z_0}{2 Z_0 Z_{0e} \cos \theta + j(Z_{0e} Z_{0o} + Z_{0e}^2) \sin \theta} + \frac{Z_0 Z_{0o}}{Z_0 Z_{0o} \cos \theta + j(Z_{0e} Z_{0o} + Z_{0o}^2) \sin \theta} \right\} \\ &= V_0 \left\{ \frac{Z_0}{2 Z_0 \cos \theta + j(Z_{0e} + Z_{0o}) \sin \theta} + \frac{Z_0}{Z_0 \cos \theta + j(Z_{0o} + Z_{0e}) \sin \theta} \right\} \\ &= V_0 \frac{2 Z_0}{2 Z_0 \cos \theta + j(Z_{0e} + Z_{0o}) \sin \theta} = V_0 \frac{2 Z_0 / (Z_{0e} + Z_{0o})}{2 Z_0 / (Z_{0e} + Z_{0o}) \cos \theta + j \sin \theta} = V_0 \frac{\sqrt{1 - C^2}}{\sqrt{1 - C^2} \cos \theta + j \sin \theta} \end{aligned} \quad (18)$$

## 2

## Design Equations of Coupled Line Coupler

- Similarly, total voltage at port 4 (isolation port)

$$V_4 = V_4^e + V_4^o = V_2^e - V_2^o = V_0 \left\{ \frac{Z_0}{Z_0 \cos \theta + j(Z_{0e} + Z_{0o}) \sin \theta} - \frac{Z_0}{Z_0 \cos \theta + j(Z_{0e} + Z_{0o}) \sin \theta} \right\} = 0 \quad (19)$$

- Voltages at ports 2, 3, and 4


$$V_3 = V_0 \frac{jC \tan \theta}{\sqrt{1-C^2} + j \tan \theta} \quad (14)$$

$$V_2 = V_0 \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta} \quad (18)$$

$$V_4 = 0 \quad (19)$$

- For  $\theta = \pi/2$ , equations (14) and (18) are
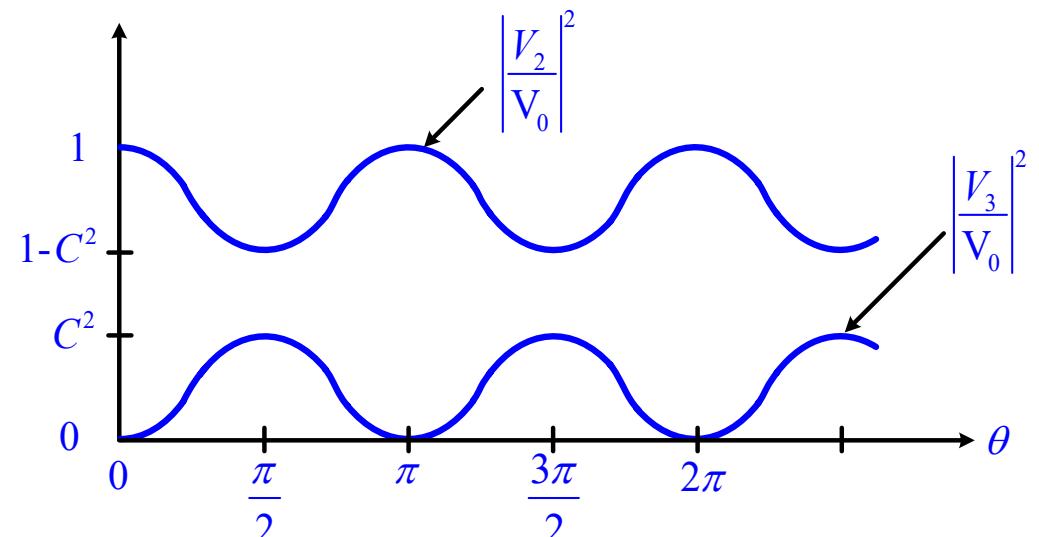
$$\frac{V_3}{V_0} = C, \quad \frac{V_2}{V_0} = -j\sqrt{1-C^2}$$



- Coupled line directional coupler
  - Input, through, coupled, and isolation ports
  - Coupling coefficient, directivity
- Design equations of coupled line coupler
  - Matched condition
  - Even and odd-mode excitations

