
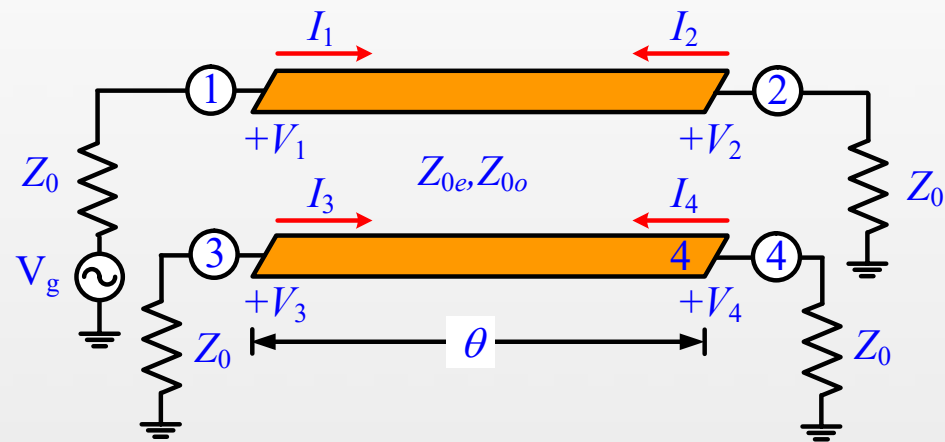


Chapter 7

Power Dividers and Couplers

Prof. Jeong, Yongchae

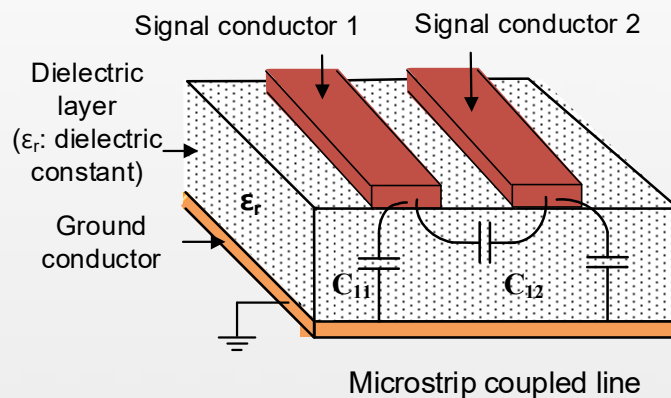

Learning Objectives

- Learn how to design and simulate coupled line coupler.
- Learn how to enhance bandwidth coupled line coupler with multi-section design.
- Learn how to design and obtain frequency response of multi-section coupled line coupler.

Learning contents

- Design Example of Single Section Coupled Line Coupler
- Multi-Section Coupled Line Coupler
- Design Example of Multi-Section Coupled Line Coupler

1

Design Example of Single-Section Coupled Line Coupler

- Design Example: 20 dB coupler
 - Design a 20 dB single-section coupled line coupler with characteristic impedance of 50Ω using PCB with a dielectric constant of 2.2 and thickness of 0.787 mm and a center frequency $f_0 = 3$ GHz.
 - Plot coupling and directivity from 1 to 5 GHz

Solution

- Voltage coupling factor C (dB) = 20 dB

$$C_{\text{dB}} = -20 \log_{10}(C)$$

$$\log_{10}(C) = -\frac{C_{\text{dB}}}{20}$$

$$C = 10^{\left(\frac{-C_{\text{dB}}}{20}\right)} = 10^{\left(\frac{-20}{20}\right)} = 0.1$$






- Even and odd-mode characteristic impedances

$$Z_{0e} = Z_0 \sqrt{\frac{1+C}{1-C}} = 50 \sqrt{\frac{1+0.1}{1-0.1}} = 50 \sqrt{\frac{1.1}{0.9}} = 55.28 \Omega$$

$$Z_{0o} = Z_0 \sqrt{\frac{1-C}{1+C}} = 50 \sqrt{\frac{1-0.1}{1+0.1}} = 50 \sqrt{\frac{0.9}{1.1}} = 45.23 \Omega$$

1 Design Example of Single-Section Coupled Line Coupler

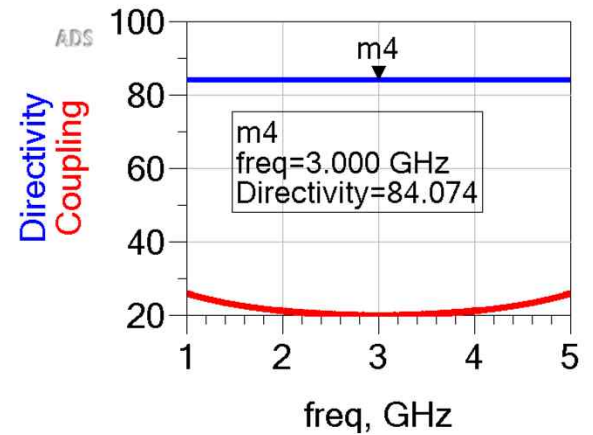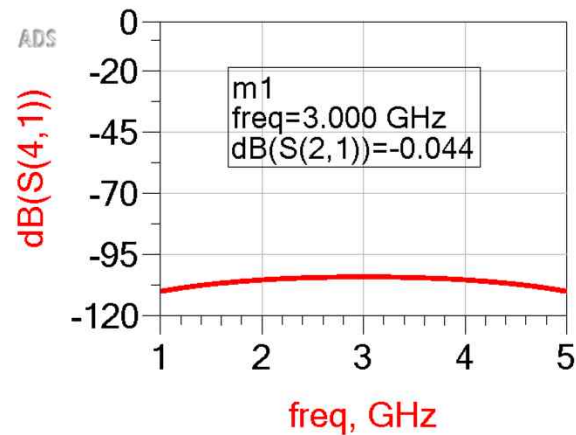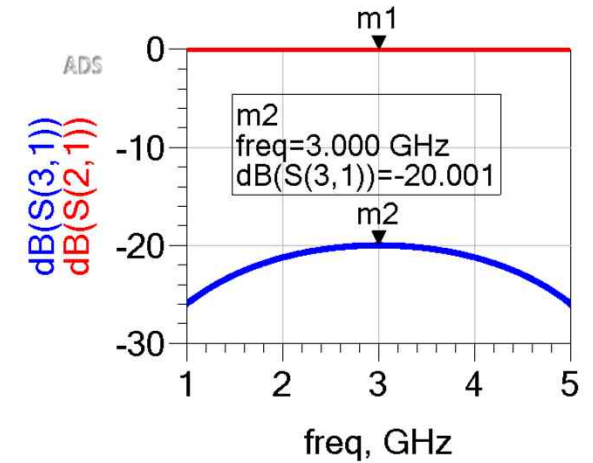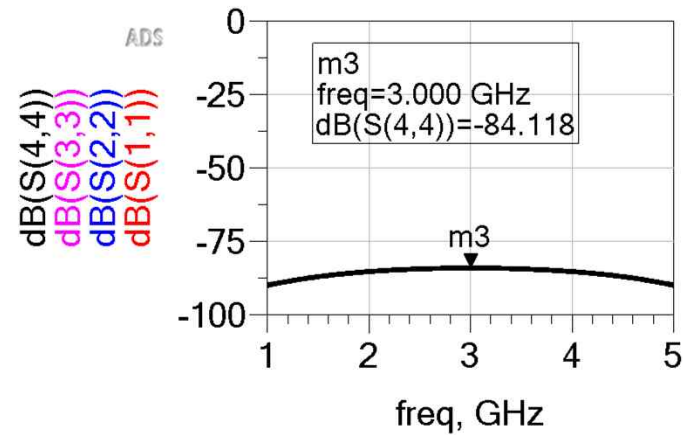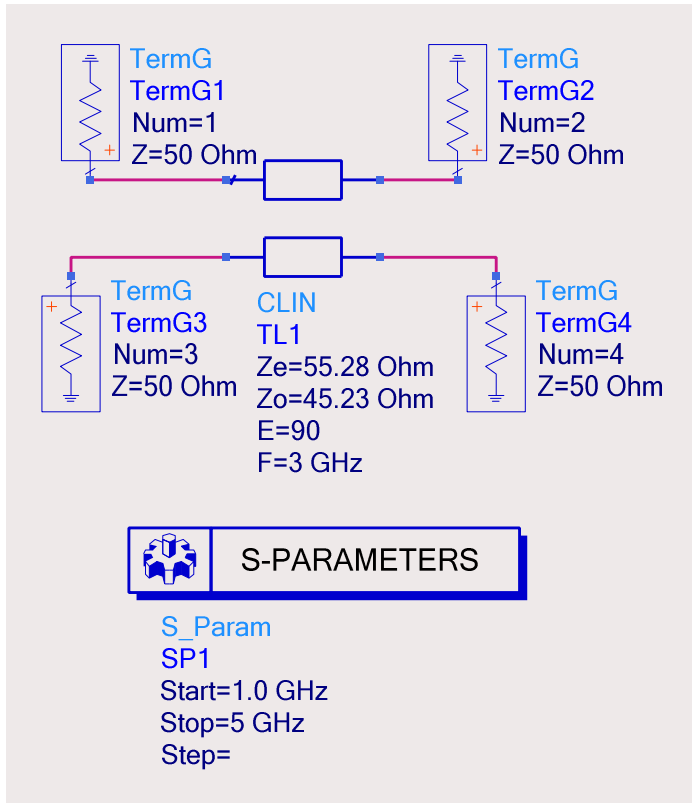- Simulation results with microwave circuit simulator: Ideal coupled line



1 Design Example of Single-Section Coupled Line Coupler

- Substrate dielectric constant $\epsilon_r = 2.20$, thickness $h = 0.787$ mm, and $f_0 = 3$ GHz
- Using microwave circuit simulator, $W = 2.34$ mm, $S = 1.03$ mm, and $L = 18.35$ mm

Substrate information →

Physical dimensions of coupled transmission lines

Substrate Parameters		
ID	MSUB_DEFAULT	
Er	2.200	N/A
Mur	1.000	N/A
H	0.787	mm
Hu	3.9e+34	mil
T	0.035	mm
Cond	4.1e7	N/A

Physical dimensions		
W	2.338040	mm
S	1.028800	mm
L	18.354200	mm

Electrical		
ZE	55.280	Ohm
ZO	45.230	Ohm
Z0	50.003144	Ohm
C_DB	-20.000864	N/A
E_Eff	90.000	deg







Calculated Results

- KE = 1.949
- KO = 1.758
- AE_DB = 0.066
- AO_DB = 0.059
- SkinDepth = 0.001

Even and odd-mode characteristic impedances

1 Design Example of Single-Section Coupled Line Coupler

- ADS layout and Simulation results

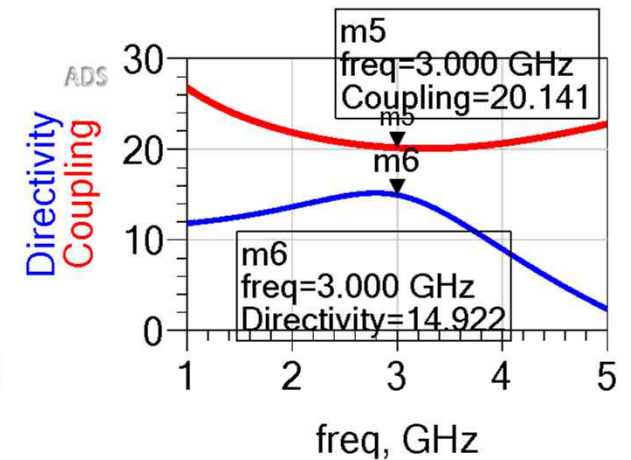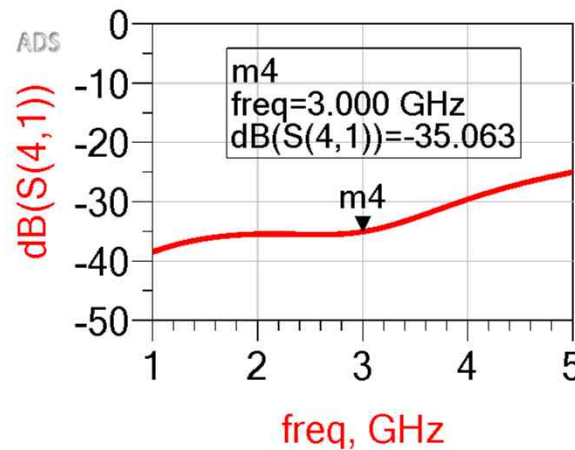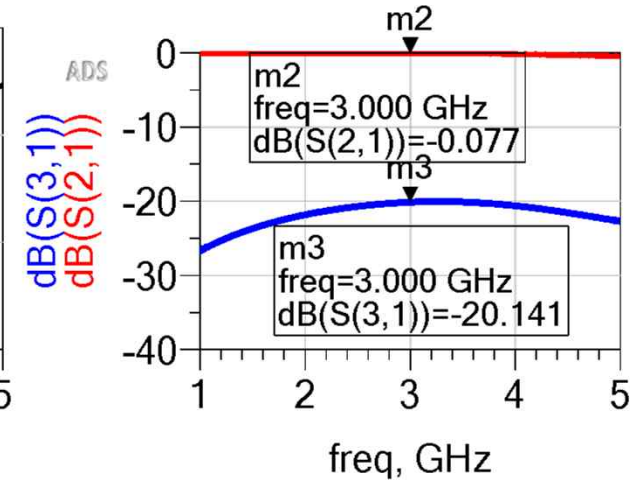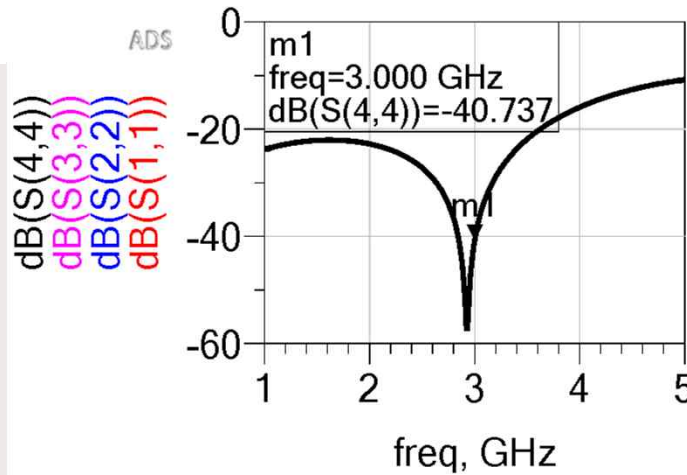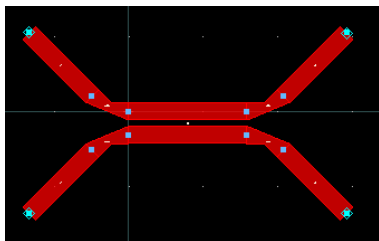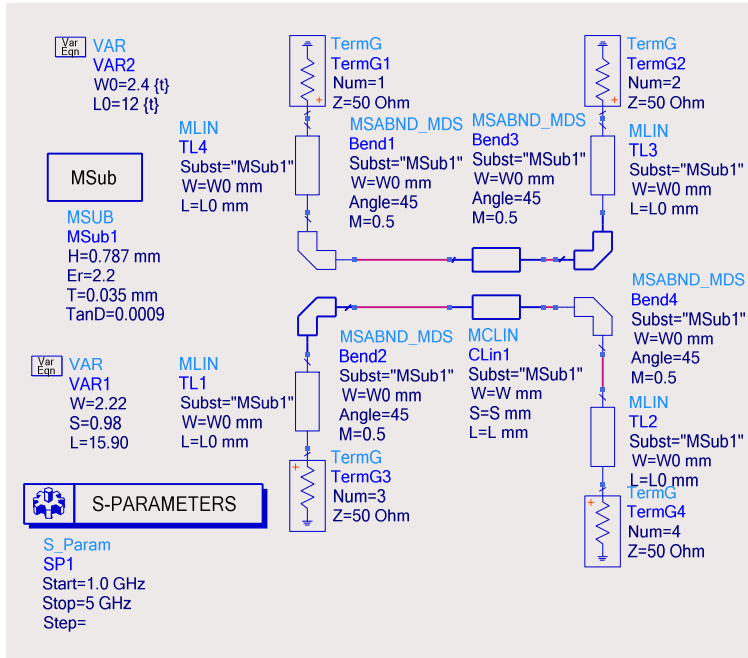


1 Design Example of Single-Section Coupled Line Coupler

- Single section coupled line coupler
 - Narrow frequency bandwidth characteristics
 - Coupling of single-section coupled line coupler is limited in bandwidth due to $\lambda/4$ length characteristics.
 - As like matching transformers and waveguide couplers, bandwidth can be increased by using multiple sections.
 - There is close relationship between multi-section coupled line couplers and multi-section quarter-wavelength transformers.
- Multi-section coupled line coupler
 - Consists of multi-section of single-coupled line coupler
 - Multi-section coupled line couplers can achieve broader bandwidth as compared to single section.
 - For multi-section coupler design, the coupling coefficient is weak ($C \geq 10$ dB)

2 Multi-Section Coupled Line Coupler

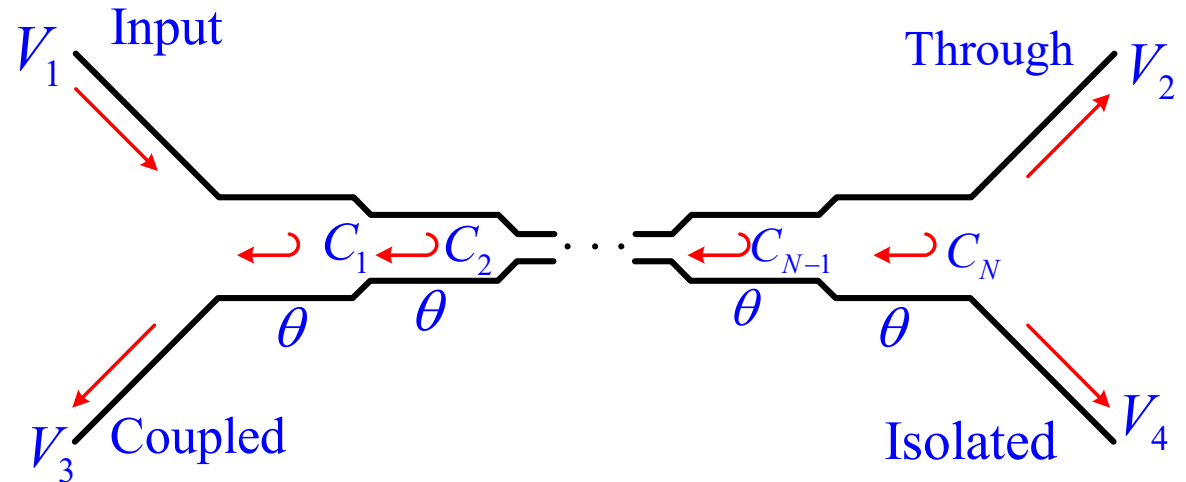- Multi-section coupled line coupler
 - Because the phase characteristics are usually better, multi-section coupled line couplers are generally made with **odd number of sections**.
 - Coupling is weak ($C \geq 10$ dB)
 - Each section is $\lambda/4$ long ($\theta = \pi/2$) at the center frequency.



- For a single-section coupled line

$$\frac{V_3}{V_1} = \frac{jC \tan \theta}{\sqrt{1-C^2} + j \tan \theta}$$

$$\frac{V_2}{V_1} = \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta}$$

- If $C \ll 1$, then design-equations of single-section coupled line can be simplified as

$$\frac{V_3}{V_1} = \frac{jC \tan \theta}{\sqrt{1-C^2} + j \tan \theta} \approx \frac{jC \tan \theta}{1 + j \tan \theta} = \frac{jC \sin \theta}{\cos \theta + j \sin \theta} = jC \sin \theta e^{-j\theta} \quad (1)$$


$$\frac{V_2}{V_1} = \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta} \approx \frac{1}{\cos \theta + j \sin \theta} = e^{-j\theta} \quad (2)$$

2 Multi-Section Coupled Line Coupler

- For $\theta = \pi/2$

$$\begin{aligned}\frac{V_3}{V_1} &= jC \sin\left(\frac{\pi}{2}\right) e^{-j\left(\frac{\pi}{2}\right)} = jC \times (-j) \\ &= -j^2 C = C\end{aligned}$$
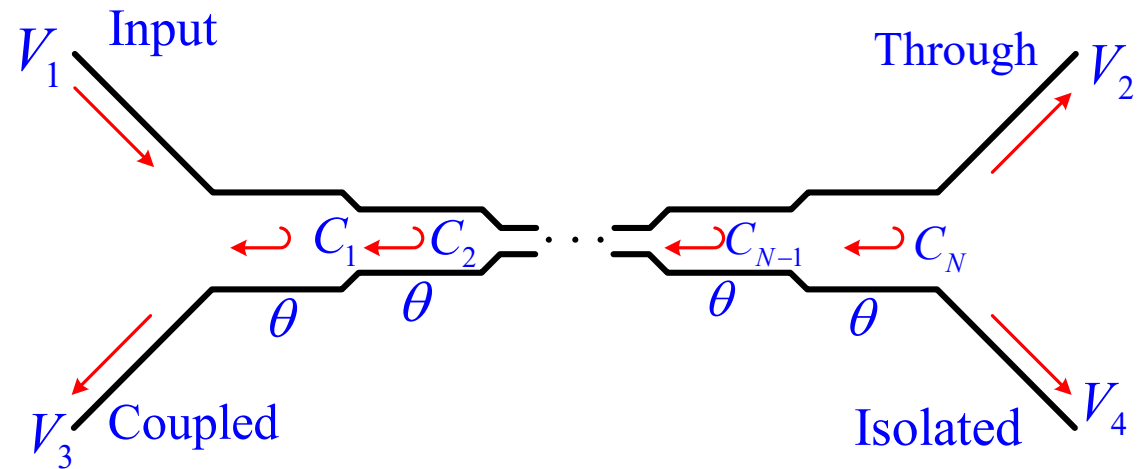
$$\begin{aligned}\frac{V_2}{V_1} &= e^{-j\left(\frac{\pi}{2}\right)} = \cos\left(\frac{\pi}{2}\right) - j \sin\left(\frac{\pi}{2}\right) = -j \\ \rightarrow \frac{V_2}{V_1} &= -j\end{aligned}$$



- No power is lost on the through path from one section to the next.
- *It is a good assumption for small C , even though power conservation law is violated.*

2 Multi-Section Coupled Line Coupler

- Total voltage at coupled port (port 3) of cascaded coupler

$$V_3 = \left\{ \begin{aligned} &(jC_1 \sin \theta e^{-j\theta})V_1 + (jC_2 \sin \theta e^{-j2\theta})V_1 e^{-j2\theta} \\ &+ \dots + (jC_N \sin \theta e^{-j\theta})V_1 e^{-j2(N-1)\theta} \end{aligned} \right\} \quad (3)$$

where C_n : voltage coupling coefficient of n^{th} section


- If we assume that the coupler is symmetric,

$$C_1 = C_N, C_2 = C_{N-1}, \dots$$

- Then equation (3) can be simplified as

$$\begin{aligned} V_3 &= jV_1 \sin \theta e^{-j\theta} \left\{ C_1 (1 + e^{-j2(N-1)\theta}) + C_2 (e^{-j2\theta} + e^{-j2(N-2)\theta}) + \dots + C_M e^{-j(N-1)\theta} \right\} \\ &= 2jV_1 \sin \theta e^{-jN\theta} \left\{ C_1 (e^{j(N-1)\theta} + e^{-j(N-1)\theta}) / 2 + C_2 (e^{j(N-3)\theta} + e^{-j(N-3)\theta}) / 2 + \dots + C_M / 2 \right\} \\ &= 2jV_1 \sin \theta e^{-jN\theta} \left\{ C_1 \cos(N-1)\theta + C_2 \cos(N-3)\theta + \dots + C_M / 2 \right\} \quad (4) \end{aligned}$$

where $M = (N+1) / 2$

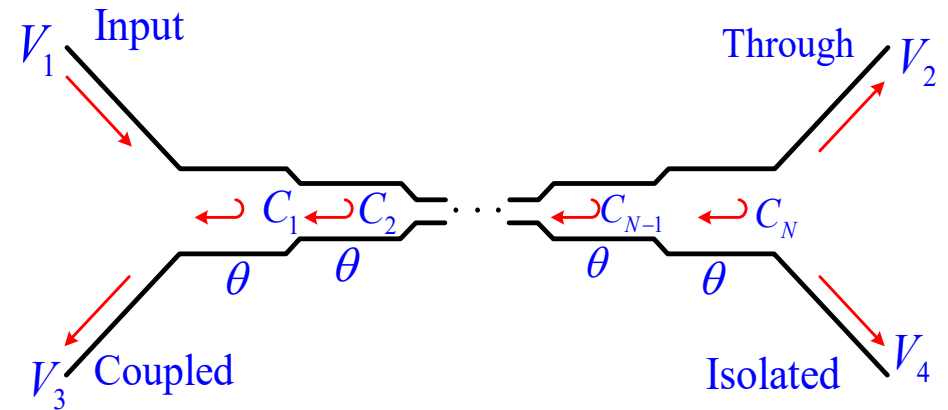

2 Multi-Section Coupled Line Coupler

- Coupling factor (C_0) at center frequency

$$C_0 = \left. \frac{V_3}{V_1} \right|_{\theta=\pi/2} \quad (5)$$

- Wideband desired coupling characteristic can be obtained by choosing the coupling coefficients, C_n .
- *Equation (4) is in form of a Fourier series of coupling as frequency function.*
- Multi-section couplers of this form can achieve decade bandwidths, but coupling levels must be low.
- Because of the longer electrical length, it is more critical to have equal even- and odd-mode phase velocities than the single-section coupler.
- *Stripline is the preferred medium* for good coupler directivity.

3 Design Example of Multi-Section Coupled Line Coupler

- Design three-section 20 dB coupler with Butterworth response for system impedance of 50Ω and center frequency of 3 GHz.

Solution

- For Butterworth response of a three section ($N = 3$) coupler

$$\left. \frac{d^n}{d\theta^n} C(\theta) \right|_{\theta=\frac{\pi}{2}} = 0 \quad \text{for } n = 1, 2$$

- From (4), we can write for $N = 3$ $\leftarrow V_3 = 2jV_1 \sin \theta e^{-jN\theta} \{C_1 \cos(N-1)\theta + C_2 \cos(N-3)\theta + \dots + C_M / 2$

$$\begin{aligned} C &= \left| \frac{V_3}{V_1} \right| = 2 \sin \theta \left\{ C_1 \cos 2\theta + \frac{C_2}{2} \right\} = 2C_1 \sin \theta \cos 2\theta + C_2 \sin \theta \\ &= C_1 (\sin 3\theta - \sin \theta) + C_2 \sin \theta = C_1 \sin 3\theta + (C_2 - C_1) \sin \theta \end{aligned}$$

3 Design Example of Multi-Section Coupled Line Coupler

- First derivative

$$\frac{dC}{d\theta} = \frac{d}{d\theta} \{C_1 \sin 3\theta + (C_2 - C_1) \sin \theta\} \Big|_{\theta=\frac{\pi}{2}} = 3C_1 \cos 3\theta + (C_2 - C_1) \cos \theta \Big|_{\theta=\frac{\pi}{2}} = 0$$

- Second derivative

$$\frac{d^2C}{d\theta^2} = \frac{d}{d\theta} \{3C_1 \cos 3\theta + (C_2 - C_1) \cos \theta\} \Big|_{\theta=\frac{\pi}{2}} = -9C_1 \sin 3\theta - (C_2 - C_1) \sin \theta \Big|_{\theta=\frac{\pi}{2}} = 10C_1 - C_2 = 0$$

- At midband, $\theta = \pi/2$, $C_0 = 20$ dB

$$C = 10^{\left(\frac{-C_0}{20}\right)} = 10^{\left(\frac{-20}{20}\right)} = 0.1$$

$$C_1 \sin 3\theta + (C_2 - C_1) \sin \theta \Big|_{\theta=\frac{\pi}{2}} = 0.1 \quad \leftarrow \text{Total coupling for } N = 3$$

$$C_2 - 2C_1 = 0.1 \quad (6)$$

$$\frac{d^2C}{d\theta^2} = 0 \rightarrow 10C_1 - C_2 = 0 \quad (7)$$

- Solving (6) and (7),

$$C_1 = C_3 = 0.0125$$

$$C_2 = 0.1 + 2C_1 = 0.1 + 2 \times 0.0125 = 0.125$$

3

Design Example of Multi-Section Coupled Line Coupler


- Even and odd-mode impedances of each section

$$Z_{0e}^1 = Z_{0e}^3 = Z_0 \sqrt{\frac{1+C_1}{1-C_1}} = 50 \sqrt{\frac{1+0.0125}{1-0.0125}} = 50.63$$

$$Z_{0o}^1 = Z_{0o}^3 = Z_0 \sqrt{\frac{1-C_1}{1+C_1}} = 50 \sqrt{\frac{1-0.0125}{1+0.0125}} = 49.38$$

$$Z_{0e}^2 = Z_0 \sqrt{\frac{1+C_2}{1-C_2}} = 50 \sqrt{\frac{1+0.125}{1-0.125}} = 56.69$$





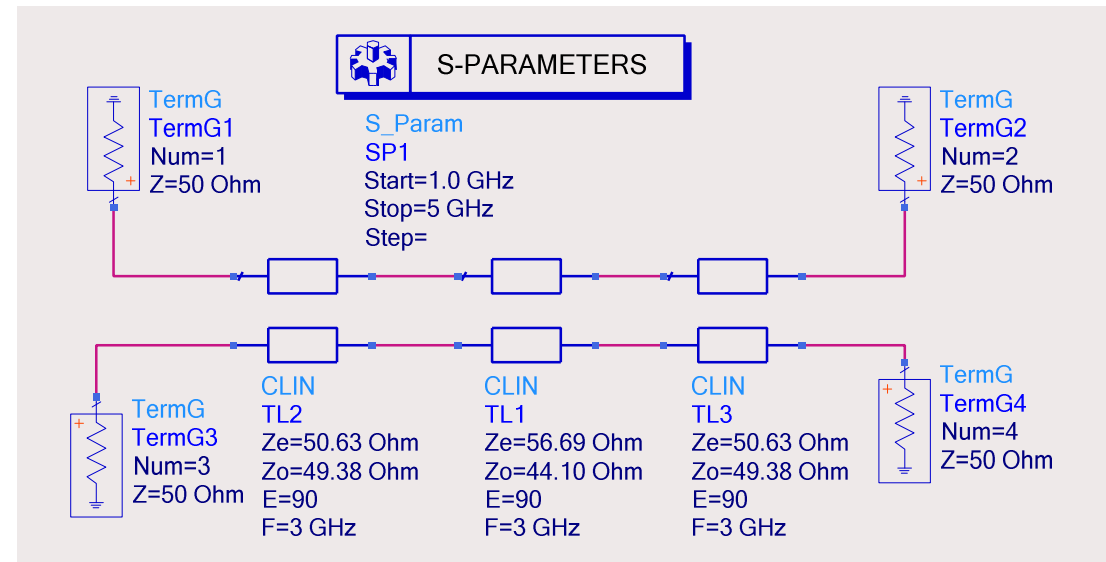
$$Z_{0o}^2 = Z_0 \sqrt{\frac{1-C_2}{1+C_2}} = 50 \sqrt{\frac{1-0.125}{1+0.125}} = 44.10$$




3

Design Example of Multi-Section Coupled Line Coupler

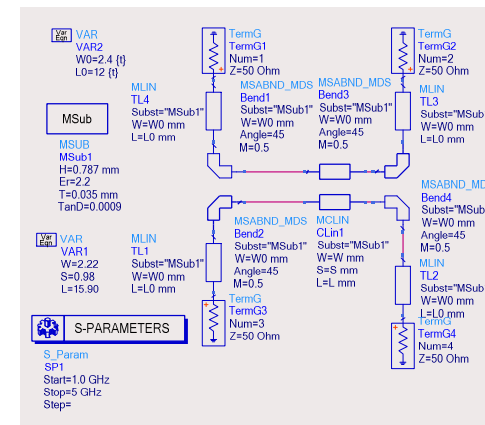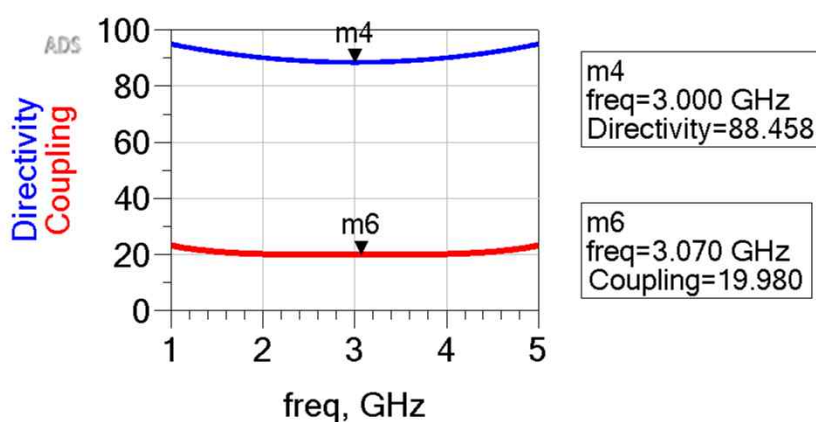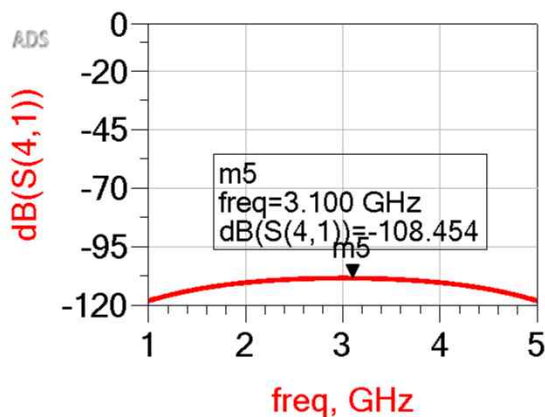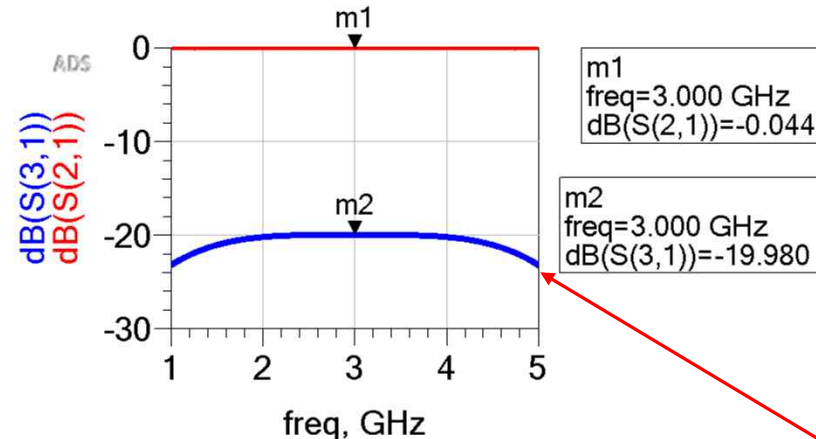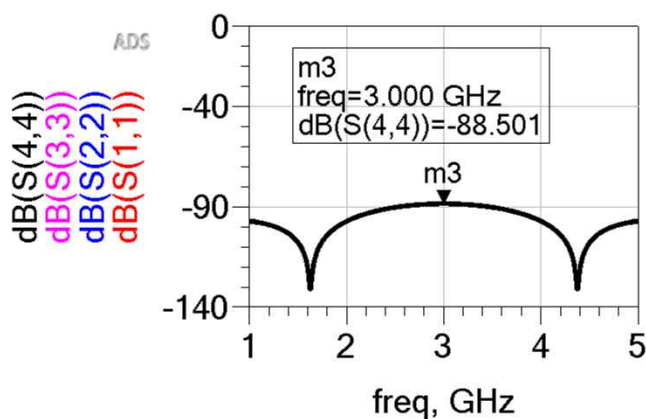- Microwave simulator simulation results of 20-dB coupler with 3-sections
- Broader frequency characteristics than single section coupler




Vs.

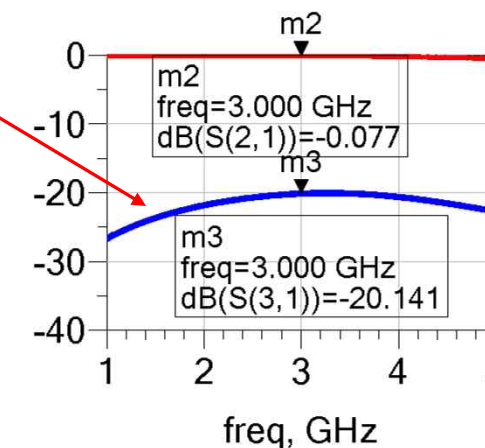

4 Review

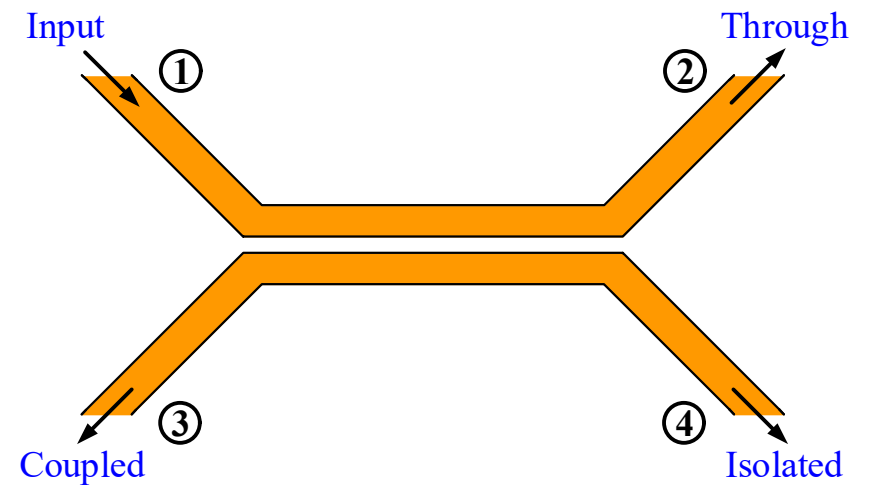- Single-Section: coupled line directional coupler
 - Narrow band performances
 - Reflection, coupling, directivity, and isolation
- Design equations of coupled line coupler
 - Matched condition
 - Even- and odd-mode excitations



4 Review

- Multi-section coupled line coupler
 - Consists of several single section couplers
 - For multi-section coupler design, loose coupling ($C \geq 10$ dB) is assumed.
 - Multi-section couplers of this form can achieve decade bandwidths, but coupling levels must be low.
 - Because of longer electrical length, it is more critical to have equal even- and odd-mode phase velocities than single-section coupler.

